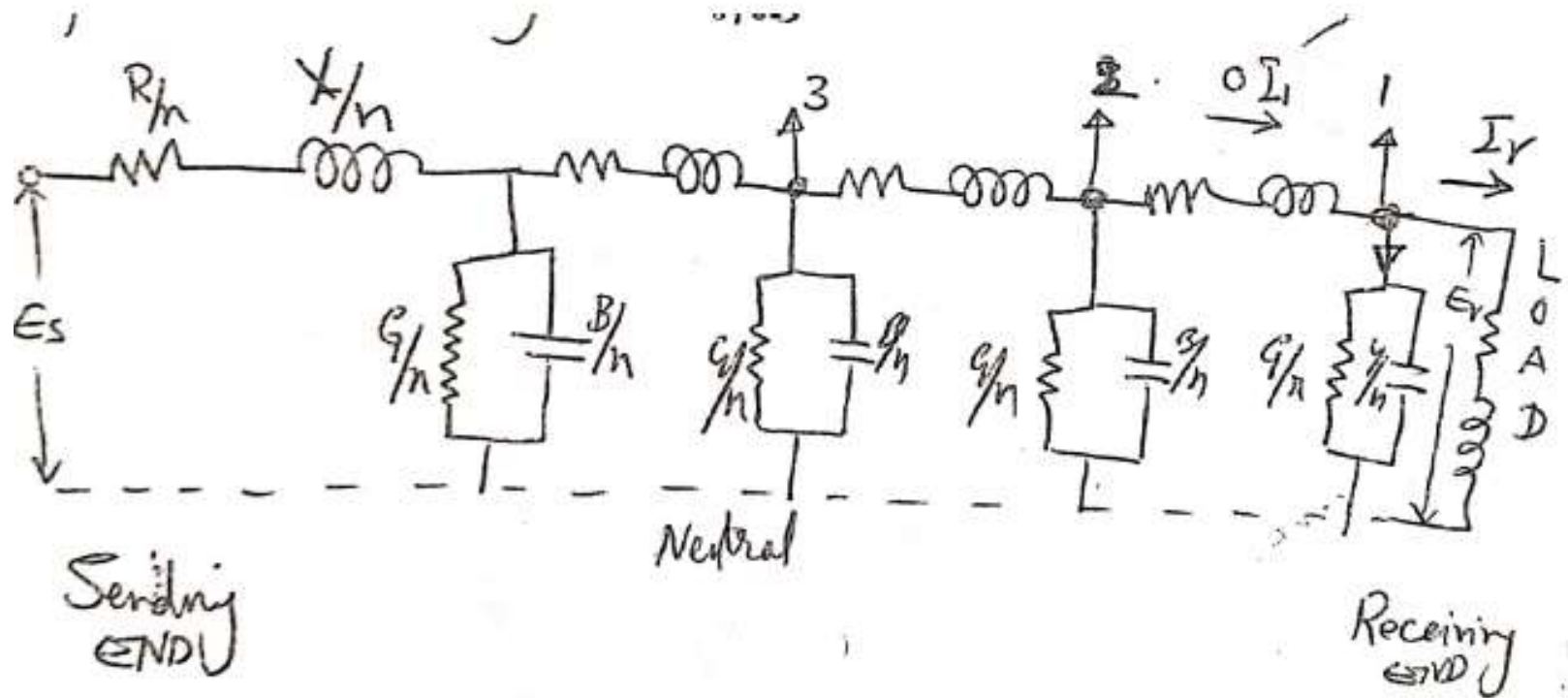



# Performance of Long Tx lines (Exact Solution)

- For Tx lines less than 200 km, the line constants or parameters are taken as lumped. But for lines more than 200 km, distributed parameters are considered for accuracy of the analysis where voltage and current varies at each point on the transmission lines.
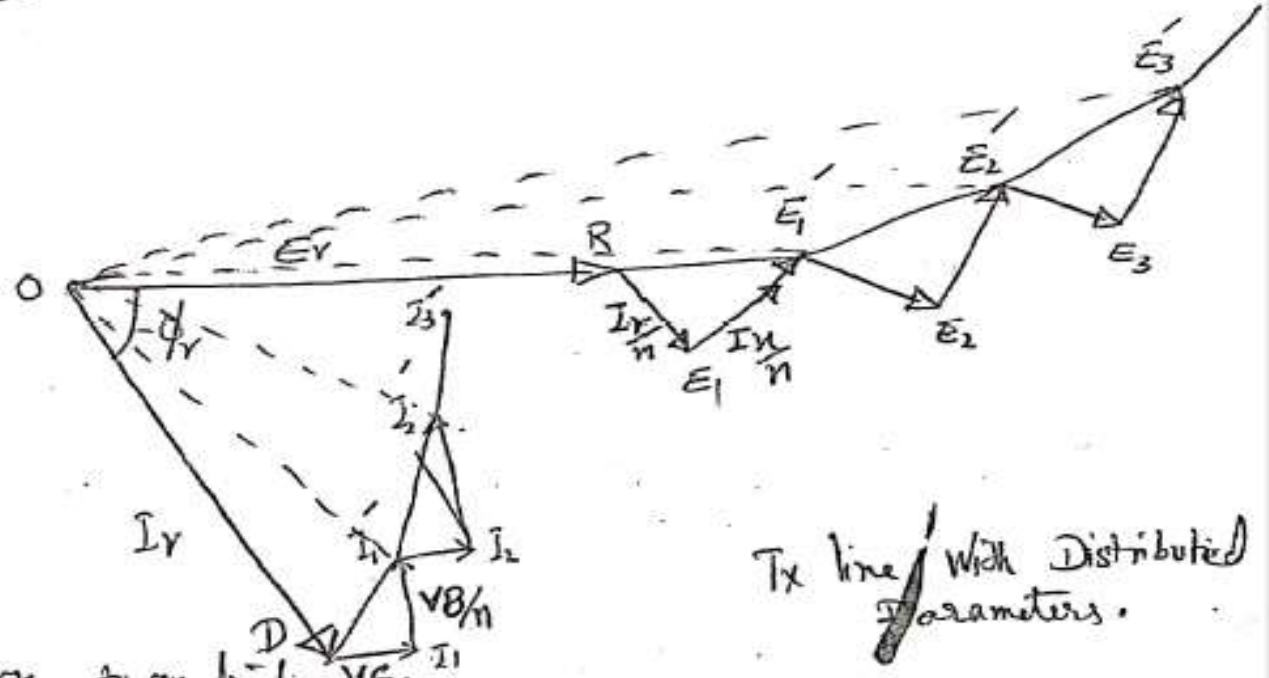
# Transmission line with Distributed constants



Starting from one end of the line, the Voltage and current at any other point can be found by taking each section in turn and constructing a diagram showing the Voltage consumed by the impedance, and the current flowing in the admittance, of each section.



~~TX line~~ With Distributed Parameters.

represent the Voltage to maintain the current at the receiving end of the line at this end.

$$I_y = \frac{V_{G/n}}{I} = IR$$

$$I_b = \frac{V_B/n}{I} = IR$$

step by step

due to  $E_r$

$E_1 E_1'$  in  $R/n$  } due to  $E_r$  (in phase to  $E_r$ )  
 $E_1 E_1'$  in  $X/n$  } due to  $E_r$  ( $90^\circ$  lead to  $E_r$ )  
 $R E_1$  drop in  $R/n$  } due to  $O I_1'$   
 $E_1 E_1'$  drop in  $X/n$  }

$O E_1' \Rightarrow$  Voltage Drop at pt (2)

Similarly for 2nd section.

$I_1' I_2$  current in  $G/n$  (in phase to  $E_1'$ )

$I_2 I_2'$  the current in  $B/n$  (lead by  $90^\circ$ )

$E_1' E_2$  drop in  $R/n \rightarrow$  in phase with  $I_2'$

$E_2 E_2'$  drop in  $X/n$  (lead current by  $90^\circ$ )

At pt (3) Voltage drop in  $O E_2'$

(2)

Exp

$$r = 0.275 \Omega/\text{mile}$$

$$X = 0.769 \Omega/\text{mile}$$

$$g = 0.15 \times 10^{-6} \text{ mhos}$$


$$b = 552 \times 10^{-6} \text{ @ mhos.}$$

$$E_r = 50 \text{ kV (l-n)}$$

$I_r = 25 \text{ Amp}$  lagging  $25^\circ$  behind the Volts

$$l = 200 \text{ miles.}$$

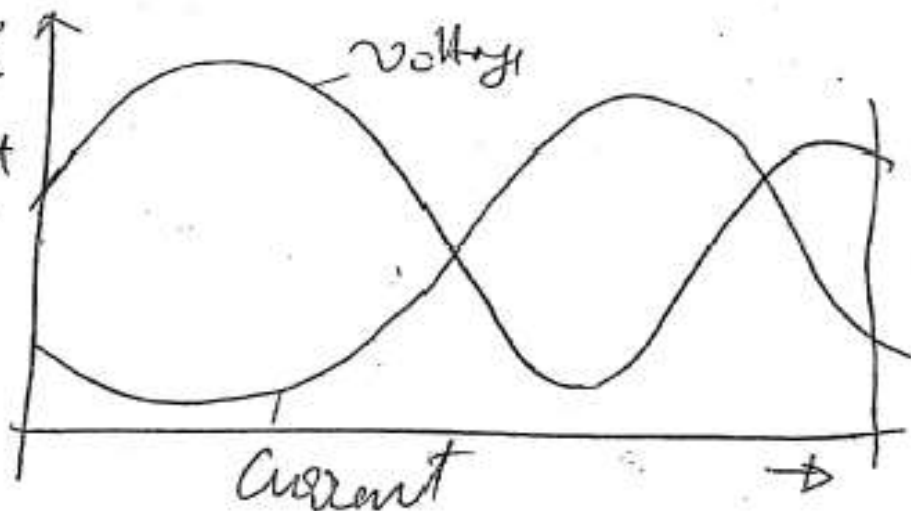The Voltage & Current  
oscillates rise & fall  
along the line and  
phase of phase different  
repeats periodically, between




lag & lead


distance from  
receiving end.


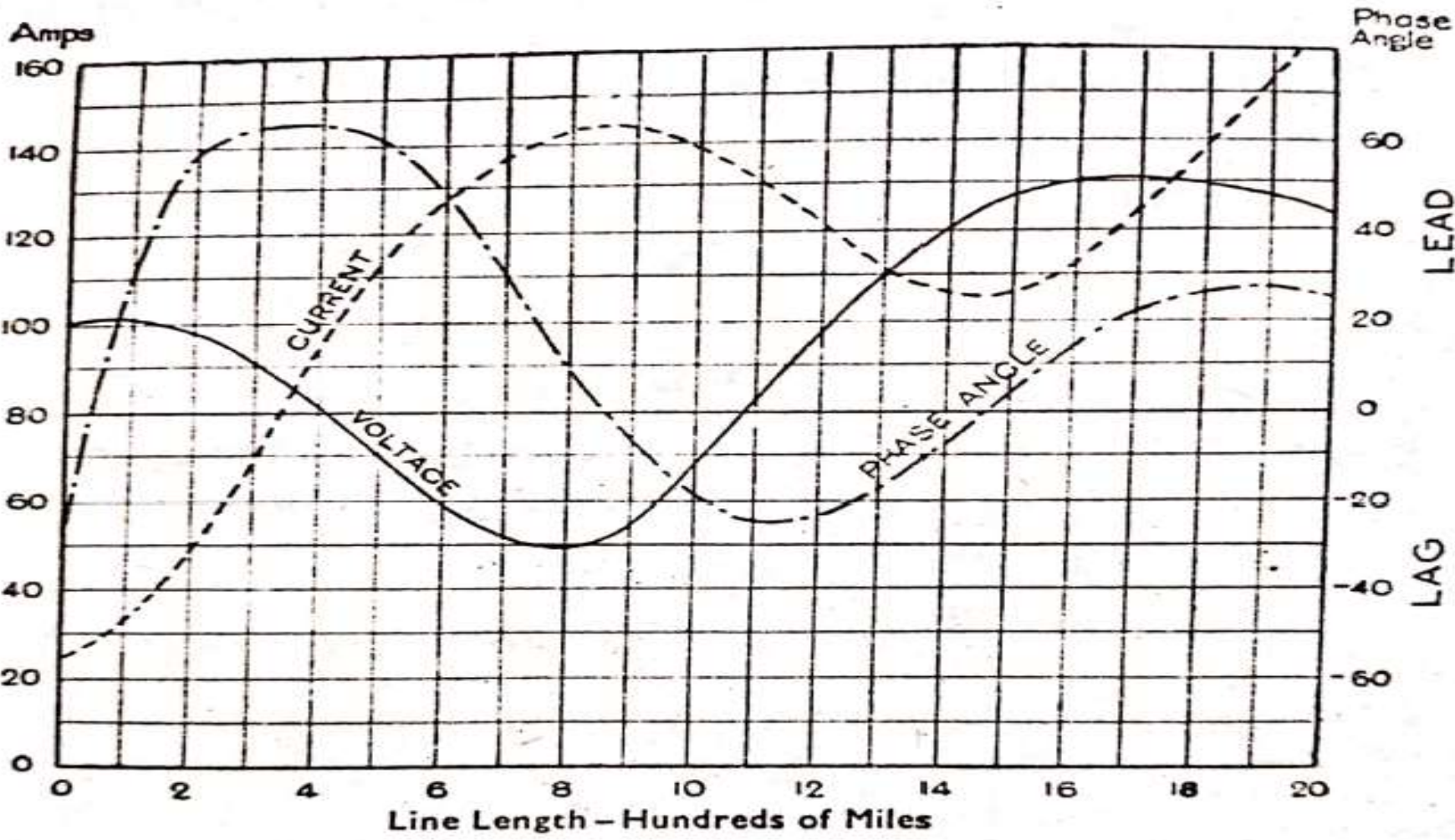
# Voltage, Current & Phase angle in a long Tx line


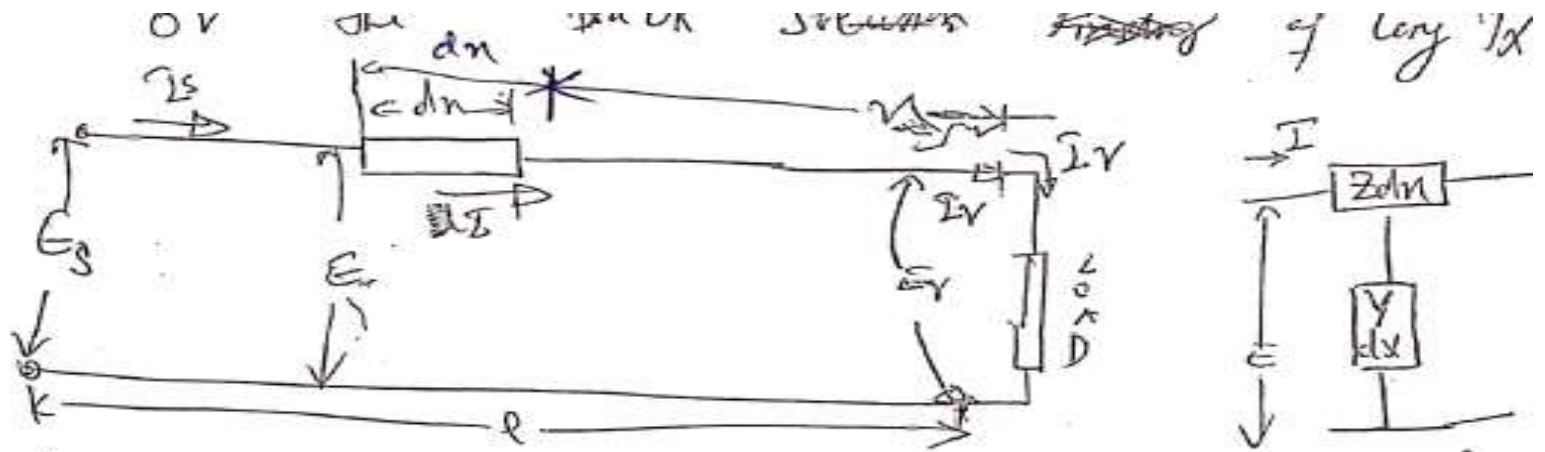
# Fundamental Differential Equation and Solution



$Z \rightarrow$  Impedance of unit length of each ckt  
 $Y \rightarrow$  Admittance of unit length of each ckt

Take a incremental length  $dx$  at  $x$  from receiving end.

Impedance of incremental length =  $Z dx$  at distance of  $x$  from receiving end.

admittance of length  $dx$  of line is  $Y dx$ .

Let Voltage Drop over length  $dx = d\varepsilon = I Z dx$

or  $d\varepsilon/dx = IZ \longrightarrow (1)$

the Shunt current drawn from a incremental length  $dx$  of the line ;  $dI = \varepsilon Y dx = \varepsilon Y dx$

or  $dI/dx = \varepsilon Y \longrightarrow (2)$

Taking derivative of (1) w.r.t  $x$ .

$$\frac{d^2\varepsilon}{dx^2} = Z \frac{dI}{dx} = Z Y \varepsilon$$

$$\frac{d^2\varepsilon}{dx^2} - Z Y \varepsilon = 0 \longrightarrow (3)$$

$$\frac{d^2I}{dx^2} = Y \frac{d\varepsilon}{dx} = Y I Z$$

$$\frac{d^2I}{dx^2} - Y I Z = 0 \longrightarrow (4)$$

★

(4)



③ → Aux Equation  $\lambda^2 - YZ = 0 \Rightarrow \lambda = \pm \sqrt{YZ}$

Gen solution  $E = A e^{\lambda x} + B e^{-\lambda x}$

$$E = A e^{\sqrt{YZ} x} + B e^{-\sqrt{YZ} x} \quad \text{--- (5)}$$

⇒  $\frac{dE}{dx} = \sqrt{YZ} \left[ A e^{\sqrt{YZ} x} - B e^{-\sqrt{YZ} x} \right]$

∴  $\frac{dE}{dx} = IZ$ , So

$$IZ = \sqrt{YZ} \left[ A e^{\sqrt{YZ} x} - B e^{-\sqrt{YZ} x} \right]$$

$$I = \sqrt{\frac{Y}{Z}} \left[ A e^{\sqrt{YZ} x} - B e^{-\sqrt{YZ} x} \right] \rightarrow 6$$

find A & B ; Apply boundary conditions to 5, 6  
receiving end  $x=0$ ,  $E = E_r$

$$E_r = A e^0 + B e^0 = A + B$$

$$I_r = \sqrt{Y}/Z [A - B e^0] = \sqrt{Y}/Z (A - B)$$

$$E_r = A + B$$

$$I_r \sqrt{Z/Y} = A - B$$

Adding

---

$$A = \frac{1}{2} \left[ E_r + \sqrt{Z/Y} I_r \right]$$

Subtracting two Equations

$$B = \frac{1}{2} \left[ E_r - \sqrt{Z/Y} I_r \right]$$

putting

A x B

values in Equation 5 & 6

$$E = \frac{1}{2} [E_r + \sqrt{\frac{Z}{Y}} I_r] e^{\sqrt{YZ} x} + \frac{1}{2} [E_r - \sqrt{\frac{Z}{Y}} I_r] e^{-\sqrt{YZ} x}$$

$$= E_r \left[ \frac{e^{\sqrt{YZ} x} + e^{-\sqrt{YZ} x}}{2} \right] + \sqrt{\frac{Z}{Y}} I_r \left[ \frac{e^{\sqrt{YZ} x} - e^{-\sqrt{YZ} x}}{2} \right]$$

$$E = E_r \cosh \sqrt{YZ} x + \sqrt{\frac{Z}{Y}} I_r \sinh \sqrt{YZ} x \quad \text{--- (7)}$$

$$\text{As } \cosh \theta = \frac{e^\theta + e^{-\theta}}{2}, \quad \sinh \theta = \frac{e^\theta - e^{-\theta}}{2}$$

For Current

$$I = \sqrt{Y/2} [A e^{\sqrt{YZ} x} - B e^{-\sqrt{YZ} x}]$$

$$I = \sqrt{Y/2} \left[ \frac{1}{2} (E_r + \sqrt{\frac{Z}{Y}} I_r) e^{\sqrt{YZ} x} - \frac{1}{2} (E_r - \sqrt{\frac{Z}{Y}} I_r) e^{-\sqrt{YZ} x} \right]$$

~~$$I = \sqrt{Y/2} \left[ \frac{1}{2} (E_r + \sqrt{\frac{Z}{Y}} I_r) e^{\sqrt{YZ} x} - \frac{1}{2} (E_r - \sqrt{\frac{Z}{Y}} I_r) e^{-\sqrt{YZ} x} \right]$$~~

$$I = \sqrt{Y/2} \left[ E_r \left( \frac{e^{\sqrt{YZ} x} - e^{-\sqrt{YZ} x}}{2} \right) + \sqrt{\frac{Z}{Y}} I_r \left( \frac{e^{\sqrt{YZ} x} + e^{-\sqrt{YZ} x}}{2} \right) \right]$$

$$I = \sqrt{Y/2} E_r \sinh \sqrt{YZ} x + I_r \cosh \sqrt{YZ} x \quad \text{--- (8)}$$

4 112

For voltage at sending end put  $x=l$  in eq 7

$$E_s = E_r \cosh \sqrt{ZY} l + \sqrt{\frac{Z}{Y}} I_r \sinh \sqrt{ZY} l$$

$Zl \rightarrow Z$  (total),  $Y = y_l =$  total admittance

$$\sqrt{ZY} l = \sqrt{zyl} = \sqrt{Zl \cdot Yl} = \sqrt{ZY}$$

$$\sqrt{\frac{Z}{Y}} = \sqrt{\frac{Zl}{Yl}} = \sqrt{\frac{Z}{Y}}$$

(6)

So

$$E_s = E_r \cosh \sqrt{ZY} + \sqrt{Z/Y} I_r \sinh \sqrt{ZY} \quad \text{--- (9)}$$

Similarly

$$I_s = \sqrt{Y/Z} E_r \sinh \sqrt{YZ} + I_r \cosh \sqrt{YZ} \quad \text{--- (10)}$$

Let

$$A = D = \cosh \sqrt{ZY}$$

$$B = \sqrt{Z/Y} \sinh \sqrt{ZY}$$

$$C = \sqrt{Y/Z} \sinh \sqrt{ZY}$$

then

Equation for  $E_s$  &  $I_s$

$$E_s = A E_r + B I_r \quad \text{--- (9')}$$

$$I_s = C E_r + D I_r \quad \text{--- (10')}$$

A, B, C, D are constant, called general  
 line constant (Distributed load constant)  
 depends upon freq etc.



# Equivalent $\pi$ & T circuit

## Equivalent $\pi$ & T circuit

A long transmission line may be replaced by a  $\pi$  or T circuit electrical equivalent in the same manner. The same electrical relations exist between the terminals of the same electrical conditions in each case. Ref. to Figure (previous for M.T. line) assume that the series impedance and shunt admittance are  $Z'$  and  $Y'$  respectively.

Then the Voltage and current equations are:

$$E_s = E_r \left(1 + \frac{Z'Y'}{2}\right) + I_r Z'$$

$$I_s = I_r \left(1 + \frac{Z'Y'}{2}\right) + E_r Y' \left(1 + \frac{Z'Y'}{4}\right)$$

While the corresponding equations of the long

lines are

$$E_s = E_r \cosh \theta + I_r \sqrt{\frac{Z}{Y}} \sinh \theta$$

$$I_s = I_r \cosh \theta + E_r \sqrt{\frac{Y}{Z}} \sinh \theta$$

where  $\theta = \sqrt{ZY}$ .

In circuits

$$Z = \sqrt{\frac{Z}{Y}} \sinh \theta$$

for equivalence between the

for  $Z$  in the  $1 + \frac{Z'Y'}{2} = \cosh \theta$  & substituting  
 the latter equation

$$1 + \frac{Y'}{2} \sqrt{\frac{Z}{Y}} \sinh \theta = \cosh \theta$$

so

$$\frac{Y'}{2} = \sqrt{\frac{Y}{Z}} \frac{\cosh \theta - 1}{\sinh \theta} = \frac{Y(\cosh \theta - 1)}{\theta \sinh \theta}$$

$$= \frac{Y}{Z} \frac{\tanh(\theta/2)}{\theta/2} \dots$$

$$\theta = \sqrt{ZY}$$

$$\sqrt{\frac{Y}{Z}} = \frac{Y}{\theta} = \frac{Y}{\sqrt{ZY}}$$

14  
The equivalent  $\pi$  circuit is of important since  
its constants, unlike the  $A, B, C, D$  constants, can  
form the basis of a physical model of  
the transmission line for use in  
network analysis. It is ~~should~~ ~~be~~  
however ~~used in network~~  
Analysis

# Evaluation of General Line Constants or A, B, C, D Constants

## Evaluation of General Line Constants A, B, C & D (for Problems)

Method #1 The expansion of convergent series of hyp from

$$\cosh x = 1 + \frac{x^2}{2!} + \frac{x^4}{4!} + \frac{x^6}{6!} + \dots$$

$$\sinh x = x + \frac{x^3}{3!} + \frac{x^5}{5!} + \frac{x^7}{7!} + \dots$$

$$\cosh \sqrt{2Y} = 1 + \frac{(\sqrt{2Y})^2}{2!} + \frac{(\sqrt{2Y})^4}{4!} = 1 + \frac{2Y}{2} + \frac{(2Y)^2}{4!}$$

Mostly  $2Y < 0.5$ , High convergent series, high values are neglected.

$$\sinh \sqrt{2Y} = \sqrt{2Y} + \frac{(\sqrt{2Y})^3}{3!} + \frac{(\sqrt{2Y})^5}{5!} + \dots$$

$$\text{So } A = D = 1 + \frac{ZY}{2} + \frac{(ZY)^2}{4} \quad \text{--- (1)}$$

$$B = \sqrt{\frac{ZY}{4}} \left[ \sqrt{ZY} + \frac{(\sqrt{ZY})^3}{6} + \frac{(\sqrt{ZY})^5}{120} \right]$$

$\sqrt{ZY}$  common

$$B = Z \left[ 1 + \frac{ZY}{6} + \frac{(ZY)^2}{120} \right] \quad \text{--- 2}$$

$$C = \sqrt{\frac{Y}{2}} \left[ \sqrt{ZY} + \frac{(\sqrt{ZY})^3}{6} + \frac{(\sqrt{ZY})^5}{120} \right]$$

$$C = Y \left[ 1 + \frac{ZY}{6} + \frac{(\sqrt{ZY})^2}{120} \right] \quad \text{--- (3)}$$



Method) Using Hyperbolic Expansion.

$$y = \sqrt{2}y = \alpha + j\beta$$

$$A = \cosh \sqrt{2}y = \cosh (\alpha + j\beta)$$

$$A = \cosh \alpha \cosh j\beta + \sinh \alpha \sinh j\beta$$

$$A = \cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = D$$

$$B = \sqrt{\frac{2}{4}} [\sinh (\alpha + j\beta)]$$

$$\begin{cases} \cosh j\beta = \cos \beta \\ \sinh j\beta = j \sin \beta \end{cases}$$

$$B = \sqrt{\frac{2}{4}} [\sinh \alpha \cosh j\beta + \sinh j\beta \cosh \alpha]$$

$$B = \sqrt{\frac{2}{4}} [\sinh \alpha \cos \beta + j \sin \beta \cosh \alpha]$$

Similarly

$$C = \sqrt{\frac{4}{2}} [\sinh (\alpha + j\beta)]$$

$$C = \sqrt{\frac{4}{2}} [\sinh \alpha \cosh j\beta + \sinh j\beta \cosh \alpha]$$