

# CHAPTER 12

## CURRENT ELECTRICITY

Date: \_\_\_\_\_

Day: M T W T F S

$$* I = \frac{Q}{t}$$

$$* V = IR$$

$$* R = \frac{\rho L}{A}$$

$$* G = \frac{1}{R} \quad (G: \text{Conductance})$$

$$* \sigma = \frac{1}{\rho} = \frac{L}{RA} \quad (\sigma: \text{Conductivity})$$

$$* R_T - R_0 = \alpha R_0 T$$

$$* \rho_T = \rho_0 (1 + \alpha T)$$

$$* \epsilon = \frac{W}{q}$$

$$* V = \epsilon - Ir \quad (r: \text{internal resistance of supply})$$

or  $IR = \epsilon - Ir$

Koracademy.com

$$* P = \frac{W}{t}$$

$$P = \frac{QV}{t}$$

$$* P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

Koracademy.com

\* Maximum Power Output

$$P = \frac{\epsilon^2}{4R}$$

\* Thermocouples

$$\epsilon = \alpha T + \frac{1}{2} \beta T^2$$

\* KCL :  $\sum I = 0$

\* KVL :  $\sum \epsilon = \sum IR$

\* Wheatstone Bridge

$$X = \frac{RQ}{P}$$

X: Unknown

P and Q: Fixed

R: Variable

\* Potentiometer

$$\frac{E_2}{E_1} = \frac{l_2}{L_1}$$

$$* \quad \alpha = \frac{R_T - R_0}{R_0 T}$$

$$* \quad \alpha = \frac{\rho_T - \rho_0}{\rho_0 T}$$

$$* \quad R = \frac{\rho^2 l^2}{m}$$

Koracademy.com

\* When 2 Resistors are connected in parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

\* If 'n' Resistors of equal magnitude are connected in parallel

$$R_{eq} = \frac{1}{n} R$$

\* To find Resistance of wire when stretched 'n' times:

$$R' = n^2 R$$

\* In series the lamp with smaller rated power shows maximum glow

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

\* When wire is stretched, why does area becomes halved when length is doubled?

Volume of wire remains constant before and after stretching

$$\text{Volume} = A \times l$$

When length is doubled area must be divided by 2 to keep volume constant

## \* TEMPERATURE CO-EFFICIENT OF RESISTANCE ( $\alpha$ )

+ve value  $\rightarrow$  Resistance increase with increasing temperature ( $R \propto T$ )

e.g metals

-ve value  $\rightarrow$  Resistance decrease with increasing temperature ( $R \propto 1/T$ )

e.g graphite, non-metals

Large  $\alpha$  Value:

Greater change in resistance per kelvin i.e. if change in resistance is rapidly taking place and with greater magnitude w.r.t temperature (e.g tungsten)

Small  $\alpha$  Value:

Not rapid change and with smaller magnitude.

e.g Copper  $\rightarrow$  that's why copper is good conductor bcz its resistance doesnot change easily

Unit of  $\alpha$ :  $K^{-1}$

# WIRE-WOUND VARIABLE RESISTORS

\* Wire wound variable resistors are:

→ Highly stable

→ Highly accurate

\* Generally nickel-chromium is used bcz of its very small temperature co-efficient of resistance

\* Wire wound resistor can be used as:

1. Rheostats

2. Potential Divider

## 1. RHEOSTAT

An electrical resistance used to control current by varying resistance.

TYPES:

1. Rotatory Rheostat (e.g. used in fans)

2. Linear Rheostat (or cylindrical Rheostat)

SYMBOL:

 or 

BASIC PRINCIPLE

$R \propto l$

( $l$  is length of coiled wire)

Rheostat is used to increase or decrease the volume of radio or increase or decrease the speed of an electric motor.

## 2 POTENTIAL DIVIDER (OR VOLTAGE DIVIDER)

A resistor or series of resistors connected to a voltage source and used to provide voltages that are fractions of that of the source.

Koracademy.com

Date: \_\_\_\_\_

Day: **M T W T F S S**

## MAXIMUM POWER OUTPUT

→ If the load resistance is less or greater than the source resistance, then the power delivered to the load will be minimum.

→ Maximum power is delivered to load  $R$  when internal resistance of the source of emf is equal to the load resistance.

The value of maximum power output is:

$$(P_{out})_{max} = \frac{\mathcal{E}^2}{4r} = \frac{\mathcal{E}^2}{4R}$$

Koracademy.com



# THERMISTOR

\* A resistor made of semiconductors having resistance that varies rapidly and predictably with temperature is known as thermistor.

\* Thermistor → short for thermal resistor

\* Temperature co-efficient of thermistor is very high. May be positive or negative (NTC or PTC)

\* Thermistors are made from semiconductor oxides of iron, nickel and cobalt

\* They may be in the form of discs or rods.  
→ The rod and bead thermistors are used in temperature probes  
→ They may be in the form of flat discs for applications where they need to be in contact with a flat surface

## ARRANGEMENT :

Pair of platinum leads are attached at the two ends of electrical connections. The arrangement is enclosed in a very small glass bulb and sealed.

Date: \_\_\_\_\_

Day: M T W T F S S

## TEMPERATURE RANGE:

Metallic oxide thermistors are generally used for temperature in range 200 to 700K.  
(-73°C to 427°C)

## APPLICATIONS

1. May be used as thermostat
2. NTC thermistors are used as thermometers in a very low-temperature measurements.

Koracademy.com

### \* CHARGE MOVING IN A CIRCLE:

If a charged particle of charge  $q$  is moving in circular path of radius  $r$  with constant speed  $v$  and constant frequency  $f$  then

$$I = fq$$

$$I = \frac{vq}{2\pi r} \quad \left( \because f = \frac{v}{2\pi r} \right)$$

\* The slope of I-V Graph of Ohm's Law is equal to reciprocal of resistance of conductor

### \* CURRENT DENSITY:

The current flowing per unit normal area of cross section is defined as current density

\* Electromotive force is not a force but it is energy or work.

### \* INTERNAL RESISTANCE:

$$r = \frac{E - V}{I}$$

$$\therefore V = E - Ir$$

$$\text{or } r = \left( \frac{E - V}{V} \right) R$$

\* Charge on  $\alpha$ -Particle  $\rightarrow +2e$

\* The resistance b/w the ends of a diameter of a circle is like two resistors in parallel. So  $4\Omega$  resistor ~~convert~~ converted to 2 resistors of  $2\Omega$ .

\* Resistance of Light Dependant Resistor LDR decreases upon increasing the intensity of falling light. It is used as light sensors.

\* DIAMETER RELATION WITH 'I' AND 'R'

$$I \propto d^2$$

$$R \propto \frac{1}{d^2}$$

\* To increase the scale of Galvanometer to twice of its initial value we need to connect a shunt?

Ans:  $R_s = R_g$

Solution:

$$R_s = \frac{I_g}{I - I_g} R_g$$

As  $I_g = 2I_g$

$$R_s = \left( \frac{I_g}{2I_g - I_g} \right) R_g$$

$$R_s = R_g$$

Koracademy.com

\* Resistivity depends on

- 1) Nature of material
- 2) Temperature

\* Silver is best conductor and copper is second best conductor of electricity.

## \* COMBINATION OF BULBS (SERIES)

1. TOTAL POWER CONSUMED

$$\frac{1}{P_{TOTAL}} = \frac{1}{P_1} + \frac{1}{P_2} + \dots$$

2. IF 'n' BULBS ARE IDENTICAL

$$P_{TOTAL} = \frac{P}{n}$$

3. BRIGHTNESS

$$P_{consumed} (\text{Brightness}) \propto V \propto R \propto \frac{1}{P_{rated}}$$

i.e. in series combination bulb of lesser wattage will give more bright light and potential difference appeared across it will be more.

## \* BULBS IN PARALLEL

### 1. TOTAL POWER CONSUMED

$$P_{TOTAL} = P_1 + P_2 + P_3 \dots P_n$$

### 2. For 'n' IDENTICAL BULBS

$$P_{TOTAL} = nP$$

### 3. BRIGHTNESS

$$P_{consumed} \text{ (Brightness)} \propto P_R \propto I \propto \frac{1}{R}$$

In parallel combination bulb of greater wattage will give more bright light and more current will pass through it.

MCQ: A 100W, 200V bulb is connected to a 160V supply. The actual power consumption would be :

$$\text{Resistance of bulb} = \frac{V^2}{P} = \frac{(200)^2}{100} = 400 \Omega$$

Actual Power Consumption

$$P = \frac{V^2}{R} = \frac{(160)^2}{400} = 64W$$

\* Neutral Temperature for Copper-Iron Thermocouple:  
518°F or 270°C

\* Inversion Temperature for Copper-Iron Thermocouple:  
1004°F or 540°C

\* Electroencephalogram (EEG)

→ to measure and record electrical activity in the brain

→ measures voltage fluctuations resulting from ionic current flows within neurons of the brain

→ Brain electrical current consist mostly of  $\text{Na}^+$ ,  $\text{K}^+$ ,  $\text{Ca}^{+2}$  and  $\text{Cl}^-$  ions that are pumped through channels in neuron membranes.

Koracademy.com