

Numerical Problems

Problem 12.1 A battery has an emf of 12.8 V and supplies current of 3.2 A. What is resistance of circuit? How many coulombs leave battery in 5 minute?

$V = 12.8 \text{ V}$ $i = 3.2 \text{ A}$ $R = ?$ $Q = ?$ if $t = 5 \text{ min} = 300 \text{ sec}$

Solution

From Ohm's law we can write $R = \frac{V}{i} = \frac{12.8}{3.2} = 4 \Omega$

Now charge $Q = i \times t = 3.2 \times 300 = 960 \text{ C}$

Problem 12.2 A carbon electrode has a resistance of 0.125Ω at 20°C . The temperature co-efficient of carbon is -0.0005 at 20°C . What will be the resistance of the electrode at 85°C .

$R_{20} = 0.125 \Omega$ $T_1 = 20^\circ \text{C}$ $\alpha = -0.0005$ $R_t = ?$ when $T_2 = 85^\circ \text{C}$

Solution

Resistance at any temperature T is given by

$$R_t = R_0 (1 + \alpha T)$$

where

$$T = T_2 - T_1 = 85 - 20 = 65^\circ \text{C}$$

$$R_t = 0.125 (1 - 0.0005 \times 65) = 0.12 \Omega$$

Problem 12.3 Calculate the resistance of wire 10 m long that has a diameter of 2 mm and resistivity of $2.63 \times 10^{-2} \Omega \text{ m}$.

$R = ?$ $L = 10 \text{ m}$ $d = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$ $\rho = 2.63 \times 10^{-2} \Omega \text{ m}$

Solution

we know that $R = \frac{\rho L}{A}$

where $A = \pi r^2 = \pi d^2 / 4 = 3.14 \times 10^{-6} \text{ m}^2$

$$R = \frac{(2.63 \times 10^{-2}) (10)}{3.14 \times 10^{-6}} = 83758 \Omega \text{ (Text book needs correction)}$$

Problem 12.4 A typical 12 V automobile battery has a resistance of 0.012Ω . What is terminal voltage of this battery when starter draws a current of 100 A? Calculate R , P_ϵ , P_R and P_r .

$\epsilon = 12 \text{ V}$ $r = 0.012 \Omega$ (a) $V_t = ?$ when $i = 100 \text{ A}$ (b) Load $R = ?$

(c) Power of source $P_\epsilon = ?$ (d) Power $P_R = ?$ (e) Power $P_r = ?$

Solution

(a) We know that emf $\epsilon = V_t + ir$

$$V_t = \epsilon - ir = 12 - (100)(0.012) = 10.8 \text{ V}$$

(b) Load resistor

$$R = \frac{V_t}{i} = \frac{10.8}{100} = 0.108 \Omega$$

- (c) $P_{\epsilon} = i^2 (R + r) = (100)^2 \times (0.108 + 0.012) = 1200 \text{ W}$
 (d) $P_R = i^2 R = (100)^2 \times 0.108 = 1080 \text{ W}$
 (e) $P_r = i^2 r = (100)^2 \times 0.012 = 120 \text{ W}$

Problem 12.5. A 10 W resistor has a value of 120Ω . What is the rated current through the resistor?

$P = 10 \text{ W}$

$R = 120 \Omega$

$i = ?$

The maximum current that a device can draw without being over-heated is called rated current.

Solution

From definition of power $P = i^2 R$

$$i = \sqrt{\frac{P}{R}} = \sqrt{\frac{10}{120}} = 0.2886 \text{ A}$$

Problem 12.6 Resistor of 50Ω has a P. D of 100 V D.C. across 1 hr. Calculate (a) Power and (b) Energy.

$R = 50 \Omega$

$V = 100 \text{ V}$

$t = 1 \text{ hr} = 3600 \text{ sec}$ (a) $P = ?$ (b) $E = ?$

Solution

(a) Power

$$P = \frac{V^2}{R} = \frac{(100)^2}{50} = 200 \text{ w}$$

(b) Energy

$$E = P \times t = 200 \times 3600 = 0.72 \times 10^6 \text{ J} = 0.72 \text{ MJ}$$

Problem 12.7 Calculate the current through a single loop circuit if $\epsilon = 120 \text{ V}$, $R = 1000 \Omega$ and internal resistance $r = 0.01 \Omega$.

$i = ?$

$\epsilon = 120 \text{ V}$

$R = 1000 \Omega$

$r = 0.01 \Omega$

Solution

Using the relation

$$\epsilon = i (R + r)$$

or

$$i = \frac{\epsilon}{R+r} = \frac{120}{1000 + 0.01} = 0.1199 \text{ A or } 120 \text{ mA}$$

Problem 12.9 Find current flowing through the resistors of the figure given.

Current $i = ?$ in the given circuit

Let $\epsilon_1 = 10 \text{ V}$

$\epsilon_2 = 6 \text{ V}$

$R_1 = 2 \Omega$

$R_2 = 1 \Omega$

$i = ?$

Solution

Applying KVL along closed loop abcda (counter clockwise)

$$-\epsilon_1 - (i_1 - i_2) R_1 = 0$$


$$-10 - (i_1 - i_2) R_1 = 0 \quad (1)$$

Similarly applying KVL along the closed

loop befcb (counter clockwise)

$$-i_2 R_2 + \epsilon_2 - (i_1 - i_2) R_1 = 0$$

$$-i_2 R_2 + 6 - (i_1 - i_2) R_1 = 0$$

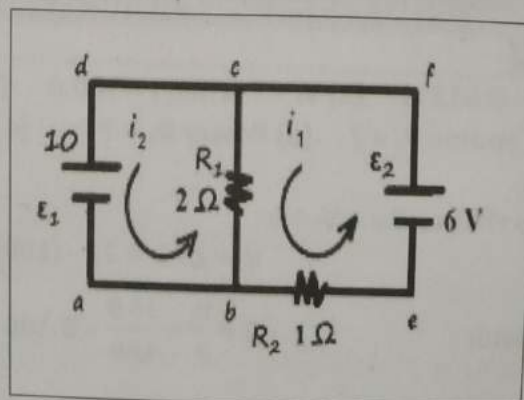

$$+ 6 - i_2 R_2 - (i_1 - i_2) R_1 = 0 \text{ ----- (2)}$$

Adding eq (1) and (2) we get

$$- i_2 R_2 - 4 = 0$$

$$i_2 = -4 \text{ A}$$

putting this value in eq (1) we get

$$- 2 i_1 + 2 (-4) - 10 = 0$$

solving for i_1 we get

$$i_1 = -9 \text{ A}$$

Current flowing through R_2 is i_2 (-4 A) and current flowing through R_1 is $(i_1 - i_2) = -5 \text{ A}$

Problem 12.10 Find terminal P.D of each cell in the circuit of figure given.

$$r_1 = 0.1 \Omega \quad r_2 = 0.9 \Omega \quad R = 8 \Omega \quad \epsilon_1 = 24 \text{ V}$$


$$\epsilon_2 = 6 \text{ V} \quad V_{t1} = ? \quad V_{t2} = ?$$

Solution

Since ϵ_1 and ϵ_2 oppose each other so net emf is equal to their difference. Resistors are all in series, so net resistance is equal to the sum of individual resistance.

$$i = \frac{\epsilon_n}{R_n} = \frac{\epsilon_1 - \epsilon_2}{r_1 + R + r_2}$$
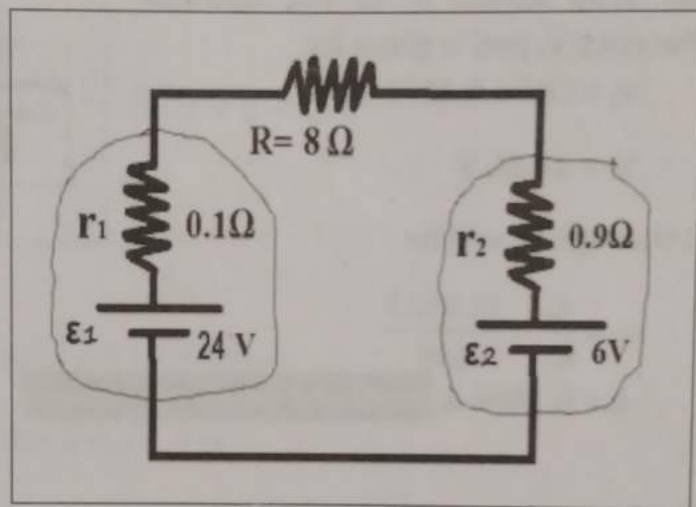
$$i = \frac{24 - 6}{0.1 + 8 + 0.9} = 2 \text{ A}$$



Now terminal P.D of both cells can be calculated as follow;

For 1st cell: eq(1) ⇒

$$V_{t1} = \epsilon_1 - i r_1 = 24 - (2 \times 0.1) = 23.8 \text{ V}$$

For 2nd cell: eq(1) ⇒

$$V_{t2} = \epsilon_2 + i r_2 = 6 + (2 \times 0.9) = 7.8 \text{ V}$$

Problem 12.11 Voltmeter in circuit may be considered to be ideal. Values are $\epsilon = 15 \text{ V}$, internal resistance $r = 5 \Omega$, $R_1 = 100 \Omega$, $R_2 = 300 \Omega$. Calculate current in R_1 .

Solution

$$\epsilon = 15 \text{ V} \quad r = 5 \Omega \quad R_1 = 100 \Omega \quad R_2 = 300 \Omega$$

Current $i = ?$ through R_1

First we need to calculate equivalent resistance R_{eq} as the given circuit contains more than one resistors. Ideal voltmeter has infinite resistance, so there will be no current through it.

R_1 and R_2 are in parallel so their net resistance will be

$$R' = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{100 \times 300}{100 + 300} = 75 \Omega$$

Now this R' is in series with r in the circuit.

So we further simplify the circuit to find total resistance. So

$$R_{eq} = R' + r = 75 + 5 = 80 \Omega$$

Now from Ohm's law

$$i = \frac{\epsilon}{R_{eq}} = \frac{15}{80}$$

$$i = 0.1875 \text{ A}$$

Now this current " i " will pass through both r and R' . Potential drop across R' is the terminal potential difference V_t and is given by

$$V_t = i R' = 0.1875 \times 75$$

$$V_t = 14.06 \text{ V}$$

Now current through R_1 will be

$$i_1 = \frac{V_t}{R_1} = \frac{14.0625}{100}$$

$$i_1 = 0.1406 \text{ A (textbook needs correction)}$$

