

CIRCUIT ANALYSIS II

Sir Amjad Khattak

Engineering Circuit Analysis
by J David Irwin 10th edition


Alternating Current Circuits
by K V Tang 3rd edition.

Course Outline

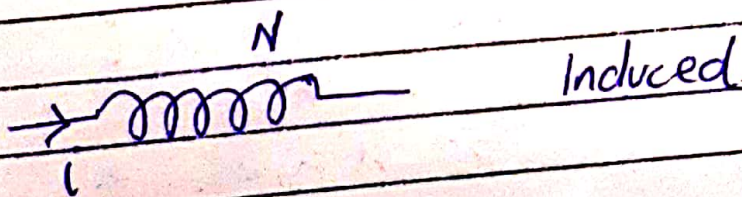
1. Magnetically Coupled Circuits.
2. 2 Port networks.
3. Laplace Transform and Its applications.
4. Transfer Functions / Poles / Zero diagrams.
5. Non sinusoidal waves analysis / Applications.
6. Filters.

Magnetically Coupled Circuits

Ampere's law \rightarrow current through a coil produces a magnetic field.



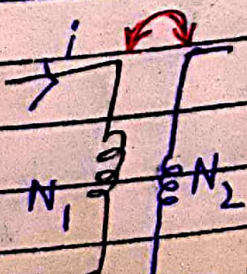magnetic flux induced due to changing current in a coil \rightarrow self induced \rightarrow self inductance $\rightarrow L \rightarrow$ unit: Henry



Flux in second coil due to first \rightarrow mutual inductance.


$$M_{12} = M_{21} = M$$

Ampere's Law:

When there is a flow of current, it will always be associated by a magnetic field.

Faraday's Law

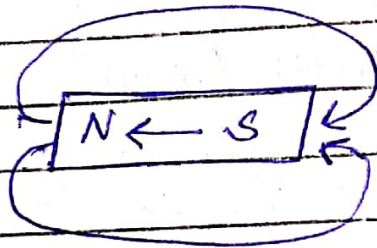If we have a magnetic field linked with a circuit (time varying magnetic field) it will induce emf in that circuit.



All the magnetic field lines complete their journey N-S independently.

Self Induction And Mutual Induction.

Flux And Flux Linkage (Φ and λ)

$$\lambda = N\Phi$$

We know that $\Phi \propto i$

$$\Rightarrow \lambda \propto i \Rightarrow \lambda = ki$$



$$k = \frac{\lambda}{i} = \frac{N\Phi}{i}$$

$k \Rightarrow$ inductance

$$L = \frac{N\Phi}{i}$$


unit = Henry (H)

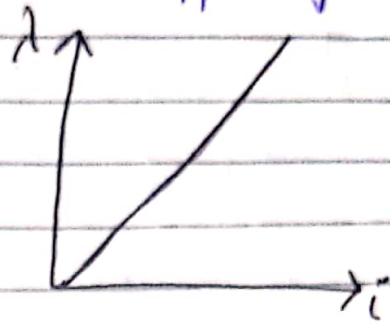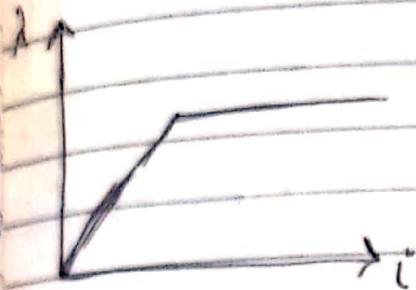Non magnetiz materials are those not attracted strongly by a magnet.
 eg wood, paper, water, copper, glass, gold and silver.



Magnetiz materials are those which are strongly attracted by a magnetiz eg iron, cobalt, nickel and their alloys.

Mutual Flux And Leakage Flux

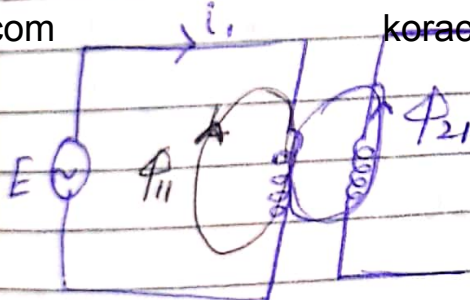


$$\Phi_1 = \Phi_{11} + \Phi_{21}$$

Φ_{11} → leakage flux.
 Φ_{21} → mutual flux

Direction of flux depends on;

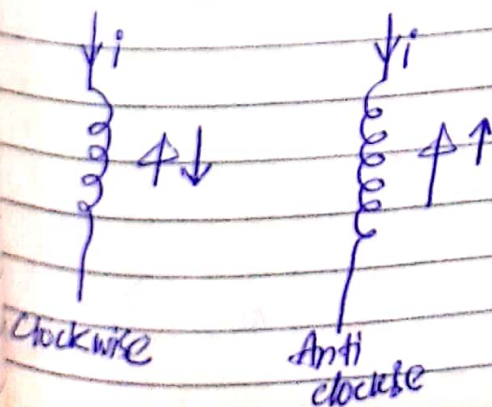- i) direction of current.
- ii) orientation of winding.



Self Inductance

$$L_1 = \frac{N_1 \Phi_1}{i_1} \quad L_2 = \frac{N_2 \Phi_2}{i_2}$$

Mutual Inductance

$$M = \frac{N_2 \Phi_{21}}{i_1} \text{ in coil 2}$$

$$M = \frac{N_1 \Phi_{12}}{i_2} \quad \text{in coil 1.}$$

Coefficient of Coupling (k)
 It is the measure of magnetic proximity of two coils.

$$k = \frac{\text{Mutual flux}}{\text{Total flux}} = \frac{\Phi_{21}}{\Phi_1}$$

$$0 \leq k \leq 1$$

$$\Phi_1 = \Phi_{11} + \Phi_{21}$$

$$\text{If } \Phi_{11} = 0 \Rightarrow \Phi_1 = \Phi_{21}$$

$$0.98 = \text{power transformers} \leftarrow k = 1$$

$$\text{Communication transformers } k = 0.5$$

↳ Here we want leakage flux.

Relationship B/w k, M, L₁, L₂

$$M = \frac{N_1 \Phi_{12}}{i_2} \rightarrow (1)$$

$$M = \frac{N_2 \Phi_{21}}{i_1} \rightarrow (2)$$

Multiply (1) and (2)

$$M^2 = \left(\frac{N_1 \Phi_{12}}{i_2} \right) \left(\frac{N_2 \Phi_{21}}{i_1} \right)$$

$$M^2 = \left(\frac{N_1 k \Phi_2}{i_2} \right) \left(\frac{N_2 k \Phi_1}{i_1} \right)$$

$$M^2 = k^2 \left(\frac{N_1 \Phi_1}{i_1} \right) \left(\frac{N_2 \Phi_2}{i_2} \right) \Rightarrow M = k^2 L_1 L_2$$

$$M = K \sqrt{L_1 L_2}$$

multiply by ω .

$$\omega M = K \omega \sqrt{L_1 L_2} = K \sqrt{\omega^2 L_1 L_2}$$

$$\omega M = K \sqrt{\omega L_1 \omega L_2}$$

$$X_m = K \sqrt{X_1 X_2}$$

Example 1.

Coil 1 of a pair of coupled coils has a constant current of 1 SA. The corresponding fluxes Φ_{11} and Φ_{21} are 20,000 and 40,000 maxwell. If the ratios are $N_1 = 200$ and $N_2 = 1500$.

Find L_1, L_2, M, K .

$$1 \text{ Wb} = 10^8 \text{ maxwell}$$

$$L_1 = \frac{N_1 \Phi_{11}}{i_1}$$

$$\text{As } \Phi_{11} = \Phi_{11} + \Phi_{21} = 60,000 \text{ maxwell} = 60,000 \times 10^{-8} \text{ Wb}$$

$$L_1 = 0.06 \text{ Henry}$$

$$K = \frac{N_2 \Phi_{21}}{\Phi_{11}} = \frac{40,000}{60,000} = \frac{4}{6} = \frac{2}{3}$$

$$M = \frac{N_2 \Phi_{21}}{i_1} = 0.12 \text{ H}$$

$$M = K \sqrt{L_1 L_2}$$


$$L_2 = 0.535 \text{ H}$$

Example 2

Two coupled coils of $L_1 = 0.8 \text{ H}$, $L_2 = 0.2$
have a $k = 0.9$. Find M and $\frac{N_1}{N_2}$.

Lecture 2

Voltage of Mutual Inductance

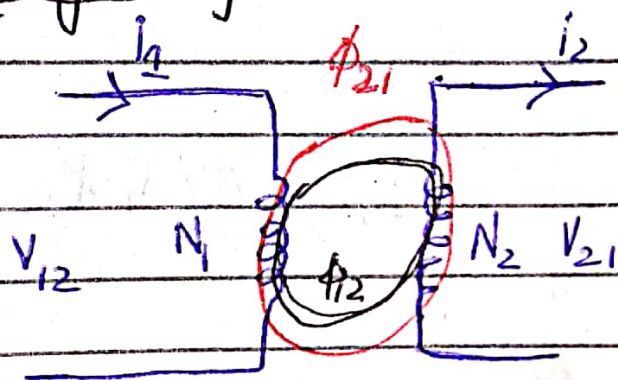

Faradays law $e = N \frac{d\phi}{dt}$

$$V_{21} = N_2 \frac{d\phi_{21}}{dt} \rightarrow (1)$$

$$V_{12} = N_1 \frac{d\phi_{12}}{dt} \rightarrow (2)$$

koracademy.com

koracademy.com

koracademy.com

$$M_{12} = M_{21} = M = \frac{N_2 \phi_{21}}{i_1} \Rightarrow M i_1 = N_2 \phi_{12} \rightarrow \text{differentiate}$$

$$\frac{M di_1}{dt} = N_2 \frac{d\phi_{12}}{dt} \Rightarrow V_{21} = M \frac{di_1}{dt} \rightarrow (3)$$


Similarly $M = \frac{N_1 \phi_{12}}{i_2} \Rightarrow M i_2 = N_1 \phi_{12} \rightarrow \text{differentiate}$

$$\frac{M di_2}{dt} = N_1 \frac{d\phi_{12}}{dt} \Rightarrow V_{12} = M \frac{di_2}{dt} \rightarrow (4)$$

Dot Rule

If both currents are directed towards the dot or away from the dot, then sign of the m term will be the same as that of the L terms.

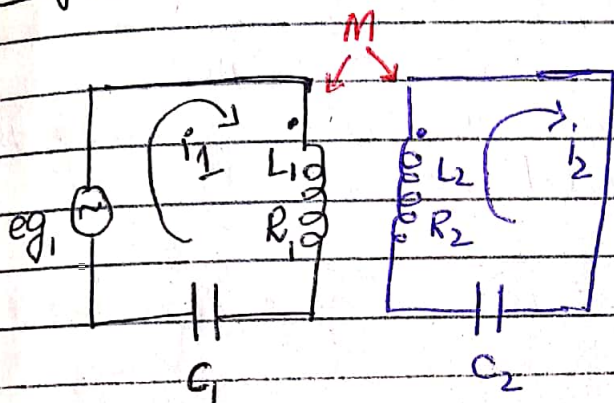Voltage Equation of Circuit With R, L, C, m



Instantaneous Equations

loop 1

$$E_{g1} = R_1 i_1 + L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int i_1 dt - m \frac{di_2}{dt}$$

$$i_1 dt - m \frac{di_2}{dt}$$

loop 2

$$0 = R_2 i_2 + L_2 \frac{di_2}{dt} + \frac{1}{C_2} \int i_2 dt - m \frac{di_1}{dt}$$

Steady state form

$$E_{g1} = R_1 I_1 + j\omega L_1 I_1 + \frac{1}{j\omega C_1} I_1 - j\omega M I_2$$

$$E_{g1} = \left(R_1 + j\omega L_1 + \frac{1}{j\omega C_1} \right) I_1 - j\omega M I_2 \rightarrow \textcircled{1}$$

$$0 = R_2 I_2 + j\omega L_2 I_2 + \frac{1}{j\omega C_2} I_2 - j\omega M I_1 \rightarrow \textcircled{2}$$

$$0 = (-j\omega M) I_1 + \left(R_2 + j\omega L_2 + \frac{1}{j\omega C_2} \right) I_2 \rightarrow \textcircled{3}$$

$$E_{g1} \textcircled{1} \Rightarrow Z_{11} I_1 - Z_m I_2 = E_{g1}$$

$$E_{g1} \textcircled{3} \Rightarrow -Z_m I_1 + Z_{22} I_2 = 0$$

$$\begin{bmatrix} E_{g1} \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & -Z_m \\ -Z_m & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

If we have n coupled circuits;

$$\begin{bmatrix} z_{11} & z_{12} & z_{13} & \dots & z_{1n} \\ z_{21} & z_{22} & z_{23} & \dots & z_{2n} \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ z_{n1} & \dots & \dots & \dots & z_{nn} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ \vdots \\ E_n \end{bmatrix}$$

Driving Point Impedance

$$z_{in} = \frac{E_{g1}}{I_1}$$

It is also known as input impedance

It is defined as the ratio of voltage

current at two specified points

$$I_1 = \begin{bmatrix} E_{g1} & -z_{1m} \\ 0 & z_{22} \end{bmatrix}$$


$$z_{11} z_{22} - z_{1m}^2$$

$$\Rightarrow z_{in} = \frac{E_{g1}}{I_1} \times \frac{z_{11} z_{22} - z_{1m}^2}{E_{g1} z_{22}}$$

$$z_{in} = z_{11} - \frac{z_{1m}^2}{z_{22}}$$

Transfer Impedance

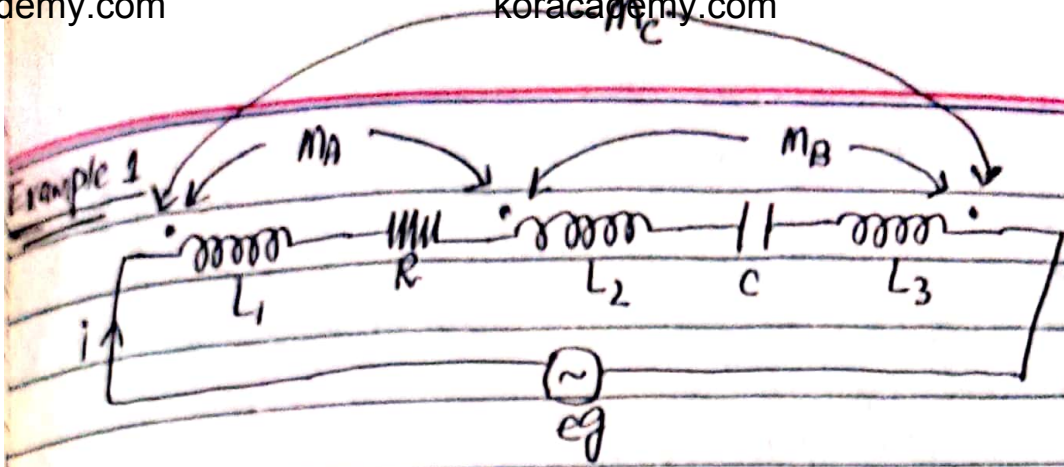Ratio of voltage in one part of circuit to current in the other part of circuit




Instantaneous eqs

$$e_g = Ri + L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \frac{1}{C} \int i dt + L_3 \frac{di}{dt} + M_A \frac{di}{dt}$$

$$- M_C \frac{di}{dt} + M_A \frac{di}{dt} - M_B \frac{di}{dt} - M_C \frac{di}{dt} - M_B \frac{di}{dt}$$

Steady state

Example 2

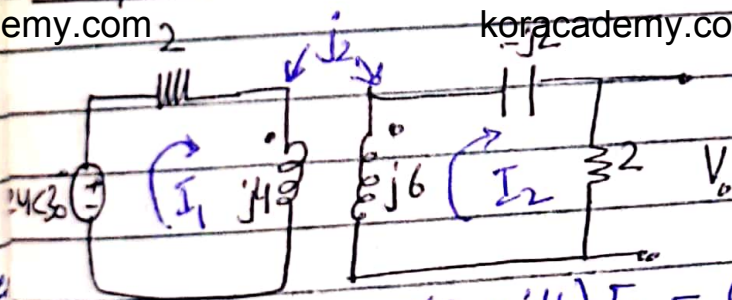


loop 1 $24\angle 30^\circ = (2 + j4)I_1 - (j2)I_2 \rightarrow \textcircled{1}$

loop 2 $0 = (-j2)I_1 + (2 + j4)I_2 \rightarrow \textcircled{2}$

$$\begin{bmatrix} 2 + j4 & -j2 \\ -j2 & 2 + j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 24\angle 30^\circ \\ 0 \end{bmatrix}$$

$$I_2 = \frac{\begin{vmatrix} 2 + j4 & 24\angle 30^\circ \\ -j2 & 0 \end{vmatrix}}{\begin{vmatrix} 2 + j4 & -j2 \\ -j2 & 2 + j4 \end{vmatrix}}$$

$$V_0 = 2I_2 = 5.36\angle 3.45^\circ$$

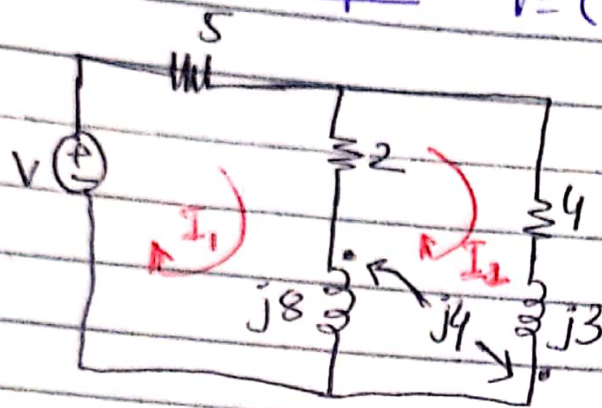

$$V = (7 + j8)I_1 - (2 + j8)I_2 \quad \text{--- (1)}$$

$$V = (7 + j8)I_1 - (2 + j2)I_2$$

loop 2


$$0 = (6 + j11)I_2 - (2 + j8)I_1 + j4I_2 + j4(I_2 - I_1) \quad \text{--- (2)}$$

$$0 = (-2 - j8 - j4)I_1 + (6 + j11 + j4 + j4)I_2$$

$$0 = (-2 - j12)I_1 + (6 + j19)I_2 \quad \text{--- (2)}$$

$$\begin{bmatrix} 7 + j8 & -(2 + j2) \\ -(2 + j12) & (6 + j19) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V \\ 0 \end{bmatrix}$$

Example 4

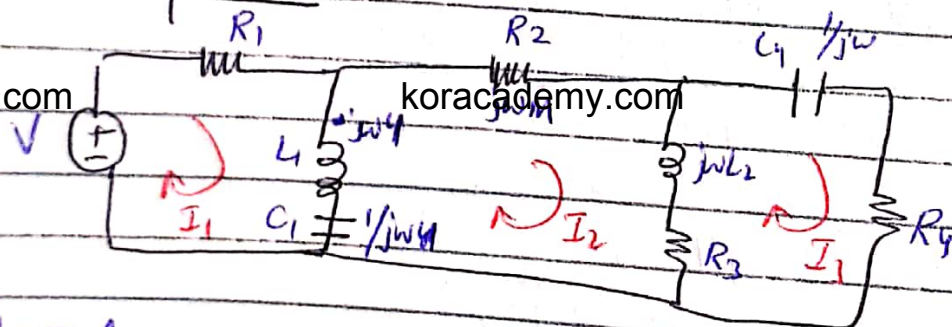

loop 1

$$V = (R_1 + jwL_1 + \frac{1}{jwC_1})I_1 + (-jwL_1 - \frac{1}{jwC_1})I_2 + jwM(I_2 - I_3)$$

$$V = (R_1 + jwL_1 + \frac{1}{jwC_1})I_1 + (-jwL_1 - \frac{1}{jwC_1} + jwM)I_2 - jwMI_3 \quad \text{--- (1)}$$

loop 2

$$0 = (R_2 + R_3 + jwC_1 + jwC_2 + \frac{1}{jwC_1})I_2 + (-jwL_1 - \frac{1}{jwC_1})I_1 + (-R_3 - jwL_2)I_3 - jwM(I_2 - I_3) - jwM(I_2 - I_1)$$

$$0 = (-j\omega L_1 - \frac{1}{j\omega C_1} + j\omega M) I_1 + (R_2 + R_3 + j\omega L_1 + j\omega L_2 + \frac{1}{j\omega C_1} - 2j\omega M) I_2 + (-R_3 - j\omega L_2 + j\omega M) I_3 \rightarrow (2)$$

Wop 3

$$0 = (R_3 + R_4 + j\omega L_2 + \frac{1}{j\omega C_4}) I_3 + (-j\omega L_2 + R_3) I_2 + j\omega M (I_2 - I_1)$$

$$0 = -j\omega M I_1 + (-R_3 - j\omega L_2 + j\omega M) I_2 + (R_3 + R_4 + j\omega L_2 + \frac{1}{j\omega C_4}) I_3 \rightarrow (3)$$

Two Port networks:

Z_{11} → open circuit input impedance
 Z_{22} → open circuit output impedance


Z_{12} and Z_{21} → Open circuit transfer impedance.

For any passive, linear and bilateral element


$$Z_{12} = Z_{21}$$

Linear elements are those elements whose value does not change with change in circuit or voltage.

Example 1

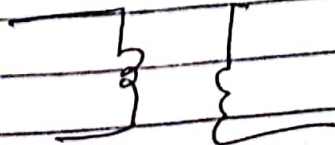

Determination of Y parameters.

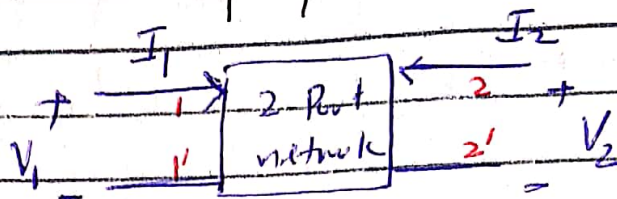


$$I_1 = Y_{11}V_1 + Y_{12}V_2 \rightarrow \textcircled{1}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \rightarrow \textcircled{2}$$

Short Circuit test

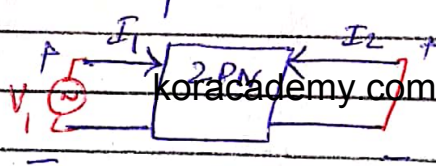
(i) Short output (2-2') and apply a source at (1-1') and find V_1, I_1, V_2, I_2



$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

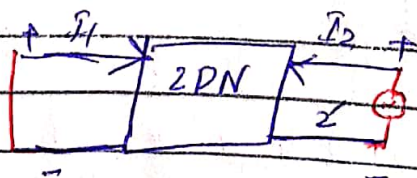(ii) Short input (1-1') and apply source at output (2-2')



$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$Y_{12} = Y_{21}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{|Y|} = \frac{Y_{22} I_1 - Y_{12} I_2}{|Y|}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$\Rightarrow Z_{11} = \frac{Y_{22}}{|Y|} \quad Z_{12} = -\frac{Y_{12}}{|Y|}$$

$$Z_{22} = \frac{Y_{11}}{|Y|} \quad Z_{21} = -\frac{Y_{21}}{|Y|}$$

ABCD parameters.

Lecture 5

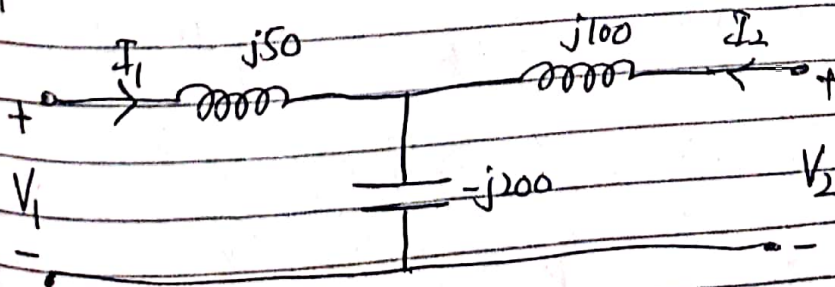Find (a) ABCD parameters. (b) Write expressions for the input values in terms of output values. (c) Write expressions for output values in terms of input values. (d) Show that $AD - BC = 1$.



$$\begin{aligned} (b) \quad V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$


$$V_2 = DV_1 - BI_1$$

$$I_2 = CV_1 - AI_1$$

(a) $A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow A = \frac{V_1}{V_1 \times \frac{-j200}{j50 - j200}} \Rightarrow A = \frac{j50}{-j150}$

$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{I_1}{I_1(-j200)} \Rightarrow C = \frac{j}{200}$

$B = \frac{-V_1}{I_2} \Big|_{V_2=0} \Rightarrow B = \frac{-V_1}{-I_1 \times \frac{-j200}{-j200 + j100}}$

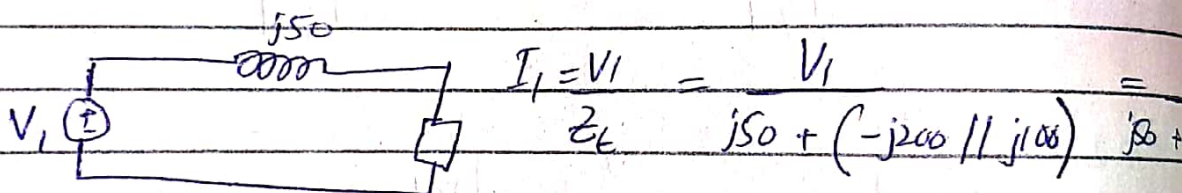

$\frac{V_1}{j50 + j200} = \frac{V_1}{j250} \Rightarrow B = \frac{V_1}{2 \times \frac{V_1}{j250}} = \frac{j250}{2}$

$D = \frac{-I_1}{I_2} \Big|_{V_2=0}$ Current source at input


$D = \frac{-I_1}{-I_1 \times \frac{-j200}{-j200 + j100}} = \frac{-j100}{-j200} \Rightarrow D = \frac{1}{2}$

(d) $\left(\frac{3}{4}\right)\left(\frac{1}{2}\right) - (j125)\left(\frac{j}{200}\right)$
 $= \frac{3}{8} + \frac{125 \times 1}{200 \times 2} = \frac{3}{8} + \frac{5}{8}$
 $= \frac{8}{8} = 1$ proved.

Series $\left\{ \begin{array}{l} \rightarrow \text{current is same} \\ \rightarrow \text{voltage divides.} \end{array} \right.$

Parallel $\left\{ \begin{array}{l} \rightarrow \text{current divides} \\ \rightarrow \text{voltage is same.} \end{array} \right.$


Current divider Rule

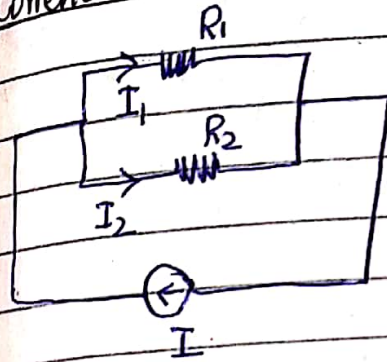

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$


Voltage Divider Rule.

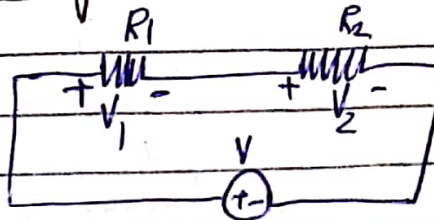

$$V_1 = V \frac{R_1}{R_1 + R_2}$$

$$V_2 = V \frac{R_2}{R_1 + R_2}$$

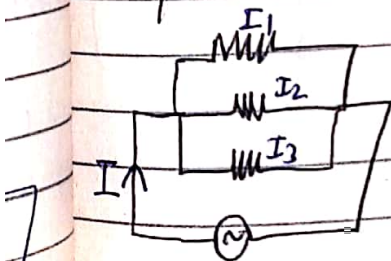If three resistors are connected in parallel.



$$I_1 = I \times \frac{(R_2 || R_3)}{R_1 + (R_2 || R_3)}$$

$$I_2 = I \times \frac{(R_1 || R_3)}{R_2 + (R_1 || R_3)}$$

$$I_3 = I \times \frac{(R_1 || R_2)}{(R_1 || R_2) + R_3}$$


If more than two resistors are connected in series;

$$V_3 = V \frac{R_3}{R_1 + R_2 + R_3}$$


and so on.

Interconnection of Two Port Networks

Parallel

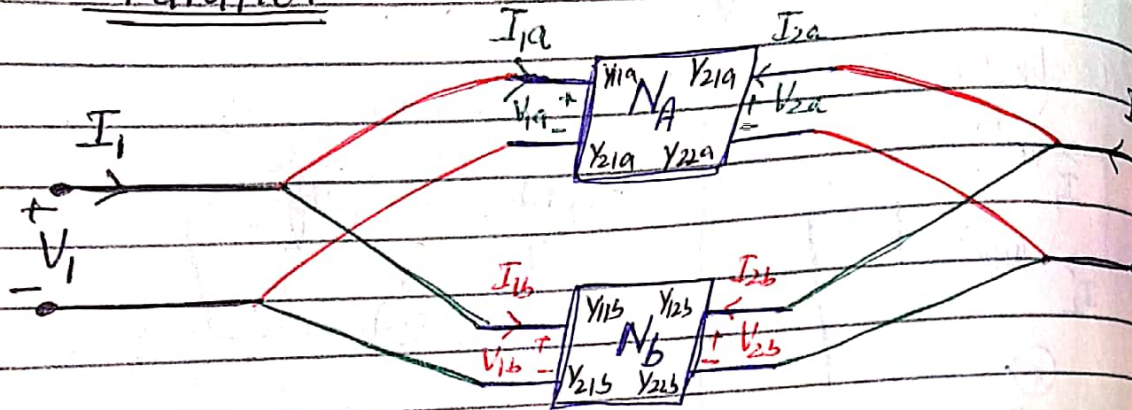

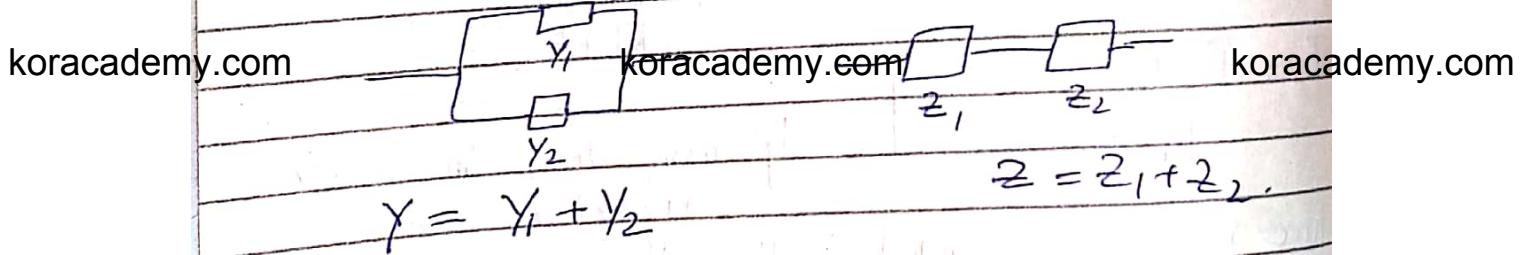
$$\begin{aligned}
 V_{1a} &= V_1 & V_{2a} &= V_2 & I_1 &= I_{1a} + I_{1b} \\
 V_{1b} &= V_1 & V_{2b} &= V_2 & I_2 &= I_{2a} + I_{2b}
 \end{aligned}$$



So

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_{11a} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix}$$

Series

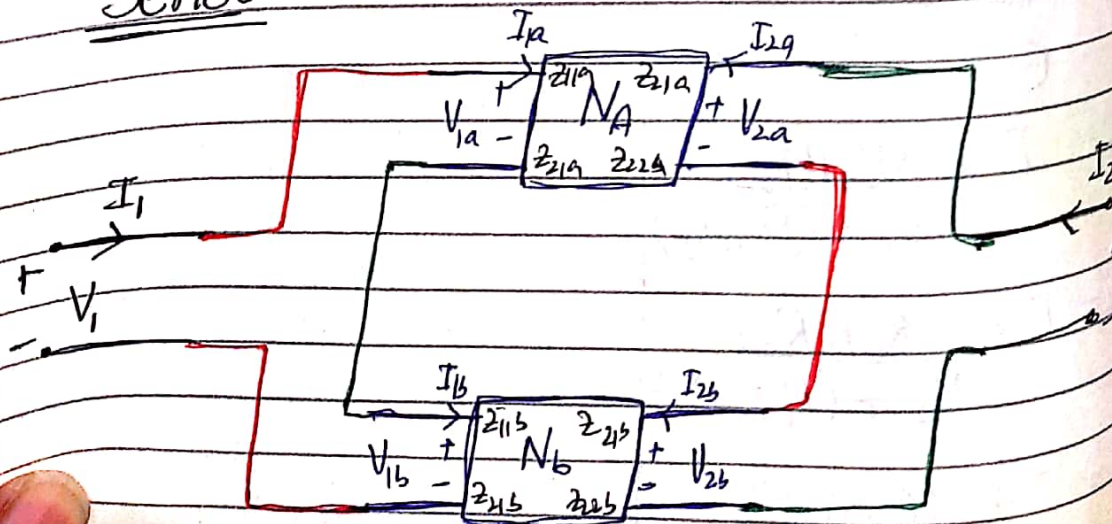


$$V_1 = V_{1a} + V_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} z_{11a} + z_{11b} & z_{12a} + z_{12b} \\ z_{21a} + z_{21b} & z_{22a} + z_{22b} \end{bmatrix}$$

Cascade



Where we connect output of one network with input of another network. for cascade we use ABCD parameters

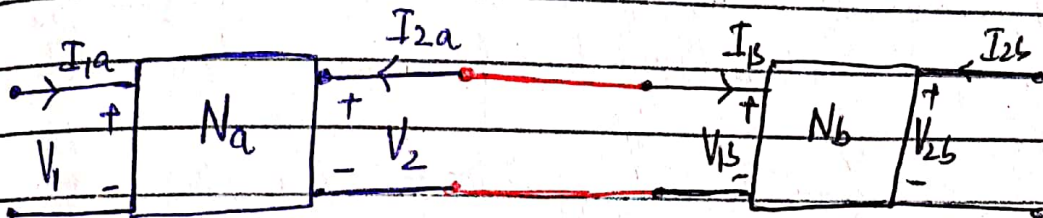


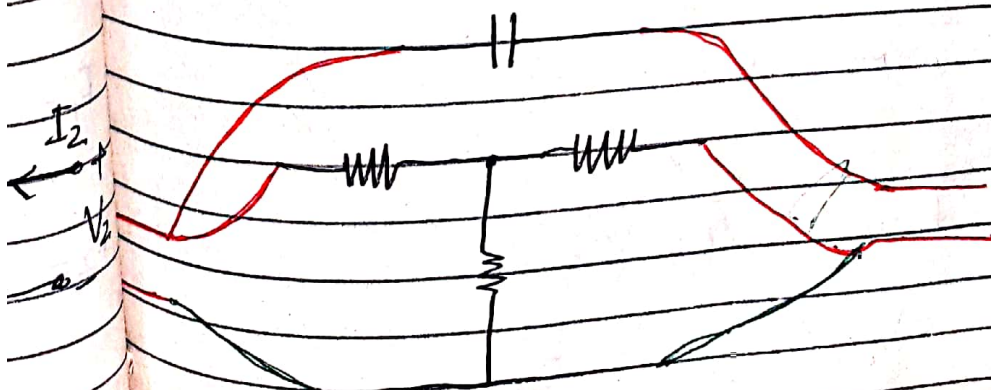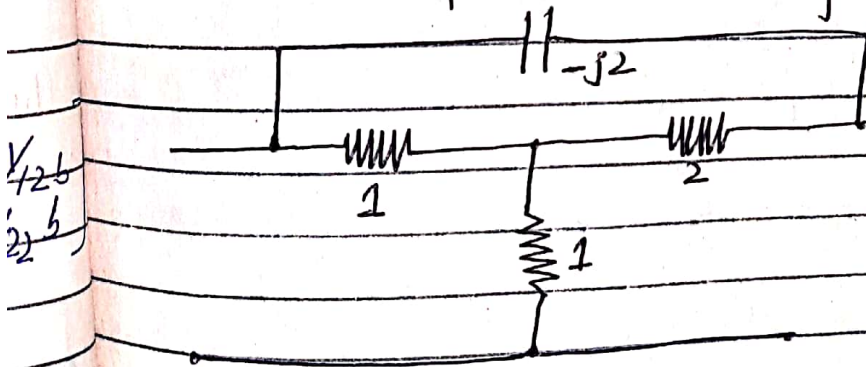Example 16.5

Find the Y parameters.

Consider it a parallel combination of two different networks.



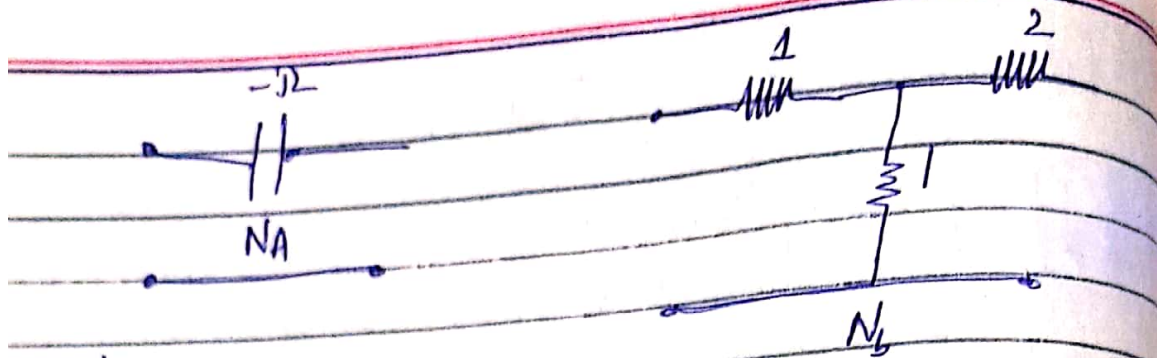


Nb

$$Y_{11b} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{V_1}{V_1 \left(1 + \frac{1 \times 2}{1+2}\right)} \Rightarrow Y_{11b}$$

$$Y_{21b} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{-I \times \frac{1}{3}}{V_1} = \frac{-V_1}{3V_1 \left(1 + \frac{1 \times 2}{1+2}\right)}$$

$Y_{21b} = -1/5$ seimen Also $Y_{12b} = -1/5$

koracademy.com $Y_{22b} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{I_2}{V_2 \left(2 + \frac{1 \times 1}{1+1}\right)} \Rightarrow Y_{22b}$ koracademy.com

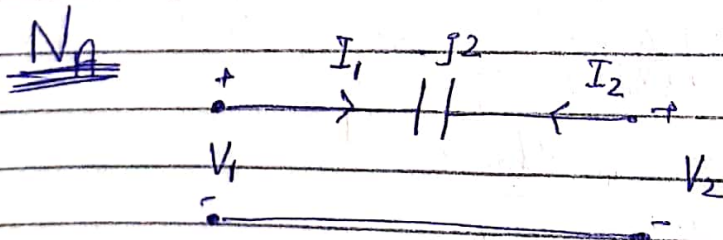

$$Y_{11a} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{V_1}{V_1 (-j2)} = \frac{j}{2} \text{ S}$$

Symmetrical network so $Y_{11} = Y_{22a} = j/2 \text{ S}$

$$Y_{12a} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{-V_2}{V_2 (-j2)} = \frac{-j}{2}$$

$$Y_{12a} = Y_{21a} = \frac{-j}{2} \text{ S}$$


$$Y_{11} = Y_{11a} + Y_{11b} = \left(\frac{j}{2} + \frac{3}{5} \right) s$$

$$Y_{12} = - \left(\frac{1}{5} + \frac{j}{2} \right) s$$


$$Y_{21} = - \left(\frac{1}{5} + \frac{j}{2} \right) s$$

$$Y_{22} = \left(\frac{j}{2} + \frac{3}{5} \right) s.$$

Example 16.6

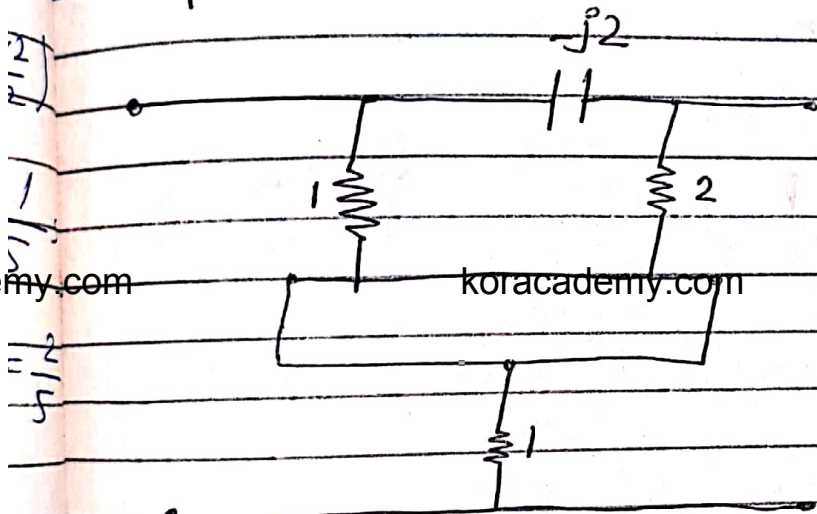

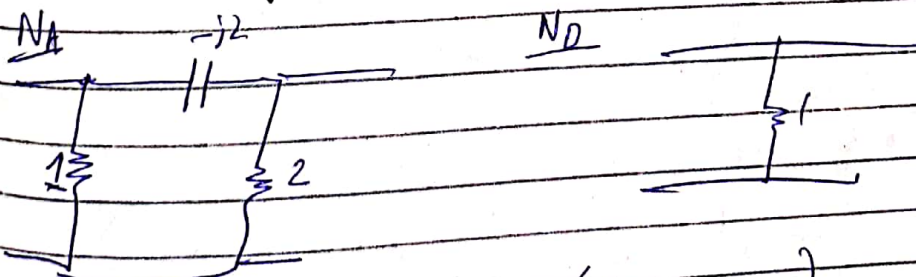Find 2 parameters by considering it to be series interconnection of two networks.



$$Z_{11a} = \frac{V_1}{I_1} \Big|_{Z_2=0} = \frac{I_1 \left((2-j2) \parallel 1 \right)}{I_1}$$

$$Z_{11a} = \frac{2-j2}{3-j2}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{I_1 \times \frac{1}{3-j2} \times 2}{I_1}$$

$$Z_{21} = \frac{2}{3-j2} \Omega$$

Linear, bilateral, passive so; $Z_{12} = Z_{21}$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \quad \text{with same st output}$$


$$= \frac{V_2}{\frac{V_2}{2 \parallel (1-j2)}} \quad Z_{22} = \frac{2-j4}{3-j2}$$


Nb
 $Z_{13} = Z_{33} = 1$

$$Z_{23} = Z_{32} = 1$$

total $Z_{11} = Z_{11c} + Z_{11s} = \frac{5-j4}{3-j2}$
 $Z_{22} = Z_{22c} + Z_{22s} = \frac{5-j2}{3-j2}$
 $Z_{31} = Z_{13} + Z_{31s} = \frac{5-j2}{3-j2}$
 $Z_{32} = Z_{23} + Z_{32s} = \frac{5-j6}{3-j2}$

Example 16.7

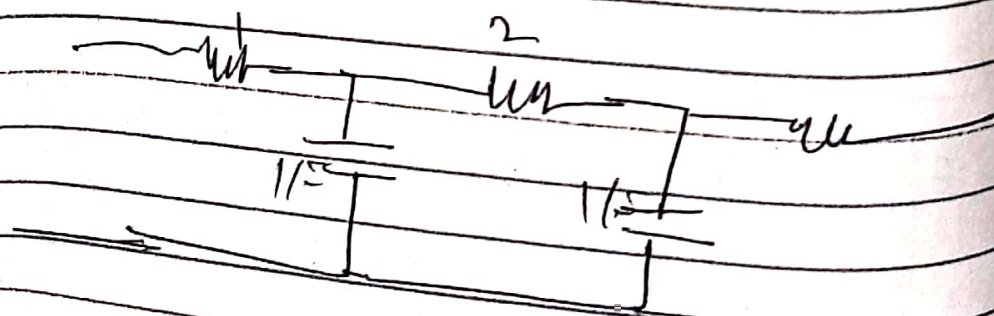

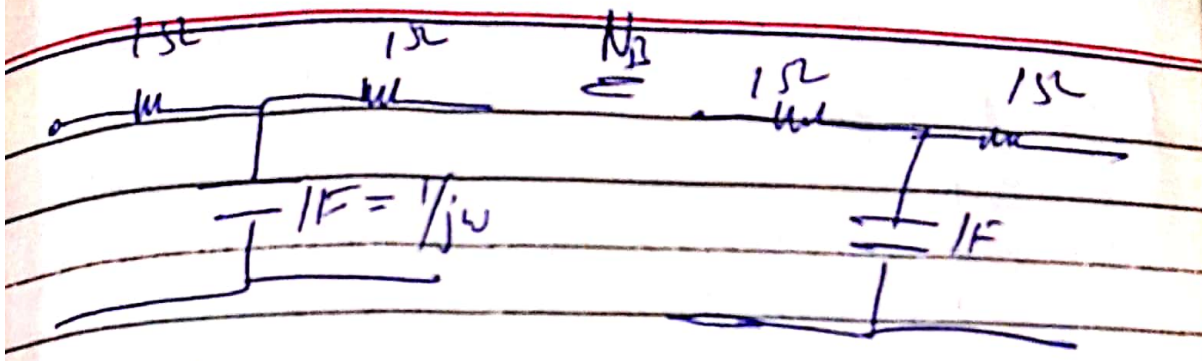

$$A_1 = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1 + j\omega = A_1$$

$$B_1 = \left. \frac{-V_1}{I_2} \right|_{V_2=0} = 2 + j\omega = B_1$$

$$C_1 = \left. \frac{I_1}{V_2} \right|_{I_2=0} = j\omega = C_1$$


$$D_1 = \left. \frac{-I_1}{I_2} \right|_{V_2=0} = 1 + j\omega = D_1$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + 4j\omega - 2\omega^2 & 4 + 6j\omega - 2\omega^2 \\ 2j\omega - 2\omega^2 & 1 + 4j\omega - 2\omega^2 \end{bmatrix}$$

lecture 6


Laplace Transforms

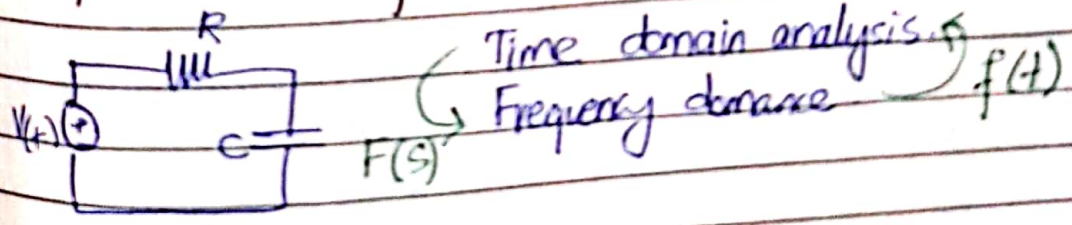

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt = \mathcal{L}\{f(t)\}$$

→ functions integrable in a specific time range.

Unit step function is a function that;

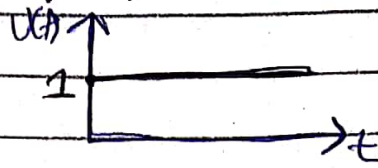

$$U(t) = 0 \quad t < 0$$

$$U(t) = 1 \quad t > 0$$

laplace transform $F(s) = \int_0^{\infty} U(t) e^{-st} dt$


$$= \int_0^{\infty} 1 e^{-st} dt = -\frac{1}{s} e^{-st} \Big|_0^{\infty} = -\frac{1}{s} (e^{-\infty} - e^{-s \cdot 0})$$

$$\Rightarrow F(s) = \frac{1}{s}$$

If time is from 0 to a.

$$\int_0^a 1 \cdot e^{-st} dt \Rightarrow F(s) = \frac{1 - e^{-sa}}{s}$$

Time shift

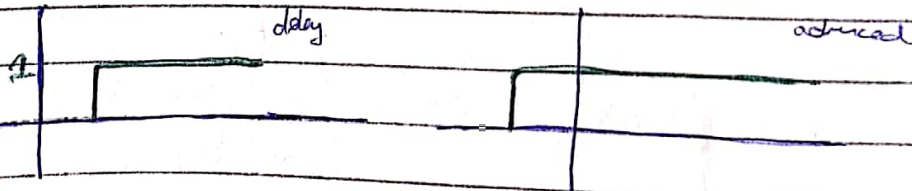

$$f(t) = U(t+a) \rightarrow \text{① Advance}$$

$$f(t) = U(t-a) \rightarrow \text{② Delay}$$

$$\int_a^{\infty} 1 e^{-st} dt = \frac{e^{-sa}}{s}$$

Inverse laplace transform. $F(s) \rightarrow f(t)$

Partial fraction.

$$F(s) = \frac{N_x(s)}{D_x(s)} = \frac{\text{Polynomial}}{\text{Polynomial}}$$

$m < n$

$$= \frac{s^m + a_1(m-1)s^{m-1} + a_2(m-2)s^{m-2} + \dots + a_0}{s^n + b_1(n-1)s^{n-1} + b_2(n-2)s^{n-2} + \dots + b_0}$$

$$F(s) = \frac{Ny}{(s-s_1)(s-s_2)(s-s_3)\dots}$$

$$F(s) = \frac{k_1}{(s-s_1)} + \frac{k_2}{(s-s_2)} + \frac{k_3}{(s-s_3)} + \dots$$

$$k_1 = F(s)(s-s_1) \Big|_{s=s_1}$$

$$k_2 = F(s)(s-s_2) \Big|_{s=s_2}$$

$$\Rightarrow f(t) = L^{-1} F(s)$$

eg. Distinct roots.

$$F(s) = \frac{s}{s^2 + 5s + 6} = \frac{k_1}{s+3} + \frac{k_2}{s+2}$$

$$k_1 = F(s)(s+3) \Big|_{s=-3} = \frac{s}{(s+2)} \Big|_{s=-3}$$

$$\frac{-3}{-3+2} \Rightarrow k_1 = 3$$

$$k_2 = \frac{s}{(s+3)} \Big|_{s=-2} = \frac{-2}{-2+3} \Rightarrow k_2 = -2$$

$$L^{-1} F(s) = L^{-1} \left(\frac{3}{s+3} - \frac{2}{s+2} \right)$$

$$f(t) = 3e^{-3t} - 2e^{-2t}$$

eg same roots.

$$F(s) = \frac{s+2}{s(s+1)^2(s+3)}$$

\downarrow $s = -1$
 \rightarrow $s = -1$

$$k_4 = \frac{d}{ds} \left[F(s) (s+1)^2 \right] \Big|_{s=-1}$$

$$\frac{d}{ds} \left[\frac{(s+2)}{s(s+1)^2(s+3)} \times (s+1)^2 \right] \Big|_{s=-1}$$

$$f(t) = \frac{2}{3} + \frac{1}{12} e^{-3t} - \frac{3}{4} e^{-t}$$

Complex Roots:

$$F(s) = \frac{s}{s^2 + 2s + 5} \rightarrow s = 1 \pm j2 \Rightarrow \begin{matrix} s_1 = 1 + j2 \\ s_2 = 1 - j2 \end{matrix}$$

$$F(s) = \frac{k_1}{\underbrace{s + 1 + j2}_{s_1}} + \frac{k_2}{\underbrace{s + 1 - j2}_{s_2}}$$

$$k_1 = F(s) (s + 1 + j2) \Big|_{s = -1 - j2} \quad k_2 =$$

$$e^{-t} \left(\frac{e^{j2t}}{2} + \frac{e^{-j2t}}{2} - \frac{1}{2} \times \frac{e^{j2t} - e^{-j2t}}{2j} \right)$$

$$e^{-t} \left(\cos 2t - \frac{1}{2} \sin 2t \right)$$

Laplace transform is an important technique in circuit for a given set of initial conditions. It will yield the total response of a circuit consisting of both the natural and forced responses. In one operation,

Using the Laplace transform we transform the circuit problem from time domain into complex frequency domain and finally we transfer the solution to time domain.


Laplace transform is an integral transform that convert a set of linear, simultaneous, integro-differential to a set of simultaneous algebraic equations.

complementary function \rightarrow natural / transient response
particular integral \rightarrow forced / steady state response

pg 672

$$L\left(\frac{d}{dt} f(t)\right) = sF(s) - f(0^+)$$
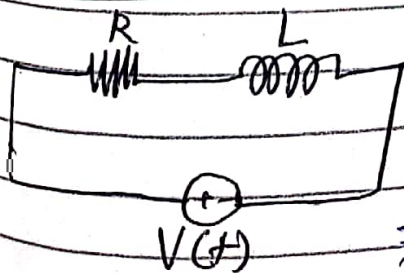
$$L\left(\int f(t) dt\right) = \frac{F(s)}{s} + \frac{f^{-1}(0^+)}{s}$$




$$V(t) = R i(t) + L \frac{di(t)}{dt}$$

$$\frac{V}{s} = R I(s) + L(s I(s) - i(0^+))$$

$$\frac{V}{s} = (R + sL) I(s)$$

$$I(s) = \frac{V/s}{R + sL} = \frac{V(s)}{s(R + sL)}$$

Draw s domain circuit

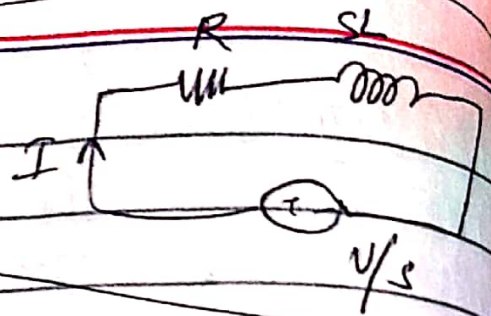

$$I(s) = \frac{V/L}{s(s+R/L)} = \frac{k_1}{s} + \frac{k_2}{s+R/L}$$

$$k_1 = \frac{V}{R} \quad k_2 = \frac{-V}{R}$$

$$I(s) = \frac{V/R}{s} + \frac{-V/R}{s+R/L}$$

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-R/L t}$$

$$V_L = L \frac{di}{dt} = L \left(0 - \frac{V}{R} \left(\frac{-R}{L} \right) e^{-R/L t} \right)$$


$$V_L = V e^{-R/L t} = V e^{-t/\tau}$$

$$\tau = \frac{L}{R}$$

Final
code 1




$$V = IR$$

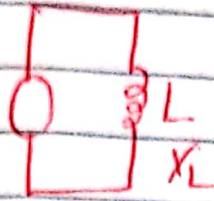

$$V = L \frac{di}{dt}$$

$$Z = R + j\omega L$$

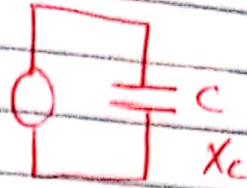


$$V_C = \frac{1}{C} \int i dt$$

$$Z = R + j\omega C$$

1st order equations.

Non linear behavior.

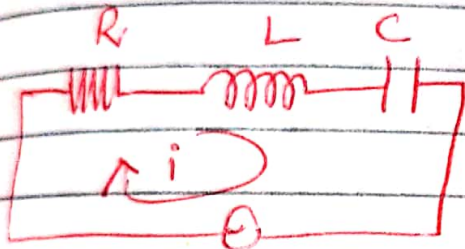

$$V(t)$$


Time domain eq; KVL

$$V(t) = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

Generally $j\omega \equiv s$ domain.

Frequency response.
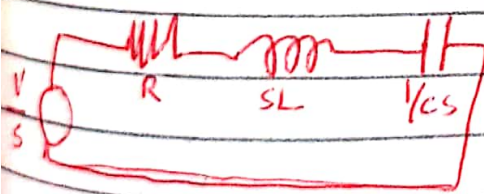
$$\frac{V}{s} = sLI(s) + \frac{1}{Cs} I(s) + R I(s)$$



$$\frac{V}{s} = I(s) \left\{ R + sL + \frac{1}{Cs} \right\}$$

$$I(s) = \frac{V/s}{R + sL + \frac{1}{Cs}}$$

$$T(s) = \frac{V/L}{(s^2 + \frac{R}{L}s + \frac{1}{LC})} \rightarrow \text{laplace transform}$$

$$s = \frac{-R/L \pm \sqrt{(R/L)^2 - 4(1/LC)}}{2}$$

$$s = \alpha \pm \beta$$

$$\textcircled{1} \left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$


$$I(s) = \frac{k_1}{s - (\alpha + \beta)} + \frac{k_2}{s - (\alpha - \beta)}$$

Inverse Laplace;

$$L^{-1} I(s) = i(t) = k_1 e^{(\alpha + \beta)t} + k_2 e^{(\alpha - \beta)t}$$

$$i(t) = e^{\alpha t} (k_1 e^{\beta t} + k_2 e^{-\beta t})$$

Overdamped

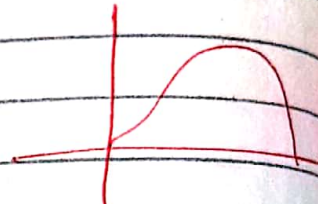

$$\textcircled{2} \left(\frac{R}{2L}\right)^2 < \frac{1}{LC} \text{ underdamped imaginary}$$

$$\textcircled{3} \left(\frac{R}{2L}\right)^2 = \frac{1}{LC} \text{ critically damped}$$

$$R^2 = \frac{4L^2}{LC} \Rightarrow R_{cr} = 2\sqrt{\frac{L}{C}}$$

Damping ratio $\xi = \text{zeeta} = \frac{R}{R_c}$

$$\omega \xi = \frac{R}{2\sqrt{L/C}}$$

showing it in terms of frequency;

$$2\omega_n \xi = \frac{2R}{2\sqrt{L/C}} \times \frac{1}{\sqrt{LC}}$$

↳ natural frequency.

$$2\omega_n \xi = \frac{R}{L}$$

As the characteristic equation is;

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Showing in terms of natural frequency

$$s^2 + 2\omega_n \xi s + \omega_n^2 = 0$$

$$s = \frac{-2\omega_n \xi \pm \sqrt{4\omega_n^2 \xi^2 - 4\omega_n^2}}{2}$$

$$s_1 = -\omega_n \xi + \omega_n \sqrt{\xi^2 - 1}$$

$$s_2 = -\omega_n \xi - \omega_n \sqrt{\xi^2 - 1}$$

$$i(t) = k_1 e^{(-\omega_n \xi + \omega_n \sqrt{\xi^2 - 1})t} + k_2 e^{(-\omega_n \xi - \omega_n \sqrt{\xi^2 - 1})t}$$

i) $\xi > 1$ overdamped.


koracademy.com $\xi < 1$ underdamped koracademy.com

koracademy.com

ii) $\xi = 0$ Oscillating

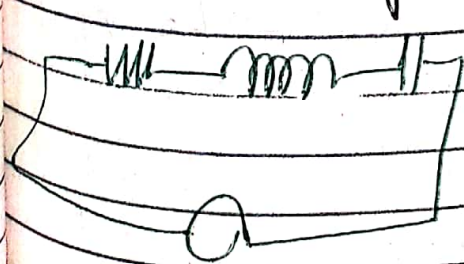iii) $\xi = 1$ critically damped.

Q. A series RLC circuit with $R = 100 \Omega$, $L = 0.1 \text{ H}$, $C = 100 \mu\text{F}$ has a DC voltage source of 200V applied at $t = 0$. Find the expression for transient current by assuming initial relaxed condition.



relaxed $\Rightarrow i_L(0) = 0$
 $V_C(0) = 0$

$$V(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i dt$$

$$200 \text{ V} = 100 i(t) + 0.1 \frac{di}{dt} + \frac{10^6}{100} \int i dt$$

laplace

$$\frac{200}{s} = 100 I(s) + 0.1 [s I(s) - i(0^+)]$$

$$\frac{200}{s} = \left(100 + 0.1s + \frac{10^4}{s} \right) I(s)$$

$$I(s) = \frac{200/s}{0.1s + 100 + 10^4/s} = \frac{2000}{0.1s^2 + 100s + 10^4}$$

$$I(s) = \frac{2000}{s^2 + 1000s + 10^5}$$

$$\rightarrow s_1 = -112.7$$

$$\rightarrow s_2 = -887.3$$

$$I(s) = \frac{2000}{(s+112.7)(s+887.3)} = \frac{K_1}{s+112.7} + \frac{K_2}{s+887.3}$$

$$K_1 = \frac{I(s)(s+112.7)}{s=-112.7} = \frac{2000}{s+887.3} \Big|_{s=-112.7}$$

$$K_1 = 2.58$$

$$K_2 = \frac{I(s)(s+887.3)}{s=-887.3} = \frac{2000}{s+112.7} \Big|_{s=-887.3}$$

$$K_2 = -2.58$$

$$I(s) = \frac{2.58}{s+112.7} - \frac{2.58}{s+887.3}$$

$$i(t) = 2.58 e^{-112.7t} - 2.58 e^{-887.3t}$$

Example 2 $C = ?$ in previous example will make the system critically damped \rightarrow Also find the transient current using this value of C .

For critical $\frac{R^2}{4L^2} = \frac{1}{LC}$


$$C = \frac{4L^2}{R^2 L} \Rightarrow C = \frac{4L}{R^2} = \frac{4 \times 0.1}{(100)^2}$$

$$C = 40 \mu F$$

\downarrow $i(t) = 2000t e^{-500t}$ Ans.

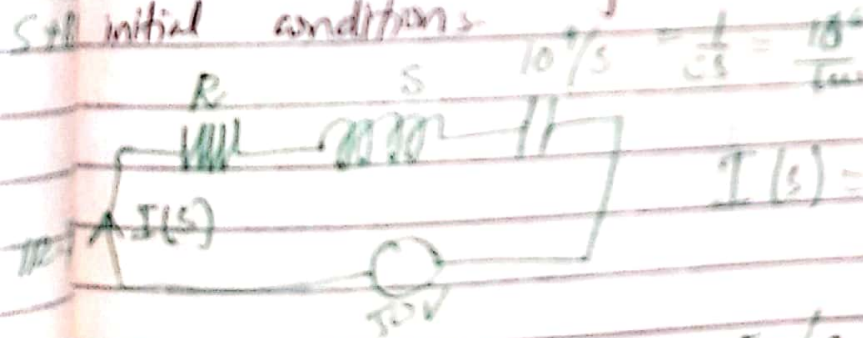Example 3 Series RLC with $R = 300 \Omega$ $L = 1 H$ and $C = 100 \mu F$ $V = 50V$ applied at $t = 0$.

Find the max value of current by assuming zero initial conditions.



$$I(s) = \frac{V(s)}{Z(s)}$$

$$= \frac{50/s}{300 + s + 10^5/s}$$

$$I(s) = \frac{50}{s^2 + 300s + 10^4} \quad s = -38.19, -261.8$$

$$I(s) = \frac{50}{(s + 38.19)(s + 261.8)} = \frac{k_1}{s + 38.19} + \frac{k_2}{s + 261.8}$$

$$k_1 = 0.2236 \quad k_2 = -0.2236$$

$$I(s) = \frac{0.2236}{s + 38.19} - \frac{0.2236}{s + 261.8}$$

$$i(t) = 0.2236 e^{-38.19t} - 0.2236 e^{-261.8t}$$

$$i(t) = 0.2236 \left[e^{-38.19t} - e^{-261.8t} \right]$$

derivate = 0 \Rightarrow time \rightarrow in factory \rightarrow f_u ms

$$\Rightarrow \frac{di(t)}{dt} = 0$$

$$\Rightarrow 0.2236 \left[e^{-38.19t} (-38.19) - e^{-261.8t} (-261.8) \right]$$

koracademy.com

koracademy.com

koracademy.com

$$\Rightarrow 0 = -38.19 e^{-38.19t} + 261.8 e^{-261.8t}$$

$$38.19 e^{-38.19t} = 261.8 e^{-261.8t}$$

$$e^{-38.19t + 261.8t} = \frac{261.8}{38.19}$$

$$e^{223.61t} = 6.855$$

$$223.61 t = \ln(6.855)$$


$$\Rightarrow t = 0.00861 \text{ s}$$

$$\Rightarrow i(t)_{\text{max}} = 0.137 \text{ A}$$

Transfer functions / System Response / Behavior etc

$$T.F = \frac{\text{Laplace transform of output}}{\text{Laplace transform of input}}$$

With the initial conditions as zero.

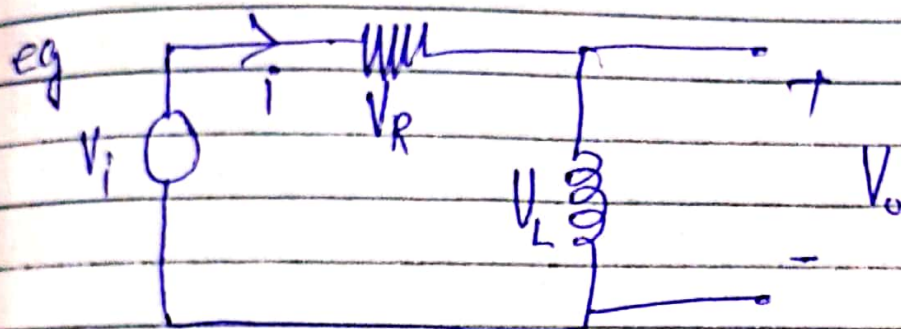


$$T.F = \frac{V_o}{V_i} \quad \text{Voltage gain}$$

$$T.F = \frac{I_o}{I_i} \quad \text{Current gain}$$

$$\frac{V_o}{I_i} = \text{Transfer impedance}$$

$$\frac{I_o}{V_i} = \text{Transfer admittance}$$
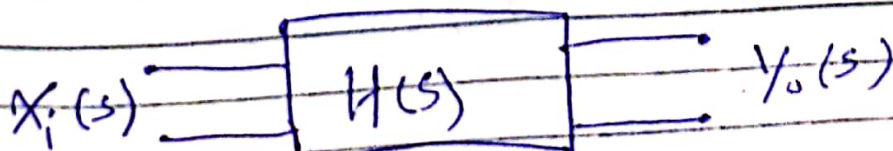
$$H(s) = \frac{\text{output}}{\text{input}} = \frac{Y_o(s)}{X_i(s)}$$



$$\frac{Y_o(s)}{X_i(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + a_{m-2} s^{m-2} + \dots + a_0}{b_n s^n + b_{n-1} s^{n-1} + b_{n-2} s^{n-2} + \dots + b_0}$$

The roots;

$$= \frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_m)}$$

Two extremes


$z \rightarrow s$ Zeros of the system (no response)

$p \rightarrow s$ Poles of the system

$$\text{let } H(s) = \frac{s+2}{s+5}$$

$$\text{Zero} = -2 = -2 + 0j\omega$$
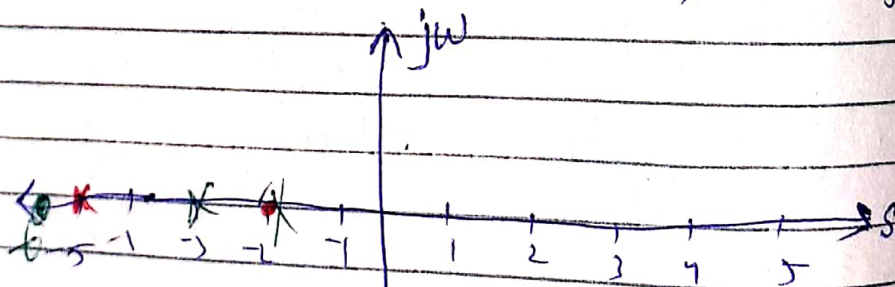
$$\text{Poles} = X = 0, -5 = 0, -5 + 0j\omega$$



Poles zero plot

let a system with

$$H(s) = \frac{s+6}{(s+2)(s+3)}$$

$$\text{Zero} = -6$$



$$\text{Poles} = -2, -3$$

Pde zero diagram deals with the stability of the system.

Stability?

How system reacts to events.

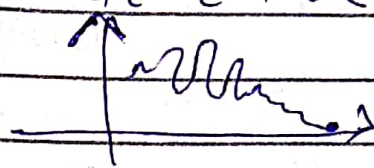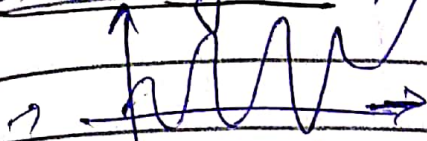→ Stable system $\Rightarrow f(t) \rightarrow 0$ at $t \rightarrow \infty$




→ Unstable system

$\Rightarrow f(t) \rightarrow \infty$ at $t \rightarrow \infty$

→ marginally stable

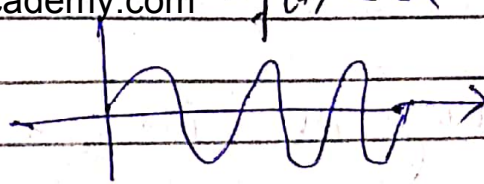
oscillating system $\Rightarrow 0 < f(t) < \infty$




$$W \quad H(s) = \frac{1}{s+a}$$

$$L^{-1}[H(s)] = h(t) = e^{-at}$$


if $a > 0$ $h(t) = e^{-at}$

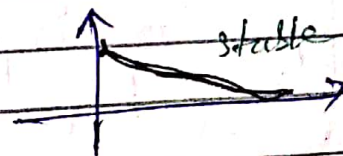


if $a = 0$ $h(t) = 1$

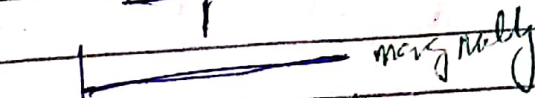

if $a < 0$ $h(t) = e^{at}$

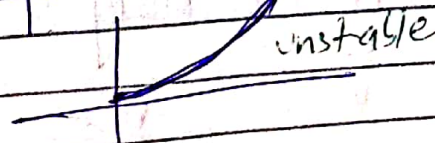

Ex 14.3

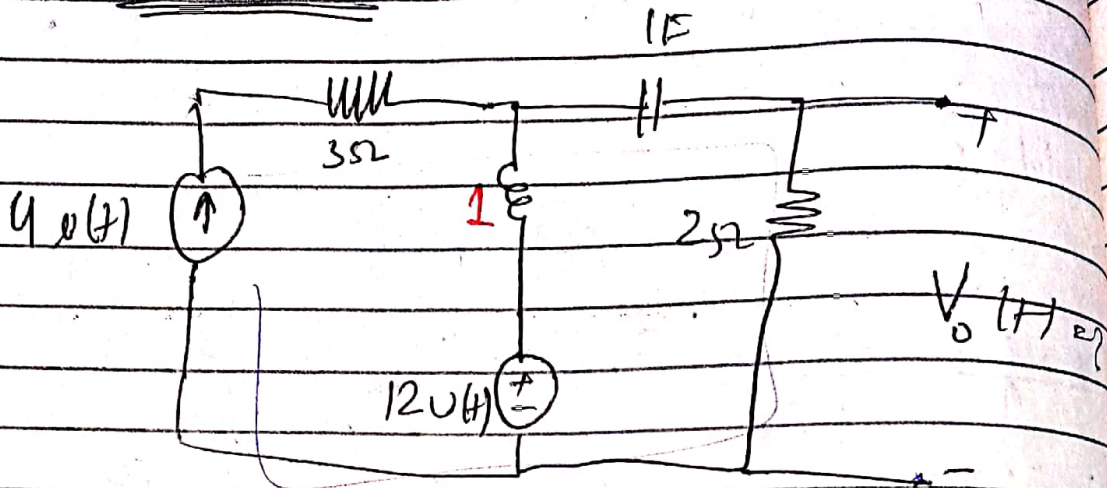


For $t < 0$ $i_L(0) = 0$ $V_C(0) = 0$

$U(t)$ means start at $t = 0$.

$U(t-2)$ means start at $t = 2$. \rightarrow delay

$U(t+2)$ means start at $t = -2$. \rightarrow advance

Drawing the circuit in s domain;

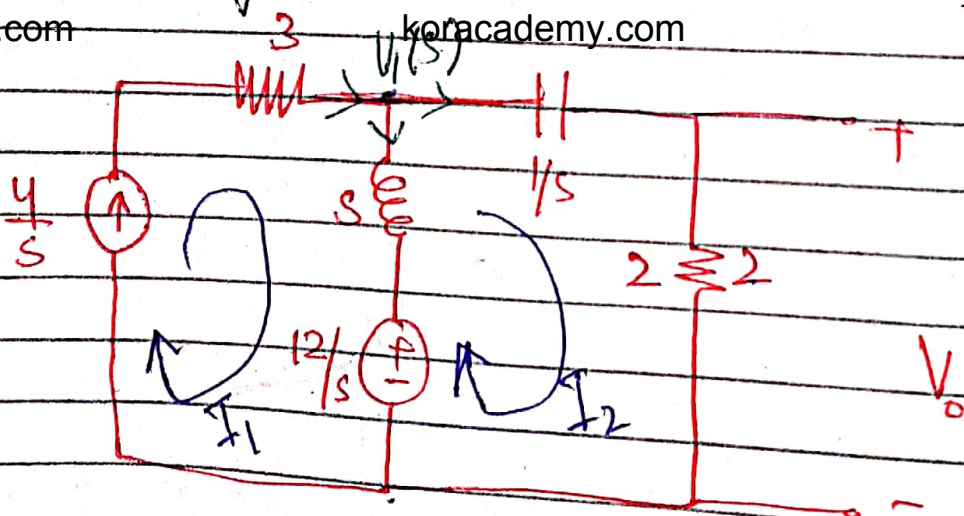

① Nodal Analysis

KCL

$$\frac{4}{s} = \frac{V_1(s)}{2 + 1/s} + \frac{V_1(s) - 12/s}{s}$$

$$\frac{4}{s} = V_1(s) \left(\frac{1}{2 + 1/s} + \frac{1}{s} \right) - \frac{12}{s^2}$$

$$\frac{4}{s} + \frac{12}{s^2} = V_1(s) \left(\frac{s}{2s+1} + \frac{1}{s} \right)$$

$$\frac{4s+12}{s^2} = V_1(s) \left(\frac{s^2+2s+1}{s(2s+1)} \right)$$

$$V_1(s) = \frac{(4s+12)(2s+1)}{s(s^2+2s+1)}$$

$$V_0(s) = V_1(s) \times \frac{2}{2+1/s}$$

$$= \frac{4(s+3)(2s+1)}{s(s^2+2s+1)} \times \frac{2}{(2s+1)}$$

$$V_0(s) = \frac{8(s+3)}{s^2+2s+1}$$

$$V_0(s) = \frac{8(s+3)}{(s+1)^2}$$

Mesh is the smallest possible loop.

② Mesh Analysis

$$I_1 = \frac{4}{s}$$

$$\frac{12}{s} = -sI_1 + \left(s + 2 + \frac{1}{s} \right) I_2$$

$$\frac{12}{s} = -s \times \frac{4}{s} + \left(\frac{s^2+2s+1}{s} \right) I_2$$


$$I_2 = \frac{4(s+3)}{(s+1)^2}$$

$$V_o(s) = 2 I_2(s)$$

$$\Rightarrow V_o(s) = \frac{8(s+3)}{(s+1)^2}$$

③ Superposition theorem

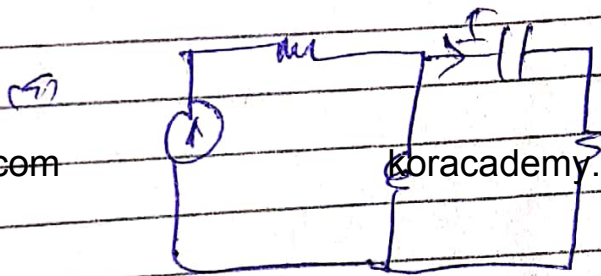
If you have more than one sources in a circuit; consider only one source at a time and make all other sources zero (if source is open ckt and if source is short ckt) and finally the answer (output) will be sum of all the answers (outputs).



$$V_o = 2 I_1$$

$$= 2 \times 4 \times \frac{s}{s+2+1/s}$$

$$V_o = \frac{8s}{s^2 + 2s + 1}$$

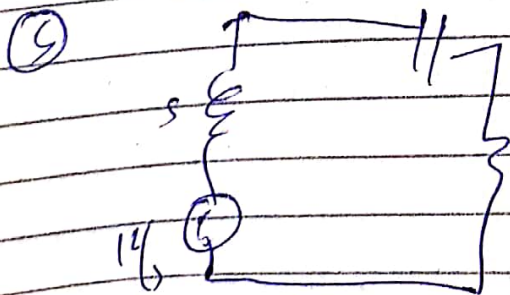


$$V_o(s) = \frac{12}{s} \times \frac{2}{s+2+1/(2s)}$$

$$= \frac{24s}{s(s^2 + 2s + 1)}$$

$$V_o(s) = \frac{24}{s^2 + 2s + 1}$$

$$V_o(s) = V_{o1}(s) + V_{o2}(s) = \frac{8(s+3)}{(s+1)^2}$$

Source Conversion

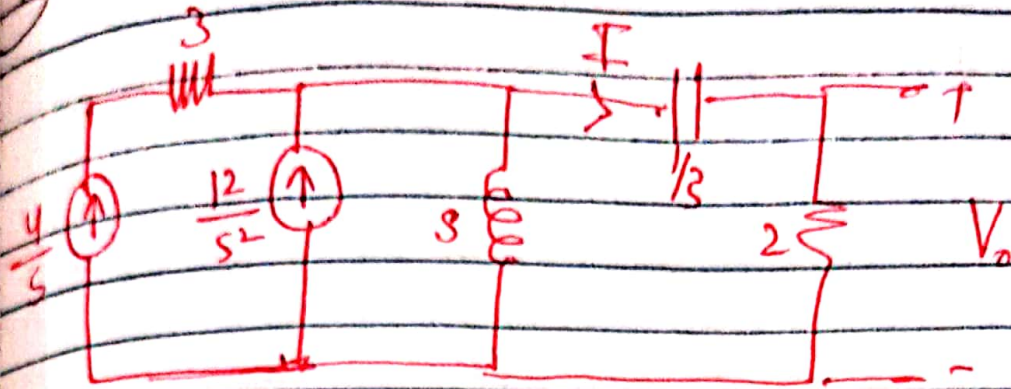


$$V_o(s) = 2I$$

$$= 2 \left(\frac{4}{s} + \frac{12}{s^2} \right) \left(\frac{s}{s + 2 + 1/s} \right)$$

$$= 2 \left(\frac{4s + 12}{s} \right) \left(\frac{s^2}{s^2 + 2s + 1} \right)$$

$$V_o(s) = \frac{8(s+3)}{(s+1)^2}$$

(5) Thevenin theorem

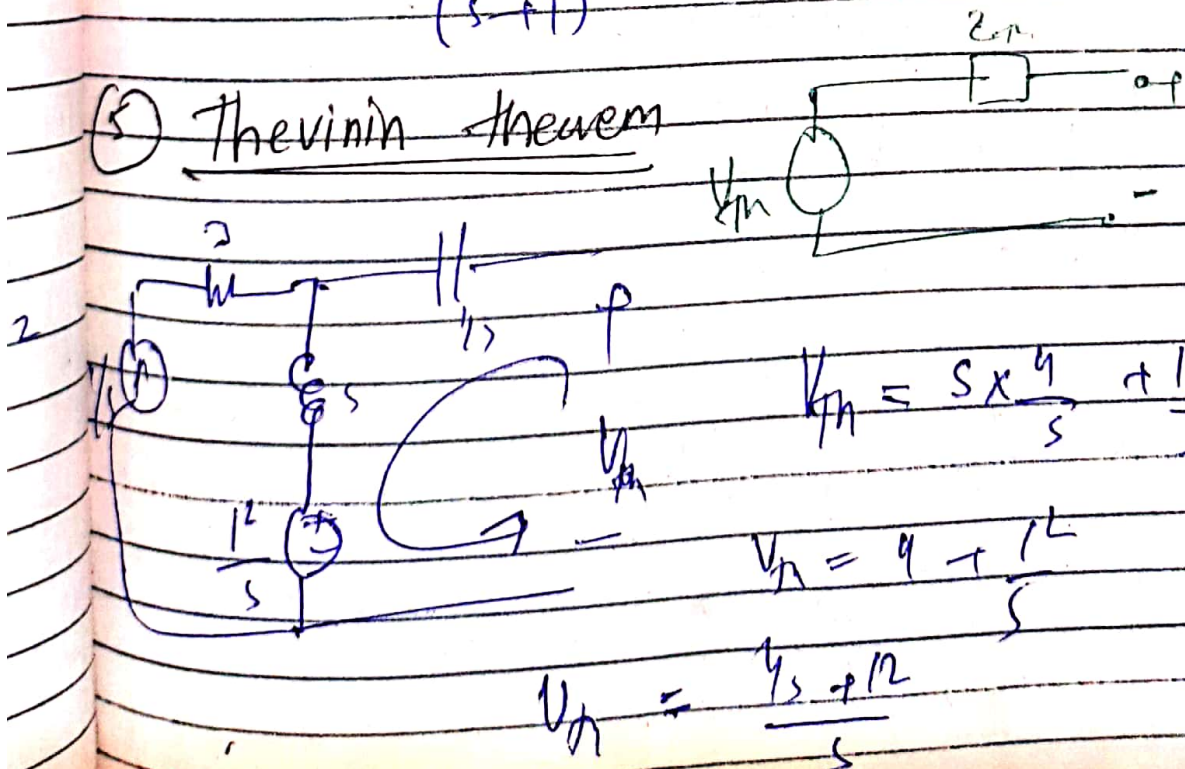


$$V_{th} = s \times \frac{4}{s} + \frac{12}{s}$$

$$V_{th} = 4 + \frac{12}{s}$$

$$V_{th} = \frac{4s + 12}{s}$$
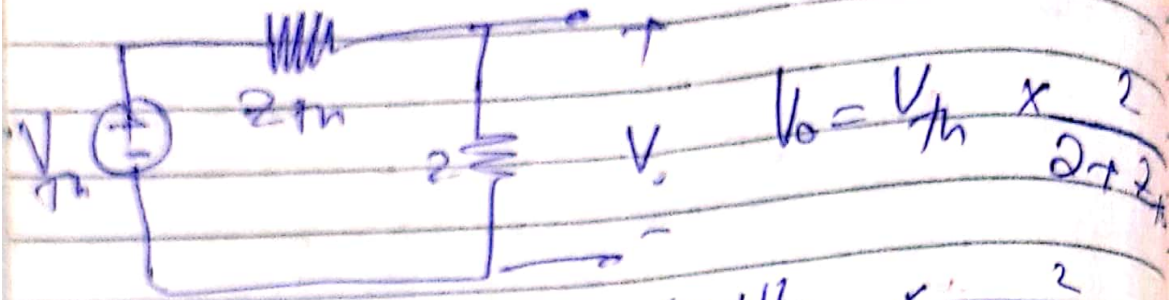
$$Z_{Th} = s + \frac{1}{s} = \frac{s^2 + 1}{s}$$



$$V_o = V_{Th} \times \frac{2}{2 + \frac{s^2 + 1}{s}}$$

$$= \frac{4s + 12}{s} \times \frac{2s}{s^2 + 2s + 1}$$

$$V_o(s) = \frac{8(s+3)}{(s+1)^2}$$

Newton's

Changing to time domain

$$V_o(s) = \frac{8(s+3)}{(s+1)^2} = \frac{k_1}{(s+1)^2} + \frac{k_2}{(s+1)}$$

$$k_1 = V_o(s) \cdot (s+1)^2 \Big|_{s=-1}$$

$$= 8(s+3)$$

$$\Rightarrow k_1 = 16$$

$$k_2 = \frac{1}{1!} \times \frac{d}{ds} \left(V_o(s) \cdot (s+1)^2 \right) \Big|_{s=-1}$$

$$k_n = \frac{1}{(n-1)!} \frac{d^{n-1}}{ds^{n-1}} \left(V_o(s) \cdot (s+k) \right)^n \Big|_{s=-k}$$

$$k_2 = \frac{d}{ds} (8(s+3)) \Big|_{s=-1} \Rightarrow k_2 = 8$$

$$V_o(s) = \frac{16}{(s+1)^2} + \frac{8}{s+1}$$

$$V_o(t) = (16te^{-t} + 8e^{-t}) u(t) \text{ volts}$$

Ex 14.5

Ex 14.13

Leche 3

$$H(s) = \frac{s+10}{s^2+4s+8}$$

$$V_o(s) = H(s) V_i(s) = \frac{s+10}{s(s^2+4s+8)} = \frac{s+10}{s(s+2-j2)(s+2+j2)}$$

$$V_o(s) = \frac{k_1}{s} + \frac{k_2}{s+2-j2} + \frac{k_3}{s+2+j2}$$

$$k_1 = 5/4 \quad k_2 = -5/8 + j3/8 \quad k_3 = k_2^* = -5/8 - j3/8$$

$$V_o(s) = \frac{5/4}{s} + \frac{-5/8 + j3/8}{s+2-j2} + \frac{(-5/8 - j3/8)}{s+2+j2}$$

$$V_o(t) = \frac{5}{4} + \left(\frac{-5}{8} + j\frac{3}{8} \right) e^{-(2-j2)t} + \left(\frac{-5}{8} - j\frac{3}{8} \right) e^{-(2+j2)t}$$

$$= \frac{5}{4} - e^{-2t} \left[\frac{5}{8} e^{j2t} - j\frac{3}{8} e^{j2t} + \frac{5}{8} e^{-j2t} + j\frac{3}{8} e^{-j2t} \right]$$

$$= \frac{5}{4} e^{-2t} \left[\frac{5}{4} \frac{(e^{12t} + e^{-12t})}{2} + \frac{3}{4} \left(\frac{e^{12t} - e^{-12t}}{j2} \right) \right]$$


$$V_0(t) = \left[\frac{5}{4} + e^{-2t} \left\{ \frac{5}{4} \cos 2t + \frac{3}{4} \sin 2t \right\} \right] u(t)$$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$


$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

↓ (cas)

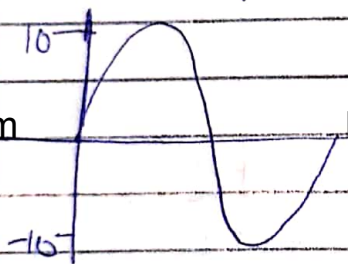Synthesis of wave Building up of a wave from its harmonics is called synthesis



$$V = 10 \sin \omega t$$

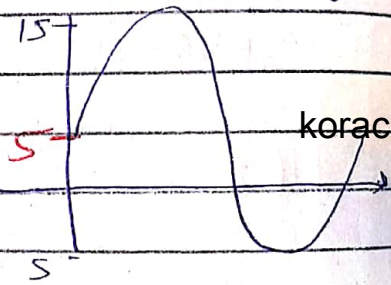

Fundamental + DC \rightarrow unsymmetrical

Fundamental + even \rightarrow unsymmetrical

Fundamental + odd harmonics \rightarrow symmetrical

For symmetrical wave $a_0 = 0$ even harmonics = 0

Average Value of Non-sinusoidal EMF or current

$$e = E_0 + \frac{E_1}{m_1} \sin(\omega t + \phi_1) + \frac{E_2}{m_2} \sin(\omega t + \phi_2) + \dots$$

$$\boxed{\text{avg}(e) = E_0 + 0 + 0 + \dots}$$

Average value of any parameter is the constant (dc) part of it.

Effective or RMS value of Nth sinusoidal waveform

$$E = \text{Rms } (e)$$

$$E = \sqrt{\frac{1}{T} \int_0^T e^2 dt} \quad \& \quad E = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} e^2 d\omega t}$$

$$E = \frac{1}{2\pi} \int_0^{2\pi} \left(E_0 + E_{m1} \sin(\omega t + \phi_1) + E_{m2} \sin(\omega t + \phi_2) + \dots \right)^2 d\omega t$$

$$\Rightarrow E = \sqrt{E_0^2 + E_1^2 + E_2^2 + \dots}$$

$$E_1 = \frac{E_{m1}}{\sqrt{2}}, \quad E_{m2} = E_2, \quad \dots$$

Example

$$i = 10 + 100\sqrt{2} \sin \omega t + 50\sqrt{2} \sin(3\omega t + 60^\circ) - 10\sqrt{2} \sin(\omega t - 210^\circ)$$

$$I_{\text{avg}} = ? \quad I_{\text{rms}} = ? \quad I_{\text{avg}} = 10 \text{ A}$$

$$I_{\text{rms}} = \sqrt{I_0^2 + I_1^2 + I_2^2 + \dots}$$

$$= \sqrt{(10)^2 + (100)^2 + (50)^2 + (10)^2}$$

$$\Rightarrow I_{\text{rms}} = 112.7 \text{ A}$$

Power Calculation

$$e = E_0 + E_{m1} \sin(\omega t + \phi_1) + E_{m2} \sin(2\omega t + \phi_2) + E_{m3} \sin(3\omega t + \phi_3) + \dots$$

$$i = I_0 + I_{m1} \sin(\omega t + \theta_1 + \beta_1) + I_{m2} \sin(2\omega t + \theta_2 + \beta_2) + I_{m3} \sin(3\omega t + \theta_3 + \beta_3) + \dots$$

Instantaneous power; $p = ei$
 Reading of voltmeter = Average power.

$$P = \frac{1}{2\pi} \int_0^{2\pi} p dt$$

$$\text{or } P = \frac{1}{2\pi} \int_0^{2\pi} ei dt$$

$$P = VI \cos \phi$$

If voltage and current both sources are sinusoidal
 Applying superposition theorem;

$$P = E_0 I_0 + E_1 I_1 \cos \beta_1 + E_2 I_2 \cos \beta_2 + E_3 I_3 \cos \beta_3$$

$$E_1 = \frac{E_{m1}}{\sqrt{2}}$$

$$I_1 = \frac{I_{m1}}{\sqrt{2}}$$

Example

$$e = 20 + 100\sqrt{2} \sin \omega t + 50\sqrt{2} \sin(3\omega t + 90^\circ) - 10\sqrt{2} \sin(5\omega t)$$

$$i = 2 + 10\sqrt{2} \sin(\omega t - 30^\circ) + 5\sqrt{2} \sin(5\omega t - 270^\circ)$$

$$P = (20 \times 2) + (100 \times 10 \cos 30^\circ) + (0) + (10 \cos 0^\circ) \cos 180^\circ$$

$$\Rightarrow P = 881 \text{ W}$$

* Analysis of Waves By Fourier Series.

Generally Fourier series is represented as;

$$f(\omega t) = a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t + \dots + a_n \cos n\omega t$$

$$+ b_1 \sin \omega t + b_2 \sin 2\omega t + \dots + b_n \sin n\omega t$$

Analytical method.

Determination of constant term (a_0)

Multiply eq (1) with $d\omega t$ and integrate over period T .

$$\int_0^{2\pi} f(\omega t) d\omega t = \int_0^{2\pi} a_0 d\omega t + \int_0^{2\pi} a_1 \cos \omega t d\omega t + \int_0^{2\pi} b_1 \sin \omega t d\omega t$$

$$+ \int_0^{2\pi} a_2 \cos 2\omega t d\omega t + \dots + \int_0^{2\pi} a_n \cos n\omega t d\omega t + \int_0^{2\pi} b_n \sin n\omega t d\omega t$$

$$+ \int_0^{2\pi} b_2 \sin 2\omega t d\omega t + \dots + \int_0^{2\pi} b_n \sin n\omega t d\omega t$$

average value of Sin and Cos = 0.

$$\int_0^{2\pi} f(\omega t) d\omega t = a_0 (2\pi) \Rightarrow a_0 = \frac{1}{2\pi} \int_0^{2\pi} f(\omega t) d\omega t$$

Determination of Cos terms (a_n)

multiply eq(1) with $(\cos n\omega t d\omega t)$ and integrate

$$\int_0^{2\pi} f(\omega t) \cos n\omega t d\omega t = \int_0^{2\pi} a_0 \cos n\omega t d\omega t + \int_0^{2\pi} a_1 \cos \omega t \cos n\omega t d\omega t + \dots + \int_0^{2\pi} a_n \cos^2 n\omega t d\omega t + \int_0^{2\pi} b_1 \sin \omega t \cos n\omega t d\omega t + \dots + \int_0^{2\pi} b_n \sin n\omega t \cos n\omega t d\omega t$$

$$\int_0^{2\pi} f(\omega t) \cos n\omega t d\omega t = a_n \int_0^{2\pi} \left(\frac{1 + \cos 2n\omega t}{2} \right) d\omega t$$

As $\cos^2 \theta = \frac{1 + \cos 2\theta}{2}$ and $\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$

$$\Rightarrow = \frac{a_n}{2} \left((\omega t) \Big|_0^{2\pi} + 0 \right) = \frac{a_n}{2} (2\pi) = a_n (\pi)$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \cos(n\omega t) d\omega t$$

Determination of sine terms (b_n)
 King eq (1) with $\sin n\omega t d\omega t$ and integrate


$$\int_0^{2\pi} f(\omega t) \sin n\omega t d\omega t = \int_0^{2\pi} a_0 \sin n\omega t d\omega t + \int_0^{2\pi} a_1 \cos \omega t \sin n\omega t d\omega t + \dots + \int_0^{2\pi} a_n \cos n\omega t \sin n\omega t d\omega t + \dots + \int_0^{2\pi} b_n \sin^2 n\omega t d\omega t$$

$$\Rightarrow \int_0^{2\pi} f(\omega t) \sin n\omega t d\omega t = \frac{b_n}{n} \int_0^{2\pi} (1 - \cos 2n\omega t) d\omega t$$

$$= \frac{b_n}{2} (2\pi - 0) = b_n(\pi)$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \sin n\omega t d\omega t$$

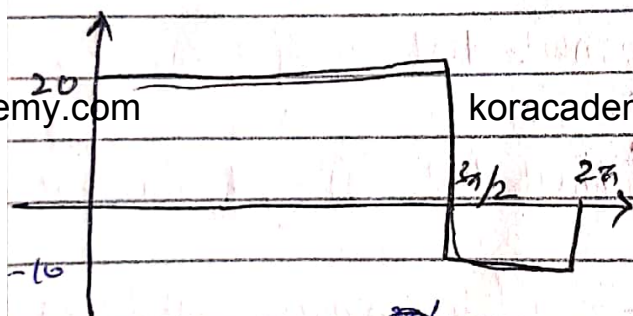Q. One cycle of a periodic rectangular wave is shown in figure. Find the first few harmonics.



Mathematical model = ?

$$f(\omega t) = \begin{cases} 20, & 0 \leq \omega t < 3\pi/2 \\ -10, & 3\pi/2 < \omega t < 2\pi \end{cases}$$

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} f(\omega t) d\omega t$$

$$a_0 = \frac{1}{2\pi} \left(\int_0^{3\pi/2} 20 d\omega t + \int_{3\pi/2}^{2\pi} (-10) d\omega t \right)$$

$$= \frac{1}{2\pi} \left(20 (\omega t) \Big|_0^{3\pi/2} - 10 (\omega t) \Big|_{3\pi/2}^{2\pi} \right)$$

$$= \frac{1}{2\pi} \left(20 \left(\frac{3\pi}{2} - 0 \right) - 10 \left(2\pi - \frac{3\pi}{2} \right) \right) = \frac{1}{2\pi} (30\pi - 5\pi)$$

$$a_0 = 12.5$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \cos n\omega t \cdot d\omega t$$

$$a_n = \frac{1}{\pi} \left(\int_0^{3\pi/2} 20 \cos n\omega t \cdot d\omega t + \int_{3\pi/2}^{2\pi} (-10) \cos n\omega t \cdot d\omega t \right)$$

$$= \frac{1}{\pi} \left(20 \frac{\sin n\omega t}{n} \Big|_0^{3\pi/2} - 10 \frac{\sin n\omega t}{n} \Big|_{3\pi/2}^{2\pi} \right)$$

$$= \frac{1}{n\pi} \left(20 \sin \left(n \frac{3\pi}{2} \right) - \sin 0 \right) - 10 \left(\sin n \left(2\pi \right) - \sin n \frac{3\pi}{2} \right)$$

$$= \frac{1}{n\pi} \left(30 \sin \frac{n 3\pi}{2} \right)$$

$$n = 2, 4, 6, \dots \text{ even } a_n = 0$$

$$n = 1, 3, 5, \dots \text{ odd } a_1 = -9.54 \quad a_2 = 3.18$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} f(\omega t) \sin n\omega t \cdot d\omega t$$

$$b_n = \frac{1}{\pi} \left[\int_0^{3\pi/2} 20 \sin n\omega t \cdot d\omega t + \int_{3\pi/2}^{2\pi} (-10) \sin n\omega t \cdot d\omega t \right]$$

$$= \frac{1}{\pi} \left[\frac{-20}{n} \cos n\omega t \Big|_0^{3\pi/2} + \frac{10}{n} \cos n\omega t \Big|_{3\pi/2}^{2\pi} \right]$$

$$= \frac{1}{n\pi} \left[-20 \left(\cos n \frac{3\pi}{2} - 1 \right) + 10 \left(1 - \cos \left(n \frac{3\pi}{2} \right) \right) \right]$$

$$= \frac{1}{n\pi} \left[-20 \cos \left(\frac{n 3\pi}{2} \right) + 20 + 10 - 10 \cos \left(\frac{n 3\pi}{2} \right) \right]$$

$$b_n = \frac{1}{n\pi} \left[30 - 30 \cos \left(\frac{n 3\pi}{2} \right) \right]$$

$$b_1 = \frac{1}{\pi} (30) = 30/\pi$$

$$b_2 = \frac{1}{2\pi} (30 + 30) = \frac{30}{\pi}$$

$$b_3 = \frac{-10}{\pi}$$

Example 23.6

Effect of Symmetry On Fourier Series

① Constant term = 0

If a wave has equal area above and below the horizontal axis in a complete cycle then a_0 will be zero.

② Half wave symmetry $f(\omega t) = -f(\omega t + \pi)$
 $a_0 = 0$ and all the even harmonics will be zero.

③ Odd function $f(\omega t) = -f(-\omega t)$
 eg sin wave is an odd function. If a given function is odd then a_0 and all cosine terms will be zero.

④ Even function $f(\omega t) = f(-\omega t)$ eg cos function.
 (An odd function must always pass through the origin).
 If a function is even, then all of sine terms are zero.

The limits of integration are taken over one period, necessarily 0 to 2π , eg may be $-\pi$ to π .


If we want to integrate with T ;

$$a_0 = \frac{1}{T} \int_0^{t+T} f(\omega t) dt$$

$$a_n = \frac{2}{T} \int_0^{t+T} f(\omega t) \cos n\omega t dt$$

$$b_n = \frac{2}{T} \int_t^{t+T} f(\omega t) \sin n\omega t dt$$

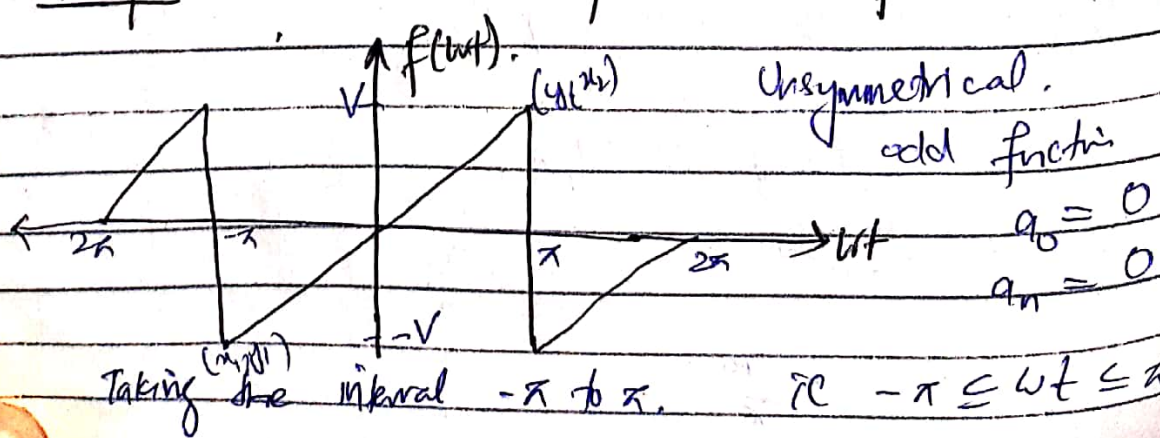Example Find the Fourier series of the sawtooth wave



$$f(\omega t) = m\omega t + c$$

$$= \left(\frac{y_2 - y_1}{x_2 - x_1} \right) (\omega t) + c$$

$$= \frac{V - (-V)}{\pi - (-\pi)} (\omega t) + 0 \Rightarrow \boxed{f(\omega t) = \frac{V}{\pi} (\omega t)}$$

$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(\omega t) \sin n\omega t \, d\omega t$$

$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} \frac{V}{\pi} (\omega t) \sin(n\omega t) \, d\omega t$$

$$= \frac{V}{\pi^2} \int_{-\pi}^{\pi} (\omega t) \sin n\omega t \, d\omega t \quad \int ab = a \int b - \int a' b$$

$$= \frac{V}{\pi^2} \left[-(\omega t) \cdot \frac{\cos n\omega t}{n} + \int \frac{\cos n\omega t}{n} \, d\omega t \right]_{-\pi}^{\pi}$$

$$b_n = \frac{V}{n\pi^2} \left[-(\omega t) \cos n\omega t + \sin \left(\frac{n\omega t}{n} \right) \right]_{-\pi}^{\pi}$$

$$b_n = \frac{V}{n\pi^2} \left[\left(-\pi \cos n\pi + \frac{\sin n\pi}{n} \right) - \left(\pi \cos n\pi - \frac{\sin n\pi}{n} \right) \right]$$

$$b_n = \frac{V}{n\pi^2} \left[-\pi \cos n\pi - \pi \cos n\pi \right] = \frac{V}{n\pi^2} (-2\pi \cos n\pi)$$

$$b_n = \frac{-2V}{n\pi} \cos n\pi$$

$$n = 1, 3, 5, \dots \text{ odd} \Rightarrow b_n = \frac{2V}{n\pi}$$


$$n = 2, 4, 6, \dots \text{ even} \Rightarrow b_n = -\frac{2V}{n\pi}$$

Lecture 4

Application of Non Sinusoidal waves to linear circuit

Superposition theorem is only for linear elements

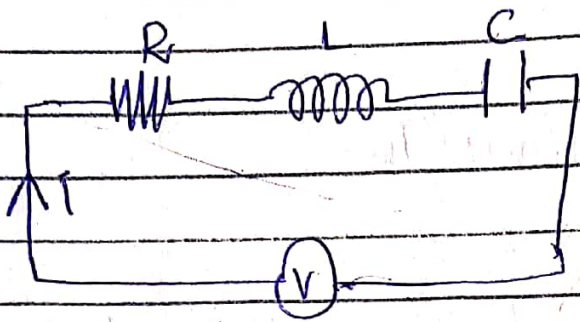→ Relationship for voltage in RLC series circuit
current is non sinusoidal



No dc component
current (i_0)

$$i = i_1 + i_2 + i_3 + \dots$$

$$i = I_{m1} \sin(\omega t + \theta_1) + I_{m2} \sin(2\omega t + \theta_2) + \dots + I_{mn} \sin(n\omega t + \theta_n)$$

$$X_L = 2\pi f L \quad X_C = \frac{1}{2\pi f C} \quad Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = IZ \quad \beta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$V \angle \phi = I \angle \theta \quad Z \angle \beta \Rightarrow V \angle \phi = I \angle \theta + Z \angle \beta$$

$$V = I_{m1} Z_1 \sin(\omega t + \theta_1 + \beta_1) + I_{m2} Z_2 \sin(2\omega t + \theta_2 + \beta_2) + \dots + I_{mn} Z_n \sin(n\omega t + \theta_n + \beta_n)$$

$$Z_1 = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$\beta_1 = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$Z_2 = \sqrt{R^2 + \left(2\omega L - \frac{1}{2\omega C} \right)^2}$$

$$\beta_2 = \tan^{-1} \left(\frac{2\omega L - \frac{1}{2\omega C}}{R} \right)$$

$$Z_n = \sqrt{R^2 + \left(n\omega L - \frac{1}{n\omega C} \right)^2}$$


$$\beta_n = \tan^{-1} \left(\frac{n\omega L - \frac{1}{n\omega C}}{R} \right)$$

$X_C > X_L \Rightarrow$ capacitive \Rightarrow current leads voltage

$X_L > X_C \Rightarrow$ inductive \Rightarrow voltage leads current

If for the first harmonic, circuit is inductive then it will be inductive for all the rest harmonics

Example

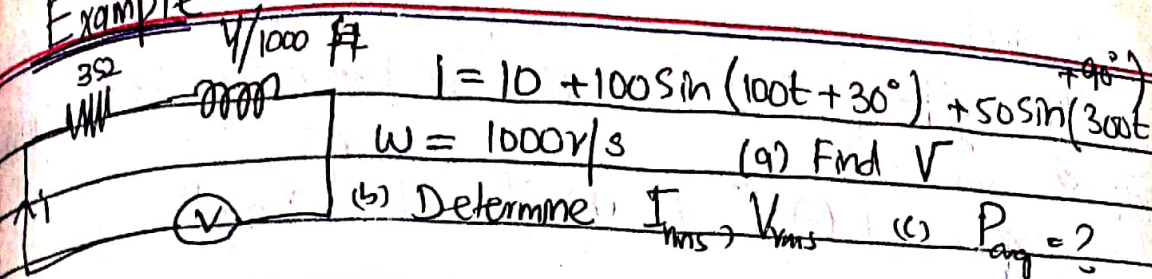

$$v = 10Z_0 + 100Z_1 \sin(100t + 30^\circ + \beta_1) + 50Z_2 \sin(300t + 90^\circ + \beta_2)$$

$$Z_0 = R = 3\Omega \quad Z_1 = \sqrt{R^2 + \omega L^2} = \sqrt{3^2 + 4^2} = 5\Omega$$

$$\beta_1 = \tan^{-1} \frac{\omega L}{R} = \frac{4}{3} = 53.13^\circ$$

$$Z_3 = \sqrt{R^2 + (\omega L)^2}$$

$$\beta_3 = \tan^{-1} \frac{3 \times 4}{3} = 76^\circ$$

$$L = 12.4\mu\text{H} = \sqrt{3^2 + (3 \times 4)^2}$$

$$v = 10 \times 3 + 100 \times 5 \sin(100t + 30^\circ + 53.13^\circ) + 50 \times 12.4 \sin(300t + 90^\circ + 76^\circ)$$

$$v = 30 + 500 \sin(100t + 83.13^\circ) + 620 \sin(300t + 166^\circ)$$

$$I_{\text{rms}} = \sqrt{I_0^2 + I_1^2 + I_2^2}$$

$$I_{\text{rms}} = \sqrt{(10)^2 + (100/\sqrt{2})^2 + (50/\sqrt{2})^2} \Rightarrow I_{\text{rms}} = 79.7 \text{ A}$$

$$V_{\text{rms}} = \sqrt{V_0^2 + V_1^2 + V_2^2}$$

$$= \sqrt{(30)^2 + (500/\sqrt{2})^2 + (620/\sqrt{2})^2} = 565 \text{ W}$$


$$(c) \quad P_{\text{avg}} = I_{\text{rms}}^2 R \quad \text{or} \quad \frac{V_{\text{rms}}^2}{R} \quad \left(\begin{array}{l} I_{\text{rms}}^2 V_{\text{rms}}^2 \text{ gives} \\ \text{pput pwr} \end{array} \right)$$

$$P_{\text{avg}} = 79.7^2 \times 3 = 19 \text{ kW}$$

$$P_{\text{avg}} = (10)(30) + \left(\frac{500}{\sqrt{2}} \right) \left(\frac{100}{\sqrt{2}} \right) \cos 53.13^\circ + \left(\frac{620}{\sqrt{2}} \right) \left(\frac{50}{\sqrt{2}} \right) \cos 76^\circ$$

$$= 19 \text{ kW}$$

Example

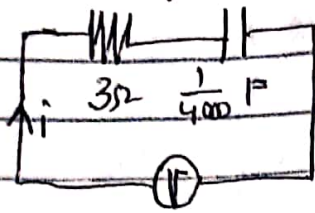

$$i = 100 \sin(100t + 30^\circ) + 50 \sin(300t + \dots)$$

$$\omega = 1000 \text{ r/s}$$

$$(a) V = ? \quad (b) V_{\text{rms}}, I_{\text{rms}} = ? \quad (c) P_{\text{avg}} = ?$$

$$Z_1 = \sqrt{R^2 + \frac{1}{(\omega C)^2}} = 5 \Omega$$

$$\beta = \tan^{-1} \left(\frac{-1/\omega C}{R} \right) = -53.1^\circ$$

-ve s/o $X_L - X_C$ and $X_L = 0$

$$Z_3 = \sqrt{R^2 + \left(\frac{1}{3\omega C} \right)^2} = 3.3 \Omega$$

$$\beta_3 = \tan^{-1} \left(\frac{-1/3\omega C}{R} \right) = -24^\circ$$

$$V = (100/5) \sin(100t + 30^\circ - 53.1^\circ) + (50)(3.3) \sin(300t + \dots)$$

$$V = 500 \sin(100t - 23.1^\circ) + 165 \sin(300t + 66^\circ)$$

$$(b) V_{\text{rms}} = \sqrt{\left(\frac{500}{\sqrt{2}} \right)^2 + \left(\frac{165}{\sqrt{2}} \right)^2} = 373 \text{ V}$$

$$I_{\text{rms}} = \sqrt{\left(\frac{100}{\sqrt{2}} \right)^2 + \left(\frac{50}{\sqrt{2}} \right)^2} = 79 \text{ A}$$

$$(c) P_{\text{avg}} = I_{\text{rms}}^2 R = 79^2 \times 3 = 18.7 \text{ kW}$$


(*)

$$P_{\text{avg}} = \frac{500}{\sqrt{2}} \times \frac{100}{\sqrt{2}} \cos 53.1^\circ + \frac{165}{\sqrt{2}} \times \frac{50}{\sqrt{2}} \cos 24^\circ = 18.7 \text{ kW}$$

Current due to Non sinusoidal voltage

Current cannot have a dc term even if ω has.

-B

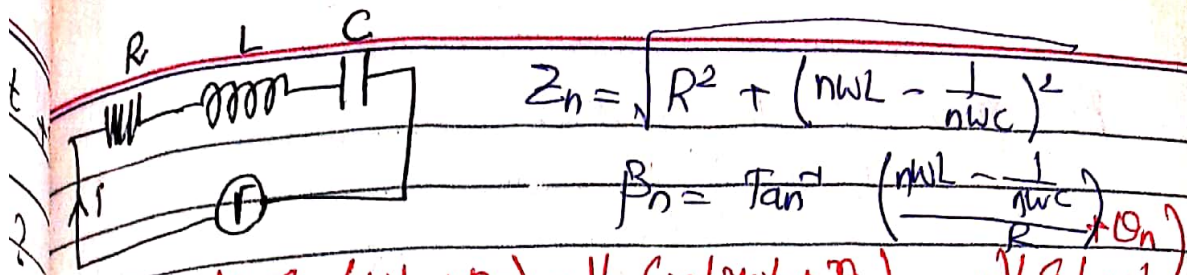

$$Z_n = \sqrt{R^2 + \left(n\omega L - \frac{1}{n\omega C}\right)^2}$$

$$\beta_n = \tan^{-1} \left(\frac{n\omega L - \frac{1}{n\omega C}}{R} \right) + \theta_n$$


$$v = v_0 + V_{m1} \sin(\omega t + \theta_1) + V_{m2} \sin(2\omega t + \theta_2) + \dots + V_{mn} \sin(n\omega t)$$

$$i = \frac{V_{m1}}{Z_1} \sin(\omega t + \theta_1 - \beta_1) + \frac{V_{m2}}{Z_2} \sin(2\omega t + \theta_2 - \beta_2) + \dots$$

$$+ \frac{V_{mn}}{Z_n} \sin(n\omega t + \theta_n - \beta_n)$$

$$i_0 = 0A \quad Z_0 = \infty \Omega$$

Example $X_L = 2 \quad X_C = 8$

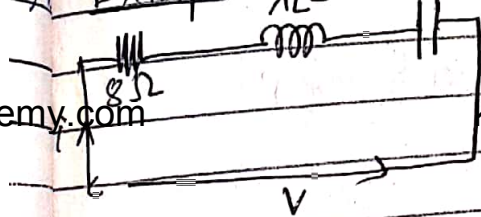

$$\omega = 1000 \text{ r/s}$$

$$v = 20 + 100 \sin 100t + 50 \sin(300t + 60^\circ)$$

$$i_0 = 0A \text{ as } Z_0 = \infty \Omega$$

$$Z_1 = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{8^2 + (2-8)^2} = 10 \Omega$$

$$\beta_1 = \tan^{-1} \left(\frac{\omega L - 1/\omega C}{R} \right) = \tan^{-1} \left(\frac{2-8}{8} \right) = -36.8^\circ$$

capacitive

$$Z_3 = \sqrt{R^2 + \left(3\omega L - \frac{1}{3\omega C}\right)^2} = 8.65 \Omega$$

$$\beta_3 = \tan^{-1} \left(\frac{3\omega L - 1/3\omega C}{R} \right) = 22.6^\circ \rightarrow \text{inductive}$$

$$i = \frac{100}{Z_1} \sin(100t - \beta_1) + \frac{50}{Z_3} \sin(300t + 60^\circ - \beta_3)$$

$$i = \frac{100}{10} \sin(100t + 36.8^\circ) + \frac{50}{8.65} \sin(200t + 60^\circ - 22.6^\circ)$$

$$i = 10 \sin(100t + 36.8^\circ) + 5.78 \sin(200t + 37.4^\circ)$$


lead

Resonance in RLC Series

$$Z_A = R \quad I_A =$$

AC circuit reads RMS value

Example (parallel network)

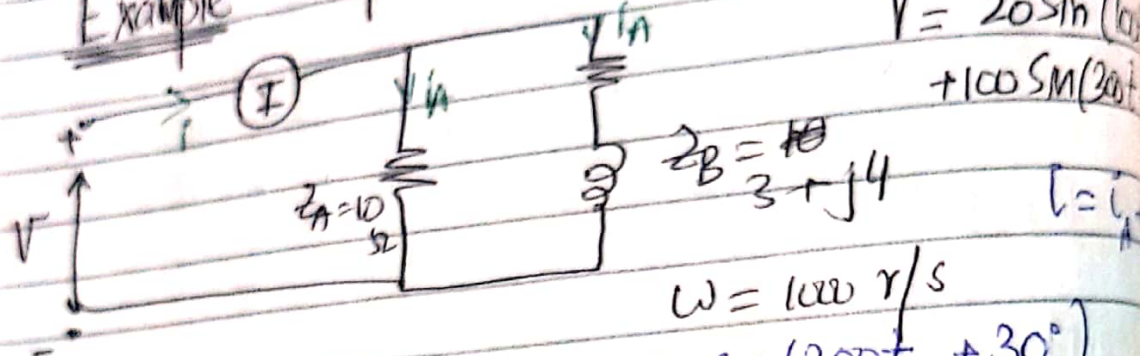

$$V = 20 \sin(100t + 10^\circ) + 100 \sin(300t + 30^\circ)$$

$$i_A = \frac{20 \sin(100t + 10^\circ)}{10} + \frac{100 \sin(300t + 30^\circ)}{10}$$

$$i_A = 2 \sin(100t + 10^\circ) + 10 \sin(300t + 30^\circ)$$

For i_B

$$Z_1 = \sqrt{3^2 + 4^2} = 5 \Omega$$

$$\beta_1 = \tan^{-1} \frac{4}{3} = 53.2^\circ$$

$$Z_3 = \sqrt{R^2 + (\omega L)^2} = 12.4 \Omega$$

$$\beta_3 = \tan^{-1} \frac{\omega L}{R} = \tan^{-1} \frac{3}{4} = 36.9^\circ$$

$$i_B = \frac{20 \sin(100t + 10^\circ - 53.2^\circ)}{5} + \frac{100 \sin(300t + 30^\circ - 36.9^\circ)}{12.4}$$

$$i_B = 4 \sin(100t - 43.2^\circ) + 8.08 \sin(300t - 46^\circ)$$

$$i = i_A + i_B$$

$$i = 2 \sin(100t + 10^\circ) + 10 \sin(300t + 30^\circ) + 4 \sin(100t - 43.2^\circ) + 8.08 \sin(300t - 46^\circ)$$

$$\sin(\alpha + \beta) = \sin \alpha \cos \beta + \cos \alpha \sin \beta$$

$$i = 48.9 \sin 100t - 23.8 \cos 100t + 14.28 \sin 300t - 0.81 \cos 300t$$

$$i = 54.4 \sin(100t - 26^\circ) + 14.3 \sin(300t - 3.25^\circ)$$

$$I_{rms} = \sqrt{I_1^2 + I_3^2} = \sqrt{\left(\frac{54.4}{\sqrt{2}}\right)^2 + \left(\frac{14.3}{\sqrt{2}}\right)^2}$$

$$I_{rms} = 30.7 A$$

$$a_n \cos n\omega t + b_n \sin n\omega t = C_n \sin(n\omega t + \theta_n)$$

$$C_n = \sqrt{a_n^2 + b_n^2}, \quad \theta_n = \tan^{-1}\left(\frac{b_n}{a_n}\right)$$

Lecture 5

Filters

Electrical filter: frequency

① Active filters.

R, L, C, Op Amp, Buffer.

② Passive filters.

R, L, C, diode.




- ↳ gain is low $A = 1$
- ↳ Shaping of waves.
- ↳ Frequency selectivity.

Types (ideal)




- Low pass filter
- High pass filter
- Band pass filter
- Band stop filter

First order filters


A.P.F

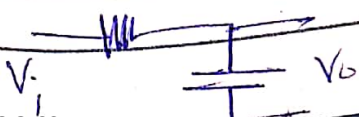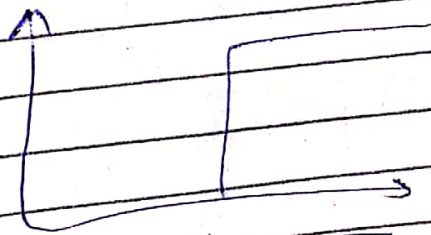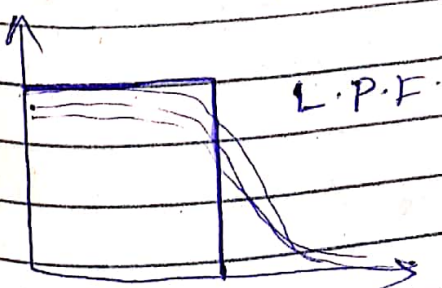

Second order filters

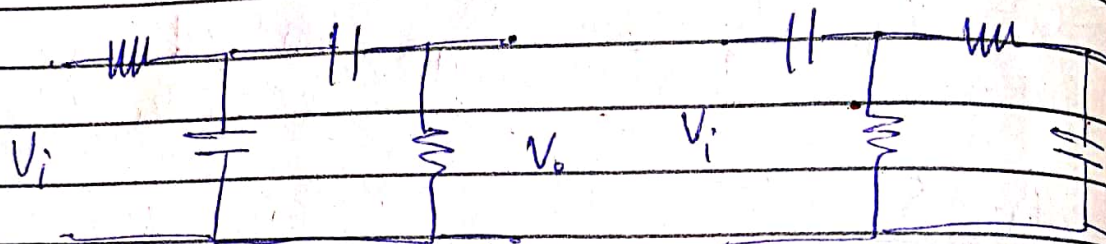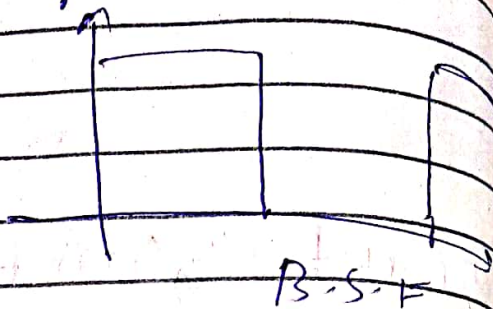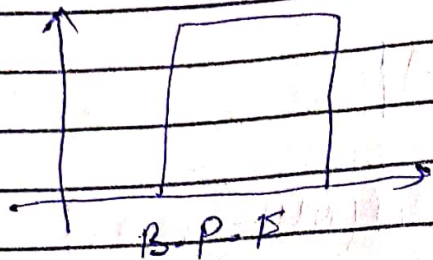

Operational Amplifier (Op-Amp)

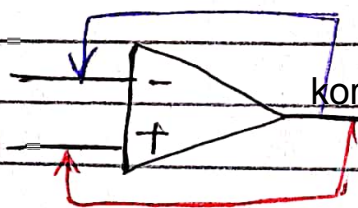

Inverting configuration

$$V_i = -V_o$$


Non inverting op amp

$$V_o = V_i$$

Characteristics

- 1) I/P impedance is ∞ .
- 2) O/P impedance is 0.
- 3) Gain is infinity.

Active low pass filter.

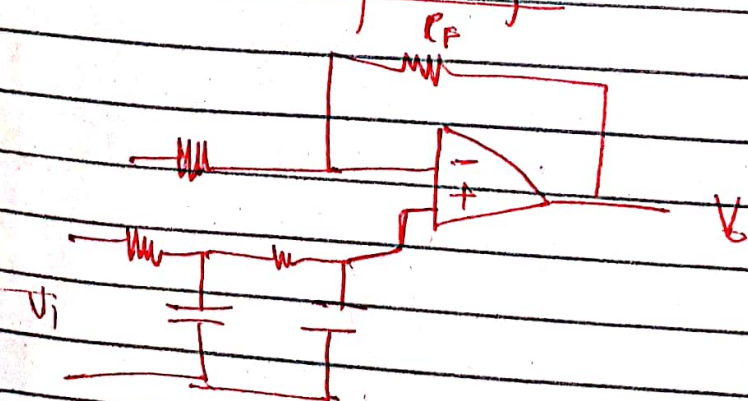

$$K=1$$

using gain

$$R = R_F$$

$$\omega = \frac{1}{R}$$

Bulk voltage
Elliptic

Lecture 6

Unity

Vi

Normal

$$\omega = 1$$

$$C_1 =$$


Buttworth elliptic

Chebyshev Bessel

Inverse chebyshev

Lecture 6

Unity Gain Sallen Key Filter

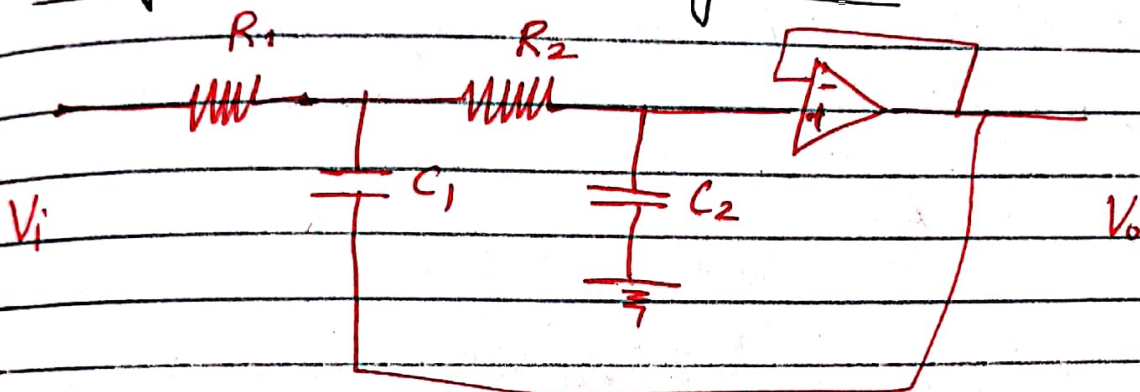

Normalization


$\omega = 1 \text{ rad/s}$

$R_1 = R_2 = 1 \Omega$

$C_1 = 2 \mu\text{F}$

$C_2 = \frac{1}{2 \mu\text{F}}$

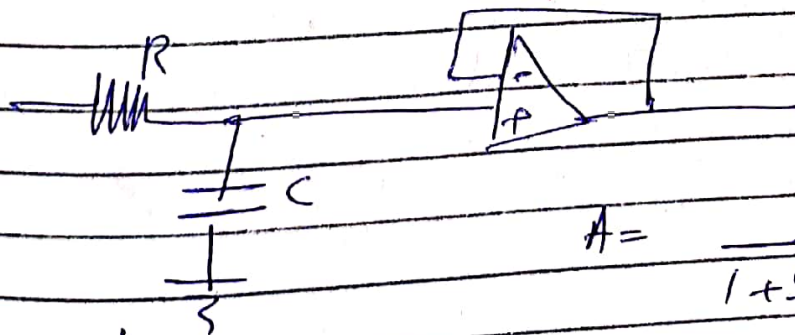$A = \frac{1}{s^2 + \frac{1}{Q}s + 1} \rightarrow \text{S.O.F}$



$A = \frac{1}{1 + sRC}$

$\omega = \frac{1}{RC}$

Normalization

$R = 1 \Omega, \omega = 1 \text{ rad/s}$

$C = 1 \mu\text{F}$

$A = \frac{1}{s+1} \rightarrow \text{F.O.F}$

$$\text{1st order F.} \quad A = \frac{1}{(s+1) \left(s^2 + \frac{1}{Q}s + 1 \right)}$$

$$\text{Fourth order F.} \quad A = \frac{1}{\left(s^2 + \frac{1}{Q_1}s + 1 \right) \left(s^2 + \frac{1}{Q_2}s + 1 \right)}$$

$$\text{5th order F.} \quad A = \frac{1}{(s+1) \left(s^2 + \frac{1}{Q_1}s + 1 \right) \left(s^2 + \frac{1}{Q_2}s + 1 \right)}$$

$$A = \frac{1}{B_n(s)}$$

$$B_n(s) = s^n + \frac{a_{n-1}}{n-1} s^{n-1} + \frac{a_{n-2}}{n-2} s^{n-2} + \dots + a_1 s + a_0$$

n polynomials

1. $s+1$

2. $s^2 + \sqrt{2}s + 1$

3. $s^3 + 2s^2 + 2s + 1$

4. $s^4 + 2.61313s^3 + 3.414s^2 + 2.63105s + 1$

Characteristics

1. Poles lies on unitary circle
2. The poles will have an angular separation $180^\circ/n$, where n is order of the filter