

ELECTRICAL MACHINES

Basics

Concept of phasors

Say $V_1(t) = V_m \sin(\omega t + \phi_1)$
or $V_1(t) = V_m \cos(\omega t + \theta_2)$

$V_m \rightarrow$ peak value $\omega \rightarrow$ frequency $\theta \rightarrow$ phase shift.

\Rightarrow If \sin is the reference;

$V_m \angle \pm \theta_1 \rightarrow$ in terms of peak value.

$\frac{V_m}{\sqrt{2}} \angle \pm \theta_1 \rightarrow$ in terms of rms value.

\Rightarrow If \cos is the reference,

$V_m \angle \pm \theta_2, \quad \frac{V_m}{\sqrt{2}} \angle \pm \theta_2$

If directly given, eg $5 \angle 30^\circ$
 \rightarrow This 5 is rms value.

Comparison b/w two sinusoids.

- i. Both signals must be in same form.
- ii. Both signals must have same frequency.
- iii. Both signals must have positive amplitude.

lead \rightarrow anticlockwise \rightarrow +ve
lag \rightarrow clockwise \rightarrow -ve

sin lags cosine by 90° .
cosine leads sine by 90° .

say my reference is sine. so my standard signal will be;

$$x(t) = x_m \sin(\omega t \pm \theta)$$


In phasor form, $x_m \angle \pm \theta$ or $x_m / \sqrt{2} \angle \pm \theta$

Consider; $x_1(t) = 5 \sin(\omega t + 60^\circ) = 5 \angle 60^\circ = \frac{5}{\sqrt{2}} \angle 60^\circ$

$$x_2(t) = -10 \sin(\omega t - 70^\circ) = 10 \angle 110^\circ$$

$$x_3(t) = -5 \cos(\omega t + 30^\circ) = 5 \angle -60^\circ$$
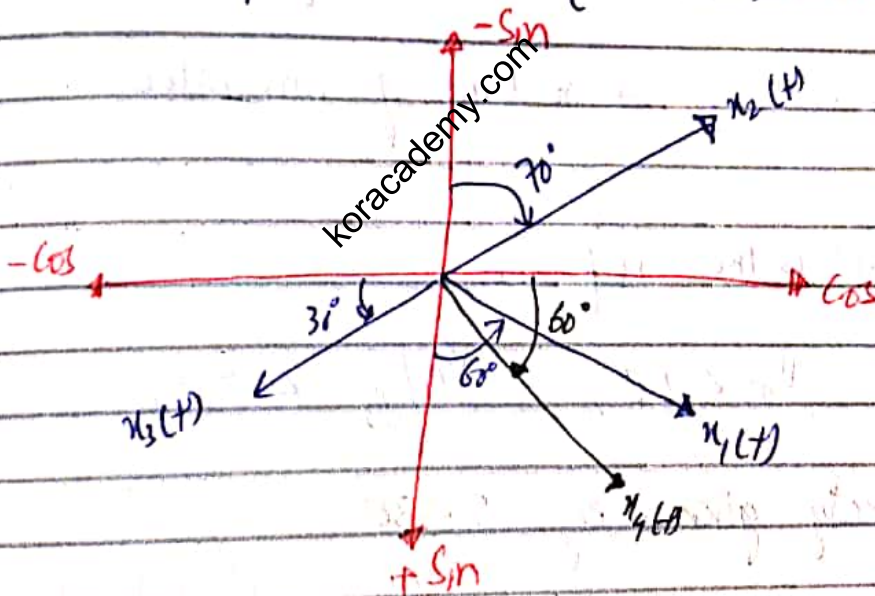
$$x_4(t) = 5 \cos(\omega t - 60^\circ) = 5 \angle 30^\circ$$



See x_2 is not in standard form.
To convert into standard form, take the reference and take it to the required signal.

ie here take +sin to $x_2(t)$

$$\text{So } x_2(t) = 10 \sin(\omega t + 110^\circ)$$

$$x_3(t) = 5 \sin(\omega t - 60^\circ)$$

$$x_4(t) = 5 \sin(\omega t + 30^\circ)$$

Talking about lead and lag.

Again we need a reference
Say $x_1(t)$ is my reference.

x_3 lags x_1 by 120°

x_4 lags x_1 by 30° etc

x_2 leads x_1 by 50° .

Say $x_2(t)$ is reference

x_4 lags x_2 by 80° .

Now talk about power

Instantaneous Power

$$p(t) = v(t) \times i(t) = V_m \sin(\omega t + \theta_1) \cdot I_m \sin(\omega t + \theta_2)$$

$$= \frac{V_m I_m}{2} \cos(\theta_1 - \theta_2) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_1 + \theta_2)$$

$$= \frac{V}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_1 - \theta_2) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_1 + \theta_2)$$

$$p(t) = \frac{V}{\sqrt{2}} I_{ms} \cos(\theta_1 - \theta_2) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_1 + \theta_2)$$

↓
independent of time
↓

average power.

$$P_{avg} = \frac{V}{\sqrt{2}} I_{rms} \cos(\theta_1 - \theta_2)$$

where $\cos(\theta_1 - \theta_2) = \cos \phi = PF$

$P_{avg} = \text{Real power} = \text{Wattage} = \text{Active} = \text{Useful}$
 $= \text{AC power} \rightarrow \text{avg. dc quantity} \rightarrow \text{dc quantity of resistive part (AC power)}$

ii. Complex power

$$= (V_{rms} \times I_{rms}^*) \quad \text{DC power is AC}$$

$$= P + jQ$$

$$= |V_{rms}| \angle \theta_1 \cdot |I_{rms}| \angle -\theta_2$$

DC power is AC
w/ pf included

$$= |V_{rms}| |I_{rms}| \angle \theta_1 - \theta_2 \quad \text{DC } P = V_{dc} I_{dc}$$

$$= \boxed{V_{rms} I_{rms} \cos(\theta_1 - \theta_2) + j V_{rms} I_{rms} \sin(\theta_1 - \theta_2)}$$

↓
Avg


↓
Reactive power (Q)

iii. Apparent power

$$\boxed{V_{rms} \times I_{rms}}$$

As $P = V_{rms} I_{rms} \cos \phi$

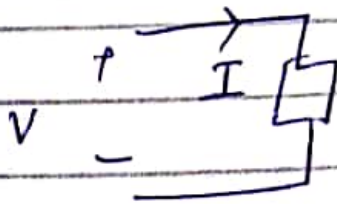ϕ is the angle b/w V and I if they are defined at the same terminals.



ϕ is the angle b/w phases not b/w line quantities.



absorbing delivering

Short circuit $\rightarrow V = 0V$
Open circuit $\rightarrow I = 0A$


Three types of magnetic materials.

- i. Diamagnetic materials do repulsion when placed in an external magnetic field.
- ii. Paramagnetic materials are like diamagnetic but they can create a little attraction when subjected to a magnetic field.
- iii. Ferromagnetic materials strongly attract when an external magnetic field is applied.
Their permeability is very high.

The type of magnetic material is decided by the alignment of dipoles in the atom.

Residual magnetism \rightarrow When the external magnetic field is removed and the material is still somewhat magnetized.


The magnetization curve is as;

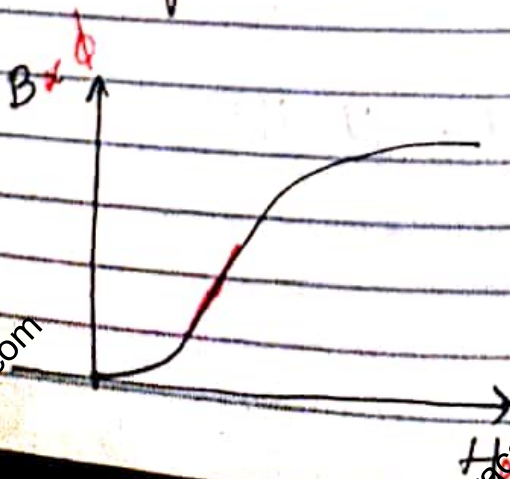

The slope in the linear region represent permeability.

$$B = \mu H$$

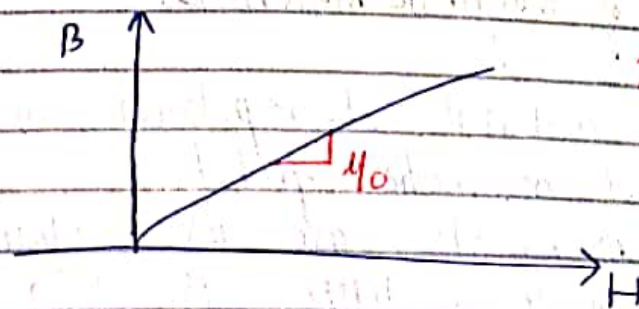For air, μ is very low, $= \mu_0$
So the BH curve is assumed to be linear.



The air do not saturate.

Some important relations;

$$B = \mu H$$

$B \rightarrow$ flux density, $H \rightarrow$ field intensity

Also $B = \frac{\phi}{A} \Rightarrow \phi = BA$

Also $H = \frac{B}{\mu} = \left(\frac{\phi}{A \mu} \right) = \frac{\text{mmf}}{R \mu A} = \frac{N \cdot i(t)}{R \cdot \mu A}$

$\left[\phi = \frac{\text{mmf}}{\text{Reluctance}}, \text{mmf} = N \cdot i(t), R = \frac{l}{\mu A} \right]$

$H = \frac{N \cdot i(t)}{\frac{l}{\mu A}}$

$$H = \frac{N \cdot i(t)}{l}$$

Important Points for Rotating Machine

If a material is being magnetized for the first time, the curve is known as virgin curve.

Conditions for induced voltages

$$e = N \frac{d\phi}{dt}$$

$$e \propto \frac{d\phi}{dt}$$

$$e = \frac{d\psi}{dt}$$

$\psi = \text{Flux linkage.}$

$$\psi = N \cdot \phi$$

i. If the magnetic field is fixed, the conductor should be rotating in nature.

ii. If the mag field is changing in nature, the conductor is fixed.

iii. If both mag field and conductor are changing in nature.

i. Dynamically induced emf.

ii. Statically induced emf eg transformer.

iii. static + dynamic.

Fleming Right Hand Rule is applicable in generator.

Fleming Left hand rule is applicable in motors.

Thumb \rightarrow motion or speed or torque.

First finger \rightarrow Flux direction

Middle finger \rightarrow Direction of current.

⊗ into the surface.

⊙ out of the surface.

Thumb Rule

Thumb = current
Finger curl = magnetic flux.




↳ or the Screw rule.

Fixed pole if poles do not change N S

- ↳ natural magnet.
- ↳ using DC supply.

For wrapping of coil, thumb rule is opposite.

ie thumb = flux curl = current

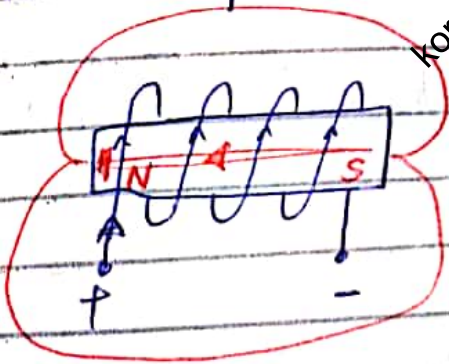

fixed pole.

$$\phi = \frac{N \cdot i(l)}{R}$$

~~Electromagnet~~

Varying pole from electromagnet.

- ↳ poles change.
- ↳ using AC supply
- ↳ during the red-ve cycles.

Reluctance Torque is only possible in salient pole machine. ie it is not possible in cylindrical machine.

Electromagnetic Torque is possible in both salient pole and cylindrical machine.



Rotary initially non magnetized.
 ↳ Reluctance torque
 ↳ will align the rotor in direction to get minimum reluctance path.

Initially magnetized.
 N-S will lock each other.
 No further movement.
 ↳ Electromagnetic torque.
 ↳ due to interaction of fluxes of stator and rotor.

If cylindrical rotor;



Each and every point has almost same reluctance
 ↳ no rotation → no torque.

$$T_e \propto \phi_r \phi_s \sin \delta$$

δ is angle b/w axis of stator and rotor.

Some Important terms -

Conductor: The length of wire in the influence of mag field.

Turn (t): Minimum no. of conductors to form a turn = 2.

if t no. of conductors - total turn possible

$$T = \frac{Z}{2}$$

Coil Minimum turn = 1 \rightarrow Minimum conductor = 2

slot where you have (put) a conductor.

Coil side The part of the coil in a slot.

Pole pitch The angular displacement from pole to pole.

1 pole pitch = 180° electrical.

$$\phi_{\text{per pole}} = \frac{4 B_p l r}{P} \quad (\text{magnitude})$$

\rightarrow The amount of flux useful for induction processes

\hookrightarrow This is not the flux generated by individual pole

$$\theta_e = \frac{P}{2} \theta_m$$

$$N = \frac{120 f}{P}$$

$N \rightarrow$ mechanical quantity
 $f \rightarrow$ in Hz \rightarrow electrical quantity
 \hookrightarrow rotation per minute (rpm)

$$\omega_e = \frac{P}{2} \omega_m$$

$$\omega_m = \frac{2\pi N}{60}$$

$\omega_e \rightarrow$ angular speed

$\omega_e \times$

DC Machines

Generator

→ i/p variable is a mechanical quantity (T torque, ω angular speed)

→ o/p variable is V voltage or current I .

Torque related to current.
Speed related to voltage.

Motor

→ i/p variable is an electrical quantity i.e. V or IT

→ o/p is a mechanical quantity i.e. T or ω ,
 $V \rightarrow \omega$, $I \rightarrow T$

Construction

Stator is responsible for the production of main flux

↳ stationary part
↳ the supply on the machine is always dc supply.
in the stator to get fixed poles.

Stator — field poles — field winding — produces
main flux — DC supply.

Rotor

It has armature core (if gen, you take voltage at this point and if motor you apply it at this point)

Rotor — armature core — armature winding — produces
induced voltage (AC).

$$E_{ph} = 4.44 \cdot f \cdot \phi \cdot N$$


Commutator.

In case of generator, converts AC voltage from rotor to DC.

(ii) converts bidirectional voltage / current into a unidirectional.
↳ acting as a rectifier.

In case of motor, i/p is always a dc voltage. i/p is always applied at the rotor. So the dc will not operate the rotor / machine.

So here commutator converts DC to AC.

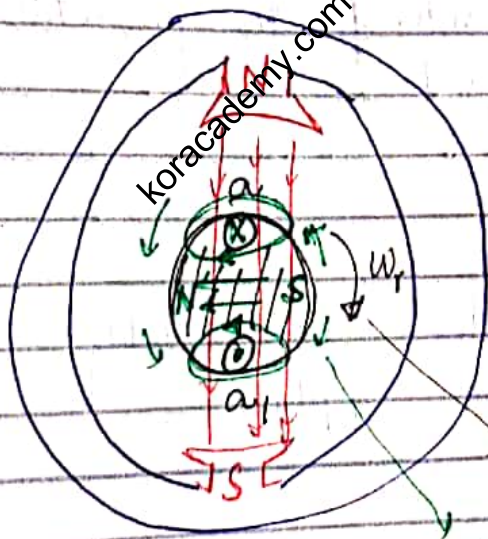


2 pole DC generator.

main flux lines / starter flux.


mechanical.
electromagnetic.

$$I_{dc} = I(+)$$

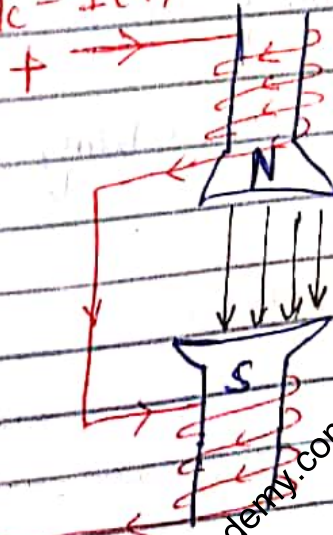

field winding.

It can also be represented as;

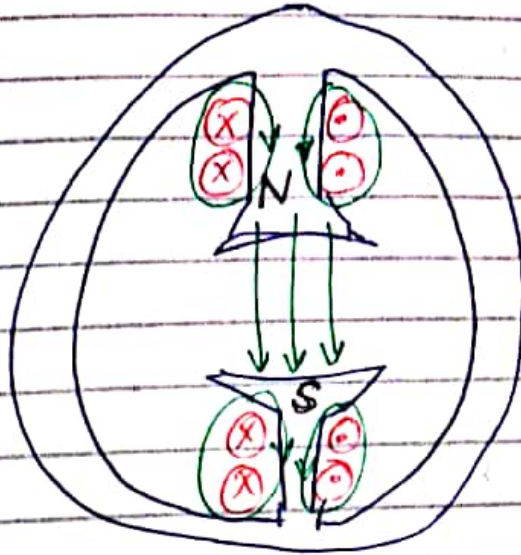


Generator







- ① Rotate the rotor with a constant speed. (ω_r)
- ② Switch on the excitation system. -

Fleming right hand rule.


current into the coil.

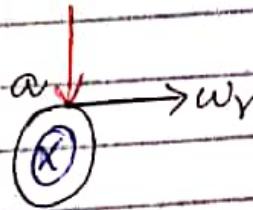


out of the coil.

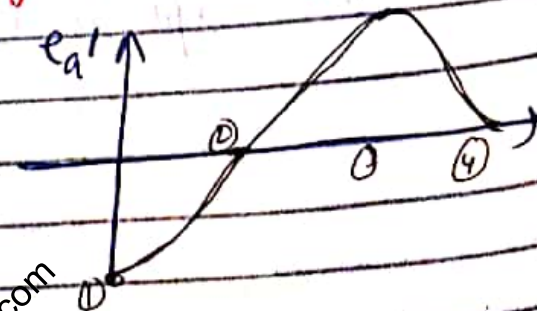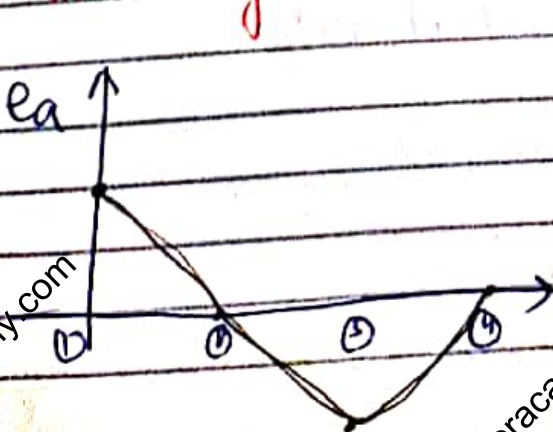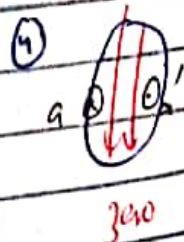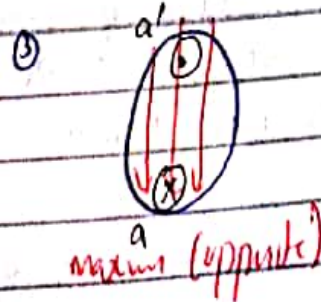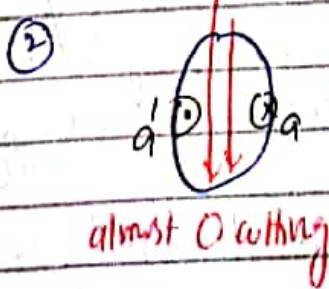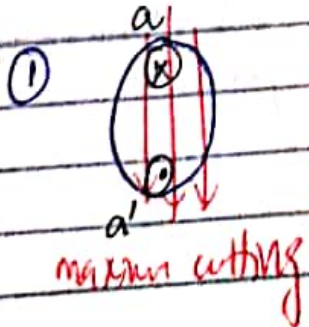

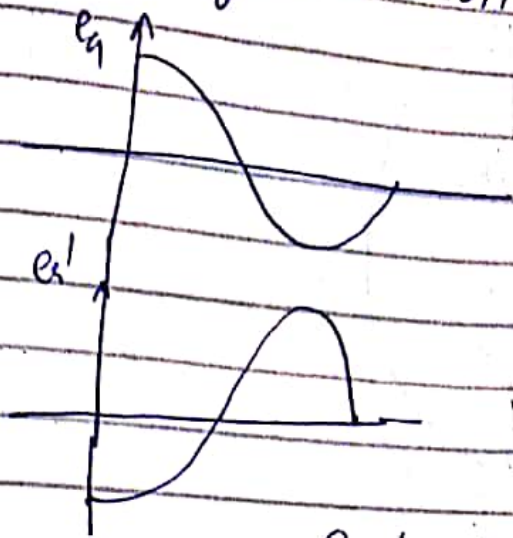The rotor waveform in rotor is always AC.
The voltage of total coil $e_{aa'}$;


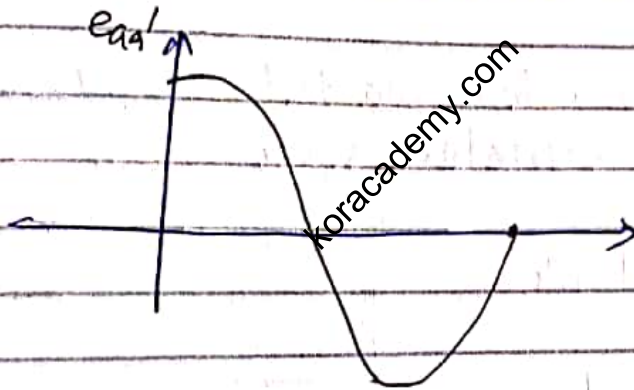
$$e_{aa'} = e_a - e_{a'} = e_a + (-e_{a'})$$



Electromagnetic torque always opposes mechanical torque.


The amount of mechanical energy wasted to compensate for the electromagnetic torque is converted into electrical energy.

DC generator \rightarrow o/p is electrical and DC.

DC motor \rightarrow i/p is DC \rightarrow at rotor

not directly.

DC Motor

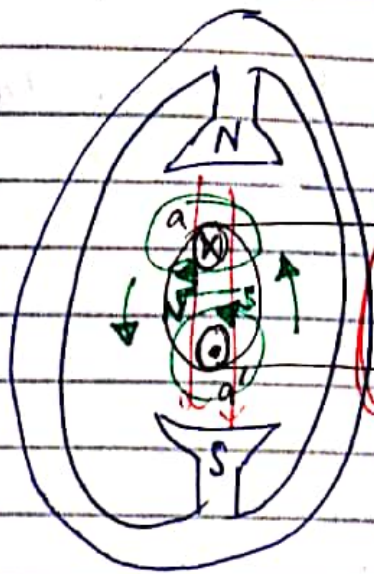


Commutator

Let DC supply is directly applied at the motor.

main flux
 T_e

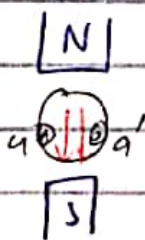After some time, N-S will lock each other.



for further rotation.

$$T = \theta_s \theta_r \cdot \sin \alpha$$

T_e will vanish in a little time if DC supply is directly connected. $\alpha = 0$

- For electromagnet torque to be produced;
- Both stator and rotor should have AC supply.
 - If one is DC, the other must have AC supply.

T_e cannot be produced if both stator and rotor have DC supplies.

So a commutator is introduced after the DC supply to get an AC current and hence get steady state torque.


T_e is called & it is produced from the interaction of stator and rotor fluxes. (called interaction torque)

Load torque and electromagnetic torque always oppose each other.

When supply is not there becomes AC after switch the τ_e is produced.




Generator

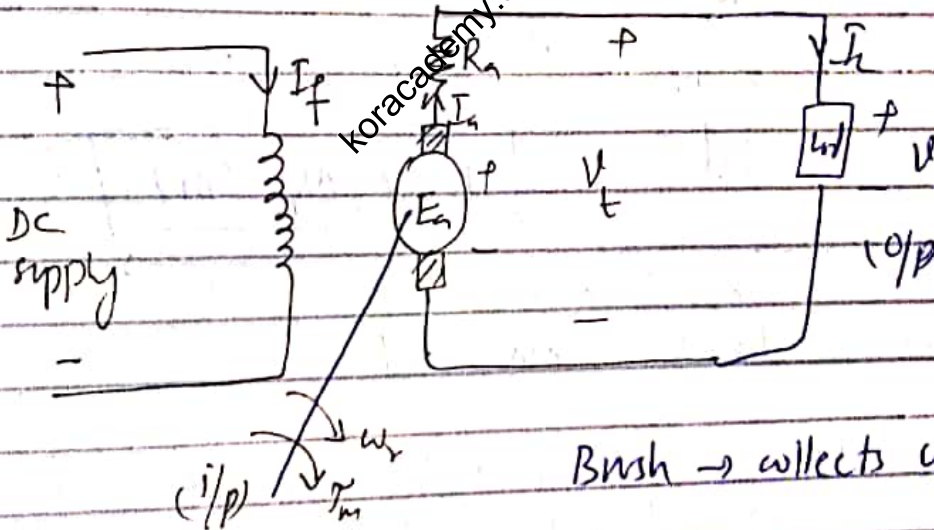

Brush \rightarrow collects current.

Motor

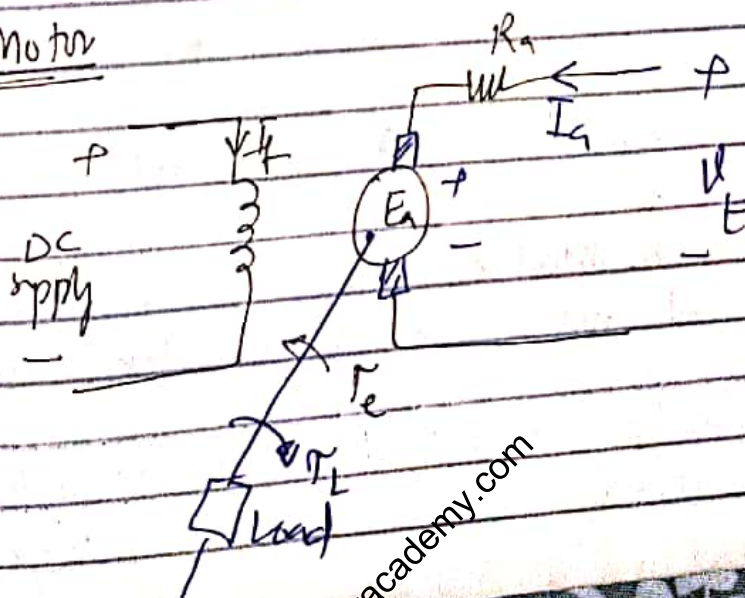

$$E_a(\text{avg}) = K \phi \omega_r$$

$\omega_r \rightarrow$ mechanical.

\rightarrow induced voltage in dc machine.

where

$$K = \frac{P Z}{2\pi A}, \quad \omega_r = \frac{2\pi N_r}{60}$$

$P =$ no. of poles.

Stator and rotor always has the same no. of poles.

\rightarrow The electromagnetiz torque developed in armature;

$$T_a(\text{avg}) = T_e = K \phi I_a$$

$$A_s \quad T_a = \frac{P_a}{\omega_r} = \frac{P_a}{\omega_r} \times I_a = \frac{K \phi \omega_r I_a}{\omega_r} = K \phi I_a$$

\rightarrow No. of parallel paths (A)

$$A = P$$

for lap windings.

$$A = 2$$

for wave windings.

$Z \rightarrow$ number of total armature conductors.

$T \rightarrow$ no. of turns = $Z/2$


$$N_r = \text{rpm} = \frac{120 f_e}{P}$$

$f_e \rightarrow$ electrical.
 \rightarrow the frequency of induced voltage in rotor.

$$\omega_r = \frac{2\pi N_r}{60}$$

Types of DC machines (Gen or motor)

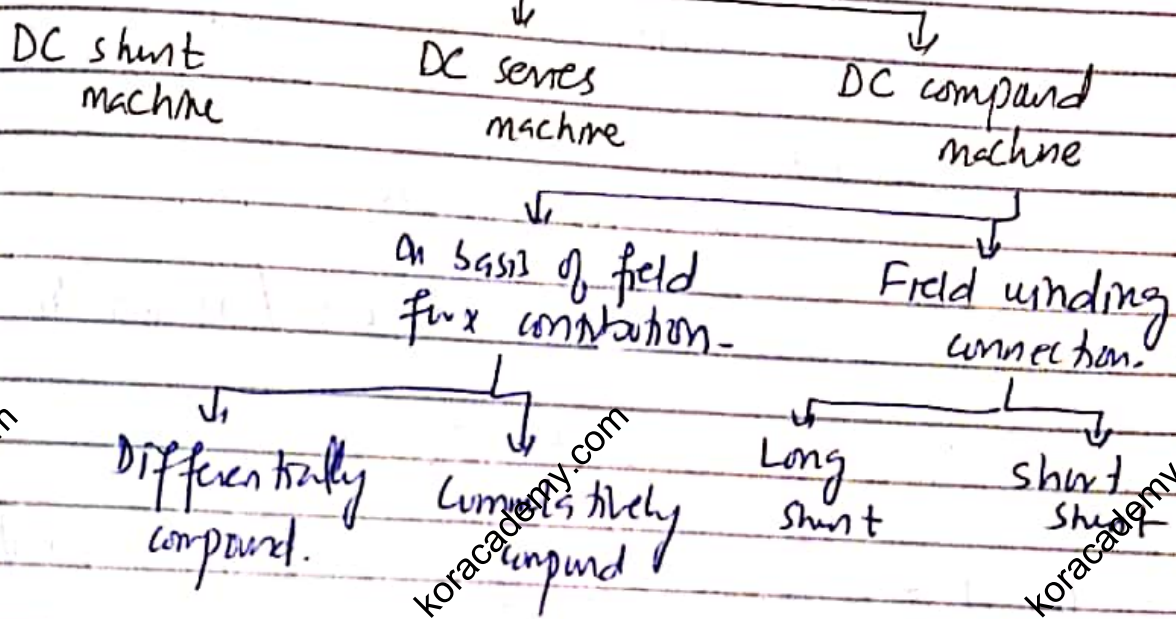- ① Separately excited DC machines.
- ② Self excited DC machine (residual flux).



→ Excitation refers to the field winding.

① If a separate DC supply is provided to the field winding → separately excited.

↳ If not mentioned → by default separately excited. ↳ little application.

② No separate supply to field winding. The supply will only be that generated or that given to the rotor.

→ If the field winding is connected in parallel with total armature → shunt machine

→ in series → series machine.

→ compound = series + shunt.



→ If series and shunt winding fluxes support each other → cumulative
 → If oppose → differential.

(1) DC Separately Excited machine.

The voltage E_g combined with the voltage of R_a is armature voltage.

i- Gen

ii- Motor

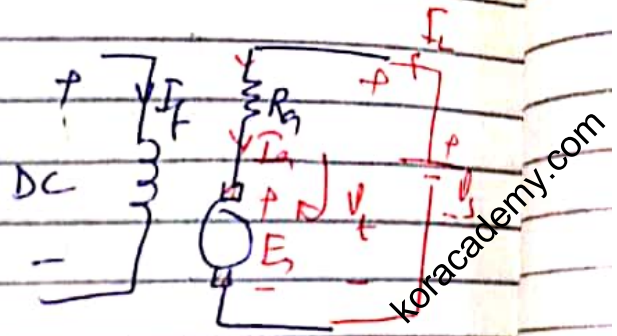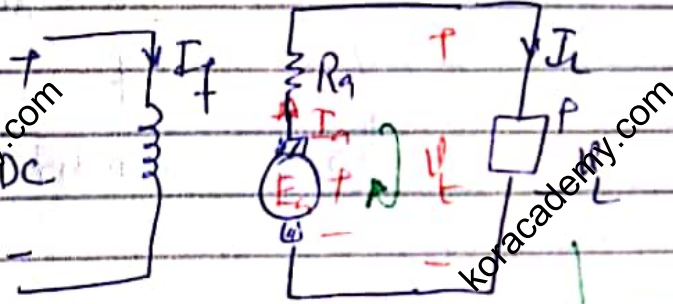

As $\phi_f \propto I_f$

$\phi = \phi_f \times I_L$

DC $\Rightarrow I_f = \text{constit} \Rightarrow \phi_f = \text{constit}$

$\phi_f \propto I_f$
 $\phi_f = \text{constit}$
 $I_f = \text{constit}$

KVL $\Rightarrow E_g = V_t + I_a R_a$

$I_a = I_L$

Armature power, $P_a = E_g I_a$

$P_a = V_t I_a + I_a^2 R$

$P_a = V_t I_a + I_a^2 R$

\downarrow \downarrow \downarrow
 i/p o/p copper losses.

\downarrow
 $\phi_{LD} \rightarrow \text{brush drop}$

KVL $\Rightarrow E_g = V_t - I_a R_a$

$I_a = I_L$

$E_g I_a = V_t I_a + I_a^2 R$

$P_{in} = V_t I_L + I_a^2 R$

$P_a = P_m + \frac{I_a^2 R}{a}$


\downarrow
 o/p

(2) Self Excited DC machine

No need of a separate DC supply.

(i) Shunt Machine

(a) Generator

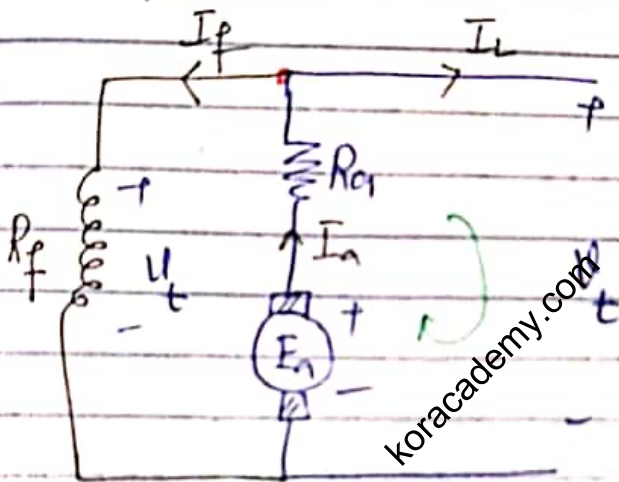

$$\text{As } \phi_f \propto I_f$$

$$I_f = \frac{V_t}{R_f} = \text{const}$$

$$\phi_f = \text{const}$$

KCL

KVL

$$\begin{aligned} I_a &= I_L + I_f \\ E_a &= V_t + I_a R_a \end{aligned}$$

$$\text{Power} = E_a I_a = V_t I_a + I_a^2 R_a$$

$$P_a = V_t (I_L + I_f) + I_a^2 R_a$$

$$= V_t I_L + V_t I_f + I_a^2 R_a$$

$$P_a = V_t I_L + I_f^2 R_f + I_a^2 R_a$$


out

field winding loss

armature resistance loss.

↳ copper loss

(b) Motor

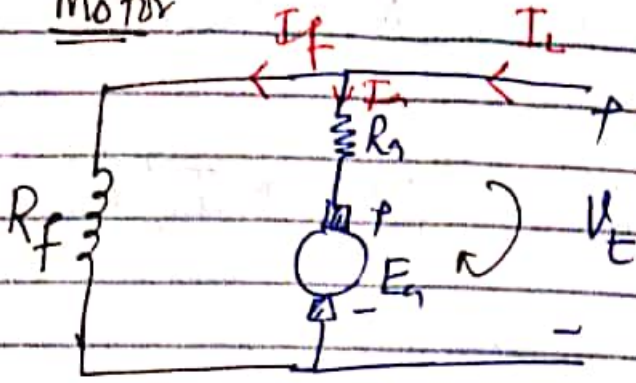

$$I_L = I_a + I_f$$

$$I_a = I_L - I_f$$

$$E_a = V_t - I_a R_a$$

$$P = E_a I_a = V_t I_a - I_a^2 R_a = V_t (I_L - I_f) - I_a^2 R_a$$

$$E_a I_a = V_t I_L - V_t I_f - I_a^2 R_a$$

$$V_t = I_f R_f$$

$$P_a = V_t I_L - I_f^2 R_f - I_a^2 R_a$$


W/P

W/P

Losses

ii. Series Machine

(a) Generator

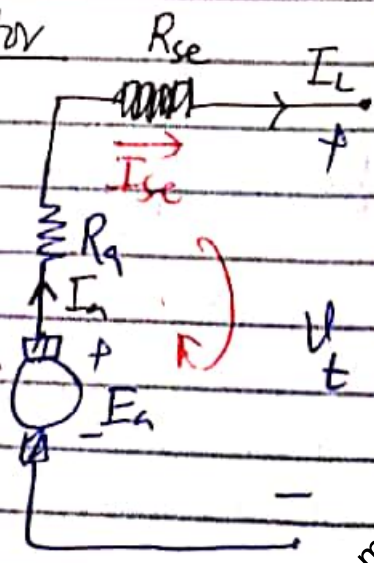

ϕ_{se} & I_{se}

$$I_{se} = I_L = I_a$$

$\phi_{se} \neq \text{constant}$

b/c I_L is not constant

→ depends on the load

KVL \Rightarrow

$$E_g = V_t + I_a (R_s + R_{se})$$

$$P = E_g I_a = V_t I_a + I_a^2 R_s + I_a^2 R_{se}$$

$$I_g = I_L = I_{se}$$


$$P_g = V_t I_L + I_a^2 R_s + I_{se}^2 R_{se}$$

developed

P_{out}

losses

(5) MOTOR

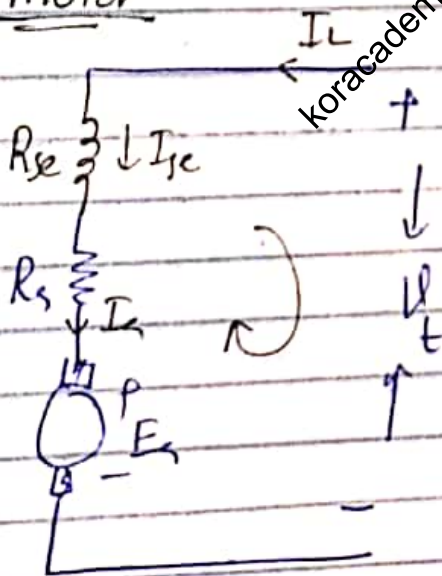

$$\Phi_{se} \propto I_{se}$$

$$I_{se} = I_L = I_a$$

$$E_g = V_t - I_a (R_s + R_{se})$$

$$Power = E_g I_a = V_t I_a - I_a^2 R_s - I_a^2 R_{se}$$

$$P_a = V_t I_L - I_a^2 R_s - I_{se}^2 R_{se}$$

$\frac{1}{2} P$


P_m

losses

DC Compound Machine

(i) Long Shunt DC machine series + shunt

(a) Generator

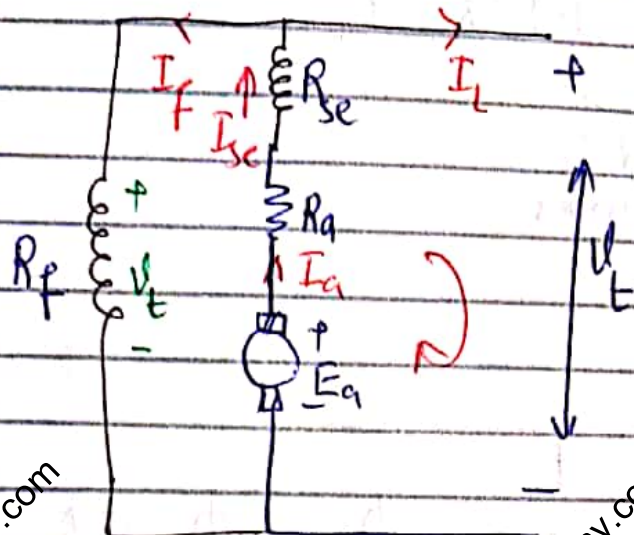

Number of turns in series winding is less but the wire is thicker.

No. of turns in shunt winding are more but the wire is thinner.

$$\phi_{total} = \phi_f + \phi_{se}$$

$$\phi_f \propto I_f$$

$$\phi_{se} \propto I_{se}$$

$$I_f = \frac{V_t}{R_f}$$

V_t is always constant.

$$I_f = \text{constant} \Rightarrow \phi_f = \text{constant}$$

$I_{se} = I_L \neq \text{constant} \Rightarrow$ depends on the load
 $\Rightarrow \phi_{se} \neq \text{constant} \Rightarrow \phi_{total} \neq \text{constant}$

Induced voltage will be effected.

$$I_a = I_{se} = I_f + I_L$$

KVL \Rightarrow


$$E_a = V_t + I_a R_a + I_a R_{se}$$

$$\text{Power} = E_a I_a = V_t I_a + I_a^2 R_a + I_a^2 R_{se}$$

$$E_a I_a = V_t I_a + I_a^2 R_a + I_{se}^2 R_{se}$$

ii. Short Shunt DC machine

(a) Generator

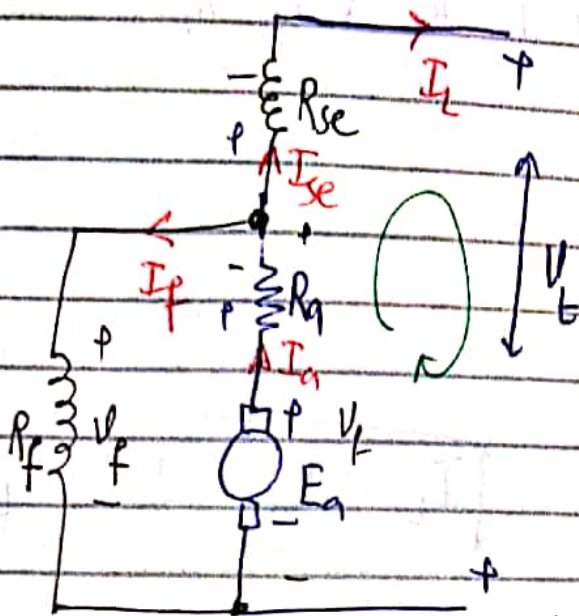

$$\phi_{total} = \phi_f + \phi_{se}$$

$$I_a = I_{se} + I_f$$

$$I_{se} = I_L$$

$\phi_{total} \neq \text{constant}$
 \rightarrow depends on the load.

$$E_a - I_a R_a - V_f = 0$$

$$V_f = E_a - I_a R_a$$

(2)

$$V_f - I_{se} R_{se} - V_t = 0$$

$$V_f = V_t + I_{se} R_{se}$$

$$I_f = \frac{V_f}{R_f} \neq \frac{V_t}{R_f}$$

Complete KVL \rightarrow

$$E_a = V_t + I_a R_a + I_{se} R_{se}$$

$$P_{out} = E_a I_a = V_t I_a + I_a^2 R_a + I_a I_{se} R_{se}$$

$$P_a = V_t (I_L + I_f) + I_a^2 R_a + (I_{se} + I_f) I_a R_{se}$$

$$P_a = V_t I_L + V_t I_f + I_a^2 R_a + I_{se}^2 R_{se} + I_{se} I_f R_{se}$$

$$P_a = V_t I_L + I_a^2 R_a + I_{se}^2 R_{se} + I_f (V_t + I_{se} R_{se})$$

$\underset{= V_f}{V_t + I_{se} R_{se}}$


$$P_g = V_t I_L + I_a^2 R_a + I_{sc}^2 R_{se} + V_f I_f$$

$$\Rightarrow P_g = V_t I_L + I_a^2 R_a + I_{sc}^2 R_{se} + I_f^2 R_f$$

$\hookrightarrow I_f = V_f / R_f$

↓ ↓ ↓
i/p *o/p* Losses

(b) Motor

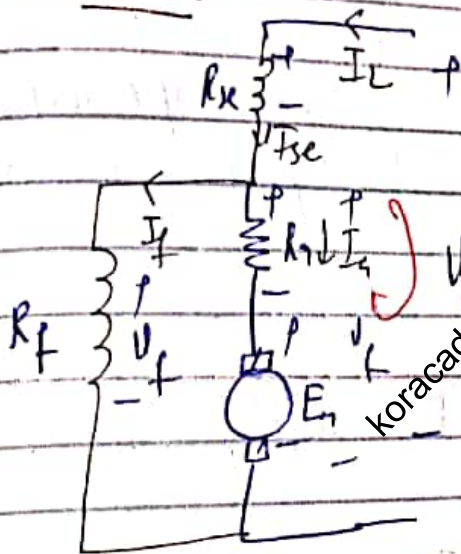

$$I_L = I_{se} = I_a + I_f$$

$$E_g + I_a R_a - V_f = 0$$

$$V_f = E_g + I_a R_a$$

$$V_f + I_{se} R_{se} - V_t = 0$$

$$V_f = V_t - I_{se} R_{se}$$

$$I_f = \frac{V_f}{R_f} = \frac{V_t - I_{se} R_{se}}{R_f}$$

KVL $\Rightarrow E_g + I_a R_a + I_{se} R_{se} - V_t = 0$


$$\Rightarrow E_g = V_t - I_a R_a - I_{se} R_{se}$$

$$\text{Power} = P_g = V_t I_L - I_a^2 R_a - I_{se}^2 R_{se} - I_f^2 R_f$$

↓ ↓
i/p *o/p*

Questions

Q1. A separately excited DC motor has $R_a = 0.5 \Omega$. It runs from 250V DC supply drawing an armature current of 20A at 1500 rpm. For the same field current (means flux is not changing), the torque developed in N-m for an armature current of 10A will be 15.278 Nm.

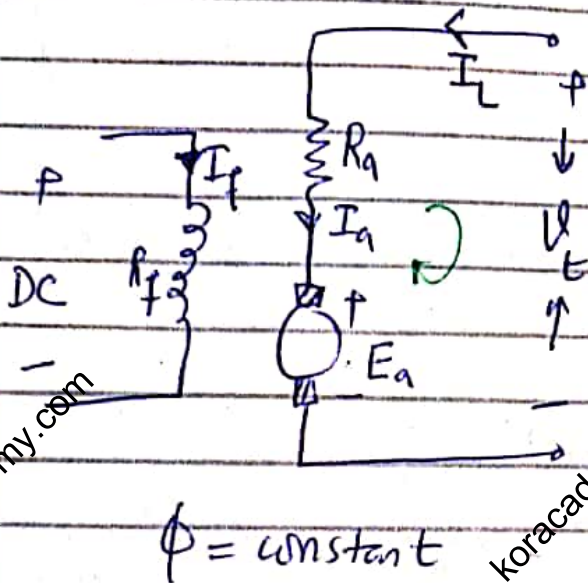

Case I

at 250V, $I_{a1} = 20A$,

$N_1 = 1500 \text{ rpm}$.

$$T = \frac{K \phi I_a}{a}$$

$$T = \frac{P_g}{\omega} = \frac{E_a I_a}{\omega}$$

$$K = \frac{P_z}{2\pi A}$$

$\phi = \text{constant}$

Also As $T \propto \phi I_a$

$$\frac{T_2}{T_1} = \frac{\phi_2 I_{a2}}{\phi_1 I_{a1}}$$

$$\Rightarrow T_2 = \frac{I_{a2}}{I_{a1}} \times T_1$$

where $T_1 = \frac{E_{a1} I_{a1}}{\omega_{r1}}$

KVL $E_{a1} = V_t - I_{a1} R_a = 250 - (20 \times 0.5)$

$$E_{a1} = 250 - 10 = 240 \text{ V}$$

$$\Rightarrow I_{a1} = \frac{(240)(20)}{2\pi \times 1500} \times 60 = 30.557 \text{ N-m}$$

Case II

$$V_t = 250V, I_{a2} = 10A, T_2 = ?$$

As $\frac{T_2}{T_1} = \frac{I_{a2}}{I_{a1}} \Rightarrow T_2 = \frac{10}{20} \times 30.557$

$$\Rightarrow T_2 = 15.28 \text{ Nm.}$$

or by another method.

$$T_2 = \frac{E_{a2} \cdot I_{a2}}{\omega_{r2}}$$

where $E_{a2} = V_t - I_{a2} R_a$

$$\omega_{r2} = ?$$

As $E_1 = K \phi \omega_{r1} \Rightarrow \frac{E_{a2}}{E_{a1}} = \frac{K \phi_2 \omega_{r2}}{K \phi_1 \omega_{r1}}$

$$\Rightarrow \frac{E_{a2}}{E_{a1}} = \frac{\omega_{r2}}{\omega_{r1}} \Rightarrow \omega_{r2} = \underline{\hspace{2cm}}$$

Q2. A 4 pole dynamo wave band armature has 51 slots containing 20 conductors in each slot. The induced emf is 357V and speed is 8500 rpm.
The fm per pole is 1.235mWb

$$P = 4, A = 2$$

$$\text{No. of slots} = 51$$

$$\text{No. of conductors/slot} = 20$$

$$N_r = 8500 \text{ rpm}$$

$$E = 357V$$

$$E_g = k \phi \omega_r = \frac{P \ell}{2 \pi A} \cdot \phi_p \times \frac{2 \pi N_r}{60}$$

$$\Rightarrow E_g = \frac{P \ell}{A} \cdot \phi_p \cdot \frac{N_r}{60}$$

$$z = ? \quad z = (\text{no. of conductors/plot}) (\text{total slots})$$

$$z = 20 \times 51 = 1020$$

$$\Rightarrow \phi_p = \frac{60 E_g A}{P \ell N_r} = \frac{(60)(357)(2)}{(800)(4)(1020)}$$

$$\Rightarrow \phi_p = 1.0235 \text{ Wb}$$

$$\text{No. of turns} = T = \frac{z}{2} = \frac{1020}{2} = 510$$


Q3. At 50% of full load, the armature current drawn by a DC shunt motor is 40A when connected to a 200V DC. By decreasing the field flux, its speed is raised by 20%, this also causes 10% increase in torque. The R_a including the brush is 1.5 Ω . The %age change in field current is _____ (neglect saturation).

$$\% \text{age change} = \frac{\phi_2 - \phi_1}{\phi_1} \times 100$$

$$\% \text{age change} = \frac{I_{f2} - I_{f1}}{I_{f1}} \times 100$$

$$E_g = V_{KO} + I_a R_a \quad (T = k \phi I_a)$$

$$E_g = k \phi \omega_r$$

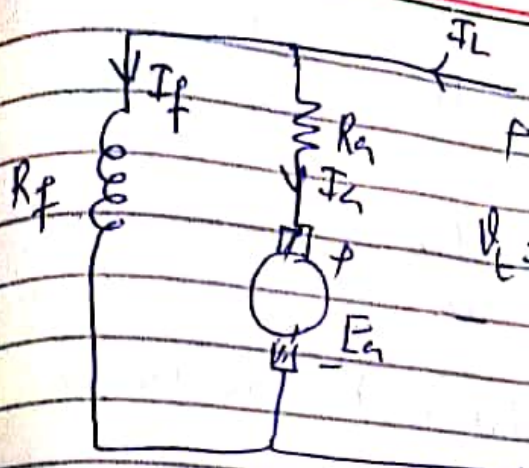

Case 1

$V_t = 200V$ $I_{a1}, E_{g1}, \omega_{r1}$
 $N_{r1}, \tau_1, \phi_1, I_{f1}$
 $I_{a1} = 40A$

Case II

$\omega_{r2} = 1.2 \omega_{r1}$, $\tau_2 = 1.1 \tau_1$

$R_a = 1\Omega$, $I_{f2} = ?$ $\phi_2 = ?$

$$\frac{T_2}{T_1} = \frac{k \phi_2 I_{a2}}{k \phi_1 I_{a1}} = \frac{\phi_2}{\phi_1} \times \frac{I_{a2}}{I_{a1}}$$

$$\Rightarrow \frac{1.1 T_1}{T_1} = \frac{\phi_2 I_{a2}}{\phi_1 I_{a1}}$$

$$\Rightarrow \frac{\phi_2}{\phi_1} = 1.1 \left(\frac{I_{a1}}{I_{a2}} \right) = \frac{1.1 \times 40}{I_{a2}}$$

$$\Rightarrow I_{a2} = 44 \times \left(\frac{\phi_1}{\phi_2} \right) \quad \text{--- let } n \text{ --- (A)}$$

Now $\frac{E_{g2}}{E_{g1}} = \frac{k \phi_2 \times \omega_{r2}}{k \phi_1 \omega_{r1}} = \frac{\phi_2}{\phi_1} \times \frac{1.2 \omega_{r1}}{\omega_{r1}}$

$$\frac{E_{g2}}{E_{g1}} = 1.2 \times \frac{\phi_2}{\phi_1} \quad \text{--- } \frac{1}{n} \text{ ---}$$

$$\text{As } E_{g1} = V_t - I_{g1} R_s = 200 - (40 \times 1) = 160 \text{ V}$$

we have;

$$\frac{E_{g2}}{160} = \frac{1}{n} (1.2) \quad , \quad I_{g2} = 44n \quad \text{where } n = \frac{\phi_1}{\phi_2}$$

$$\frac{V_t - I_{g2} R_s}{160} = \frac{1.2}{n} \Rightarrow \frac{200 - (44n)(1)}{160} = \frac{1.2}{n}$$

$$\Rightarrow (1.2)(160) = 200n - 44n^2$$

$$44n^2 - 200n + 192 = 0$$

$$\Rightarrow n = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$n = \frac{+200 \pm \sqrt{(-200)^2 - 4(44)(192)}}{2 \times 44}$$

$$\Rightarrow n = \frac{200 \pm 78.79}{88}$$

$$\Rightarrow n_1 = 3.16 = \frac{\phi_1}{\phi_2} \quad , \quad n_2 = 1.37 = \frac{\phi_1}{\phi_2}$$

Checking for the correct value of n .

(A) $\Rightarrow I_{g2} = 139.04 > \text{full load current so } n_1 \text{ X}$

Putting n_2

(A) $\Rightarrow I_{g2} = 60.2 < \text{full load } \approx 80$

$$\frac{\Phi_1}{\Phi_2} = 1.37 \Rightarrow \frac{\Phi_2}{\Phi_1} = \frac{1}{1.37} = 0.72$$

$$\% \text{ change} = \frac{\Phi_2 - \Phi_1}{\Phi_1} = \left(\frac{\Phi_2}{\Phi_1} - 1 \right) = -28\% \text{ decrease}$$

Q4. A DC shunt generator delivers 60 kW at 240 V and 360 rpm. The armature and field resistances are 0.015 Ω and 60 Ω . (Allowing 2 V per brush drop).

The speed of machine (rpm) when running as a shunt motor taking 60 kW input at 240 V will be 343.16 rpm

Rating

DC Gen

DC Motor

eg 20 kW, 200 V

eg 50 W, 100 V

↓
EI o/p power
 V_t


↓
o/p / load / mech power $\rightarrow V_t$ (i/p)

$$E_g = k \phi \omega_r$$

$$\frac{E_{g2}}{E_{g1}} = \frac{k \phi_2 \frac{\omega_{r2}}{\omega_{r1}}}{k \phi_1} = \frac{\phi_2 \times N_{r2}}{\phi_1 \times N_{r1}}$$

Ex 10 Acting as DC shunt Gen

$$V_t = 240V, R_f = 0.015\Omega$$

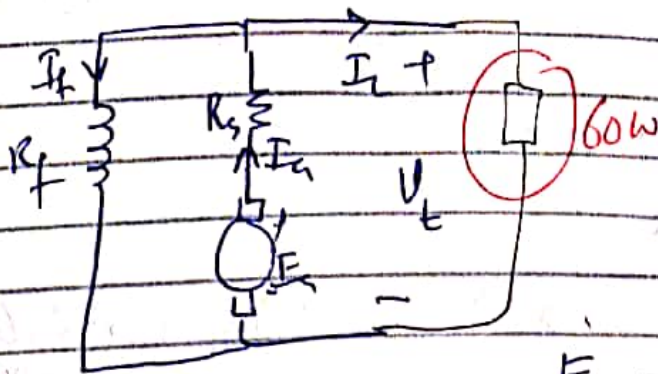

$$R_f = 60\Omega$$

$$I_f = \frac{V_t}{R_f} = \frac{240}{60} = 4A$$

$$E_{g1} = V_t + I_{a1}R_f + 2V$$

↓
brushes

$$E_{g1} = 240 + I_{a1}(0.015) + 2$$


$$60 = V_t \times I_L \Rightarrow I_L = \frac{60 \times 10^3}{240} = 250A$$

$$I_a = 250 + 4 = 254$$

$$E_{g1} = 240 + (254)(0.015) + 2$$

$$\Rightarrow E_{g1} = 245.81V$$

10 Acting as DC motor

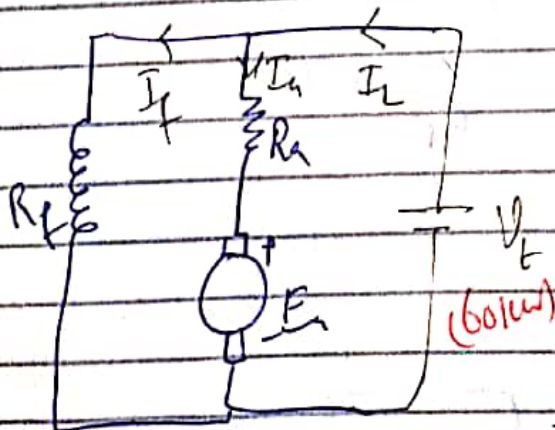

$$60 = V_t \times I_L$$

$$\Rightarrow I_L = 250A$$

$$I_f = \frac{V_t}{R_f} = \frac{240}{60} = 4A$$

$$I_{a2} = 250 - 4 = 246A$$

$$E_m = V_t - I_{a2}R_s - 2V = 240 - 246(0.015) - 2$$

$$E_{g2} = 234.31 \text{ V}$$

$$N_{r2} = ?$$


$$N_{r2} = \frac{E_{g2}}{E_{g1}} \times \frac{\Phi_1}{\Phi_2} \times N_{r1}$$

$$= \frac{234.31}{245.81} \times 1 \times 360 \Rightarrow N_{r2} = 343.16 \text{ rpm}$$

B/c $I_{f1} = I_{f2} \Rightarrow I_f = \text{const}$
 $\Rightarrow \Phi_f = \text{const}$

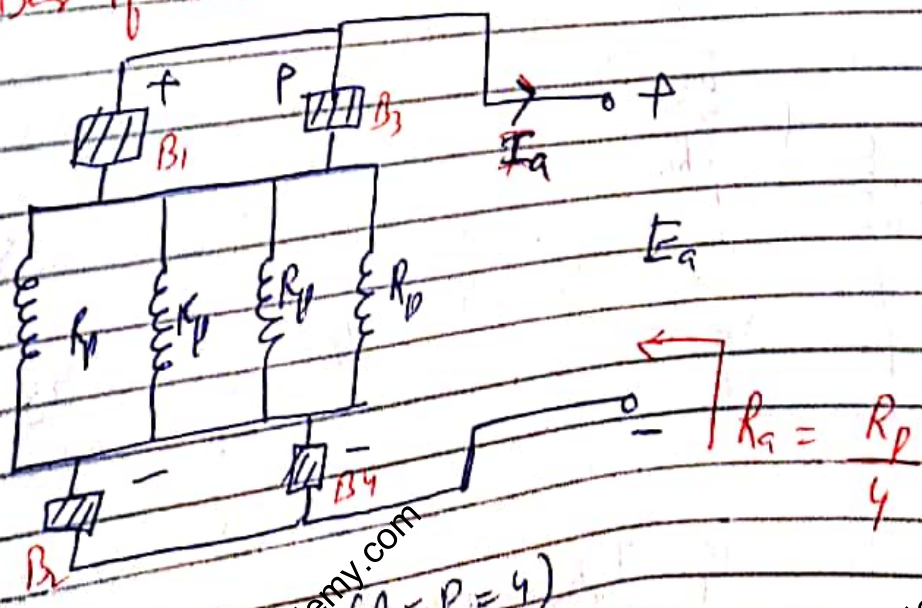
Q5. A 4 pole lap wind DC generator has developed pair of P wts and voltage of E wts. Two adjacent brushes are removed as they are worn out. If the machine operates with the remaining brushes, the developed voltage and power that can be obtained are $\frac{P}{4}, E$.

Number of brushes = No. of parallel paths.



$P = 4$
 $(A = P = 4)$

If drawn in another way;

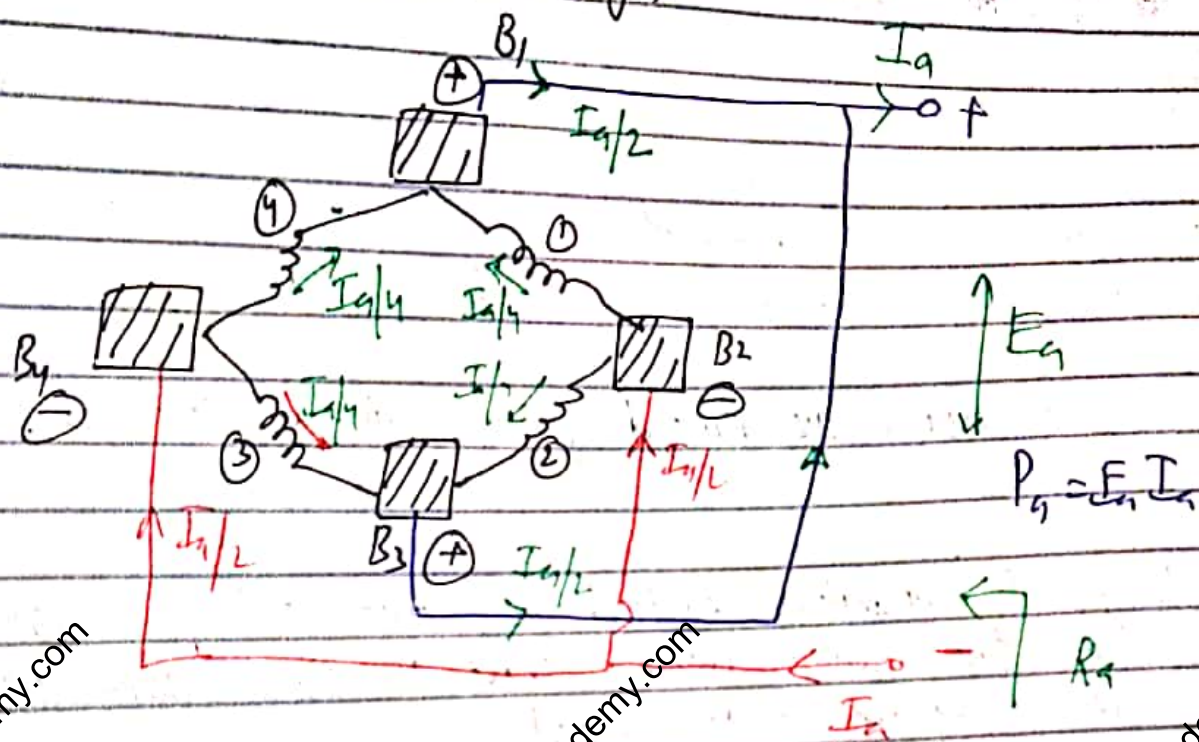

⇒ If B_1 is known, the role of ① and ② finishes.

The new current at the terminal $I' = I_a/2$

No effect on induced voltage $\because E' = E_g$

$$P' = E' \times I' = \frac{E_g I_a}{2} \Rightarrow \boxed{P' = \frac{P}{2}}$$

⇒ If two adjacent switches are known by B_2 and B_3 .
The role of ①, ② and ③ will finish.

The new current is $I' = I_a/4$

No effect on voltage $\because E' = E_g$

$$P' = E' \times I' = E_g \times I_a/4$$

$$\Rightarrow \boxed{P' = \frac{P}{4}}$$

→ If two opposite coils are removed.

$$I_a' = 0 \rightarrow P' = 0$$

(Wae winding = permanently zero > 2 brushes
s/c only two no. of parallel paths)


If n brushes are removed, $n+1$ coils are affected.

Q6. A separately excited DC shunt motor is driving a fan load whose torque is proportional to the square of its speed. When 100V is applied to the motor, the current taken is 8A, speed being 500 rpm. Assume $R_a = 1 \Omega$.

The applied voltage and current drawn by armature when speed reaches 750 rpm are 156V, 18A.

$$T_a \propto N^2$$

Case I $V_{t1} = 100V$, $I_{a1} = 8A$, $N_1 = 500 \text{ rpm}$
 $R_a = 1 \Omega$

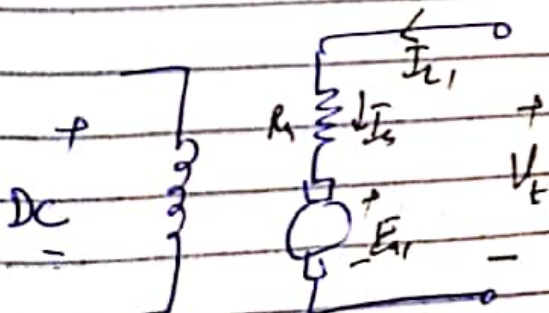

Case II

$N_2 = 750 \text{ rpm}$,
 $V_t = ?$, $I_{a2} = ?$

$$E_{b2} = V_{t2} - I_{a2} R_a$$

$\phi = \text{constant}$

(The two eqs)

$$E_b = k \phi \omega$$

$$I_a = k \phi^{-1} T$$

$$\text{Variable} = I_a^2 R_a + I_{sc}^2 R_{se} = I_a^2 (R_a + R_{se})$$

Under maximum efficiency;
constant losses = variable losses

Q7. The R_a of permanent magnet DC motor is 0.8Ω .
At no load, the motor draws 1.5 A from 25 V and
runs at 1500 rpm .

η while operating at 1500 rpm drawing current of 3.5 A for
the same speed will be 48%

Gen \rightarrow No Load $\rightarrow I_a = 0 \text{ A}$
Motor \rightarrow No Load \rightarrow Power is developed in armature
but shaft power is 0 (no power to load but developed
power is available)

\rightarrow The power i/p is only utilized to compensate the losses
inside the motor. \rightarrow No load losses.

No load power = constant = Rotational losses

Case F

No Load

$$E_{a1} = V_{t1} - I_{a1} R_a = 25 - (1.5)(0.8)$$

$$\Rightarrow E_{a1} = 23.8 \text{ V}$$

$$\begin{aligned} \hookrightarrow \text{No load power} &= E_{a1} I_{a1} = 23.8 \times 1.5 \\ \text{no load loss} &= 35.7 \text{ W} \end{aligned}$$

\hookrightarrow rotational loss.

$$N_1 = 1500 \text{ rpm}$$

Case # $V_t = 25V, 3.5A.$

$$\eta_m = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + \text{losses}}$$

$$\eta_m = \frac{P_{in} - \text{Losses}}{P_{in}}$$

$$\eta_m = 1 - \frac{\text{Losses}}{P_{in}}$$

$$P_{in} = 3.5 \times 2.5 =$$

$$\begin{aligned} \text{Losses} &= 35.7 \text{ W} + \text{Variable losses.} \\ &= 35.7 + (3.5)^2 (0.8) \\ &= 35.7 + 9.8 \quad I^2 R_s \end{aligned}$$

$$\Rightarrow \text{Losses} = 45.5 \text{ W}$$

$$\Rightarrow \eta_m = 1 - \frac{45.5}{8.75} = 48\% \quad \text{Ans}$$

If by another method.

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_a = P_d = E_{in} \times I_{in} = (V_t - I_{in} R_a) I_{in}$$

$$P_d = (25 - (3.5)(0.8)) 3.5 = 77.7 \text{ W}$$

$$P_{sh} = P_o = P_d - \text{No load losses} = 77.7 - 35.7 = 42 \text{ W}$$

$$\eta = \frac{42}{8.75} = 0.48 = 48\%$$

Q8. In a DC motor, running at 2000 rpm, the hysteresis and eddy current loss are 500 W and 200 W respectively. If the flux remains constant, the speed at which the total iron loss are halved will be 1140 rpm.

$$P_h \propto B_m^{1.6} f$$

$$P_e \propto B_m^2 f^2$$

$$P_i = P_e + P_h$$

$$B_m = \text{constant} \Rightarrow [P_h \propto f \text{ and } P_e \propto f^2]$$

$$P_h = a f \text{ and } P_e = b f^2$$

Case i: $N_1 = 2000 \text{ rpm}$, $P_{i1} = P_{e1} + P_{h1} = 500 + 200 = 700 \text{ W}$

Case ii

$$P_{i2} = \frac{P_{i1}}{2} = \frac{700}{2} = 350 \text{ W}$$

$$\Rightarrow P_{e2} + P_{h2} = 350 \text{ --- (A)}$$

$$N = \frac{120 f}{P} \Rightarrow N \propto f$$

$$\Rightarrow P_h = K_1 N, \quad P_{e2} = K_2 N^2$$

$$P_{h1} = K_1 N_1, \quad P_{e1} = K_2 N_1^2$$

$$500 = K_1 \times 2000, \quad 200 = K_2 (2000)^2$$

$$K_1 = \frac{1}{4}$$

$$K_2 = \frac{1}{2 \times 10^4}$$

$$(A) \Rightarrow 350 = \frac{1}{2 \times 10^4} N_2^2 + \frac{1}{4} N_2$$


$$\Rightarrow \frac{N_2^2}{2 \times 10^4} + \frac{N_2}{4} - 350 = 0$$

$$\Rightarrow N_2 = \frac{-\frac{1}{4} \pm \sqrt{\left(\frac{1}{4}\right)^2 + 4 \left(\frac{1}{2 \times 10^4} \times 350\right)}}{2 \times \left(\frac{1}{2 \times 10^4}\right)}$$

$$N_2 = 1140 \text{ rpm}, 6140 \text{ rpm}$$

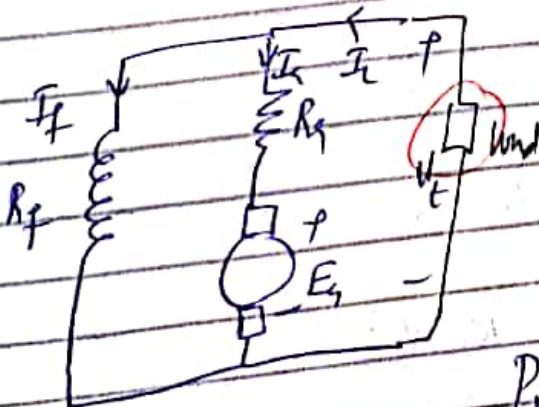Q9. A 10kW, 250V DC shunt generator has $\eta = 85\%$ at no load losses of 400W. The armature circuit and shunt field resistances are 0.5Ω and 250Ω.

- Calculate the shaft power i/p and η at rated load.
- Calculate the max η and corresponding power o/p.



At rated conditions;

$$P_{out} = 10 \text{ kW}, V_t = 250 \text{ V}$$

$$V_f = 250 \text{ V}$$

$$P_{NL} = 400 \text{ W}$$

$$R_a = 0.5 \Omega, R_f = 250 \Omega$$

$$P_m = P_{out} + \text{Losses}$$

$$P_m = 10 \text{ kW} + \text{no load losses} + I_a^2 R_a + I_f^2 R_f$$

$$P_m = 10 \text{ kW} + 400 \text{ W} + I_a^2 R_a + I_f^2 R_f$$

$$V_t = 250 \text{ V} \quad \Rightarrow \quad I_f = \frac{V_t}{R_f} = \frac{250}{250} = 1 \text{ A.}$$

$$A \quad 10 \text{ kW} = V_t \times I_L$$

$$\Rightarrow I_L = \left(\frac{10 \times 10^3}{250} \right) = 40 \text{ A}$$

$$I_a = I_L + I_f = 41 \text{ A}$$

$$\Rightarrow P_m = (10 \times 10^3) + 400 + (41)^2 (0.5) + (1)(250)$$

$$\Rightarrow P_m = 11490.5 \text{ W} = 11.49 \text{ kW}$$

Electrical equivalent of mechanical.

$$\eta_{\text{rated}} = \frac{P_{\text{out}}}{P_m} = \frac{10 \times 10^3}{11.4 \times 10^3} \Rightarrow \eta = 0.87 = 87\%$$

(ii) At maximum efficiency;
constant losses = variable losses.

The ip and op power calculated will not be considered here s/c these are rated powers.

$$\eta_{\text{max}} = \frac{P_{\text{out}} / \eta_{\text{max}}}{P_{\text{in}} / \eta_{\text{max}}} = \frac{P_{\text{out}} (\text{max})}{P_{\text{in}} (\text{max}) + 2 \times \text{constant losses}}$$

$$\text{Variable loss} = I_a^2 R_a = 400 + I_f^2 R_f = 400 + 250 = 650$$

$$I_a = \sqrt{\frac{650}{R_a = 0.5}} \Rightarrow I_a = 36.05 \text{ A}$$

$$\Rightarrow I_a = 36.05 \text{ A} \quad \eta_{\text{max}}$$

$$\Rightarrow I_L = 35.05 \text{ A}$$

$$P_{out}/\eta_{max} = 250 \times 35.05 = \boxed{8763.8 \text{ W}}$$

$$\eta_{max} = \frac{8763.8}{8763.8 + 2(650)}$$

$$\Rightarrow \boxed{\eta_{max} = 0.87 = 87\%}$$


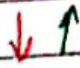
1/2 power at maximum efficiency;

$$P_m = 8763.87 + 2(650) = \underline{\underline{10.06 \text{ kW}}}$$

Armature Reaction

Armature is on the rotor.

The effect of armature flux (flux due to flow of I in armature conductor) on the stator flux is known as armature reaction.


- i. Cross magnetizing effect 
- ii. De magnetizing effect 

The commutation action (reversal of current) happens at the brush axis.

The axis at which induced voltage becomes zero is called magnetic neutral axis.
y here the axis brushes.

→ Current reversal (x mto .) takes place at the brush axis.



Case I.

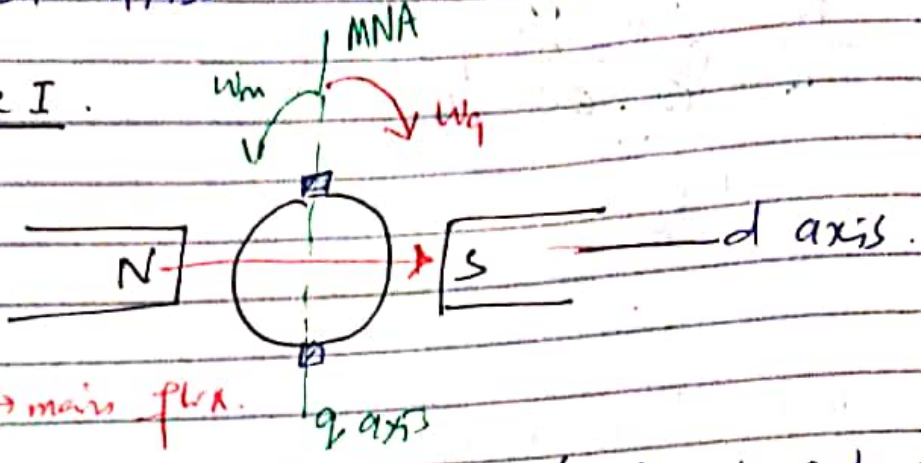

→ The axis of main flux (pole to pole axis) is known as direct axis.


→ The axis perpendicular to d axis is called quadrature axis or Multipolar axis. The d axis is called geometrically neutral axis.

Case II.

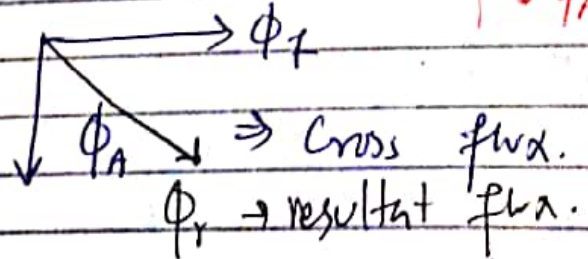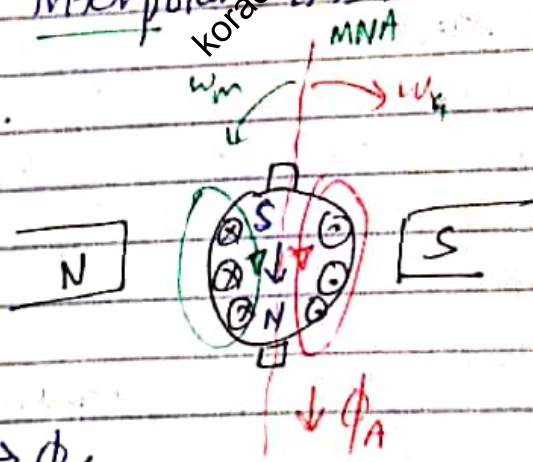

$\Phi_f = \text{fixed}$, $\Phi_A \rightarrow \text{depend load}$.
 $\hookrightarrow I_a \rightarrow \Phi_f$.

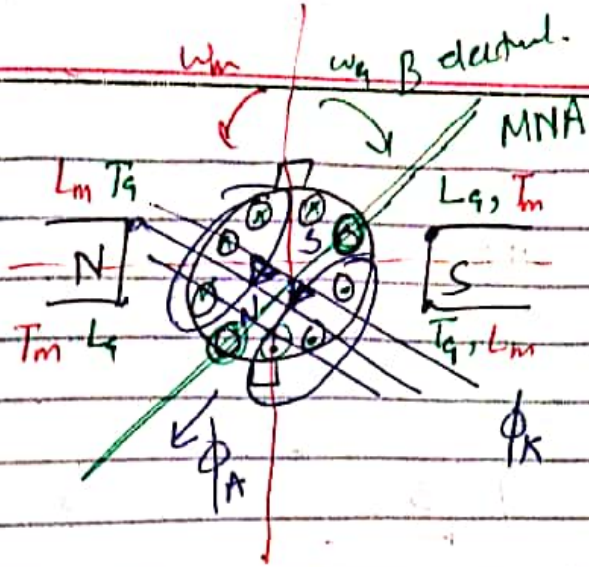When velocity component of conductor is parallel to the magnetic lines, current is zero.





Asymmetric reaction \Rightarrow Delayed commutation.
 New Brush \neq current reversal \Rightarrow sparking

Each N-S pole has two tips.
 First after rotation \Rightarrow leading pole tip and
 the one to follow \Rightarrow trailing pole tip.

From asymmetric reaction;

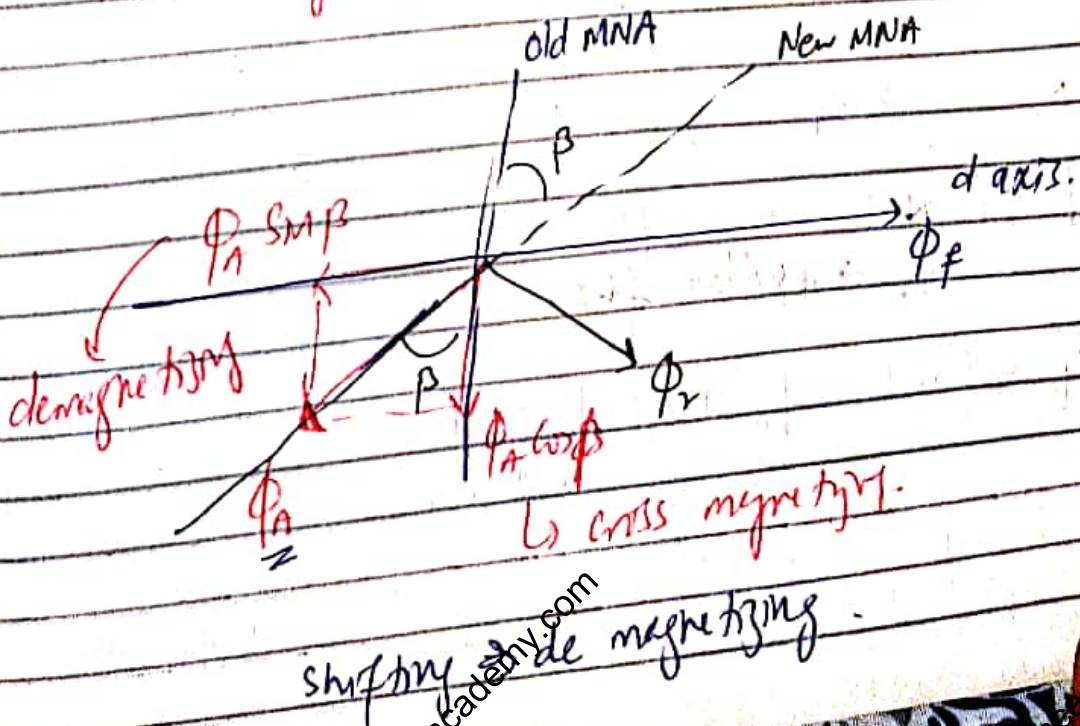In gen, weakening of flux will occur on the
 leading tips and strengthening at trailing tips.
 In motor, strengthening at leading and weakening
 at trailing pole tips.



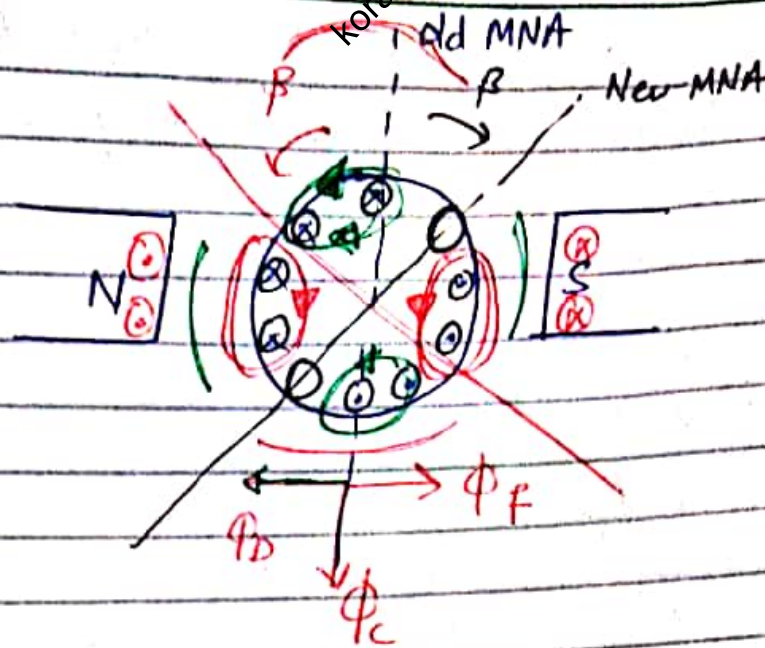

P, Z, A, I_a . ($A \rightarrow$ no. of ll paths)

The peak value of armature mmf = $\frac{1}{2} \left[\frac{Z}{P} \cdot \frac{I_a}{A} \right]$

$AT_d / \text{pole} = \frac{4\beta}{360^\circ} \left[\frac{1}{2} \frac{Z}{P} \cdot \frac{I_a}{A} \right]$

$AT_c / \text{pole} = \left(\frac{360^\circ - 4\beta}{360^\circ} \right) \frac{1}{2} \frac{Z}{P} \cdot \frac{I_a}{A}$

$\beta^\circ =$ electrical degree.


→ Compensating winding compensates for the cross magnetizing flux.

↓
dominant


$AT_{\text{compensating}} / \text{pole} = \frac{1}{2} \left[\frac{Z}{P} \cdot \frac{I_a}{A} \right] \frac{\text{Pole arc}}{\text{pole pitch}}$

Distance b/w two poles = 1 pole pitch

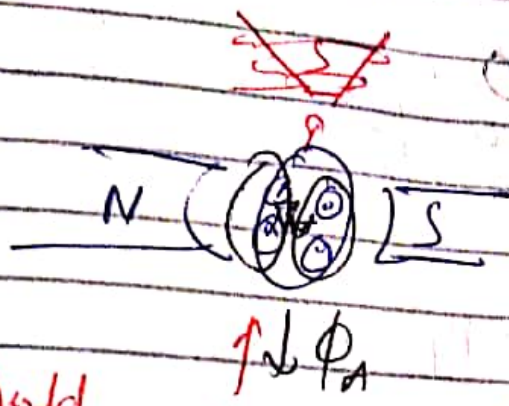If an interpole is used, the ϕ generated should be in opposite direction and equal to ϕ_A .



Current should be equal to I_a

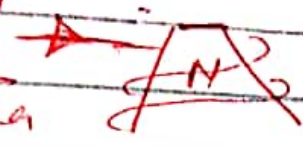

$$\phi = \frac{1}{2} \frac{Z}{P} \frac{I_a}{A}$$


compensating winding used along with interpole

$$AT_{\text{interpole/pole}} = \left(\frac{1}{2} \frac{Z}{P} \frac{I_a}{A} \right) - AT_{\text{compensator/pole}}$$

$$AT_{\text{interpole/pole}} = \frac{1}{2} \left(\frac{Z}{A} \frac{I_a}{P} \right) \left(1 - \frac{\text{Pole arc}}{\text{Pole pitch}} \right)$$

$\frac{AB_0 l}{\mu}$

MMF distribution

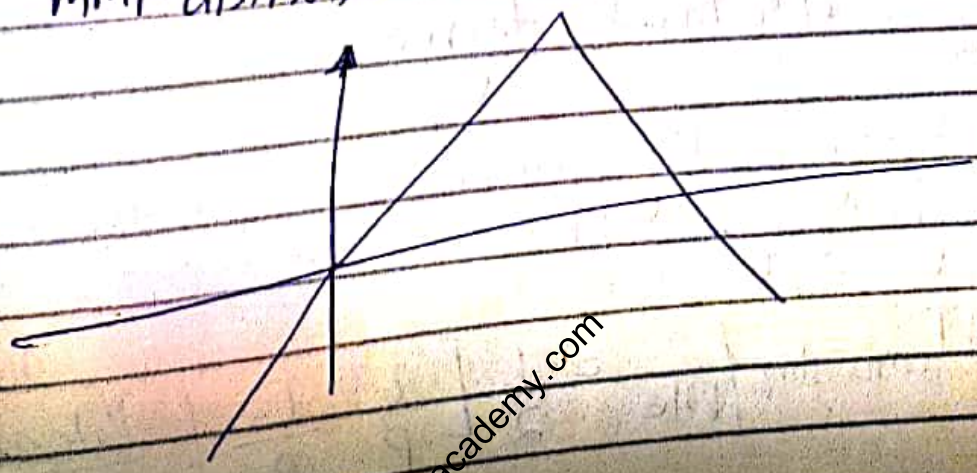

Q1. A compensated generator has 12000 AT/pole. The ratio of the pole arc to pole pitch is 0.7. The length of interpole air gap is 1.25 cm and flux density of interpole region is 0.3 T. Find AT/pole for compensating winding and interpole windings.

$$\text{Total AT/pole} = \frac{1}{2} \left[\frac{Z \cdot I_a}{P \cdot A} \right] = 12000$$

$$\frac{\text{Pole arc}}{\text{Pole pitch}} = 0.7$$

Length $l_g = 1.25 \text{ cm}$, Flux density, $B_g = 0.3 \text{ T}$

$$AT_{\text{interpole/pole}} = \frac{1}{2} \left[\frac{Z \cdot I_a}{P \cdot A} \right] \left[\frac{1 - \frac{\text{Pole arc}}{\text{Pole pitch}}}{\mu} \right] + \frac{B_g l_g}{\mu}$$

$$= (12000) (1 - 0.7) + \frac{(0.3)(1.25 \times 10^{-2})}{4\pi \times 10^{-7}} \text{ for air}$$

$$= 6584.155 \text{ AT.}$$

$$AT_{\text{compensating/pole}} = 12000 - 6584.155 = 5415.84 \text{ AT.} \quad \times$$

$$AT_{\text{compensating/pole}} = \frac{1}{2} \left[\frac{Z \cdot I_a}{P \cdot A} \right] \left[\frac{\text{Pole arc}}{\text{Pole pitch}} \right] = 8400. \quad \checkmark$$

B/c $B_g l_g$ is not part of armature reaction.
 It is the reactance voltage (commutation part).

Q2. A 250V, 14.9kW, 8 pole DC machine has single turn coil. The armature is wave wound with 94 commutator segments. The motor efficiency is 80%. Brushes are shifted by 2 segments at full load.

Calculate the cross magnetizing, demagnetizing and total AT.


$$A = 2 \quad V_t = 250V, \quad P_{out(mech)} = 14.9kW$$

$$\eta_{motor} = \frac{P_{out}}{P_{in}} = 0.8$$

$$\Rightarrow P_{in} = \frac{P_{out}}{0.8} = \frac{14.9 \times 10^3}{0.8} = 18.625kW$$

$$\text{Losses} = \text{o/p} \times \text{i/p}$$

By default separately excited;

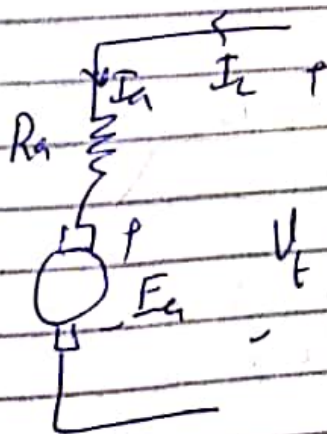

$$P_{in} = V_t \times I_a$$

$$18.625 = 250 I_a$$

$$\Rightarrow I_a = 74.5A$$

$$AT_d / \text{pole} = \frac{4\beta}{360} \left[\frac{Z I_a}{P A} \right] \left(\frac{1}{2} \right) \quad \text{--- (A)}$$

$$AT_c / \text{pole} = \frac{360 - 4\beta}{360} \left(\frac{1}{2} \right) \left[\frac{Z I_a}{P A} \right] \quad \text{--- (B)}$$

where $\frac{1}{2} \left(\frac{z}{P} \right) \left(\frac{I_a}{A} \right)$ is the total AT (peak value)

$$AT = \frac{1}{2} \left[\frac{z}{P} \frac{I_a}{A} \right] = \frac{1}{2} \left(\frac{z}{8} \right) \left(\frac{74.5}{2} \right) \quad \text{--- (1)}$$

In DC machine,
No. of coils = No. of commutator segments = No. of slots

$$\Rightarrow \text{No. of coil} = 94$$

$$\Rightarrow z = 94 \times 2 = 188$$

$$\text{(1)} \Rightarrow AT = 437.80$$

Now $\beta = ?$

$$94 \text{ slots (mech cycle)} = 360^\circ$$

$$\Rightarrow 1 \text{ slot (mech)} = \frac{360^\circ}{94} = 3.829^\circ$$

$$2 \text{ segment shift} \Rightarrow \beta_{\text{mech}} = 2 \times 3.829 \\ = 7.659$$

$$\beta^\circ (\text{elect}) = \frac{P}{2} (\beta^\circ \text{ mech}) = \frac{8}{2} \times 7.659 \\ \beta = 30.638^\circ$$

$$\text{(A)} \Rightarrow AT_a / \text{pole} = \frac{4(30.6)}{360} (437.80) = 149.04 \text{ AT}$$


$$\text{(B)} \Rightarrow AT_c / \text{pole} = 288.76 \text{ AT}$$

No Load Characteristics of DC Machine

(ϕ vs I_f) also known as Magnetization characteristics @ Saturation X hrs & Open Circuit X hrs.

Let induced emf, $E_g = k\phi\omega_r$.

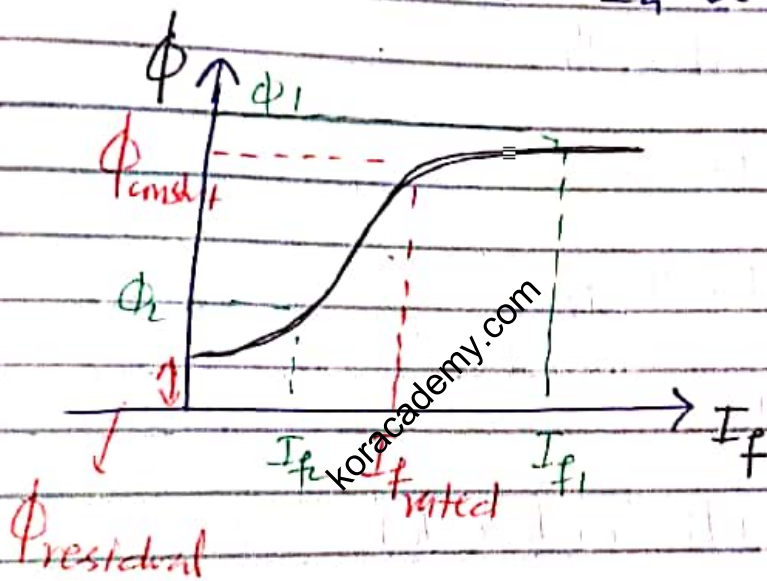
If $\omega_r = \text{constant} \Rightarrow E_g \propto \phi$



Weakness is very stronger than strengthening effect.

* $\omega_r = \text{fixed}$
 $E_g \rightarrow I_f \rightarrow \phi$

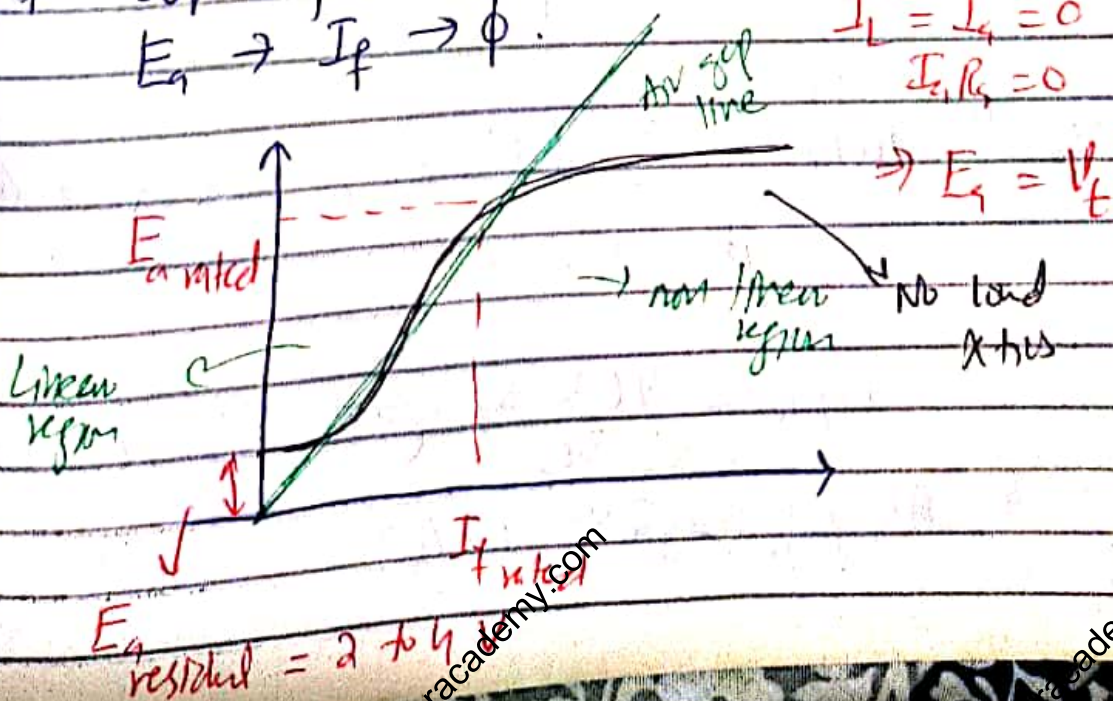No load \Rightarrow
 $I_L = I_a = 0$
 $I_f R_f = 0$





Air does not saturate. self excited = residual flux

Voltage Build up in shunt Generator

(self excited)

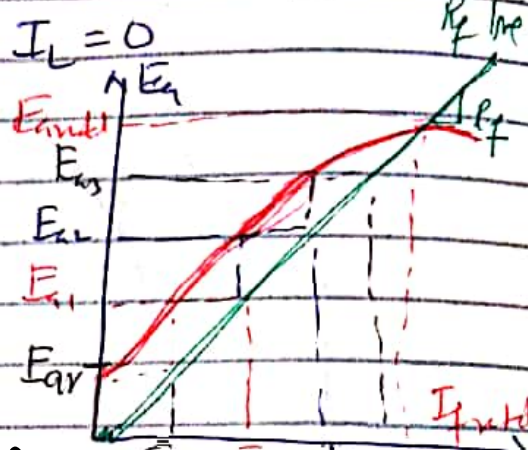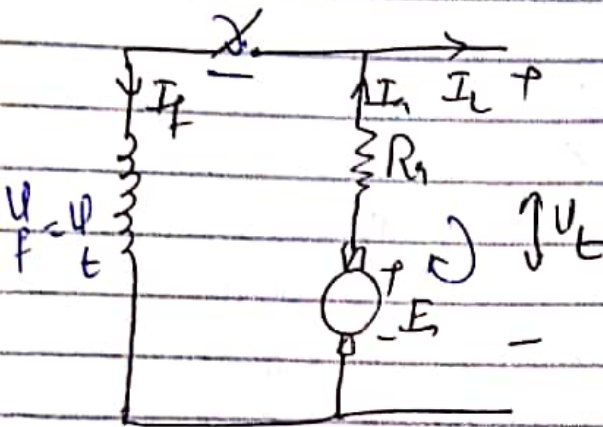There should be a driving force to operate the machine.



Case i) when switch is off & under no load condition

$$E_a = E_{ar} = \text{residual voltage}$$

Switch is closed;

$$E_a = V_t + I_a R_a$$

↳ neglect → as smaller current due to no load

$$\boxed{E_a = V_t = V_f = I_f R_f}$$

$$I_f = \frac{E_a}{R_f}$$

As the switch is closed, the residual E_{ar} will flow a current I_{f1} .

$$E_a \propto \phi$$


↳ so induced emf increases.

After I_{f1} is established, core is saturated.

The point where X_{f2} cut the R_f line is the operating point (rated V and I)

Case I

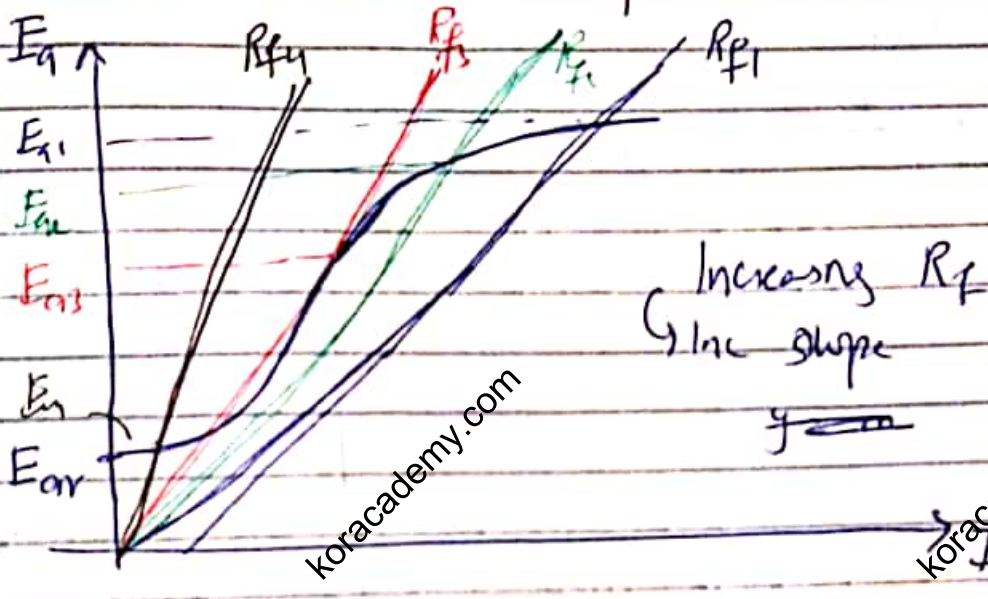$\omega_y = \text{constant}$. $R_f = \text{variable}$.




$\uparrow m = \frac{y}{x}$

$R_{f4} > R_{f3} > R_{f2} > R_{f1}$

\downarrow critical.

\rightarrow $R_f < R_{f \text{ critical}}$ we will have build up process.

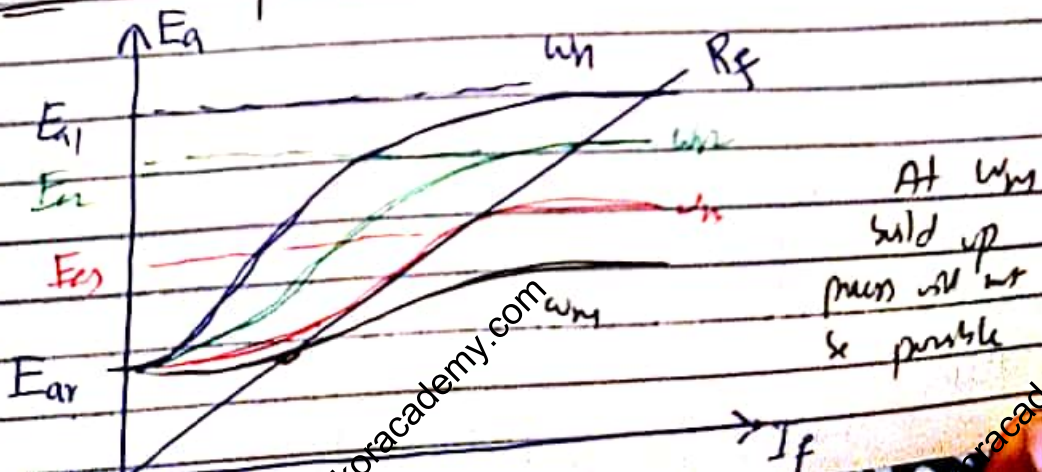Case II $R_f = \text{constant}$ $\omega_y = \text{variable}$.



$\omega_{cr} \rightarrow$ critical speed.

$$\omega_m < \omega_{cr} < \omega_n < \omega_{kl}$$

$$\omega_r > \omega_{cr, \text{critical}}$$

for build up process

① Speed Reversed.

$$E_a \rightarrow \ominus$$

$$\phi \rightarrow \oplus$$

no build up

② Flux reversed


$$\phi \rightarrow \ominus$$

$$E_a \rightarrow \oplus$$

still no build up.

③ $-k I_f$ and speed reversed.
 $\phi \rightarrow \ominus, \omega_r \rightarrow \ominus$

$$I_f \uparrow \quad E_a^-$$

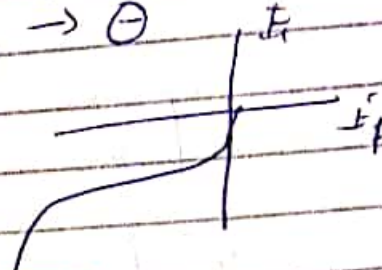


$$R_f \text{ critical} \propto N$$

As $E_a = k \phi \omega_r \approx V_c$
↳ as under no load condition neglected armature

$$I_f R_f = k \phi \omega_r$$

$$\Rightarrow \begin{matrix} R_f \propto \omega_r \\ R_f \propto N \end{matrix}$$

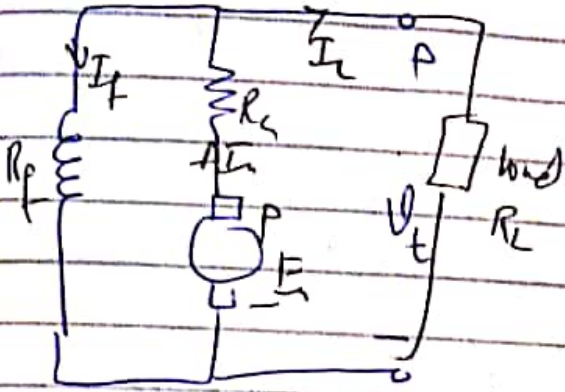External Xtras $\rightarrow V_t$ vs I_L \rightarrow user
 Internal Xtras $\rightarrow E_g$ vs I_a \rightarrow manufacturer.



$$I_f = \frac{V_t}{R_f}$$

$$E_g = V_t + I_a R_s$$

$$\uparrow I_L = \frac{V_t}{R_L}$$

$$\uparrow I_a = \uparrow I_L + I_f$$

$$\downarrow V_t = E_g - I_a R_s$$


$$\downarrow I_f = \frac{\downarrow V_t}{R_f} \Rightarrow \phi \downarrow$$

$$\downarrow E_g \propto \phi \downarrow \quad \downarrow \downarrow V_t = \downarrow E_g - \uparrow I_a R_s$$


$$\downarrow \uparrow I_L = \frac{\downarrow V_t}{\downarrow R_L} \quad \downarrow \rightarrow \text{dominating}$$

$\Rightarrow I_a \uparrow \rightarrow \phi \downarrow$

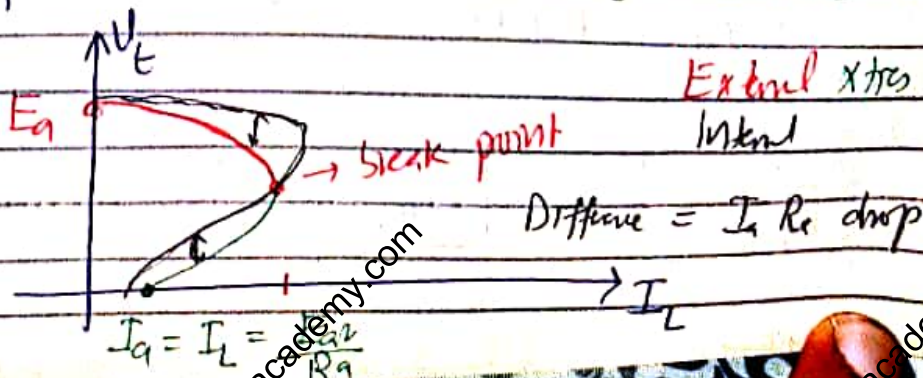\hookrightarrow armature reaction also increases \rightarrow reduce the flux more $\Rightarrow E \downarrow \Rightarrow V_t \downarrow \Rightarrow I_L \downarrow$



Voltage Build up in DC Series Generator.

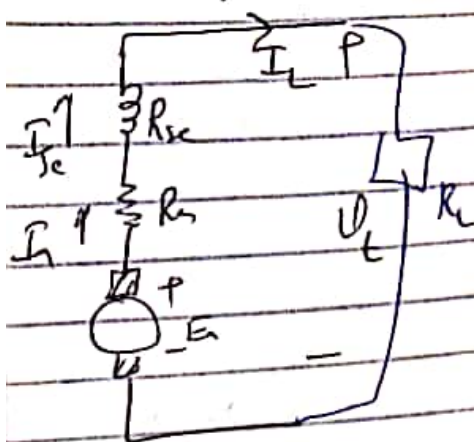

$$I_a = I_L = I_{se}$$

$$V_t = I_L R_L$$

$$E_g = V_t + I_a (R_a + R_{se})$$


$$E_g = I_L R_L + I_a (R_a + R_{se})$$

$$E_g = I_L (R_a + R_{se} + R_L)$$

$$I_L = I_a = I_{se} = \frac{E_g}{R_a + R_{se} + R_L}$$

No load $\Rightarrow I_L = 0 = I_{se} = I_a$

$$E_g = V_t = E_{ar}$$

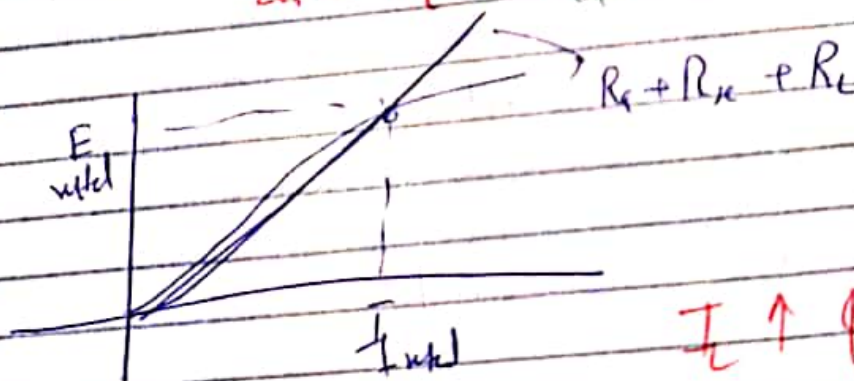

$$I \uparrow \Rightarrow P \uparrow \Rightarrow E \uparrow$$

Internal X-axis

External X-axis

If another winding is needed

Best region

E_g V_t

$$E_g = V_t + I_a (R_a + R_{se})$$

$$V_t = E_g - I_a (R_a + R_{se})$$

$$= I_L$$

E_{ar}

I_L I_a

Value of R_{se} is small \therefore it has to carry the load current.

R_m is larger \therefore it carries field current which is smaller.

where $V_t = V$

\hookrightarrow
Synchronous generator is used as a booster in transmission line.

The drop $I_a(R_a + R_{se})$ is not included in internal Xres

Speed Control of DC Motor

$$E_a = k \phi \omega_r, \quad T = k \phi I_a$$

$$E_a = V_t - I_a R_s$$

$$k \phi \omega_r = V_t - I_a R_s$$

$$\boxed{\omega_r = \frac{V_t - I_a R_s}{k \phi}}$$

- i. Flux control.
- ii. Armature control
- iii. Voltage control.

$$T_{load} = \text{constant}$$


$$As \quad T_e = T_l \quad \therefore \frac{d\omega}{dt}$$

At steady state; $\boxed{I_e = I_L}$

Base speed = Rated speed \rightarrow Name plate

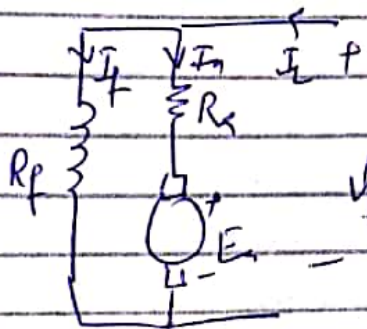Q1. A 220V, 15kw, 1000rpm shunt motor with $R_a = 0.25\Omega$ has rated line current of 68A and rated field current of 2.2A.

The change in field flux required to obtain a speed of 1600rpm while drawing current of 52.8A and field current of 1.8A.



$$I_{L1} = 68\text{A}, I_{f1} = 2.2\text{A}$$

$$N_1 = 1000\text{rpm}$$

$$R_a = 0.25, V_t = 220\text{V}$$

$$N_2 = 1600, I_{L2} = 52.8, I_{f2} = 1.8$$

As $E_b = k \phi \omega_r$.

$$\boxed{\frac{E_{b2}}{E_{b1}} = \frac{\phi_2 \times N_2}{\phi_1 \times N_1}} \quad \text{--- (A)}$$

$$E_{b1} = V_t - I_{a1} R_a = 220 - (68 - 2.2)(0.25) = 203.55\text{V}$$

$$E_{b2} = V_t - I_{a2} R_a = 220 - (52.8 - 1.8)(0.25) = 207.25\text{V}$$

$$\text{(A)} \Rightarrow \frac{207.25}{203.55} = \frac{\phi_2}{\phi_1} \times \frac{1600}{1000} \Rightarrow \frac{\phi_2}{\phi_1} = 0.6363$$

$$\text{Change} = \frac{\phi_2 - \phi_1}{\phi_1} = \frac{\phi_2}{\phi_1} - 1$$

$$= 0.6363 - 1 = -0.3636 = -36.36\%$$

↓
value

TRANSFORMER

$$\text{mmf} = \text{No. of turns} \times \text{current} \quad (\text{AT})$$

$$\text{Flux, } \phi(t) = \frac{\text{mmf}}{\text{reluctance}} \quad (\text{wb})$$

$$\text{Reluctance, } R = \frac{l}{\mu A}$$


$\mu \rightarrow$ permeability $\sigma \rightarrow$ conductivity

$$\text{Flux density, } B = \mu H$$

$$\left[\begin{array}{l} \text{mmf} \Leftrightarrow \text{emf} \\ \text{reluctance} \Leftrightarrow \text{resistance} \end{array} \right] \quad \left[\begin{array}{l} \text{Flux} \Leftrightarrow \text{current} \end{array} \right]$$

Case 1

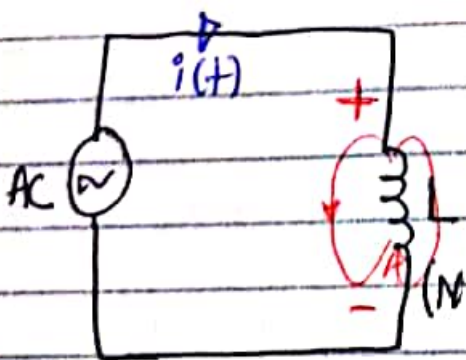Single coil excited with AC supply.
 \hookrightarrow inductance, $N \rightarrow$ no. of turns.



* AC voltage $\rightarrow i(t) \rightarrow$ mmf
 $\phi(t) = \frac{N i(t)}{R} \leftarrow = N \cdot i(t)$
 \hookrightarrow induced voltage $e(t) = N \frac{d\phi}{dt}$

Say $i(t) = I_m \sin \omega t$

$$\Rightarrow \text{mmf} = N \cdot I_m \sin \omega t$$

$$\Rightarrow \phi(t) = \frac{N \cdot I_m \sin \omega t}{R} = \phi_m \sin \omega t$$


\hookrightarrow Flux produced will be a function of current

$$\Rightarrow e(t) = N \times \frac{d}{dt} (\Phi_m \sin \omega t)$$

$$\Rightarrow e(t) = N \Phi_m \omega \cos \omega t = E_{\max} \cos \omega t$$


↳ self induced voltage.

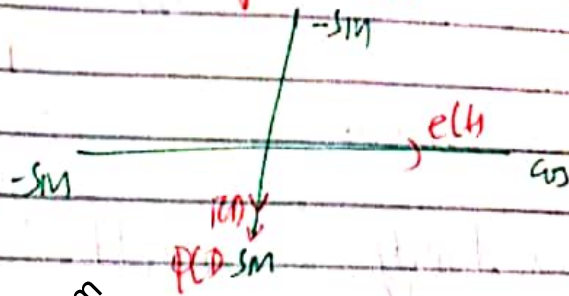In inductor, current always lags voltage by 90° .



Case ii

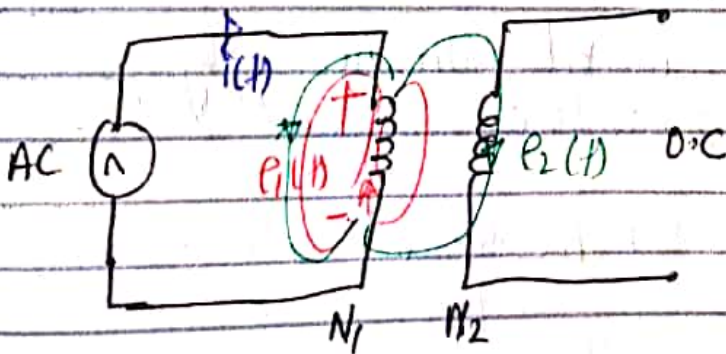When two coils are placed close to each other.



$$\text{AC supply} \rightarrow i(t) \rightarrow N_1 i(t) \rightarrow \Phi(t) = \frac{N_1 i(t)}{R}$$

$$e_1(t) = N_1 \frac{d\Phi}{dt}$$

Say $i(t) = I_m \sin \omega t$

$$e_1(t) = N_1 \times \frac{d}{dt} \left(\frac{N_1 I_m \sin \omega t}{R} \right)$$

$$e_1(t) = N_1 \phi_m \omega \cos \omega t = E_{1\max} \cos \omega t$$

All the flux of N_1 will cut into the N_2 coil and also some part of it will cut N_2 .

$$\text{Total flux } \phi(t) = \phi_m \sin \omega t$$

Say the flux linking 2 die 1 is;

$$\phi_{12} = k \phi_m \sin \omega t$$

↓
some percentage $k < 1$

$$\Rightarrow e_{12}(t) = N_2 \frac{d}{dt} (k \phi_m \sin \omega t)$$

$$\Rightarrow e_{12}(t) = k N_2 \omega \phi_m \cos \omega t$$

↳ mutually induced emf (due to another flux)

The polarity of $e_2(t)$ will be decided when we place a load.


The ratio; $\frac{e_1(t)}{e_2(t)} = \frac{N_1}{k N_2}$

↳ This we are not studying transformer, we are simply talking of two coils placed together.

Permeability of air is key law \rightarrow restrict the flux of flux.

Case iii

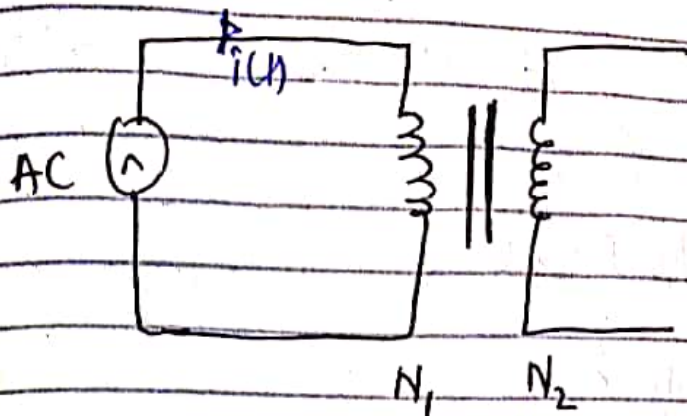Two coils placed on a core (transformer action).



$$\text{say } i_1(t) = I_m \sin \omega t$$
$$\phi(t) = \phi_m \sin \omega t$$
$$e_1(t) = -N_1 \omega \phi_m \cos \omega t$$

If the core material (II) is ideal, all the flux created in 1 will link coil 2.

$$\text{A } \phi_{12}(t) = k \phi_m \sin \omega t$$

Relative $\rightarrow 0$ \Leftarrow permeability $\rightarrow \infty$
 \rightarrow All the flux will link coil 2 $\rightarrow k=1$

$$\Rightarrow \phi_{12}(t) = \phi_m \sin \omega t$$


$$\Rightarrow e_{12}(t) = e_2(t) = N_2 \frac{d}{dt} \phi_{12}(t) = N_2 \omega \phi_m \cos \omega t$$

Now transformer turn ratio;

$$\frac{e_1(t)}{e_2(t)} = \frac{N_1}{N_2}$$

Ideal Transformer

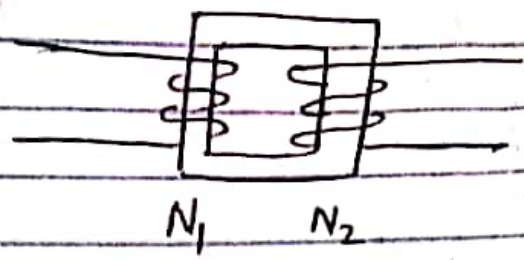
- permeability of core tends to ∞
- $R \rightarrow 0$ $R = \frac{l}{\mu A}$
- No losses → winding losses
→ core losses



- Leakage flux = 0, $k=1$
- Under no load condition, current supplied by source will be zero.
- ↳ but we will have flux.

Working

Case i Under no load.

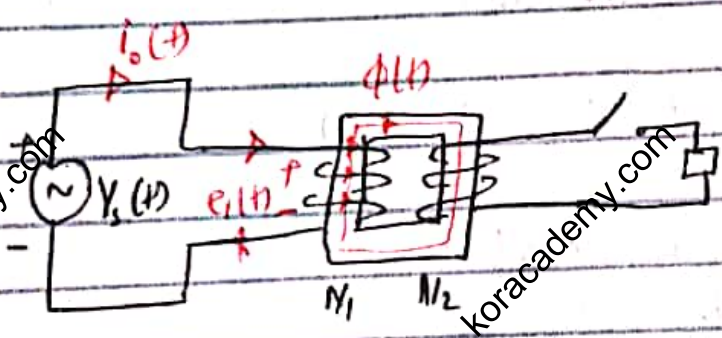

SW → open.
 $I \rightarrow 0, R \rightarrow 0$

$$I(t) = I_m \sin \omega t$$

$$\Phi(t) = \Phi_m \sin \omega t$$


$$e_1(t) = N_1 \frac{d\Phi(t)}{dt}$$

$e_1(t) = N_1 \omega \Phi_m \cos \omega t$ → self induced

and $e_2(t) = N_2 \omega \Phi_m \cos \omega t$ → mutually induced

Ratio = $\frac{e_1(t)}{e_2(t)} = \frac{N_1}{N_2}$ → turn ratio

→ only valid for ideal transformer

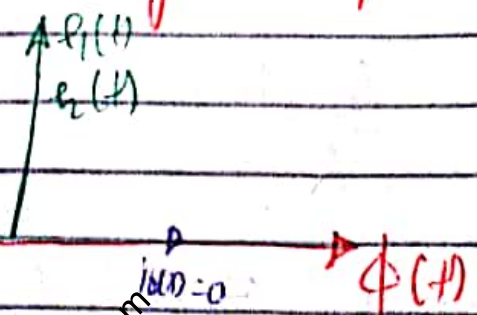

- $N_1 > N_2$ → step down
- $N_1 < N_2$ → step up
- $N_1 = N_2$ → isolation transformer

Case II Under loaded condition

Transformer is a constant flux device
 ↳ The flux at loaded condition will be the same as no load condition.


$$\phi(t) = \Phi_m \sin \omega t$$

When switch is closed, current will start flowing through the load ($i_2(t)$).

↳ current has started flow in the winding N_2 .
 The direction should be such that it opposes its case.

i_2 is developed due to $e_2 \rightarrow \phi(t)$

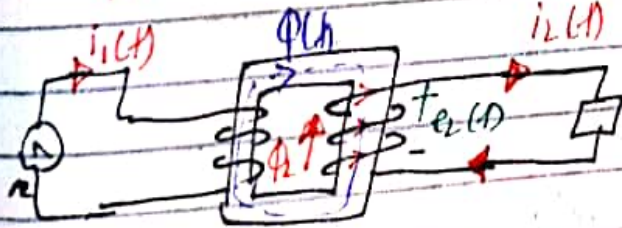The current direction in N_2 should be such that it opposes the flux $\phi(t)$.



The flux created due to I_2 will oppose the flux ϕ .
 (Lenz's law)

But we have to keep ϕ

constant. So we will need to increase it. And for that we will, an extra current from the primary side.
 require

$$\phi_2(t) = \frac{N_2 \cdot i_2(t)}{R}$$

$$m.m.f = N_1 i_1(t) = N_1 i_0(t) + N_2 i_2(t)$$

m.m.f balance equation


$\mu \rightarrow \infty \Rightarrow R \rightarrow 0$
 $R = \frac{l}{\mu A}$
 $\phi(t) = \frac{N I(t)}{R} \approx \phi(t) \text{ finite} \Rightarrow i(t) \rightarrow 0$
 $\rightarrow \frac{0}{0} = \text{finite}$
 $\Rightarrow I_0(t) = 0$

$\Rightarrow N_1 I_1 = N_2 I_2$

Ratio; $\frac{I_1}{I_2} = \frac{N_2}{N_1} \Rightarrow I_1 \text{ and } I_2 \text{ are in the same phase}$

Polarity of E_{ind} according to Lenz's law: the current will flow in such a direction that it opposes the $\dot{\phi}$.

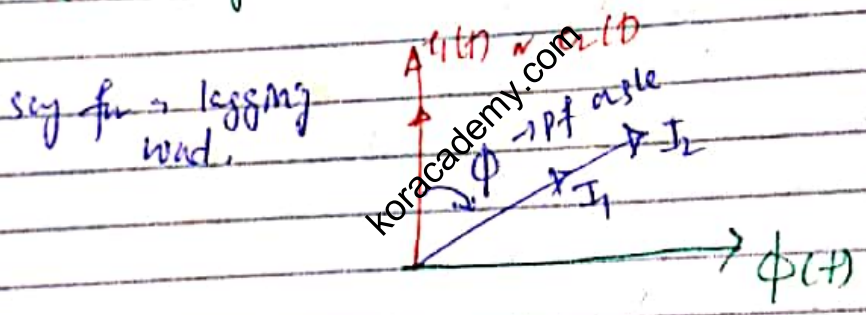(if entering \rightarrow leave at + and enter at -)




\rightarrow If permeability (μ) is finite (very high)

$\hookrightarrow I_0$ will have some value (very small)

balance equation:
 $\Rightarrow N_1 I_1 = N_1 I_0 + N_2 I_2$

$\Rightarrow I_1 = I_0 + \frac{N_2}{N_1} I_2$

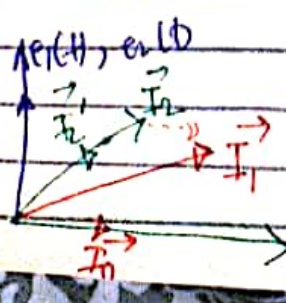
If $a = \frac{N_2}{N_1} \Rightarrow I_1 = I_0 + \frac{I_2}{a} = I_0 + I_1'$



Here $\frac{I_1}{I_2} = \frac{N_2}{N_1}$ ✗

$\frac{E_1}{E_2} = \frac{N_1}{N_2}$ ✓

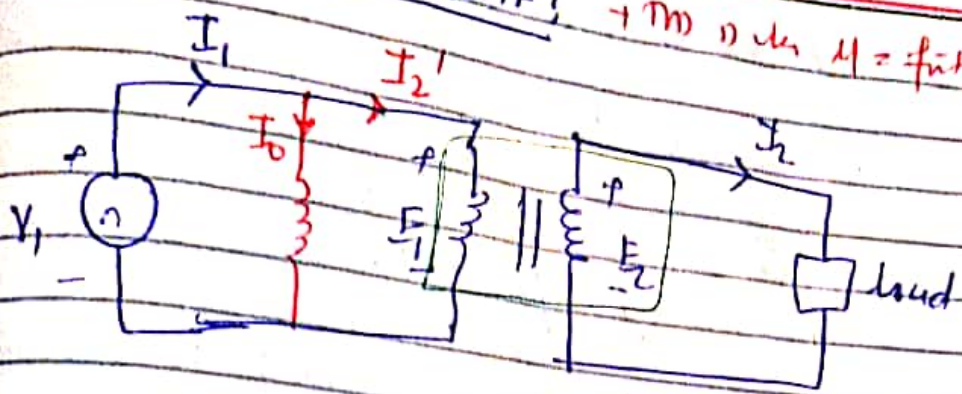Equivalent circuit; \rightarrow TM is the $M = f \cdot t \cdot c$.



$$\vec{I}_1 = \vec{I}_0 + \vec{I}_2' \rightarrow \text{so parallel circuit.}$$

for no-load, $I_0 = 0 \Rightarrow I_1 = I_2' = I_2 / a$

Current relation is valid for TM one only;

$$I_2' = \frac{I_2}{a}$$

$$e_1(t) = N_1 \omega \phi_m \cos \omega t$$

$$e_1(\text{rms}) = \frac{(N_1 \times 2\pi f \times \phi_m) \cos \omega t}{\sqrt{2}}$$


$e_1(\text{rms}) = 4.44 f \phi_m N_1$
$e_2(\text{rms}) = 4.44 f \phi_m N_2$

E_1 and E_2 will always be in the same phase.

I_2 and I_2' will always be in the same phase

\hookrightarrow secondary current referred to primary side

Practical Transformer

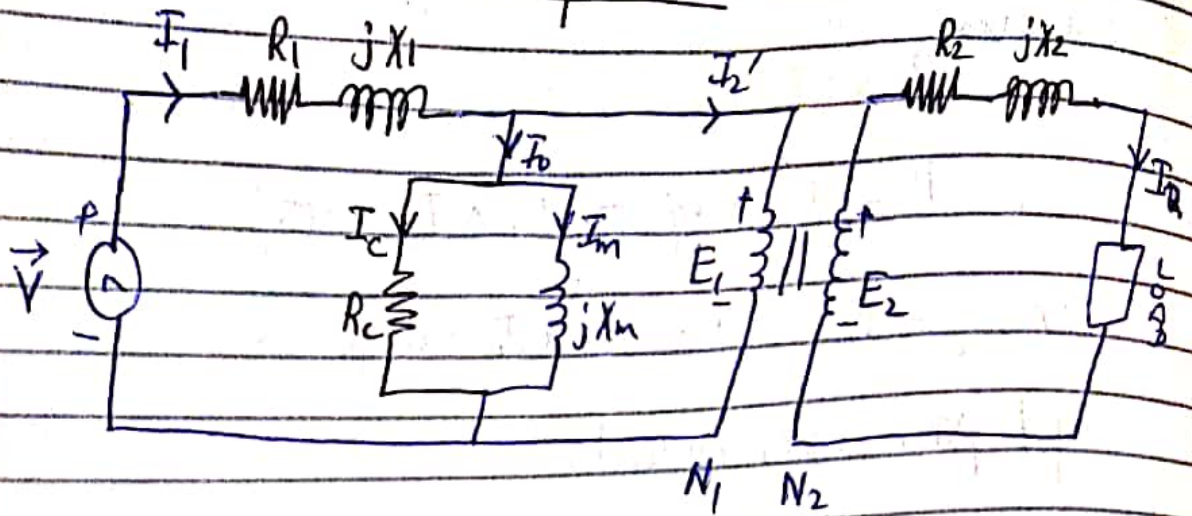


Case i No Load condition

$$I_2 = 0A \Rightarrow I_2' = 0A \Rightarrow \Phi_0$$

$\Rightarrow I_1 = I_0 = I_m + I_c$ = no load current.
(2 to 5% of full load current)

Similarly $\frac{E_1}{E_2} = \frac{N_1}{N_2} = a$

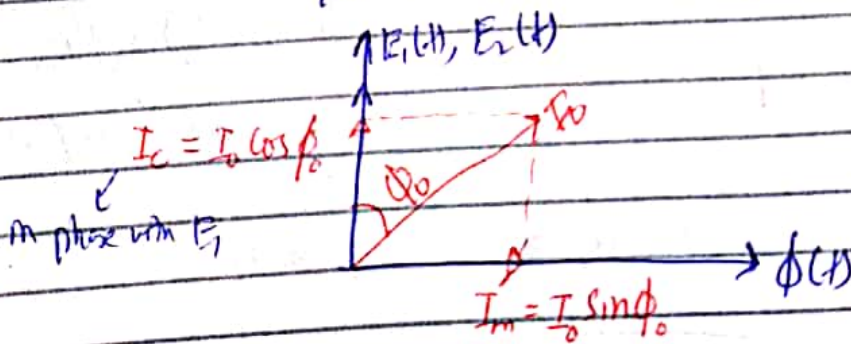current only in the core, this will develop a flux Φ_m $\sin \omega t \rightarrow$ no load flux



\hookrightarrow inductor \rightarrow will lag from E_1 by 90° .

$$I_0 = \sqrt{I_c^2 + I_m^2}$$

$$\vec{I}_0 = \vec{I}_c + \vec{I}_m$$

Core loss component = R_c
 Core losses;

$$P_c = I_c^2 R_c$$

$$\textcircled{a} P_c = V I \cos \phi = E_1 \times I_c \times \cos 0^\circ$$


$$\textcircled{b} P_c = V I \cos \phi = E_1 \times I_0 \times \cos \phi$$

Input power under no load;

$$P_{in} = V_1 \times I_1 \times \cos \phi_1$$

$\rightarrow = I_0 \rightarrow$ angle s/w V_1 and I_0

Case ii Under loaded condition

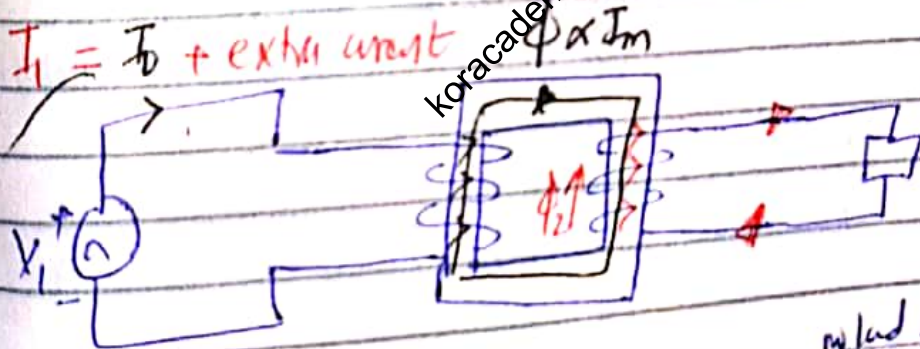

I_2 ad ϕ core loss ϕ

total mag. $N_1 I_1 = N_1 I_0 + N_2 I_2$

st. pring side

extra mag. due to load.

$$I_1 = I_0 + \frac{N_2}{N_1} I_2 = I_0 + \frac{I_2}{a}$$

$$I_1 = I_0 + I_1'$$

The equations that we can deduce are;

i. $\bar{V}_1 = \bar{I}_1 R_1 + j \bar{I}_1 X_1 + \bar{E}_1$


ii. $\bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + j \bar{I}_2 X_2$

iii. $\frac{\bar{E}_1}{\bar{E}_2} = a$ and $\frac{\bar{I}_2'}{\bar{I}_2} = \frac{1}{a}$

iv. $\bar{I}_1 = \bar{I}_0 + \bar{I}_2'$

v. $\bar{I}_0 = \bar{I}_c + \bar{I}_m$

Modelling of Transformer

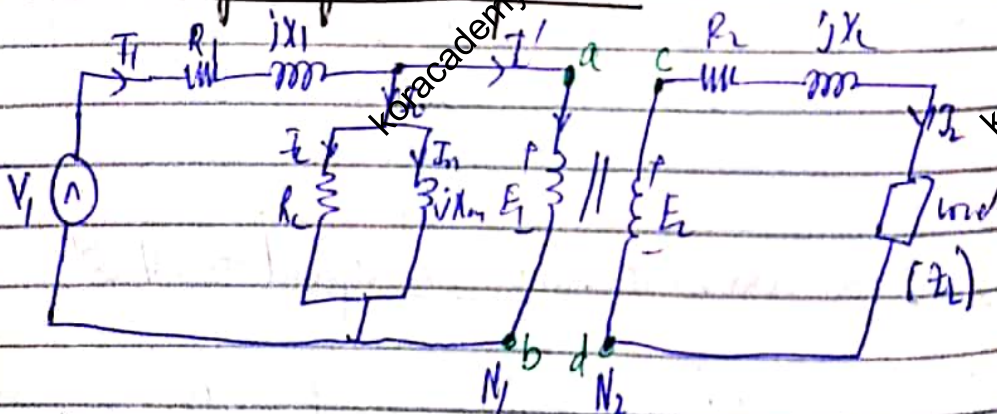

Referenced Circuit

$$a = \frac{N_1}{N_2} = \frac{E_1}{E_2}$$

↳ turn ratio is always defined from primary to secondary.


HV	LV
V ↑	V ↓ → $\times a$ or $\frac{1}{a}$
I ↓	I ↑ → $\times a$ or $\frac{1}{a}$
Ω ↑	Ω ↑ → $\times a^2$ or $\frac{1}{a^2}$

Say primary is HV and secondary is LV $\Rightarrow \frac{N_1}{N_2} > 1$
 $\Rightarrow a > 1 \Rightarrow$ step down transformer.

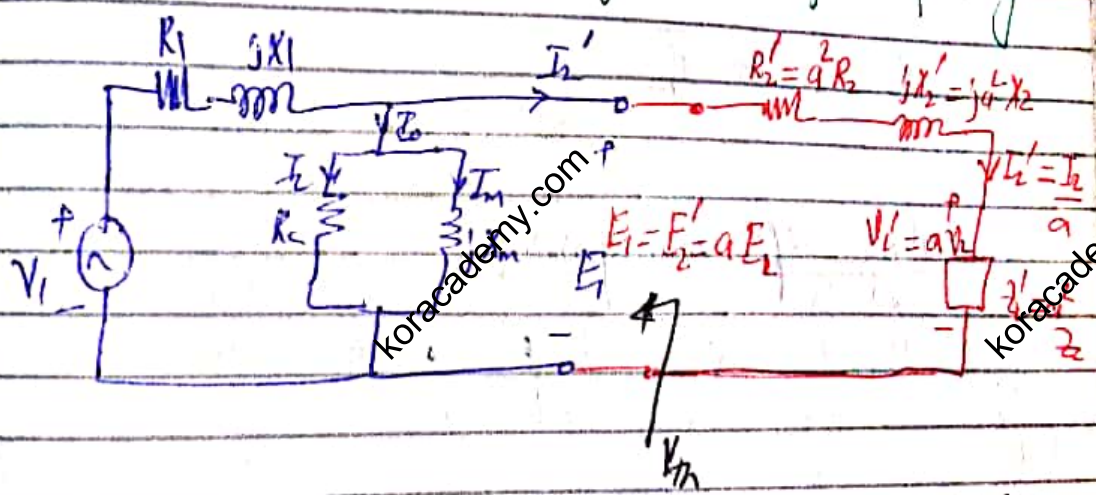
(i) Transformer equivalent circuit referred to HV side

means I need all the circuit of HV side i.e. all the secondary data needs to be on the primary side.

All the changes will be in secondary and no changes in primary.



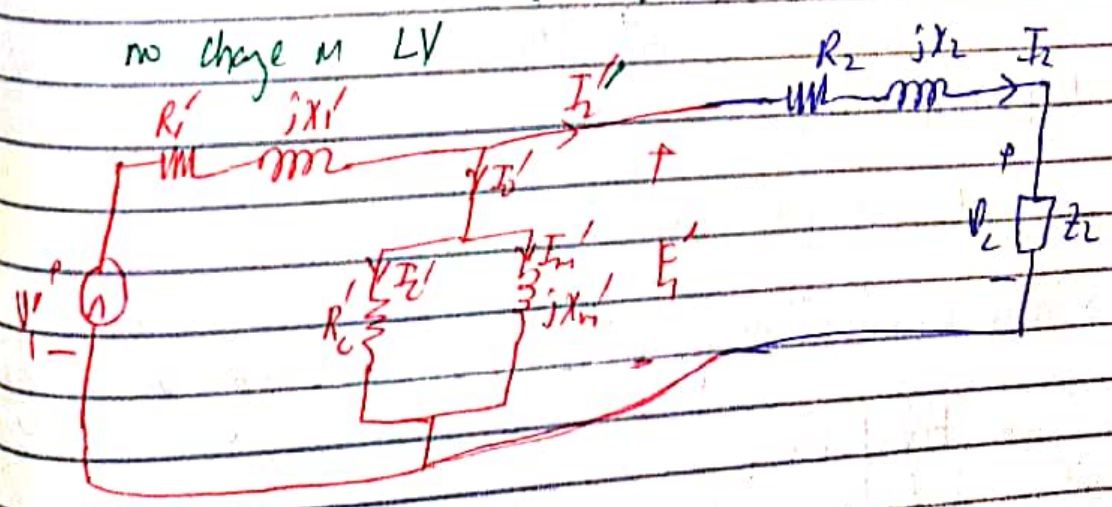ii. Transformer equivalent circuit when referred to LV side



$$V_1' = \frac{V_1}{a}, \quad E_1' = \frac{E_1}{a}, \quad R_1' = \frac{R_1}{a^2}, \quad jX_1' = \frac{jX_1}{a^2}$$

$$R_c' = \frac{R_c}{a^2}, \quad jX_m' = \frac{jX_m}{a^2}$$

$$I_1' = a I_1, I_2' = a I_2, I_m' = a I_m, I_0' = a I_0$$

$$I_2'' = I_2' a = \left(\frac{I_2}{a}\right) a \Rightarrow I_2'' = I_2$$

Approximate equivalent circuit

Consider the transformer equivalent circuit referred to HV side.

If I need to find V_{Th} (as mentioned).

of course $V_m \neq E_1$, $\% E_1$ is the voltage when switch is connected but for V_m we make open circuit.

Say $Z_1 = R_1 + jX_1$, $Z_{sh} = \frac{R_c \times jX_m}{R_c + jX_m}$


from voltage divider rule,

$$V_m = \frac{V_1 \times Z_{sh}}{Z_{sh} + Z_1}$$

$$V_{Th} \approx V_1$$

\Rightarrow drop across Z_1 is negligible

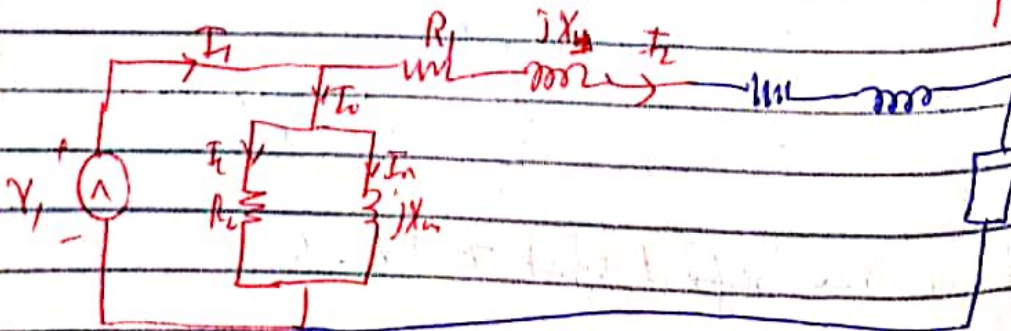So we can connect the short branch across the supply.




\hookrightarrow First approximated equivalent circuit

Now;

A The value of I_0 is only 2 to 5% of full load current.

↳ negligibly small
↳ so we can neglect the shunt Z_0 .

The final circuit will be,

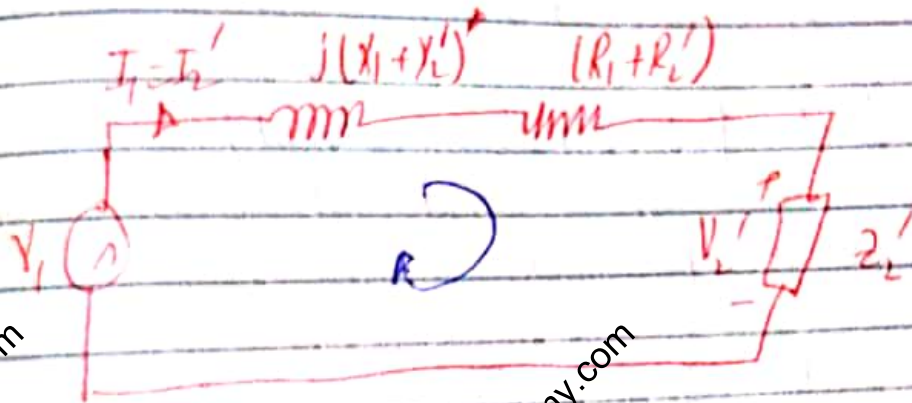

↳ Second / Final approximated model of single phase practical transformer

The equations will be as;

$$V_1 = V_2' + I_2'(R_1 + R_2') + j I_2'(X_1 + X_2')$$

Say $Z_{eq} = R_{eq} + j X_{eq}$

$$R_{eq} = R_1 + R_2', \quad X_{eq} = X_1 + X_2'$$


If we have referred circuit to LV side;

we have; $V_1', R_1', R_2, X_1', X_2, V_2, Z_L$


Dot Convention

$+ = \bullet$

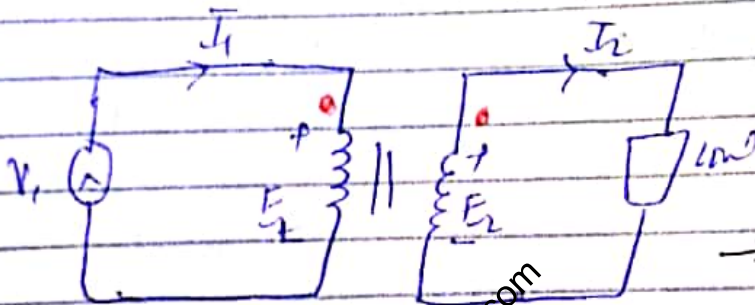If the current enters at dot in the primary and leaves at dot in the secondary, then flux will be opposing in nature \rightarrow this is the transformer principle



\rightarrow reference unit

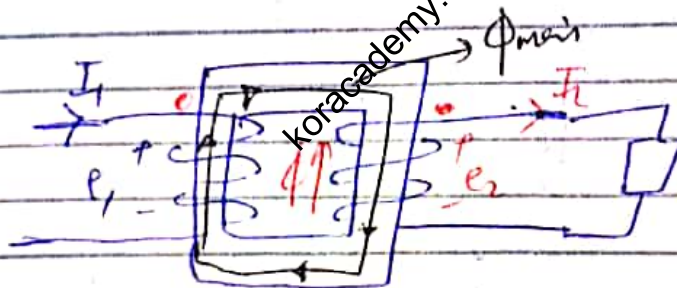


$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$


If current enters at both the dots, they will be additive in nature and this will not be in accordance with Lenz law and hence will not obey transformer principle

Examples

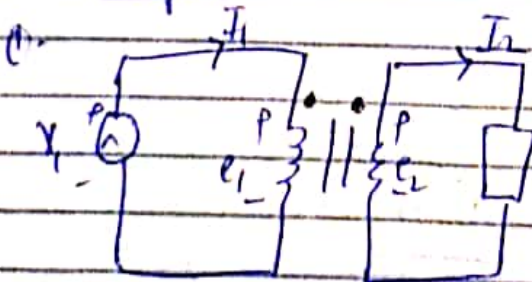


$$\frac{E_1}{E_2} = a \quad (+ve)$$
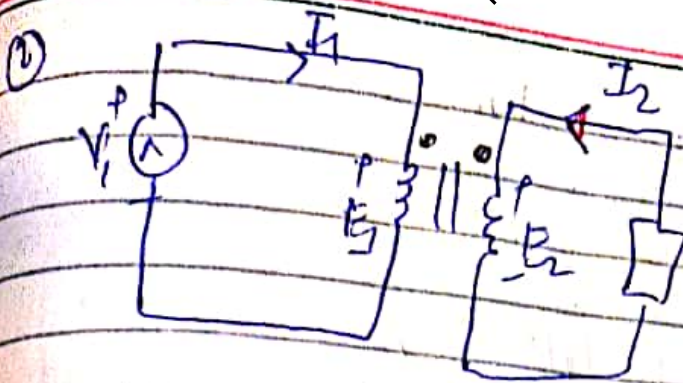
$$\frac{I_1}{I_2} = \frac{1}{a} \quad (-ve)$$




$$\frac{E_1}{E_2} = a \quad (\text{ee})$$

$$\frac{I_1}{I_2} = \frac{1}{a}$$

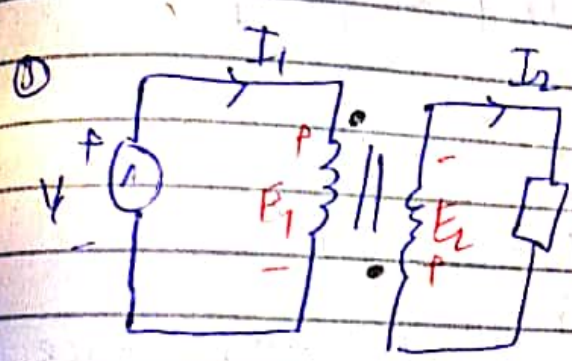

$$\frac{E_1}{E_2} = -a$$

$$\frac{I_1}{I_2} = -\frac{1}{a}$$

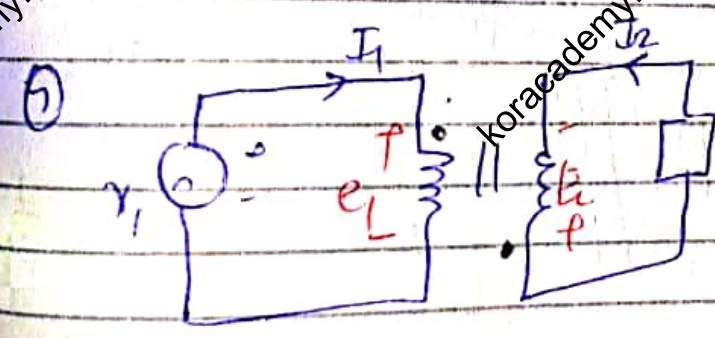

$$\frac{E_1}{E_2} = -a$$

$$\frac{I_1}{I_2} = \frac{1}{a}$$

Functions of transformer


1. Step up and step down voltage.
2. Impedance matching for maximum power transfer.
3. Filtering of DC.
4. Isolation of circuit (primary and secondary are electrically isolated).

Transformer is a constant power device $\because E_1 I_1 = E_2 I_2$
 why? for ideal $X_{pm} < 1$


$$P_1 = P_2$$

Questions

① The relation of I wrt $V_{AB} = ?$

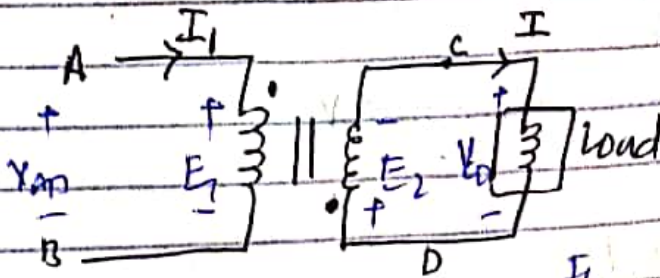

The reference is as;

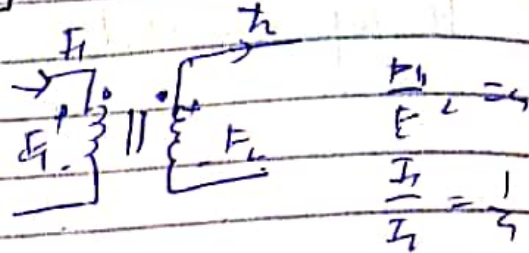

$$\frac{V_{AB}}{V_{CD}} = \frac{E_1}{-E_2} = -a$$

$$\Rightarrow V_{AB} = -a (V_{CD})$$

Current in an inductor will lag the voltage by 90°



(V_{CD} and V_{AB} are at 0° and 180° respectively)

② V_{AB} lags I by 90°
 I leads V_{AB} by 90°

Similarly if we talk about currents;


$$\frac{I_1}{I} = -\frac{1}{a} \Rightarrow I_1 = -\left(\frac{1}{a}\right) I$$

③ I_1 lags V_{AB} by 90°
 V_{AB} leads I_1 by 90°


If we have resistive load;





If capacitive load;

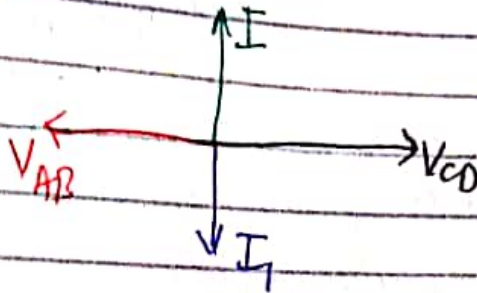

If R-L load;

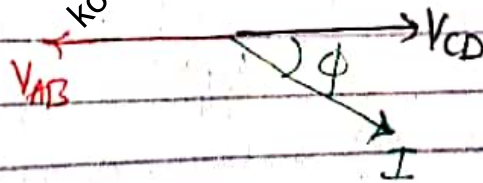

If RC load;

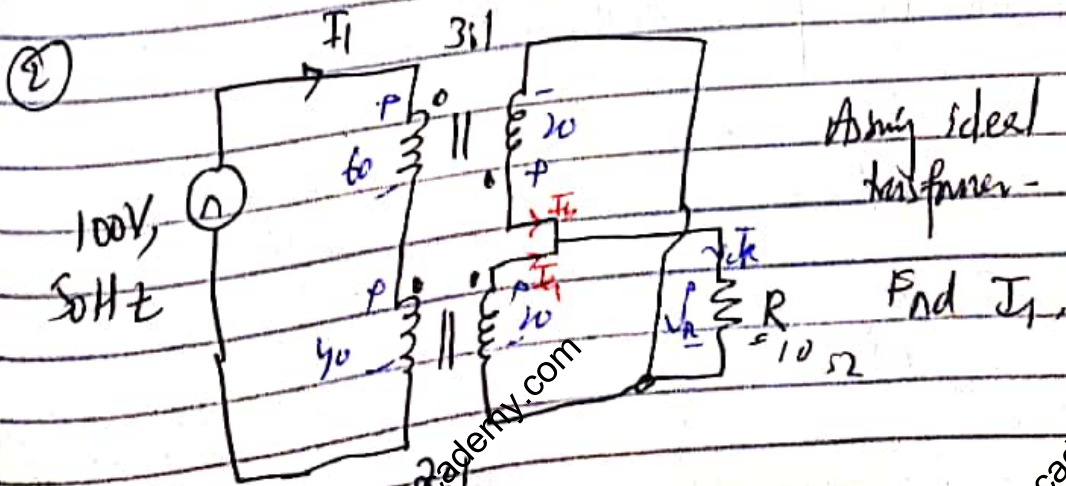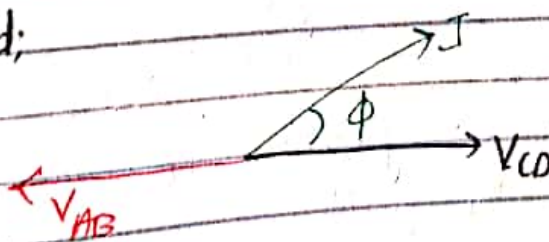

In such questions go for;
 (i) Voltage balance eq (ii) mmf balance eq.

Power balance; $P_{in} = P_{out} = (VA)_1 \times (VA)_2$

$\Rightarrow 100 \times I_1 = V_R \times I_R$

in VA \rightarrow mVA

A 100V is divided into 3:1 and 2:1;

$\Rightarrow 100 = 3n + 2n = 5n$

$\Rightarrow n = 20$

$\Rightarrow V_R = 20V \Rightarrow I_R = \frac{V_R}{R} = \frac{20}{10} = 2A$

$\Rightarrow I_1 = \frac{2 \times 2}{100} = 0.04A$

If by another method;

$I_R = I_4 + I_5$

$2 = I_4 + I_5 \quad \text{--- (A)}$

Why did we not do phasor addition?

$\frac{I_5}{I_4} = \frac{3}{1} \Rightarrow I_5 = 3I_4$

B/c this is simple resistive load at the ideal Xpm (no magnetizing mmf) therefore no concept of phase shift so we did direct addition.


$\frac{I_4}{I_5} = \frac{2}{1} \Rightarrow I_4 = 2I_5$

(A) $\Rightarrow 2 = 3I_4 + 2I_4$

$\Rightarrow I_4 = \frac{2}{5} = 0.4A$

3

120V, 50Hz

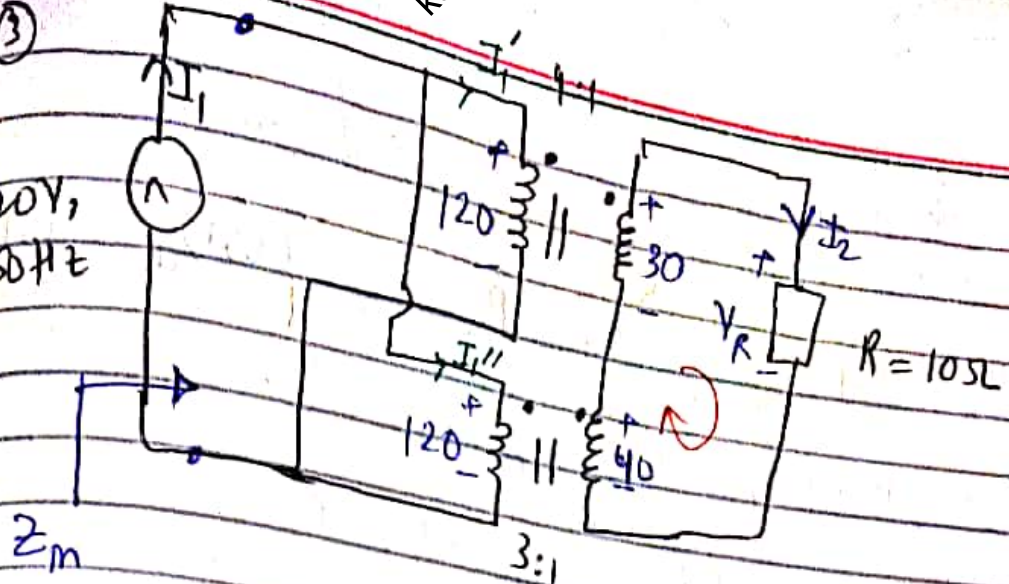

Find I_1 and input impedance?

Power balance $\Rightarrow V_1 I_1 = V_R I_2$
for ideal only

$$V_R = 30 + 40 = 70V$$

$$\Rightarrow I_2 = \frac{V_R}{R} = \frac{70}{10} = 7A$$

$$\Rightarrow I_1 = \frac{70 \times 7}{120} = 4.083A$$

1/P impedance of the whole at that kind divided by the current through that terminal without any condition.

$$\Rightarrow Z_m = \frac{120}{I_1} = \frac{120}{4.083} = 29.41 \Omega$$

If solving by another method, (using mesh)

$$I_1 = I_1' + I_1''$$

$$\frac{I_1'}{I_2} = \frac{1}{4} \Rightarrow I_1' = \frac{I_2}{4}$$


Also, $\frac{I_1''}{I_2} = \frac{1}{3} \Rightarrow I_1'' = \frac{I_2}{3}$

$\Rightarrow I_1 = \frac{I_2}{4} + \frac{I_2}{3} = \frac{7}{4} + \frac{7}{3} = 4.083 \text{ A}$

With Ampere and wattage value will be the same here b/c
no magnetizing branch and no extra reactance.

$120 \times 4.083 = \text{watt}$

4)

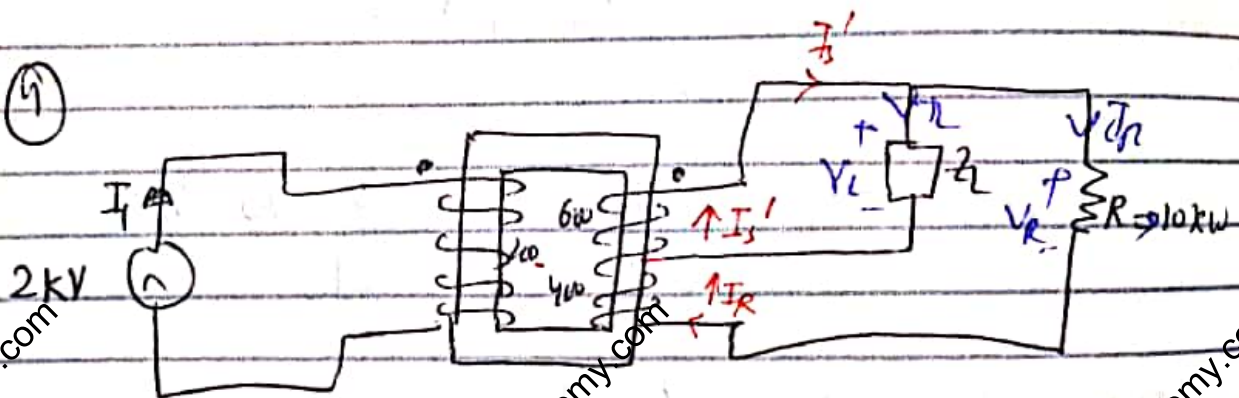

$Z_L = 2000 \angle 45^\circ \Omega \quad I_1 = ?$

Power balance $\Rightarrow V_1 I_1 = V_2 I_2 + V_R I_R \quad \text{--- (1)}$

say $V_1 = 2 \text{ kV} \angle 0^\circ = \text{reference}$

$\frac{V_1}{V_R} = \frac{200}{1000} \Rightarrow V_R = \frac{1000}{200} \times 2 \text{ k}$

$\Rightarrow V_R = 10 \text{ kV} \angle 0^\circ$

$\Rightarrow I_R = \frac{V_R}{R} = \frac{10 \text{ kV}}{10 \text{ k}\Omega} = 1 \text{ A}$

As $V_R I_R = 10 \times 1 \text{ W} \Rightarrow I_R = 1 \angle 0^\circ \text{ A}$

no cycle change with sig in ratio voltage

~~$\vec{V}_1 = 10 \angle 0^\circ$~~ $\vec{V}_1 = 10 \times 600 \angle 0^\circ = 6 \text{ kV} \angle 0^\circ$

$$\vec{I}_1 = \frac{\vec{V}_1}{Z_L} = \frac{6 \text{ kV} \angle 0^\circ}{200 \times 450} = 3 \angle -45^\circ \text{ A}$$

$$\textcircled{1} \Rightarrow 2 \times 10^3 \times \vec{I}_1 = (10 \times 10^3 \angle 0^\circ) + (6 \times 10^3 \angle 0^\circ) \times (3 \angle -45^\circ)$$

$$\vec{I}_1 = \frac{10 \angle 0^\circ + 18 \angle -45^\circ}{2}$$

$$\Rightarrow \vec{I}_1 = 5 \angle 0^\circ + 9 \angle -45^\circ \Rightarrow \vec{I}_1 = 13.02 \angle 29.24^\circ \text{ A}$$

Complex power at terminal;

$$= V_1 I_1^* = 2 \times 10^3 \angle 0^\circ \times 13.02 \angle +29.24^\circ$$

$$\textcircled{2} P = VI \cos \theta \rightarrow \text{watts power}$$
$$= (2 \times 10^3) (13.02) \cos (29.24)$$
$$= 22.72 \text{ kW}$$

$$\textcircled{3} Q = VI \sin \theta \rightarrow \text{reactive power}$$
$$= (2 \times 10^3) (13.02) \sin (29.24)$$
$$= 12.719 \text{ VAR}$$

$$\text{Also } S = \sqrt{P^2 + Q^2}$$

In mmf balance, we take current in the windings.

If solving this question by mmf balance equation;

$$N_1 I_1 = 600 \times I_3' + 400 \times I_2$$

$$\Rightarrow I_1 = \left(\frac{600}{200} \times I_3' \right) + \left(\frac{400}{200} \times I_2 \right)$$

$$= 3 \times I_3' + 2 \times I_2$$



$$= 3 (I_2 + I_R) + 2 I_2$$

$$= 3 (3 \angle -45^\circ + 1 \angle 0^\circ) + 2 (1 \angle 0^\circ)$$

$$= 9 \angle -45^\circ + 3 \angle 0^\circ + 2 \angle 0^\circ$$

$$\Rightarrow I_1 = 13.24 \angle -29.24^\circ \text{ A}$$

(5)

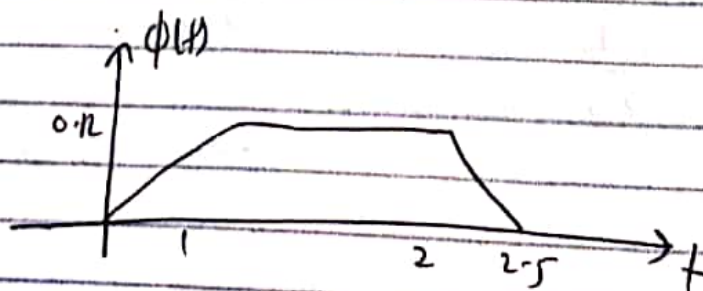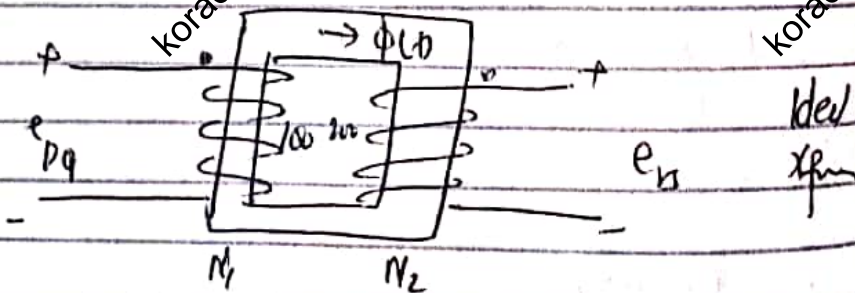

Find the waveform of e_p and e_s (induced voltage)

$$e(t) = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$e_p = N_1 \frac{d\phi}{dt}$$

$$e_s = N_2 \frac{d\phi}{dt}$$

e_{p1} and e_{s1} are in the same phase

$$\Rightarrow \frac{e_{p1}}{e_{s1}} = \frac{N_1}{N_2} = \frac{100}{200} = \frac{1}{2}$$

say

$$e_{s1} = 200 \times \frac{d}{dt} \phi(t)$$

(a) $0 < t < 1$

$$e_{s1} = 200 \times \frac{d}{dt} (0.12t) = 200 \times 0.12$$

$$= 24V$$


(b) $1 < t < 2$

$$\Rightarrow \frac{d\phi}{dt} = 0$$


(c) $2 < t < 2.5$

$$\text{slope} = \frac{0.12}{0.5} \Rightarrow e_{s1} = 200 \times \frac{0.12}{-0.5}$$

$$= -48V$$

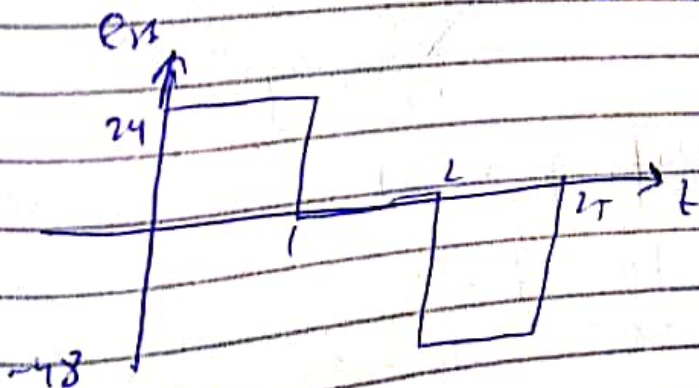


6

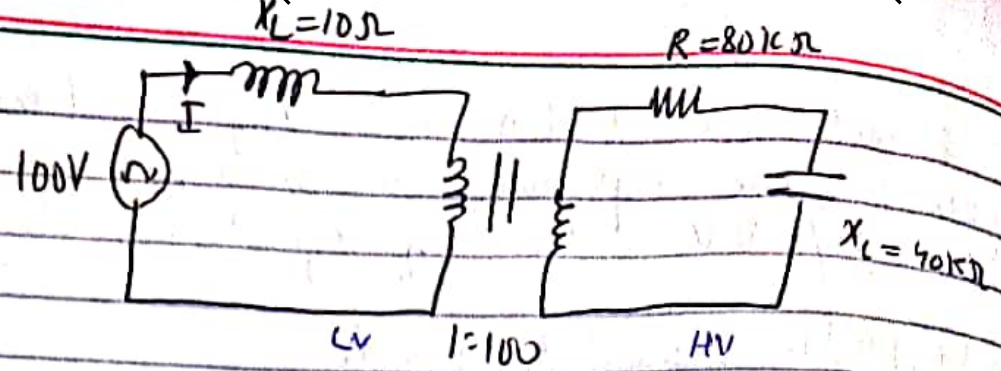

$I = ?$
 $\frac{N_1}{N_2} = \frac{1}{100} = a, \quad V_1 = 100V$

Referred to LV side.

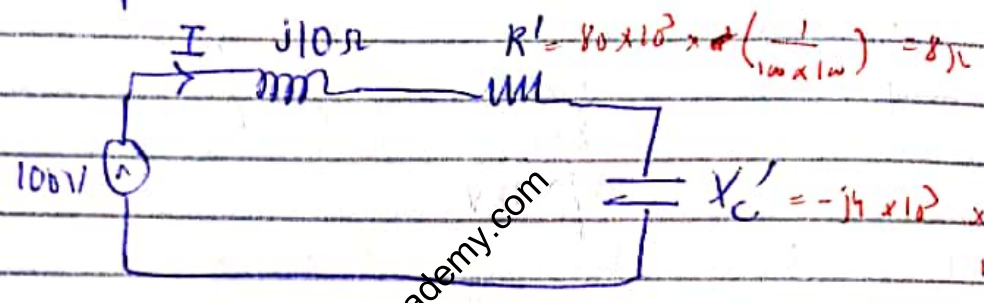

Reference; $V_1 = 100 \angle 0^\circ$

$\Rightarrow \bar{I} = \frac{100 \angle 0^\circ}{8 + j6} = \frac{100 \angle 0^\circ}{\sqrt{8^2 + 6^2} \angle \tan^{-1}(\frac{6}{8})}$

$\Rightarrow \bar{I} = 10 \angle -36.86^\circ$

$\Rightarrow I = 10A$

1/p power

$P = VI \cos \phi \rightarrow \text{active power}$
 $= 100 \times 10 \times \cos(36.86) = 800W$


$Q = VI \sin \phi \rightarrow \text{reactive power}$
 $= 100 \times 10 \times \sin(36.86) = 600VAR$

$600 = (10)^2 (6) = I^2 X$

⑦ A single phase load is fed through a feeder (33kV) whose impedance is $30 + j120 \Omega$ and X_{feeder} of equivalent impedance $(0.3 + j1.4) \Omega$ referred to LV side.


For a load of 100kW at 0.8 pf leading at 3.3 kV.

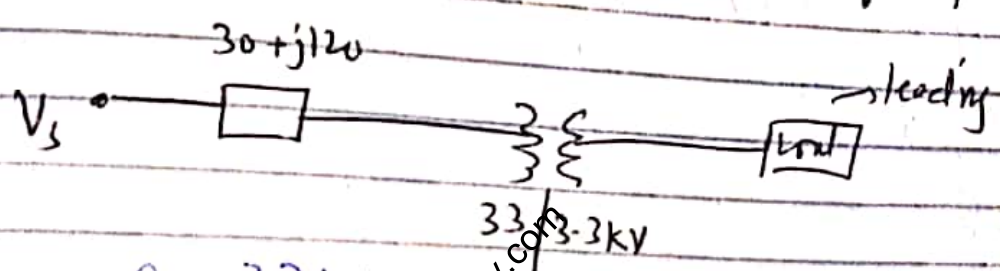- compute (i) Sending end voltage
- (ii) voltage at primary terminal of Xfeeder



$$a = \frac{33 \text{ kV}}{3.3 \text{ kV}}$$

Drawing the referred circuit to LV side;

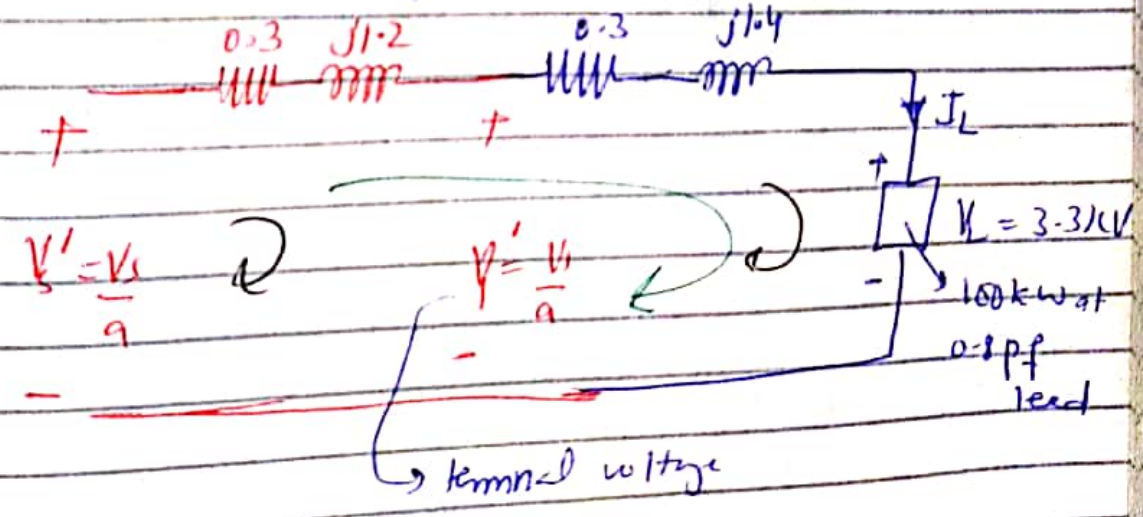

KVL
$$\vec{V}_s' = \vec{V} + \vec{I}_L (0.6 + j2.6) \quad \text{--- (1)}$$

V_L as my reference $3.3 \times 10^3 \angle 0^\circ$

$$I_L = ?$$

$$P = VI \cos \theta$$

$$100 \times 10^3 = 3.3 \times 10^3 \times I \times 0.8$$

$$I = 37.87 \text{ A}$$

$$\phi = \cos^{-1}(0.8) = 36.86^\circ$$

$$\Rightarrow \bar{I} = 37.87 \angle 36.86^\circ$$

$$\textcircled{A} \Rightarrow \bar{V}_s' = (3.3 \times 10^3 \angle 0^\circ) + (37.87 \angle 36.86^\circ)(0.6 + j2.6)$$

$$\bar{V}_s' = 3260.53 \angle 1.619^\circ$$

$$\Rightarrow V_s = V_s' \times 9 = (3260.53 \angle 1.619^\circ)(10)$$

$$\Rightarrow \bar{V}_s = 32605.3 \angle 1.619^\circ$$

Now for V_1'

$$\text{KVL} \Rightarrow V_1' = V_L + \bar{I}_L (0.3 + j1.4)$$

$$= 3300 \angle 0^\circ + 37.87 \angle 36.86^\circ (0.3 + j1.4)$$

$$V_1' = 3277.6 \angle 0.855^\circ$$

$$\text{NV} \quad V_1 = 9 V_1' = 10 \times V_1'$$


$$\Rightarrow V_1 = 32776.8 \angle 0.855^\circ$$

$$P_s = V_s \bar{I}_s \cos \theta$$

$$= 32776 \times 37.87$$

$$\times \cos(36.86 - 1.619)$$

$$\Rightarrow P_s = 100.85 \text{ kW}$$

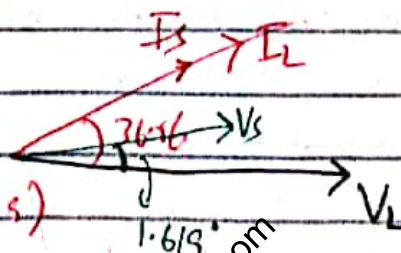

$$Q_s = V_s \bar{I}_s \sin \theta$$

Reactive power = $P \cdot \tan(\text{angle})$

DC is a constant signal.
 When DC supply is given to a coil, there will be no core losses (hysteresis, eddy current losses = 0) but winding losses are very high.


Transformer Losses

① Core loss (P_i) / Iron loss / Constant loss

(P_h) hysteresis loss ←
 (P_e) Eddy current loss ←

② Winding losses / variable losses / Copper losses


① Winding losses

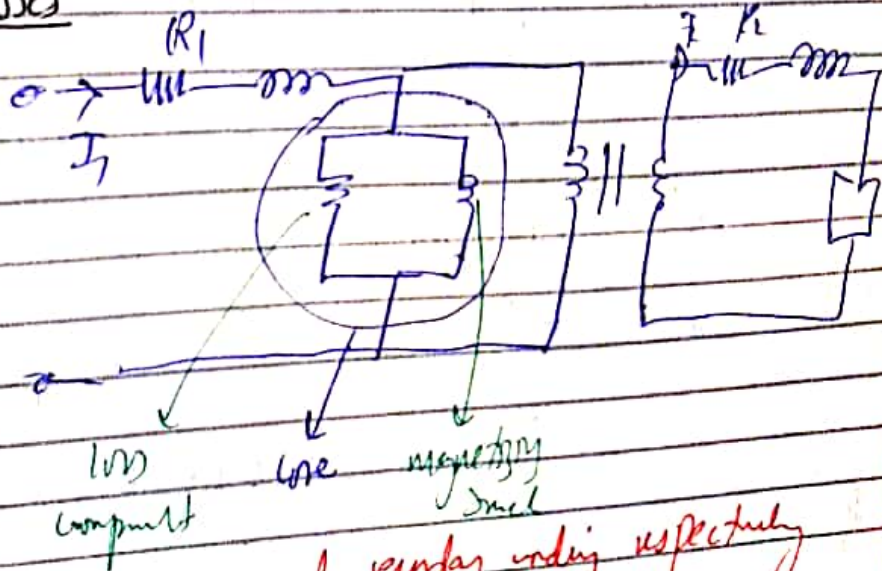


resistances of primary and secondary winding respectively are R_1 and R_2 .

$$\begin{aligned}
 P_{cu} &= I_1^2 R_1 + I_2^2 R_2 \\
 &= I_1^2 R_1 + I_2^2 R_2 \\
 &= I_1^2 R_1 + I_2^2 R_2
 \end{aligned}$$


If referred to primary;

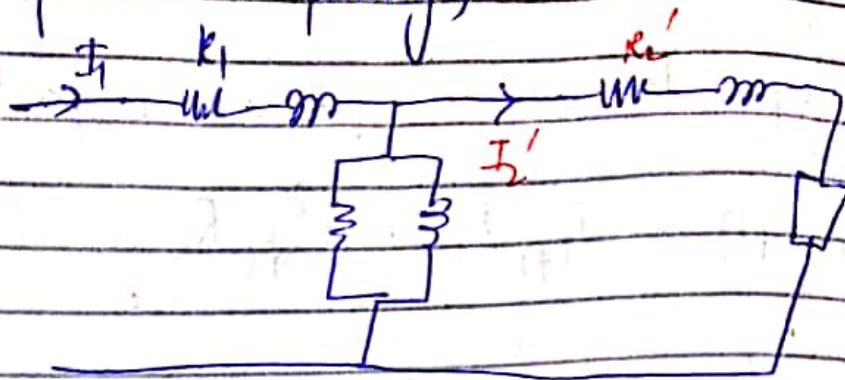

If referred from primary to secondary:

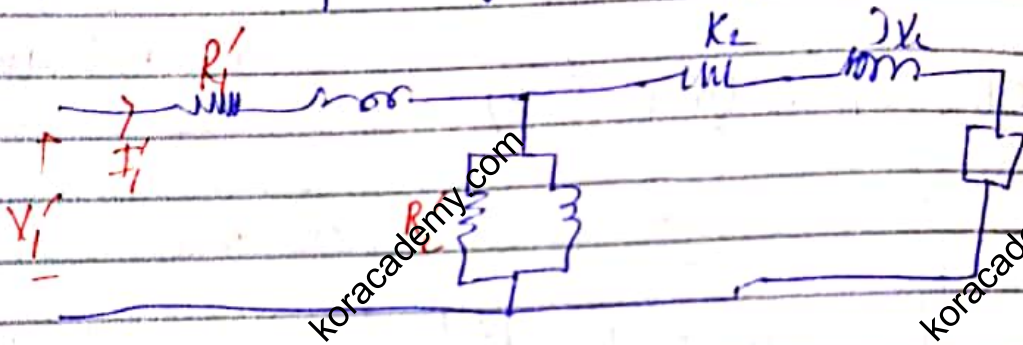

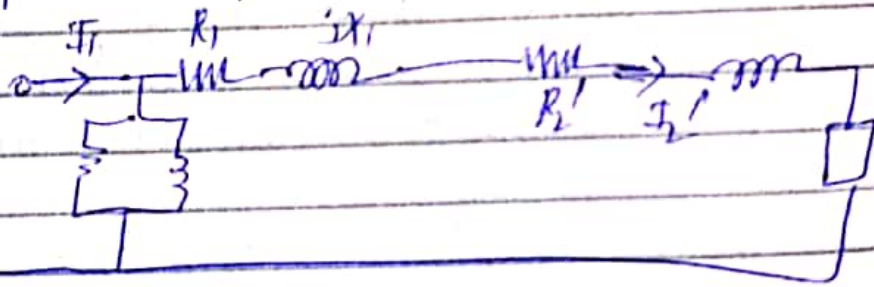Approximate equivalent model (if referred to primary)



$$P_{\text{loss}} = I_2'^2 (R_1 + R_2')$$

$$= I_1^2 (R_1 + R_2') \quad \text{if the core is neglected.}$$

If referred to secondary:

$$P_{\text{loss}} = I_2^2 (R_1' + R_2)$$

If I_1 is full load current and I_2 (f1).
 ↳ so copper loss will be full load copper loss.

$$P_w(f1) = I_{f1}^2 R_1 + I_{f1}^2 R_2$$

$$P_{cu\lambda} = x^2 P_{cu}$$

where $x = \frac{I}{I_{fl}}$

↳ fraction of load

② Eddy current losses (P_e)

↳ due to induction process in the core.

$$P_e = k_e f^2 B_m^2 t^2$$

k_e → Steinmetz constant, f → frequency.
 B_m → maximum flux density, t → thickness of lamination.

$$E = V = 4.44 f \phi_m N = 4.44 f B_m A_c N$$

$$\Rightarrow B_m = \frac{V}{4.44 f A_c N}$$

$$\Rightarrow B_m \propto \frac{V}{f}$$

Case 1 when $B_m = \text{const}$

$$\Rightarrow \frac{V}{f} = \text{constant}$$

$$\Rightarrow P_e \propto f^2$$

$$\Rightarrow P_e = A f^2$$

proportionally constant

Case ii when $B_m \neq \text{constant}$

$$\Rightarrow \frac{V}{f} \neq \text{constant}$$

$$\Rightarrow P_e = K_1 K_e f^2 \left(\frac{V}{f}\right)^2$$

as $B_m \neq \frac{V}{f}$

it is proportional to $\left(\frac{V}{f}\right)^2$

$$\Rightarrow \boxed{P_e \propto V^2} \Rightarrow P_e = k V^2$$

③ Hysteresis losses (P_h)

$$\boxed{P_h = K_h B_m^\alpha f V_{\text{core}}}$$

$K_h \rightarrow$ Steinmetz constant, $V \rightarrow$ volume of core

$\alpha \rightarrow$ Steinmetz exponent

For ferromagnetic materials $\alpha = 1.6$

Case i when $B_m = \text{constant} \Rightarrow \frac{V}{f} = \text{constant}$

$$\Rightarrow \boxed{P_h \propto f} \Rightarrow P_h = B f$$

Case ii when $B_m \neq \text{constant} \Rightarrow \frac{V}{f} \neq \text{constant}$

$$\Rightarrow P_h = K_h K_1 \left(\frac{V}{f}\right)^\alpha \cdot f \cdot V_{\text{core}}$$

$$\Rightarrow \boxed{P_h \propto V^{1.6} f^{-0.6}}$$

$$\Rightarrow P_h = K V^{1.6} f^{-0.6}$$

Q) Core loss $P_i = P_e + P_h$

Case i $B_m = \text{const}$

$$P_i = A f^2 + B f$$

Case ii $B_m \neq \text{const}$

$$P_i = k V^2 + k' V^{1.6} f^{-0.6}$$

ie core losses depend on whether the max flux density is constant or not.

Q1. A ϕ Xformer 400V, 50Hz has mm loss = 5000W at rated condition

When operated at 200V, 25Hz the mm loss is 2000W.

When operated at 416V, 52Hz, the value of hysteresis loss divided by eddy current loss is

$$P_{i1} = 5000 \text{ W}, V_1 = 400 \text{ V}, f_1 = 50 \text{ Hz}$$

$$P_{i2} = 2000 \text{ W}, V_2 = 200 \text{ V}, f_2 = 25 \text{ Hz}$$

$$V_3 = 416 \text{ V}, f_3 = 52 \text{ Hz}, \frac{P_{h3}}{P_{e3}} = ?$$

$$\frac{V_1}{f_1} = \frac{V_2}{f_2} = \frac{V_3}{f_3} = 8$$

$$\Rightarrow B_m = \text{constant}$$

$$\Rightarrow P_e \propto f^2, P_h \propto f$$

$$\Rightarrow P_e = a f^2, P_h = 5 f$$

$$\Rightarrow P_{i1} = 5000 = P_{e1} + P_{h1} = a f_1^2 + b f_1 = a(50)^2 + b(50) \quad \text{--- (1)}$$

$$P_{i2} = 2000 \text{ W} = P_{e2} + P_{h2} = a f_2^2 + b f_2 = a(25)^2 + b(25) \quad \text{--- (2)}$$

Solving $\Rightarrow a = 0.8, b = 60$

$$\Rightarrow P_{e3} = a f_3^2 = 0.8 (52)^2 = 2163.2$$

$$P_{h3} = b f_3 = (60)(52) = 3120$$

Ratio, $\frac{P_{h3}}{P_{e3}} = 1.44$ ans

Q2 For a 1 ϕ transformer, the supply voltage and frequency both have been increased by 10%. The percentage changes in the hysteresis and eddy current losses will be _____.

Say for $V_1, f_1 \rightarrow P_{i1} = P_{e1} + P_{h1}, \frac{V_1}{f_1}$

Now;

$$V_2 = 1.1 V_1, f_2 = 1.1 f_1$$

$$\frac{V_2}{f_2} = \frac{V_1}{f_1} \Rightarrow B_m = \text{const}$$

$\hookrightarrow P_e \propto f^2, P_h \propto f$

So $P_{i2} = P_{e2} + P_{h2}$

$$\left(\frac{1.1 f_1}{f_1}\right)^2 = \frac{P_{e2}}{P_{e1}} = \frac{f_2^2}{f_1^2} \quad \frac{P_{h2}}{P_{h1}} = \frac{f_2}{f_1} = \frac{1.1 f_1}{f_1}$$

$$\Rightarrow \begin{cases} P_{e2} = (1.1)^2 P_{e1} \\ P_{h2} = 1.1 P_{h1} \end{cases}$$

$$\% \Delta P = \frac{P_2 - P_1}{P_1} \times 100\%$$

$$\% \Delta P_h = \frac{P_{h2} - P_{h1}}{P_{h1}} = \frac{1.1 P_{h1} - P_{h1}}{P_{h1}} \times 100\%$$


$$= \frac{0.1 P_{h1}}{P_{h1}} \times 100\% = \boxed{10\%}$$

→ increment

$$\% \Delta P_e = \frac{P_{e2} - P_{e1}}{P_{e1}} = \frac{(1.1)^2 - 1}{1} \times 100\%$$

$$= \boxed{21\%} \rightarrow \text{increment}$$

Q3. Given that $V/f = \text{constant}$.

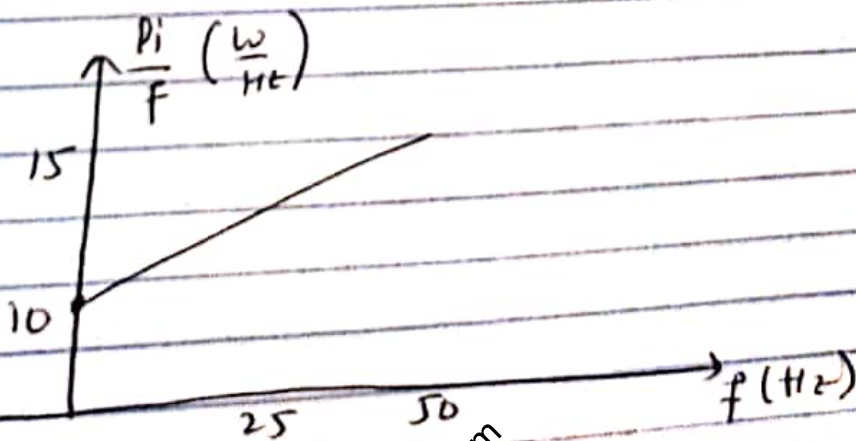

The hysteresis and eddy current losses of the motor at 25 Hz are _____ ?

$$B_m = \text{constit} \Rightarrow P_e \propto f^2, P_h \propto f$$

$$P_e = af^2, P_h = bf$$

$$\Rightarrow P_i = P_e + P_h = af^2 + bf$$

$$\Rightarrow \boxed{\frac{P_i}{f} = af + b}$$

$$y = mx + c$$

From graph.

i- when $f = 0$ Hz

$$10 = (a \times 0) + b$$

$$\boxed{b = 10}$$

$$\Rightarrow P_h = bf = (10)(25) = \underline{250 \text{ W}}$$

ii- when $f = 50$ Hz.

$$15 = (a \times 50) + b$$

$$\Rightarrow \boxed{a = \frac{1}{10}}$$

$$\Rightarrow P_e = af^2 = \left(\frac{1}{10}\right)(25)^2 = \underline{62.5 \text{ W}}$$

Q4. A 50 Hz transformer having equal hysteresis and eddy current losses at rated excitation is operated at 45 Hz at 90% of its rated voltage. compare to rated operated point, the core loss under this condition, reduced by 14.5%.

(10)

$V_1 \rightarrow \text{rated}$ $f_1 \rightarrow \text{rated} = 50 \text{ Hz}$

$$P_{i1} = P_{h1} + P_{e1} = 2P_{e1} \text{ or } 2P_{h1}$$

stc both are equal.

$$f_2 = 45 \text{ Hz}, \quad V_2 = 0.9 V_1$$

$$P_{i2} = P_{h2} + P_{e2}$$

$$\frac{V_2}{f_2} = \frac{0.9 V_1}{0.9 f_1} = \frac{V_1}{f_1}$$

$$\frac{f_2}{f_1} = \frac{45}{50} = 0.9$$

$$\Rightarrow \frac{V}{f} = \text{constant}$$

$$\Rightarrow f_2 = 0.9 f_1$$

$$\hookrightarrow P_e \propto f^2, \quad P_h \propto f$$

$$\frac{P_{h2}}{P_{h1}} = \frac{f_2}{f_1} = \frac{45}{50} = 0.9$$

$$\Rightarrow \boxed{P_{h2} = 0.9 P_{h1}}$$

$$\frac{P_{e2}}{P_{e1}} = \frac{f_2^2}{f_1^2} = \left(\frac{45}{50}\right)^2 = (0.9)^2$$

$$\Rightarrow \boxed{P_{e2} = 0.81 P_{e1}}$$

Now;

$$P_{i2} = P_{e2} + P_{h2} = 0.9 P_{h1} + 0.81 P_{e1}$$

$$\Rightarrow P_{i2} = 0.9 P_{e1} + 0.81 P_{e1} = 1.71 P_{e1}$$

$$\% \Delta P_i = \frac{P_{i2} - P_{i1}}{P_{i1}} \times 100\% = \frac{1.71 P_{e1} - 2 P_{e1}}{2 P_{e1}}$$

$$= \frac{1.71 - 2}{2}$$

$$\Rightarrow \boxed{\% \Delta P_i = -14.5\%}$$

koracademy.com y 17.5% ←

No Load Test / Open Circuit Test

↳ under no load condition.

⇒ It is performed on L.V side. (instruments)
 ↳ HV side is open. ⇒ $I_2 = 0A$

With this test, we find;

- i. Core loss.
- ii. Shunt branch parameters (X_m and R_c)

It is done at rated voltage and frequency.

(It can also be performed on HV side but recommended on LV side).


$I_0 \rightarrow 2 + 5\%$ of I_{FL}

LV	HV
V ↓	V ↑
I ↑	I ↓


↳ more precise ammeter will be required.
 ↳ voltage size will increase → cost

Three readings;

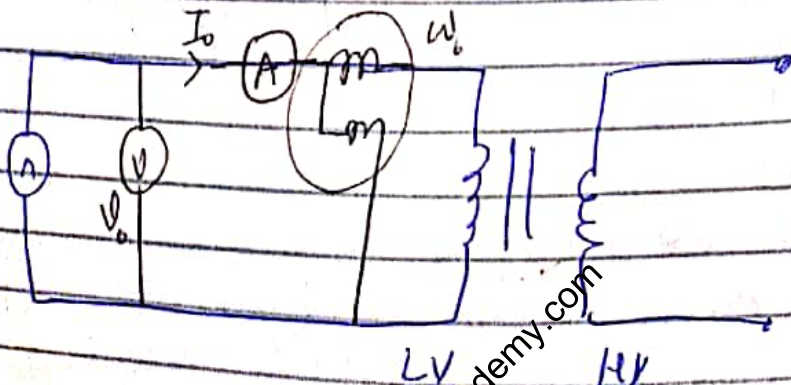
- i. Voltmeter reading (V_0) → rated voltage.
- ii. Ammeter reading (I_0) → 2 to 5% of full load current
- iii. Wattmeter reading (W_0) → Iron losses (P_i)



Drawing the equivalent circuit;

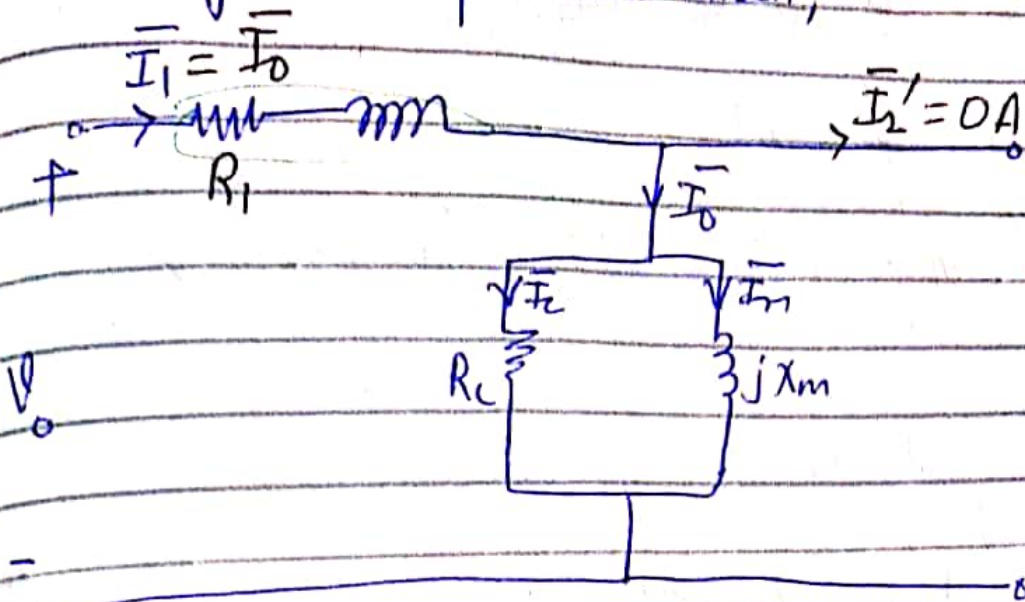


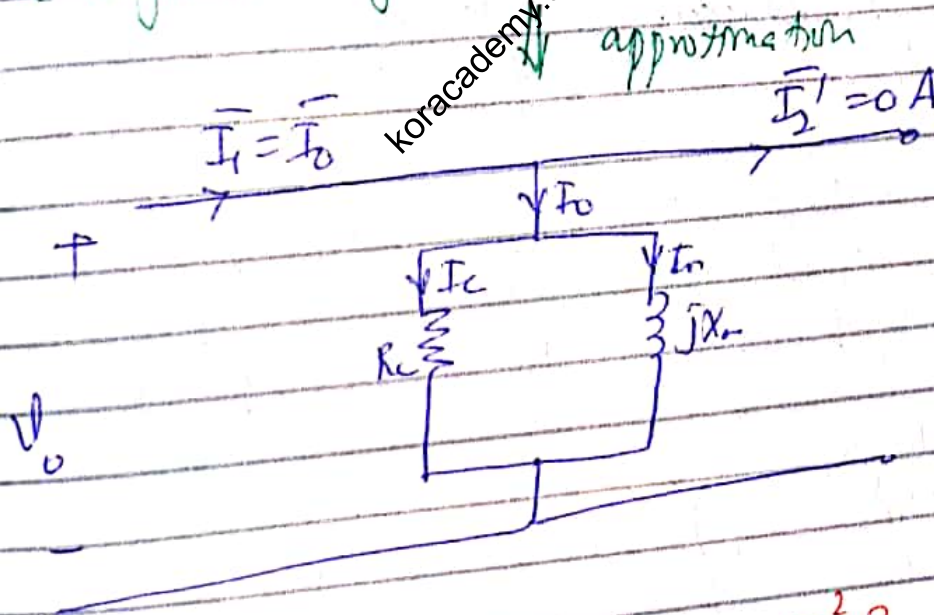No load $\Rightarrow I_0$ is also very less \Rightarrow the drop will also be very less \Rightarrow neglect



$$(i) W_0 = P_i = V_0 I_0 \cos \phi_0 = I_c^2 R_c$$

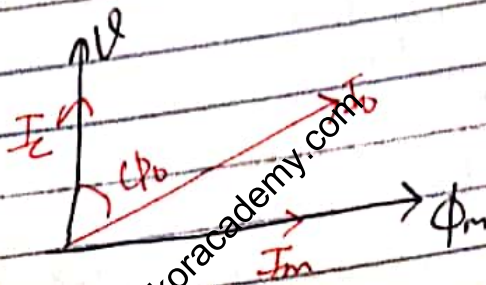i/p p.f \leftarrow where $\cos \phi_0 = \frac{W_0}{V_0 I_0}$



$$ii. |I_c| = I_0 \cos \phi_0$$

$$|I_m| = I_0 \sin \phi_0$$

$$iii. R_c = \frac{V_0}{I_0}, \quad X_m = \frac{V_0}{I_m}$$

If the winding resistance (R_1) is not neglected;


$$W_0 = P_i + I_0^2 R_1$$

Wattmeter will give us the total power taken from the input.

⇒ If no load test performed at rated voltage and reduced frequency.

$$V = \text{rated}, \quad f \neq \text{rated}$$

$$\uparrow B_m \propto \frac{V}{f}$$

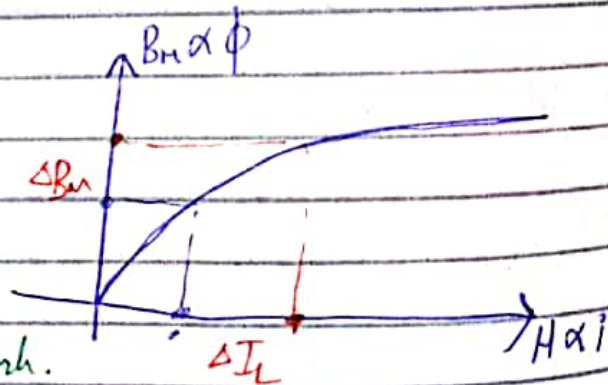

ΔB_m will be very less due to saturation but to bring this change the ΔI will be very much.

If frequency is reduced than the rated, the core will move to deep saturation. → not advisable to reduce f than rated.

$$\Rightarrow \uparrow I_m = \frac{V}{\downarrow jX_m} = \frac{V}{2\pi f L}$$

⇒ demand of magnetizing current for supply will increase

→ $B_m \neq \text{constant}$


$P_e \propto V^2$

$\uparrow P_h \propto \frac{V^{1.6}}{f^{0.6}}$

↳ no effect if f is changed.

$\uparrow P_i = P_c + \uparrow P_h$

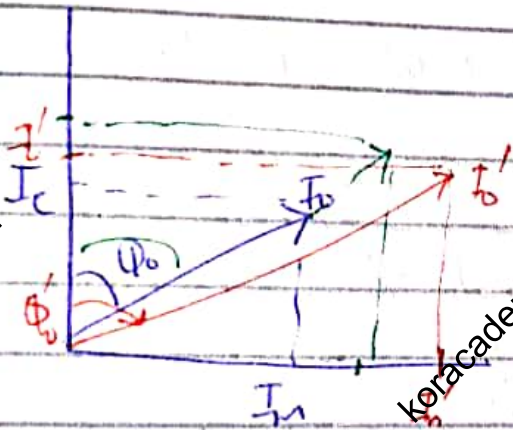$\uparrow P_i = I_c^2 R_c \Rightarrow \uparrow I_o = \sqrt{\uparrow I_c^2 + I_m^2}$



$I_o \uparrow$
 ↳ If I_c and I_m increase the same rate.
 ↳ p.f. angle will increase the same which generally does not happen

Usually I_m increases it a much faster rate than I_c .

$\phi_0' > \phi_0 \Rightarrow$ p.f. angle has increased.

$\omega \phi_0' < \omega \phi_0 \Rightarrow$ p.f. has reduced.


(angle ↓ ⇒ ω ↑)

not good sign ↓

Short Circuit Test

↳ to know the series parameters.

It is performed on HV side (recommended)

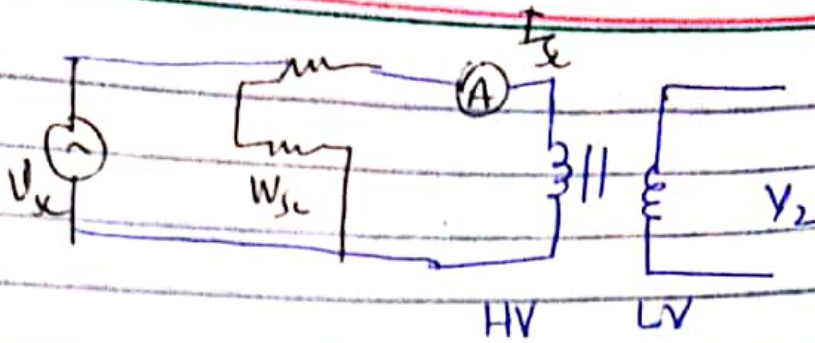

The readings will be;


$$W_{sc}, V_{sc}, I_{sc}$$

↳ reduced voltage (a fraction of V_{rated})

Using the approximated equivalent circuit referring from secondary to primary -

$$R_{eq} = R_1 + R_2'$$

$$X_{eq} = X_1 + X_2'$$

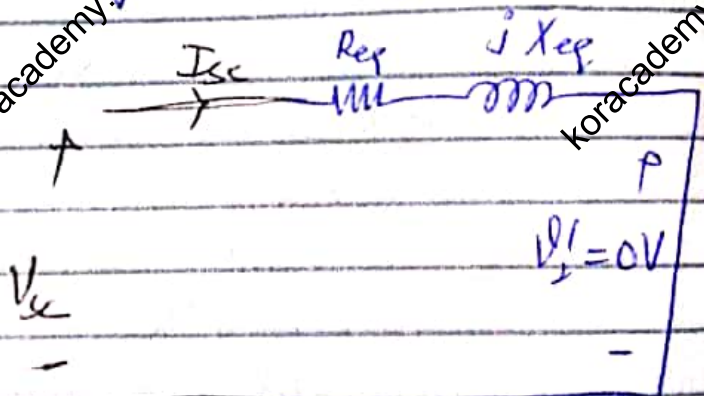


$$i) Z_{eq} = \frac{|V_{sc}|}{|I_{sc}|}$$

$$ii) W_{sc} = I_{sc}^2 R_{eq} = V_{sc} I_{sc} \cos \phi_{sc}$$

$$iii) \text{ p.f. at s.c } \cos \phi_{sc} = \frac{W_{sc}}{V_{sc} I_{sc}}$$

$$iii) Z_{eq} = \sqrt{R_{eq}^2 + X_{eq}^2} \Rightarrow X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

If we change LV and HV.

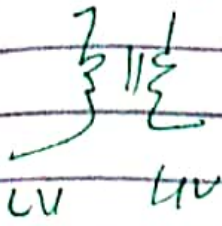


HV side short circuited.


Refer from primary to secondary.

$$\Rightarrow V_{sc}', I_{sc}', V_2, R_{eq} = R_1' + R_2$$
$$X_{eq} = X_1' + X_2$$

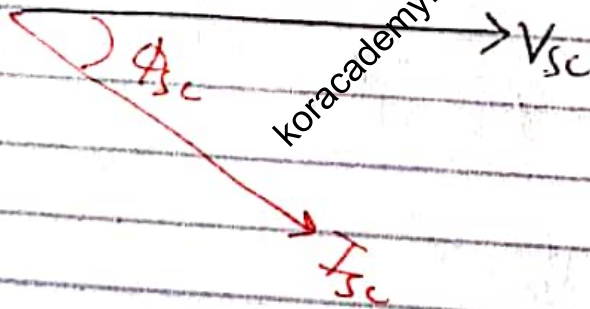Drawing phasor diagram for the equivalent circuit;



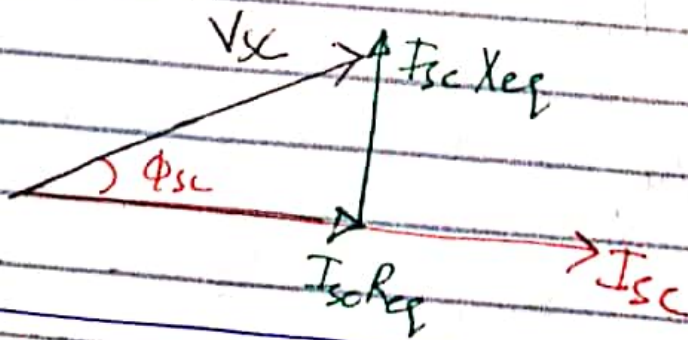
$$V_{sc} = I_{sc} R_{eq} + j I_{sc} X_{eq}$$



$$\cos \phi_{sc} = \frac{I_{sc} R_{eq}}{V_{sc}}$$

Tallying of Impedance triangle;
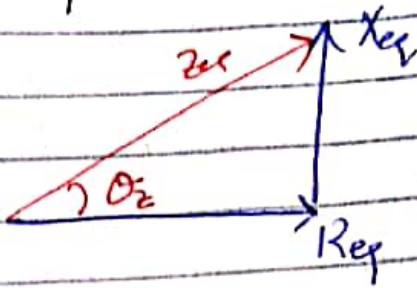
$$\cos \theta_2 = \frac{R_{eq}}{Z_{eq}}$$




$$Z_{eq} = \frac{\bar{V}_{sc}}{\bar{I}_{sc}} = \frac{|V_{sc}| \angle \phi_{sc}}{|I_{sc}| \angle 0^\circ} = |Z_{eq}| \angle \theta_2$$

→ In case of S.C test;

$$\phi_{sc} = \theta_2$$

Important Points.

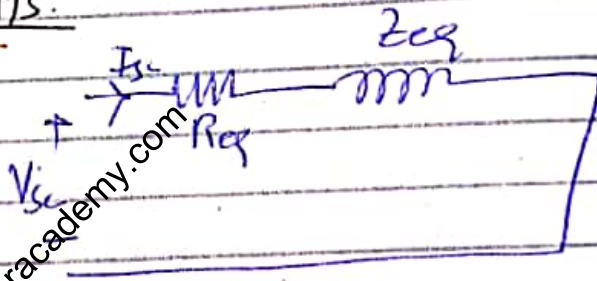

1. Rated S.C current and steady state sc current

(a) When V_{sc} is a reduced voltage

$$V_{sc(\text{reduced})} < V_{sc(\text{rated})}$$

$$\Rightarrow I_{sc(\text{rated})} = \frac{V_{sc(\text{reduced})}}{Z_{eq}}$$

(b) when V_x is rated voltage.

$$V_{sc} = V_x(\text{rated})$$

$$I_{sc(\text{steady})} = \frac{V_{sc(\text{rated})}}{Z_{eq}}$$

→ 10 to 15% higher than $I_{sc(\text{rated})}$ → in next column

$$I_{sc} \text{ (Steady)} = \frac{V}{Z_{eq} \text{ (pu)}}$$

$$I_{sc} \text{ initial (pu)} = 1 \text{ pu}$$

Let $V_{sc} = \text{constant}$ and $f \neq \text{constant}$

If f is reduced \downarrow If increased \uparrow

$$Z_{eq} = \sqrt{R_{eq}^2 + X_{eq}^2}, \quad R_{eq} = \frac{V_{sc}}{I_{sc}}, \quad X_{eq} = 2\pi f L_{eq}$$

$$\cos \phi_{sc} = \frac{R_{eq}}{Z_{eq}}, \quad \frac{I_{sc}}{V_{sc}} = \frac{1}{Z_{eq}}$$

$$\phi_{sc} \downarrow \uparrow \quad \uparrow W_{sc} = \downarrow \uparrow I_{sc}^2 R_{eq}$$

P.f. will improve
P.f. will deteriorate.

Transformer Efficiency

$$\% \eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$= \frac{P_{out}}{P_{out} + \text{Losses}} \times 100\%$$

$$\eta = \frac{VI \cos \phi}{VI \cos \phi + P_i + P_{cu}}$$

Generally for any load;

$$\eta_{\text{at any load}} = \frac{x \cdot (VI)_{\text{rated}} \cos \phi}{x(VI)_{\text{rated}} \cos \phi + P_i + x^2 P_{cu}}$$

PF of load

x = fraction of loading, $x = I/I_{\text{rated}}$

$(VI)_{\text{rated}}$ = given volt ampere rating of transformer.

$$\Rightarrow \text{also } x = \frac{VA}{(VA)_{\text{rated}}}$$

$$P_i = P_h + P_e, \quad P_{cu} = \text{full load copper loss} \\ = (I_{fl})^2 \times R_{eq}$$

Under maximum efficiency;

$$\frac{d\eta}{dx} = 0$$

$$P_i = P_{cu} = x^2 P_{cu}$$

copper loss become equal to iron loss

$$\Rightarrow i. \quad P_{cu} = P_i \Rightarrow x^2 P_{cu} = P_i$$

\Rightarrow

$$x = \sqrt{\frac{P_i}{P_{cu}}}$$

$$ii. \quad \boxed{I_{max} = \frac{VA}{V_{rated}}}$$

$$iii. \quad P_{cu} = (I_{rated})^2 R_{eq}$$

where $I_{rated} = \frac{VA_{rated}}{V_{rated}}$

Now:

$$P_{cu} (pu) = \frac{P_{cu}}{(P_{out})_{base}} = \frac{I_{rated}^2 \cdot R_{eq}}{V_{rated} \times I_{rated}}$$

$$= \frac{R_{eq}}{V_{rated} / I_{rated}} = \frac{R_{eq}}{(Z)_{base}} = R_{eq} (pu)$$

$$\Rightarrow \boxed{P_{cu} (pu) = R_{eq} (pu)}$$

↳ only true at full load conditions.

Efficiency in terms of pu.

$$As \quad \eta = \frac{\eta \cdot (VA)_{rated} \cdot \cos\phi}{\eta \cdot (VA)_{rated} \cos\phi + P_1 + \eta^2 P_{cu}}$$

$$\boxed{\eta_{pu} = \frac{\eta \cdot I \cdot \cos\phi}{\eta \cdot I \cdot \cos\phi + P_1 (pu) + \eta^2 P_{cu} (pu)}}$$

$$P_1 (pu) = \frac{P_1}{VA}$$

Q1. O.C and S.C test data are given below for a 1- ϕ 5 MVA, 200/400V, 50 Hz transformer.

O.C (LV) \rightarrow 200V, 1.25 A, 150 W.

S.C (HV) \rightarrow 20V, 12.5 A, 175 W.

Transformer efficiency at 75% load at 0.7 pf

Given transformer rating 200/400V, VA_{rated} = 5 MVA
LV HV

$V_o = 200V$, $I_o = 1.25A$, w_o or $P_i = 150W$

$V_{sc} = 20V$, $I_{sc} = 12.5A$, w_{sc} or $P_{cu} = 175W$

$$\eta_n = \frac{\eta (VA)_{rated} \cos \phi}{\eta (VA)_{rated} \cos \phi + P_i + \eta^2 P_{cu}}$$

$$(I_{rated})_{HV} = \frac{(VA)_{rated}}{(V_{rated})_{HV}} = \frac{5 \times 10^6}{400} = 12.5$$

rated current corresponds full load copper loss

$$\Rightarrow P_{cu} = 175 \text{ W}$$

$$\Rightarrow \eta = \frac{(0.75)(5 \times 10^6)(0.7)}{(0.75)(5 \times 10^6)(0.7) + 150 + (0.75)^2(175)}$$

$$\Rightarrow \eta = 91.35\% \text{ Ans.}$$

At what load will we have maximum efficiency.

$$P_i = \eta^2 P_{cu} \Rightarrow \eta = \sqrt{\frac{P_i}{P_{cu}}} = \sqrt{\frac{150}{175}} = 0.92$$

Similarly $(VA)_{full} = \eta (VA)_{rated}$

$= 0.925 \times 5 = 4.62 \text{ MVA}$

Q2 For the following data 10KVA, 500/250V X_{form}

D.C test \rightarrow 250V, 3A, 200W. (LV)

S.C test \rightarrow 15V, 30A, 300W. (HV)

X_{former} efficiency at full load at 0.8 pf is _____?

$V_o = 250V, I_o = 3A, P_i = 200W.$

$V_{sc} = 15V, I_{sc} = 30A, P_{cu} = 300W.$

Full load $\Rightarrow \eta = \frac{1}{1}$ $VA_{rated} = 10 \times 10^3$

$\cos \phi = 0.8, P_i = 200W.$

$I_{rated} = \frac{(VA)_{rated}}{V_{rated}} = \frac{10 \times 10^3}{500} = 20A$

$P_{cu} = \eta^2 P_w \Rightarrow 300 = \left(\frac{30}{20}\right)^2 P_w$

$\Rightarrow P_w = 133.3W.$

$\Rightarrow \eta = \frac{1 \times 10 \times 10^3 \times 0.8}{1 \times 10 \times 10^3 \times 0.8 + 200 + \eta^2 (133.3)}$

$\Rightarrow \eta = 96\% \text{ Ans.}$

$Z_{eq} = \frac{V_{sc}}{I_{sc}} = \frac{15}{30} = \frac{1}{2} \Omega.$

$$\rightarrow P_{\text{loss}} = I^2 R_{\text{eq}}$$

$$300 = (30)^2 R_{\text{eq}} \Rightarrow R_{\text{eq}} = \frac{1}{3} \Omega$$

$$\Rightarrow X_{\text{eq}} = \sqrt{Z_{\text{eq}}^2 - R_{\text{eq}}^2} = \sqrt{\left(\frac{1}{4}\right)^2 - \left(\frac{1}{9}\right)^2}$$

$$\Rightarrow X_{\text{eq}} = \sqrt{\frac{5}{36}} = 0.37 \Omega$$

$$\rightarrow Z_{\text{eq}} (\text{pu}) = \frac{Z_{\text{eq}}}{Z_{\text{eq}} (\text{base})} = \frac{1}{2 \times \frac{V_{\text{rated}}}{I_{\text{rated}}}}$$

$$= \frac{1}{2 \times \frac{500}{20}} \Rightarrow Z_{\text{eq}} (\text{pu}) = \frac{1}{50} \text{ pu}$$

$$\rightarrow R_{\text{eq}} (\text{pu}) = \frac{1}{3 \times \frac{500}{20}} \Rightarrow R_{\text{eq}} (\text{pu}) = 0.0133 \text{ pu}$$

Q3 A 1 kVA, 200/100V, 50 Hz, 1 ϕ X-former have following results at 50 Hz

O.C (LV) \rightarrow 100V, 20 watt.

S.C (HV) \rightarrow 5A, 25 watt.

If it is assumed that no load loss component are equally divided. The above tests were then conducted on the same transformer at 40 Hz. The results were;

O.C (HV) \rightarrow 160V $W_1 = ?$

S.C (LV) \rightarrow 10A $W_2 = ?$

At 50 Hz, $P_{in} = 20 \text{ Watt}$

$$\left(\frac{T_{rated}\right)_{HV} = \frac{1 \times 10^3}{200} = 5 \text{ A}$$

$$\Rightarrow P_{\omega(50)} = 25 \text{ watt.}$$

Similarly $\left(\frac{T_{rated}\right)_{LV} = \frac{1 \times 10^3}{100} = 10 \text{ A}$

$$\Rightarrow W_2 = 25 \text{ watt.}$$

Full load upper loss is independent of frequency.

↳ upper loss will change at full load will not change

$$P_{in} = 20 \text{ W} = P_{e1} + P_{h1} = 2P_{e1} \text{ or } 2P_{h1}$$

$$P_{e1} = \frac{20}{2} = 10 \text{ W as equally divided}$$

At 40 Hz,

checking if B_m is constant or not.

$$\frac{V_1}{f_1} = \frac{V_2}{f_2}, \quad \frac{200}{50} = \frac{160}{40} \Rightarrow 4 = 4.$$

$$\Rightarrow B_m = \text{constant}$$

$$\Rightarrow P_e \propto f^2, \quad P_h \propto f$$

$$\frac{P_{e2}}{P_{e1}} = \left(\frac{f_2}{f_1}\right)^2 \quad \text{or} \quad \frac{P_{h1}}{P_{h2}} = \frac{f_1}{f_2}$$

$$\rightarrow P_{e2} = \left(\frac{40}{50}\right)^2 \times (10) = 6.4$$



$$P_{h2} = \left(\frac{40}{50}\right)^2 \times (10) = 8 \text{ Watt}$$

$$\Rightarrow P_{12} = P_{e2} + P_{h2} = 14.4 \text{ Watt} = \text{Ans}$$

Q4 A 50 Hz 1 ϕ transformer, draws a short circuit current of 30A at 0.2 pf lags when connected to 16V, 50 Hz source.

What will be the s.c current and its pf when the same Xformer is energized from 16V, 25 Hz source.

The Xformer equivalent circuit is

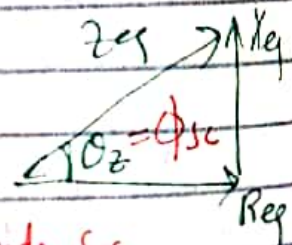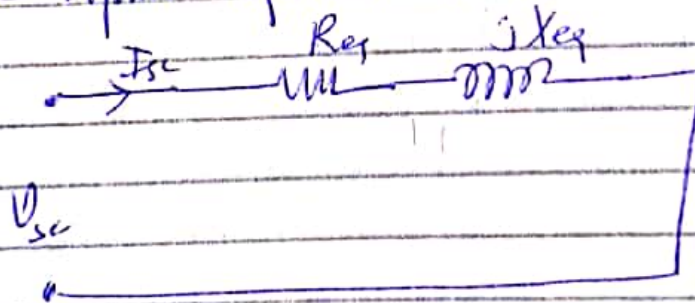

under s.c

$$\cos \phi_{sc} = \frac{R_{eq}}{Z_{eq}}$$

$$\text{At } 16V, 50Hz : \cos \phi_{sc1} = 0.2$$

$$I_{sc1} = 30A, \quad V_{sc1} = 16V, \quad f_1 = 50Hz$$

$$\text{we know } I_{sc1} = \frac{V_{sc1}}{Z_{eq1}}$$

Now; $V_{sc2} = 16V$, $I_{sc2} = ?$, $\cos \phi_{sc2} = ?$

$$f_2 = 25 \text{ Hz}, \quad I_{sc2} = \frac{V_{sc2}}{Z_{eq2}}$$

$$\frac{I_{sc2}}{I_{sc1}} = \frac{Z_{eq1}}{Z_{eq2}} = \left(\frac{Z_{eq1}}{R_{eq1}} \right) \left(\frac{R_{eq1}}{Z_{eq2}} \right)$$

$$\Rightarrow \frac{I_{sc2}}{I_{sc1}} = \frac{\cos \phi_{sc2}}{\cos \phi_{sc1}} \quad \text{--- (1)}$$

Also $\tan \phi_{sc} = \frac{X_{eq}}{R_{eq}}$

$$\Rightarrow \frac{\tan \phi_{sc2}}{\tan \phi_{sc1}} = \frac{X_{eq2}}{X_{eq1}} = \frac{1}{2}$$

As $X_{eq} \propto f$

$$\Rightarrow \frac{X_{eq2}}{X_{eq1}} = \frac{f_2}{f_1} = \frac{25}{50} = \frac{1}{2}$$

$$\Rightarrow X_{eq2} = \frac{X_{eq1}}{2}$$

$$\Rightarrow \tan \phi_{sc2} = \frac{1}{2} \times \tan \phi_{sc1} = \frac{1}{2} \times 1 (\cos^{-1} 0.2)$$

$$\Rightarrow \tan \phi_{sc2} = 2.448$$

$$\Rightarrow \phi_{sc2} = \tan^{-1}(2.448) = 67.78^\circ$$

$$\textcircled{1} \Rightarrow I_{sc} = 30 \times \left(\frac{\cos 67.78^\circ}{0.2} \right)$$

$$\Rightarrow I_{sc} = 57.72 \text{ A}$$

$$\text{Now pf} \Rightarrow \cos \phi_{sc} = \cos(67.78^\circ) = 0.378$$

Method 2

$$\bar{I}_{sc1} = \frac{\bar{V}_{sc}}{\bar{Z}_{eq}} \Rightarrow \bar{Z}_{eq} = \frac{\bar{V}_{sc}}{\bar{I}_{sc}} = \frac{16 \angle 0^\circ}{30 \angle -67.78^\circ}$$

$$\Rightarrow \bar{Z}_{eq} = \frac{16 \angle -7.46^\circ}{30} = 0.106 + j0.5225$$

\downarrow
 R_{eq1}

\downarrow
 X_{eq1}

Now

$$I_{sc2} = \frac{V_{sc}}{Z_{eq2}}$$

$$Z_{eq2} = R_{eq2} + jX_{eq2} = 0.106 + j \left(\frac{0.5225}{2} \right)$$

$$\Rightarrow I_{sc2} = \frac{16 \angle 0^\circ}{0.106 + j} = 56.7 \angle -67.78^\circ$$

$$\downarrow$$

$$\cos 67.76^\circ = 0.378$$

Q5. A 1 ϕ transformer has no load loss of 64W as obtained from O.C test, when a S.C test is performed on it with 90% of rated current flowing both in LV and HV windings, the maximum loss is 81W.

The transformer has maximum efficiency when operated at 80% of rated current.

Under maximum efficiency condition,

$$P_i = P_{cu} = \eta^2 P_o$$

$$\Rightarrow \eta = \sqrt{\frac{P_i}{P_o}} = \sqrt{\frac{64}{100}} = 0.8 = 80\%$$

$$P_{cu} = \eta^2 P_o$$

$$\Rightarrow P_o = \frac{81}{(0.8)^2} = 100W.$$

Ans.

~~Ans = $\frac{100}{0.8^2}$ W~~
~~100W at 0.8 pf~~

Q6. A 10KVA, 400/200V 1 ϕ transformer with 10% impedance draws a steady state short circuit current of 250 A.

0.1 pu

$$\rightarrow I_{sc} (\text{steady state}) = \frac{V_{sc}}{Z_{eq}} = \frac{V_{sc \text{ rated}}}{Z_{eq}}$$

$$\rightarrow I_{sc} \text{ steady state (pu)} = \frac{1}{Z_{eq} (\text{pu})} = \frac{1}{0.1} = 10$$

$$I_{sc} = \frac{I_{sc} \text{ rated}}{I_{sc} \text{ base}} \Rightarrow I_{sc} \text{ Act} = I_{sc} \text{ rated} \times \frac{I_{sc} \text{ base}}{I_{sc} \text{ rated}}$$

$$I_{sc} \text{ base} = \frac{10 \times 10^3}{400}$$

$$I_{sc} = \frac{10 \times 10 \times 10^3}{400} = \frac{1000}{4} = 250 \text{ A}$$

Method 2

$$Z_{base} = \frac{V_{rated}}{I_{rated}} = \frac{V_{rated}^2}{VA_{rated}}$$

$$I_{sc} \text{ study site} = \frac{V_{sc}}{Z_{eq}} = \frac{400}{0.1 \times \frac{(400)^2}{10 \times 10^3}}$$

$$\Rightarrow I_{sc} = 250 \text{ A}$$

Q7. An 11/0.4 kV, 25 Hz, 1 φ transformer has ohmic, hysteresis and eddy current losses of 1.8%, 0.8%, 0.3%, respectively.

The transformer is now operated at 22 kV, 20 Hz supply.

The unit is assumed to remain same in both cases.

The %age increase in efficiency is _____.

$$P_{cu} (\%) = 0.018, \quad P_{h, m} = 0.008, \quad P_{e, m} = 0.003$$

$$V_1 = 11 \text{ kV}, \quad f_1 = 25 \text{ Hz}$$

Now, $V_1 = 22V$, $f_1 = 50\text{Hz}$

$\therefore P_w = \frac{I^2 R_{eq}}{f_1} \rightarrow \text{actual value}$

$P_w (pw) = \frac{I_{ret}^2 R_{eq}}{V_{ret} I_{ret}} \Rightarrow P_w \propto \frac{1}{V_{ret}}$

$\Rightarrow \frac{P_{w1}}{P_{w2}} = \frac{V_{ret2}}{V_{ret1}} = \frac{11}{22} = \frac{1}{2}$

$\Rightarrow \frac{P_{w2}}{P_{w1}} = \frac{P_{w1}}{2} = \frac{0.018}{2} = 0.009$

$\Rightarrow P_{i1} = 0.008 + 0.009$

check V/f ratio.

$\frac{V_1}{f_1} = \frac{V_2}{f_2} \Rightarrow \frac{11}{25} = \frac{22}{50} = 0.44$

$\Rightarrow B_m = \text{const}$

$\Rightarrow P_e \propto \frac{f^2}{VA}$, $P_m \propto \frac{f}{VA}$

Watt is also const

$\Rightarrow P_e \propto \frac{f^2}{V}$, $P_m \propto \frac{f}{V}$

$$\Rightarrow \frac{P_{e2} p_v}{P_{e1} p_v} = \left(\frac{50^2}{22 \times 10^3} \right) \times \frac{1}{\frac{(25)^2}{11 \times 10^3}} = 2$$

$$\Rightarrow \frac{P_{e2}}{p_v} = 2 \frac{P_{e1}}{p_v} = 2(0.003)$$

$$\Rightarrow \frac{P_{e2}}{p_v} = 0.006 \quad \text{twice } p_v$$

Now for P_h

$$\frac{P_{h2} p_v}{P_{h1} p_v} = \left(\frac{50}{22 \times 10^3} \right) \times \left(\frac{11 \times 10^3}{25} \right) = 1$$

$$\Rightarrow \frac{P_{h2}}{p_v} = \frac{P_{h1}}{p_v} = 0.008$$

↳ hysteresis \Rightarrow $\frac{P_{e2}}{p_v}$ will not change
 \Rightarrow The actual value will change however.

$$\eta_1 = \frac{\eta VA_{\text{rot}} \cos \phi}{\eta VA_{\text{rot}} \cos \phi + P_i + \omega^2 p_v} = 97.18 \%$$

$$\eta_{1 p_v} = \frac{\eta \times 1 \times 1}{\eta + 0.011 + \eta^2(0.018)}$$

↳ assume $\eta = 1$

$$\Rightarrow \eta_{1 p_v} = 0.9718 p_v$$

$$\text{Now } \eta_2 = \frac{1 \times 1}{1 \times 1 + (0.006 + 0.008) + 0.058}$$

$$= 0.9777 p_v = 97.75 \%$$

% reg. mouse = ?

$$\% \eta = \frac{\eta_2 - \eta_1}{\eta_1} = \frac{0.9775 - 0.9714}{0.9714}$$

$$= 5.865 \times 10^{-3} \times 100\%$$

$$= 0.5865\%$$

= Ans.

Name plate rating of transformer

eg 50 kVA, 220/110 V, 50 Hz

↓
Rated kVA

↓
LV rated voltage

↓
operating frequency

↓
HV rated voltage

↳ At no load condition

Rated means at manufacturer end. It does not mean full load uses.

Voltage regulation,
$$V_R = \frac{V_{\text{no load}} - V_{\text{load}}}{V_{\text{rated}}}$$

and

$$V_R = \frac{r}{\text{pu}} \cos \phi + \frac{X}{\text{pu}} \sin \phi$$


+ → lag, - → lead

At the consumer end, we need the voltage to be constant (not fluctuating) but actually we have fluctuations due to voltage drops (depending on the loading condition). To study this change is called voltage regulation.

Auto Transformer

In a simple two winding transformer, the windings (i.e. primary and secondary) are electrically isolated.

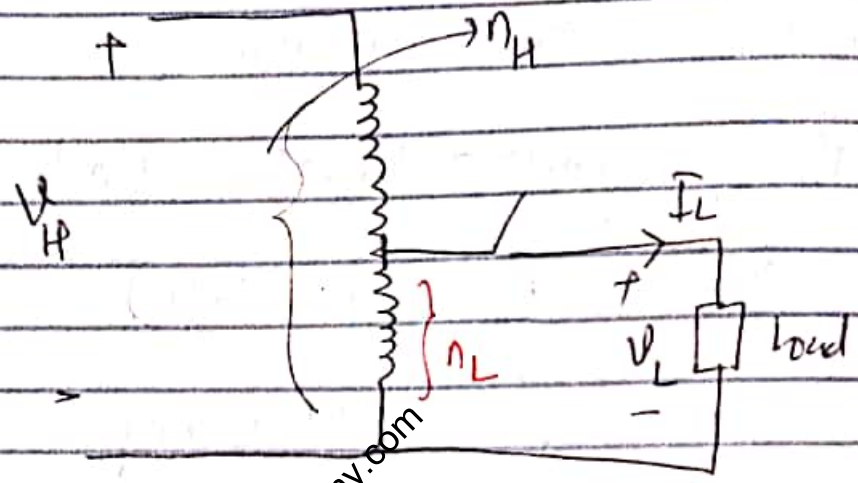
whereas in auto transformer both the windings are electrically connected.



We can also connect two ordinary X-forms into auto X-form. (There is a difference in a connected one and an independent auto X-form so don't confuse it).

Three Phase Transformer

Star Connection

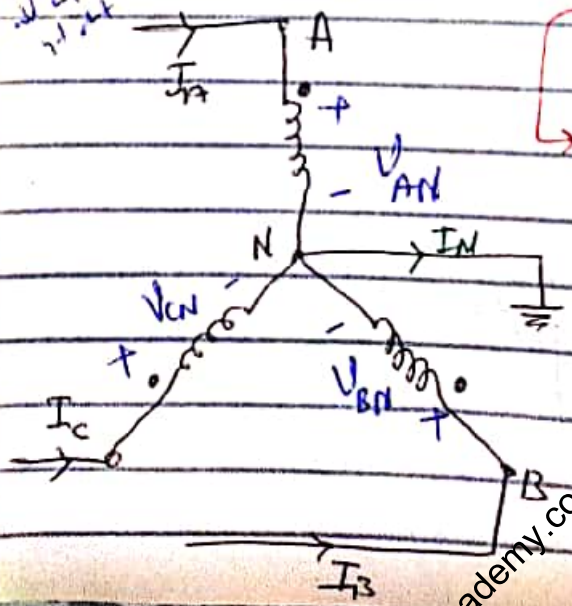

say phase sequence = ABC
and balanced 3 Φ system.

Phase voltage = Live to neutral
→ magnitude is same while 120° apart.

$$V_{AN} = V_p \angle 0^\circ = V_m \sin \omega t$$

$$V_{BN} = V_p \angle -120^\circ = V_m \sin(\omega t - 120^\circ)$$

$$V_{CN} = V_p \angle -240^\circ = V_p \angle 120^\circ = V_m \sin(\omega t - 240^\circ)$$

In star connection;

$$I_L = I_p$$

and for a balanced system

$$\bar{I}_A + \bar{I}_B + \bar{I}_C = 0$$

$$\Rightarrow \bar{I}_N = 0$$

For an unbalanced system the summation may or may not be zero.

Line voltages (Line to line voltage)

$$V_{AB} = V_A - V_B = V_m \sin \omega t - V_m \sin(\omega t - 120^\circ)$$

$$= V_m (\sin \omega t - \sin(\omega t - 120^\circ))$$


$$= 2 V_m \left[\cos \left(\frac{\omega t - 120^\circ}{2} \right) \times \sin \left(\frac{120^\circ}{2} \right) \right]$$

$$\sin A - \sin B = 2 \cos \left(\frac{A+B}{2} \right) \cdot \sin \left(\frac{A-B}{2} \right)$$

$$= 2 \times V_m \times \cos(\omega t - 60^\circ) \times \frac{\sqrt{3}}{2}$$

$$\bar{V}_{AB} = \sqrt{3} V_m \cos(\omega t - 60^\circ) = \sqrt{3} V_p \cos(\omega t - 60^\circ)$$


↳ Comparing with the reference:

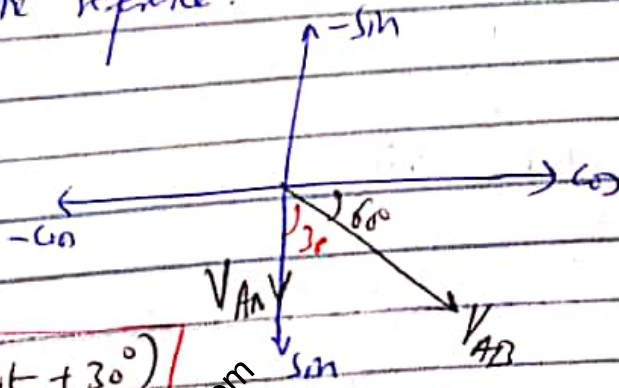

$$\bar{V}_{AB} = \sqrt{3} V_m \sin(\omega t + 30^\circ)$$

$$V_{BC} = \sqrt{3} V_{p,m} \sin(\omega t + 30 - 120^\circ)$$

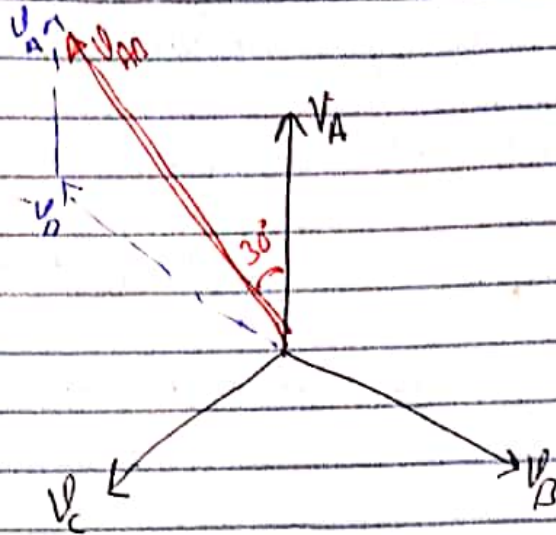
$$V_{CA} = \sqrt{3} V_p \sin(\omega t + 30^\circ + 120^\circ)$$



Line voltage will lead phase voltage by 30°

$$|V_{AB}| = \sqrt{3} V_p$$

Delta Connection

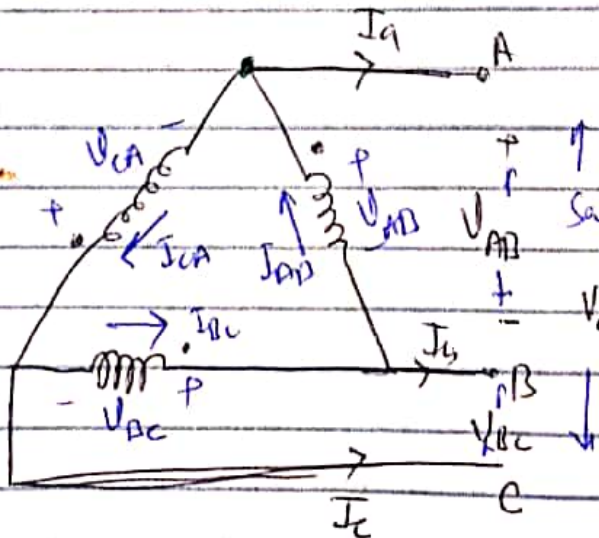

Assuming the delta connection
is a supply.
Current will leave at dot.

Say phase sequence = ABC
Balanced system
No neutral

Line voltages

($w_{il} = \text{phase}$)

$I_{AB}, I_{BC}, I_{CA} \rightarrow$ phase currents

$I_A, I_B, I_C \rightarrow$ line currents

In delta connection;

$$V_L = V_p$$

Phase current

$$I_{AB} = I_p \angle 0^\circ = I_m \sin \omega t$$

$$I_{BC} = I_p \angle -120^\circ = I_m \sin(\omega t - 120^\circ)$$

$$I_{CA} = I_p \angle +120^\circ = I_m \sin(\omega t + 120^\circ)$$

↳ my I_p is peak value or rms value ($I_{pm} = \frac{I_m}{\sqrt{2}}$)

Line current

$$KCL \Rightarrow I_A + I_{CA} = I_B$$

$$\Rightarrow I_A = I_B - I_{CA} = I_m \sin \omega t - I_m \sin(\omega t + 120^\circ)$$

$$\Rightarrow I_A = \sqrt{3} I_p \angle -30^\circ$$

↳ lag phase angle by 30°

$$I_B = \sqrt{3} I_p \angle -30^\circ$$

$$I_C = \sqrt{3} I_p \angle -30^\circ - 120^\circ$$

$$I_C = \sqrt{3} I_p \angle -30^\circ + 120^\circ$$

Power

$$\text{Instantaneous power} = 3 V_{p_m} I_{p_m} \cos \phi = P_{avg}$$

↳ don't use $\cos \phi$

$$P_{avg} = \sqrt{3} V_{Lm} I_{Lm} \cos \phi$$

$$\textcircled{a} = \sqrt{3} V_p I_p \cos \phi$$

Reactive power:

$$Q = \sqrt{3} V_{Lm} I_{Lm} \sin \phi$$

$$\textcircled{a} = \sqrt{3} V_p I_p \sin \phi$$

$$\text{VA}_{\text{max}} = \sqrt{3} V_{Lm} I_{Lm}$$

$$\text{Complex} = \sqrt{3} V_{Lm} I_{Lm}^*$$

Connections of 3 ϕ system

Group 1 \rightarrow 12° clock \rightarrow 0° \rightarrow Y_{12} or D_{12} \rightarrow

Group 2 \rightarrow 6° clock \rightarrow 180° \rightarrow Y_{12} or D_{12}

Group 3 \rightarrow 12° clock \rightarrow 30° lag \rightarrow Y_{12} or D_{12}

Group 4 \rightarrow 11° clock \rightarrow 30° lead \rightarrow Y_{12} or D_{12}

$\Delta-\Delta$ or $Y-Y \rightarrow$ even number

$\Delta-Y$ or $Y-\Delta \rightarrow$ odd number

\rightarrow The degrees are always checked for secondary or primary
 is the reference.

eg 0° represents that secondary is shifted 0° w.r.t primary
 180° " " " " " 180° " "

\rightarrow All the degrees are for line voltages.

→ For any group connection, the phase voltages in primary and secondary are always in phase.

$$a = \frac{V_{p1}}{V_{p2}} = \frac{I_{p2}}{I_{p1}}$$

→ turn ratio always in terms of line voltages.
 → In line voltage, it may or not be




→ capital letter = HV small letter = LV

→ How = LV, mmk = HV

→ Phase sequence ABC, abc



→ Y has neutral, Δ no neutral (mag mag)

→ All the terminals (i/p or o/p) will have a subscript 2.

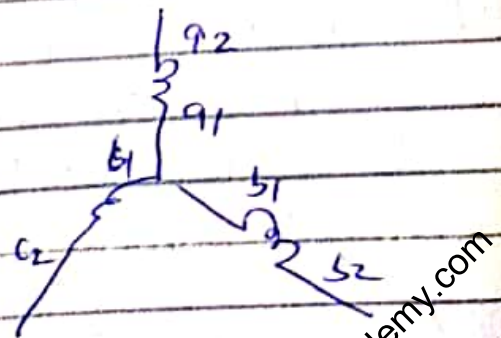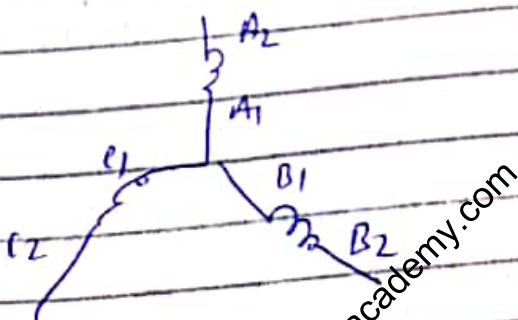
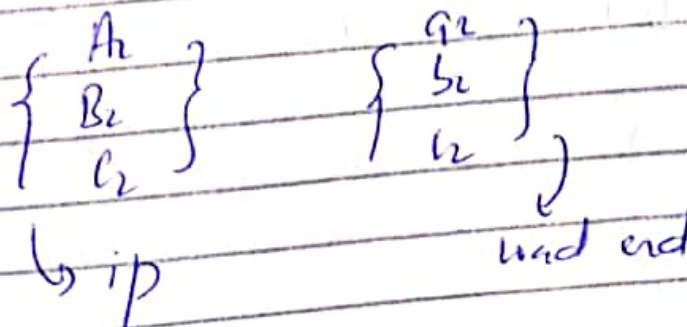


Group 1



① X_{y0}

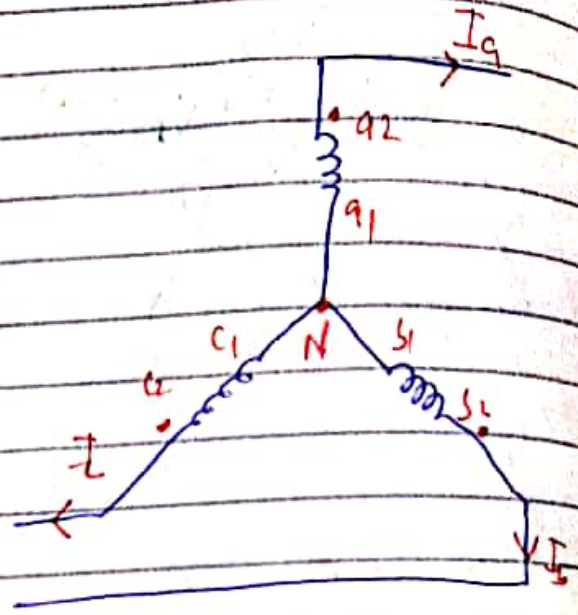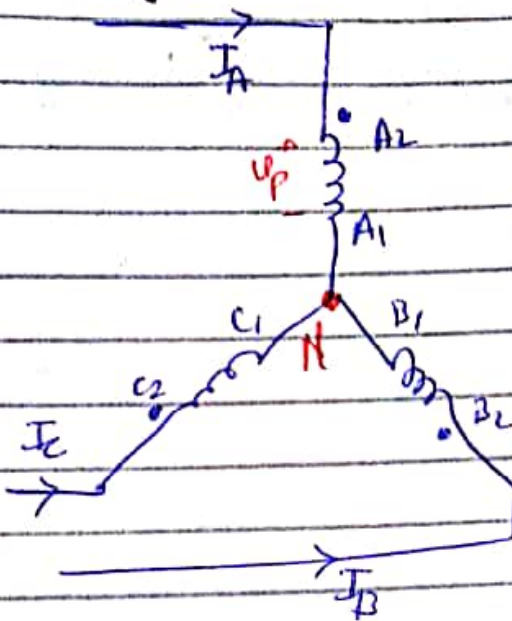

$$V_p = V_{A2} V_{A1}$$

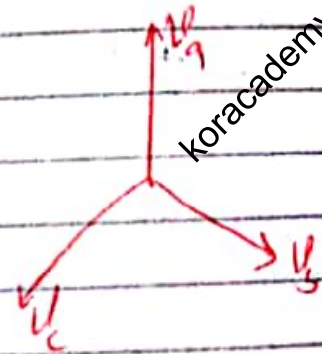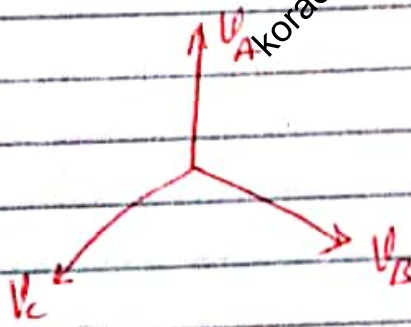



or by another method;

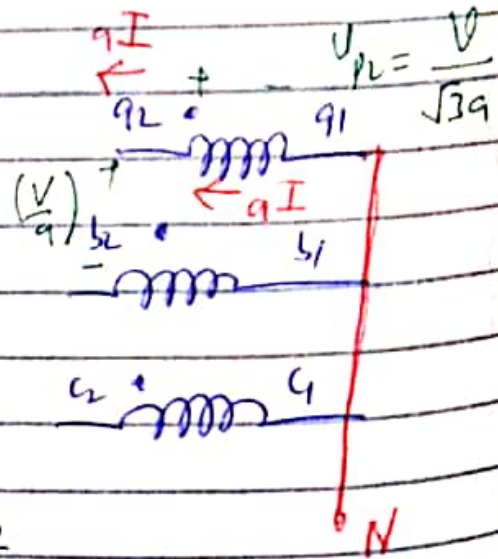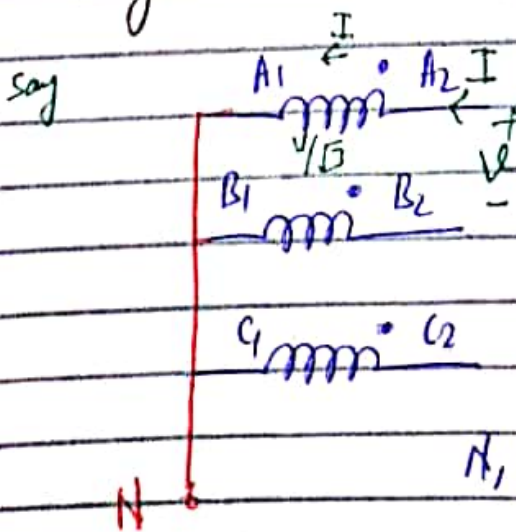


$$N_1 : N_2$$

$$a = \frac{V_p}{V_s} \Rightarrow \frac{V_p}{V_s} = \frac{a_1}{a_2}$$


② Ddo

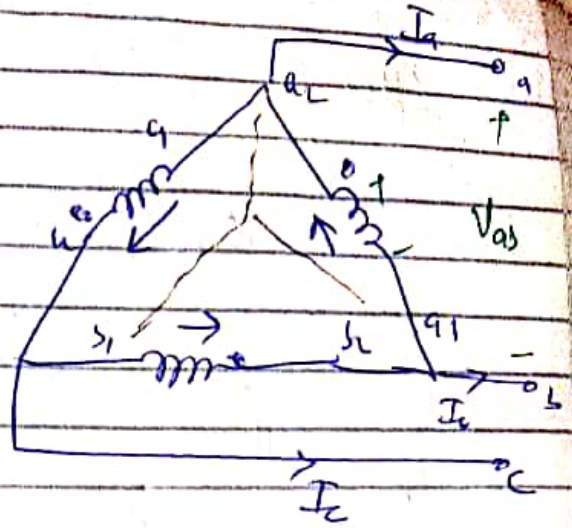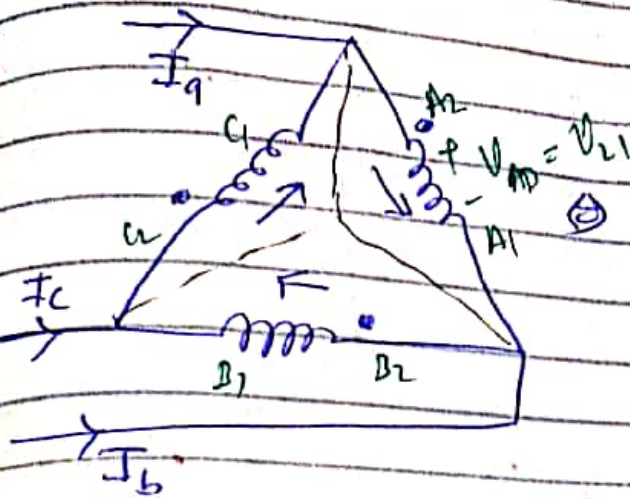
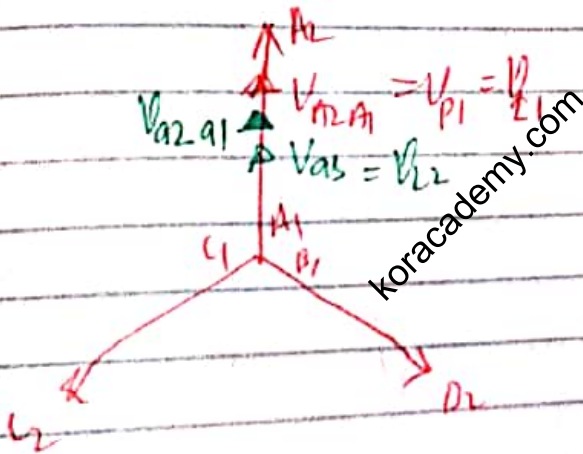
$$V_p = V_L = \frac{V_{A_2 A_1}}{A_2 A_1} = \frac{V_{A_1 B_1}}{A_1 B_1}$$



③

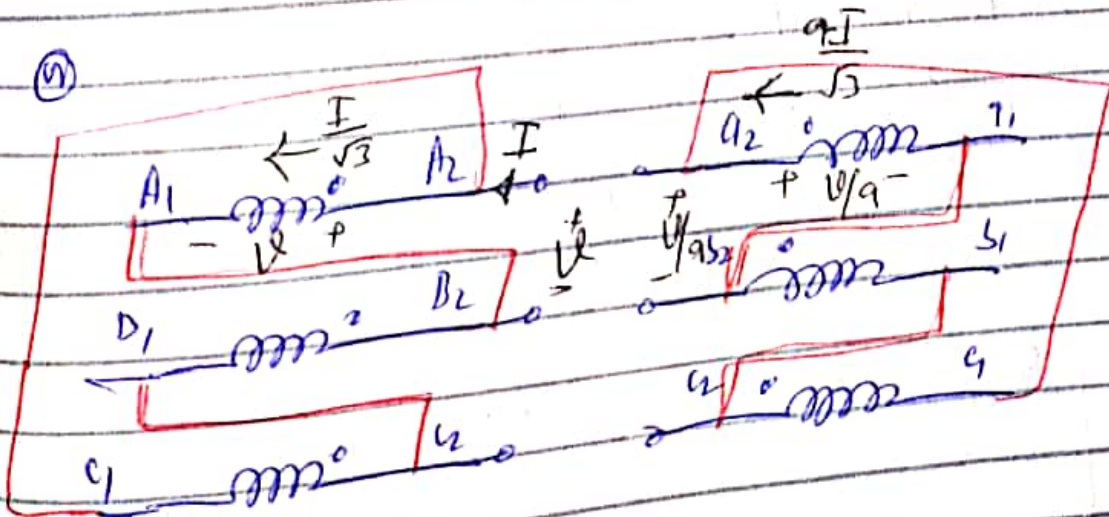

noted unneeded to detail



$$\frac{V_{p2}}{V_{p1}} = \frac{1}{9} \Rightarrow V_{p2} = \frac{1}{9} V_{p1}$$

$$I_{p1} = 9 I_{p2}$$

Power, $P = \sqrt{3} V I$
 $= 3 V_{ph} I_{ph} = 3 V \cdot \frac{I}{\sqrt{3}}$


Group 2 (180° connection). $\Delta \rightarrow Y$

① Yy6:

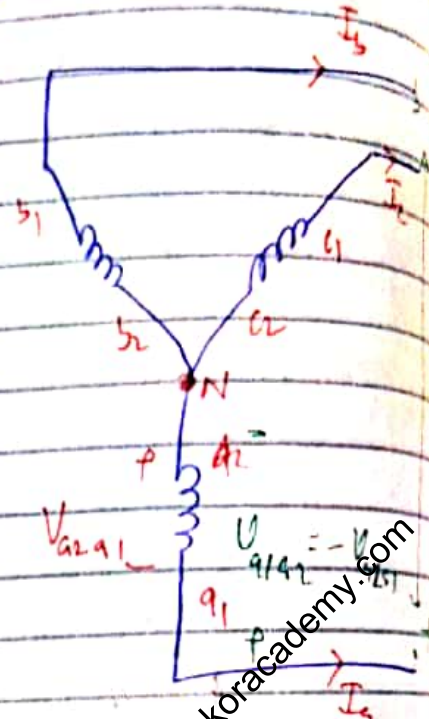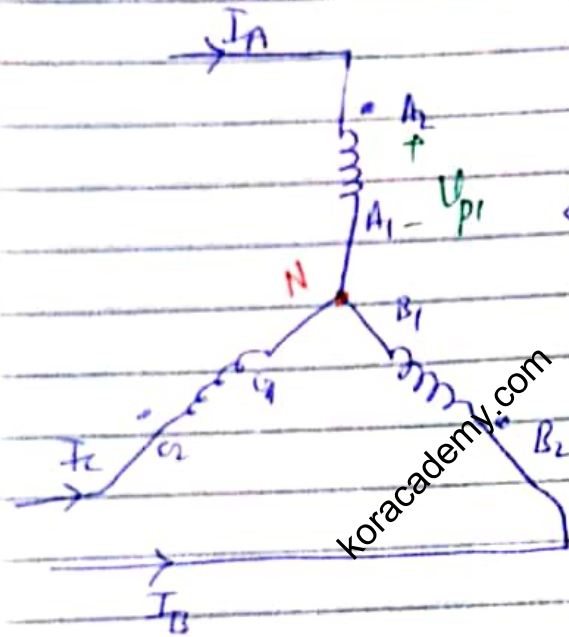


$V_{pL} = -V_{s2s1}$


$V_{p1} = V_{A2A1}$
 $V_{s1} = V_{a1a2}$

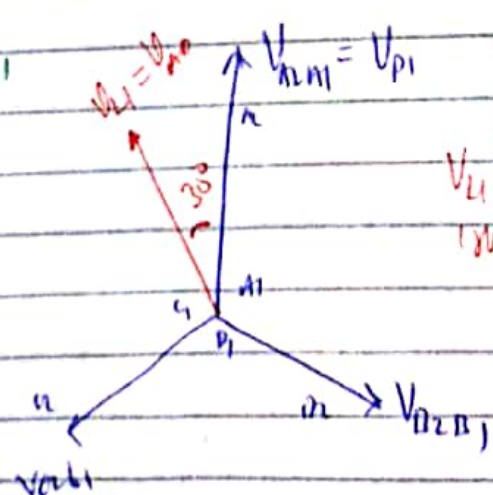


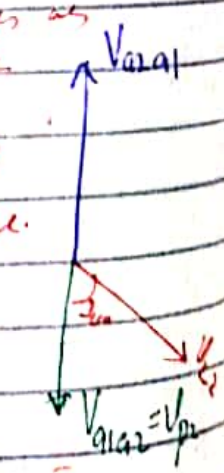
coil voltages are still same
 V_{L1} and V_{L2} are 180° out of phase.



②

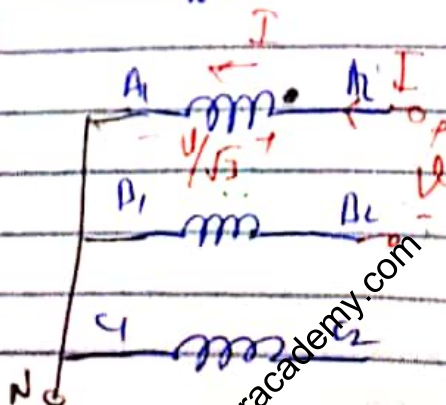


② Dd6

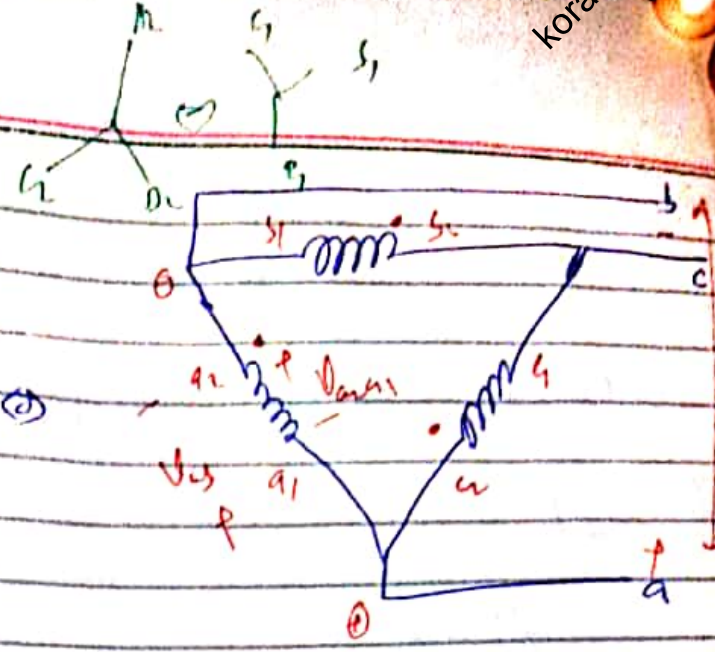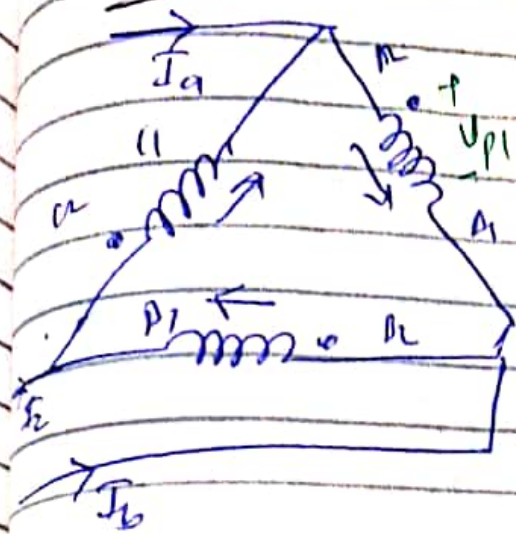


$$U_{pl} = U_{a2a1}$$

$$U_{a1a2} = U_{p2} = U_{b2} = U_{c2} = -U_{a1}$$

$$U_{AB} = U_{c1} = U_{a2a1}$$

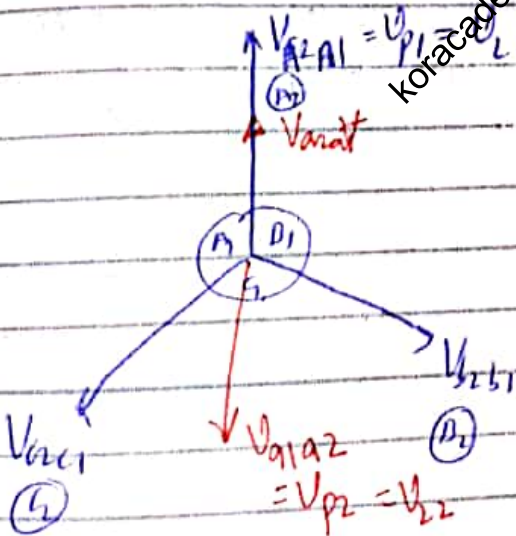




wil diagram

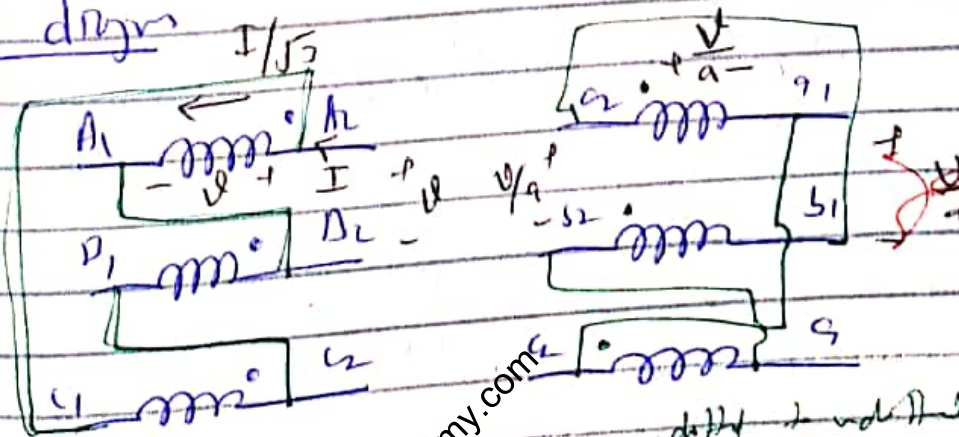


dotted + dotted.

Group 3

① Yd1

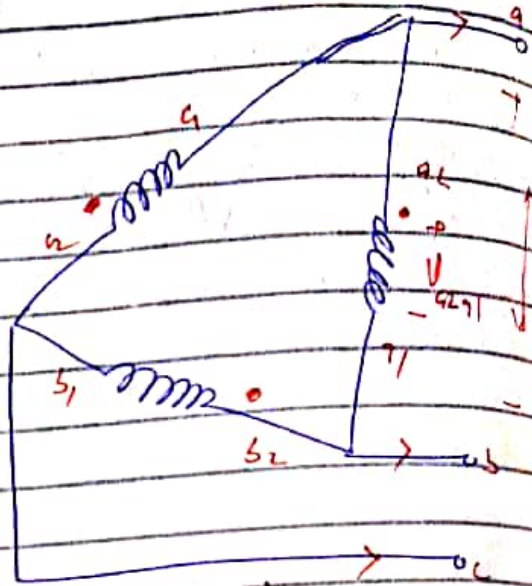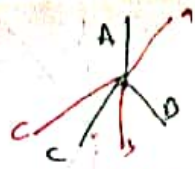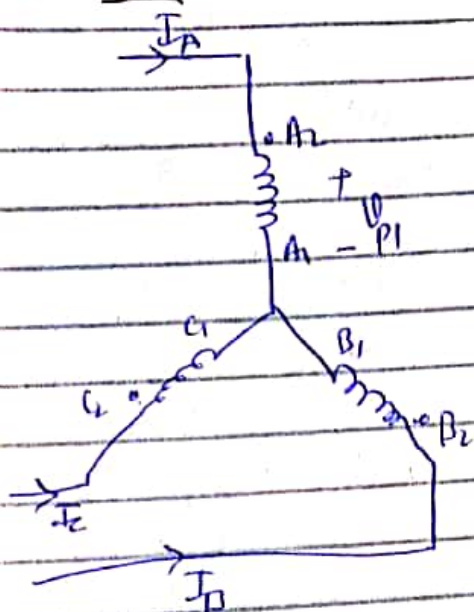


$V_{a0} = V_{b2} = V_{c1}$

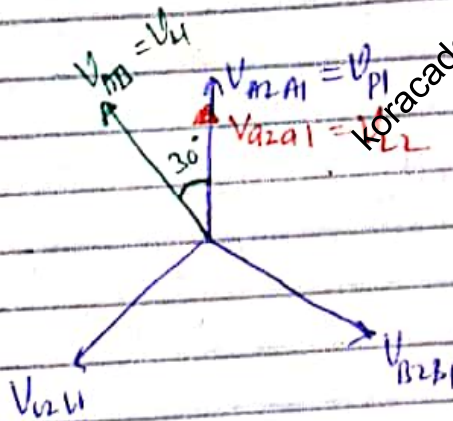

$V_{p1} = \frac{1}{\sqrt{3}} V_{p1}$



$I_{p1} = \sqrt{3} I_{p1}$

coil connection

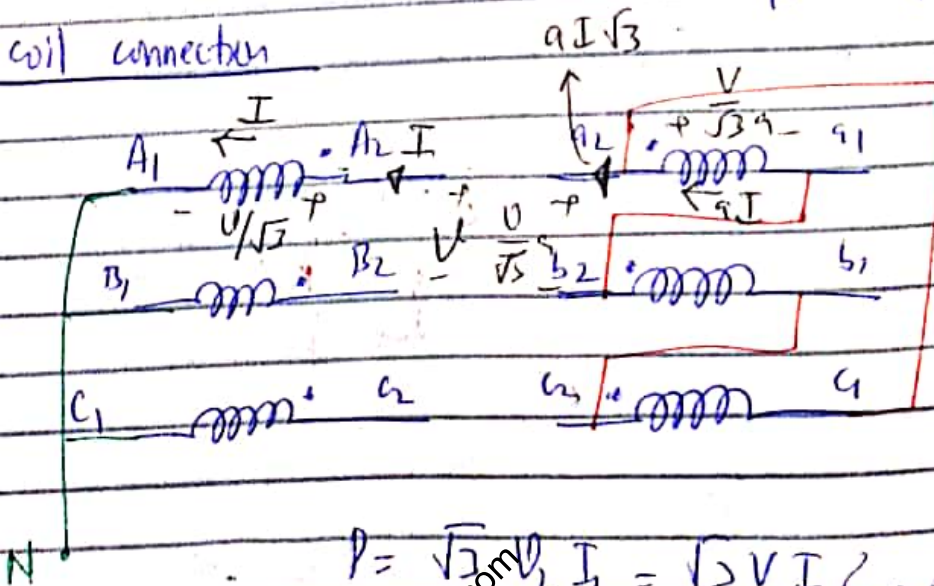



$P = \sqrt{3} V_L I_L = \sqrt{3} V I \rightarrow puig$

Q Dy 4

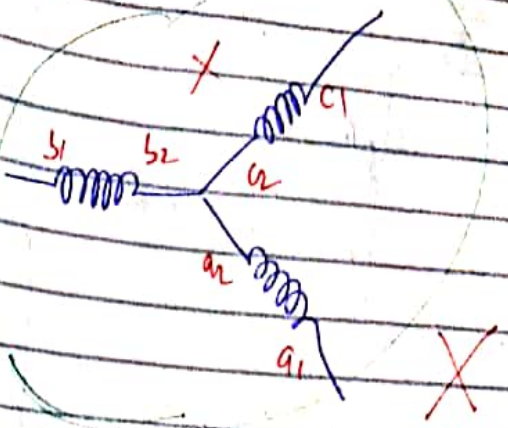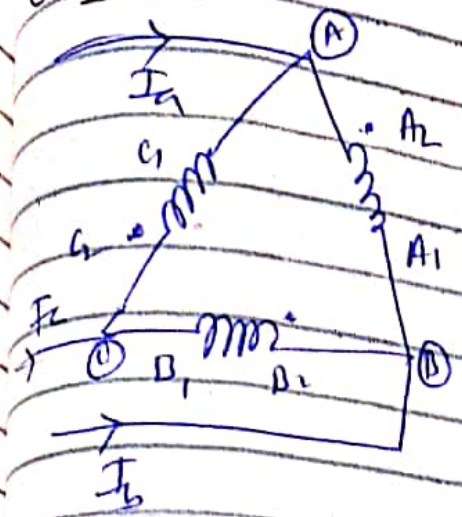


see the shift of (a)


So we do some manipulation method

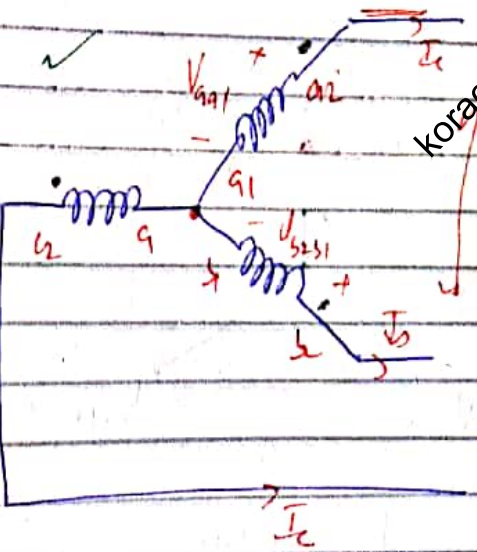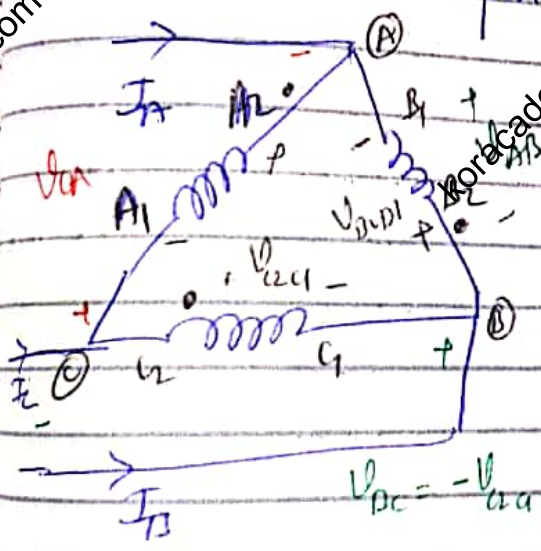

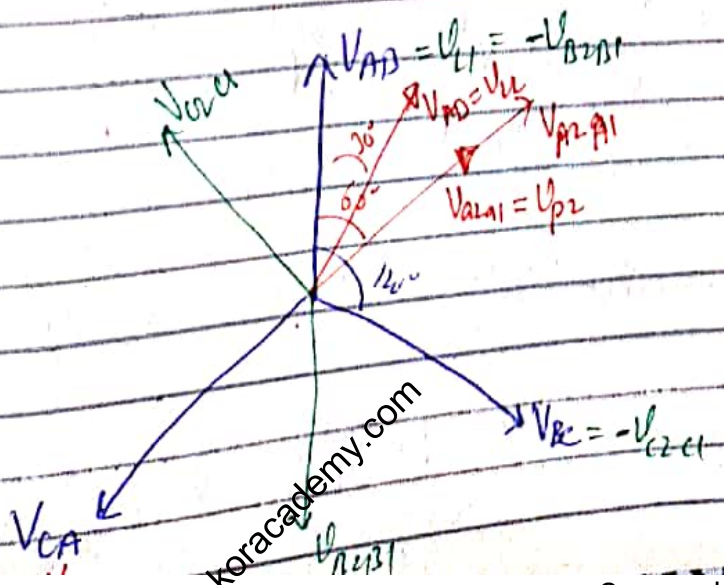
$$V_{PI} = V_{L1} = V_{AB} = V = -V_{BCA}$$




coil connection

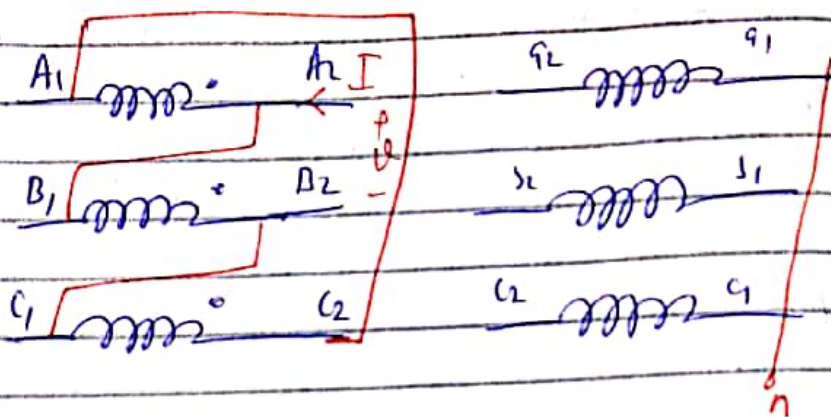

Group 4

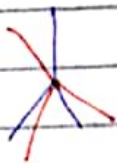


① Yd11

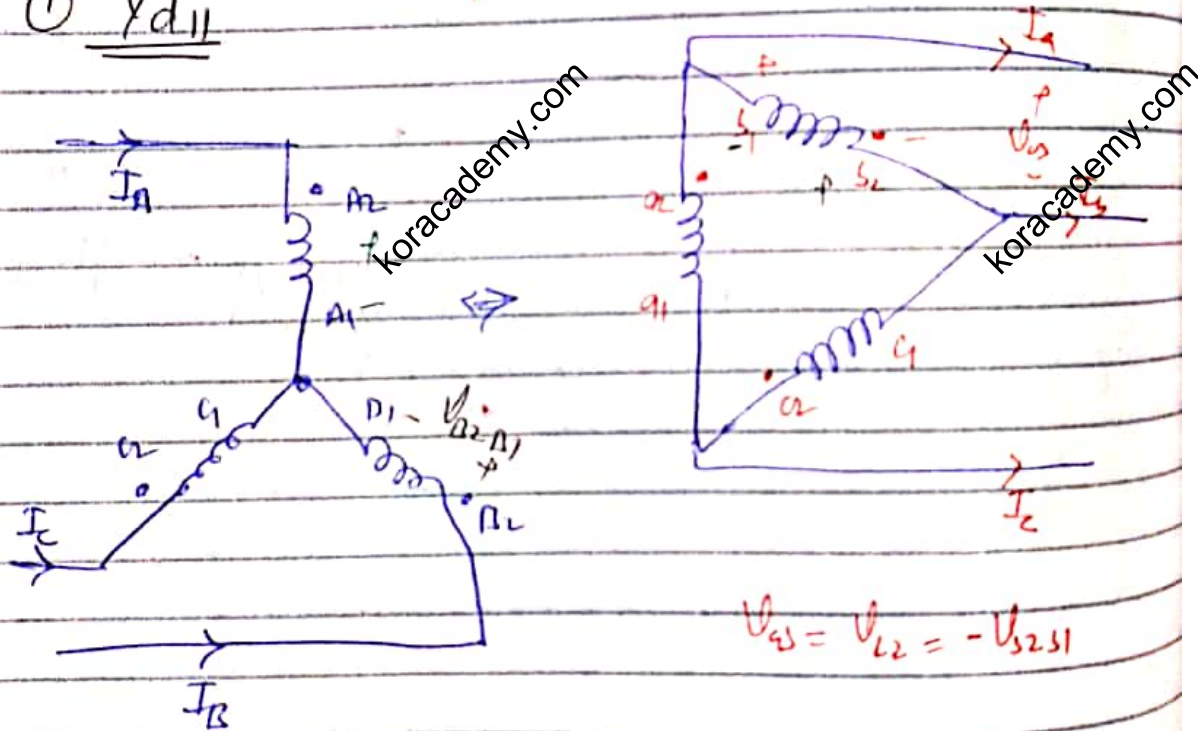


$U_{P1} = U_{AN} = U_{A2A1}$

U_{a2} leads U_{a1} by 30°

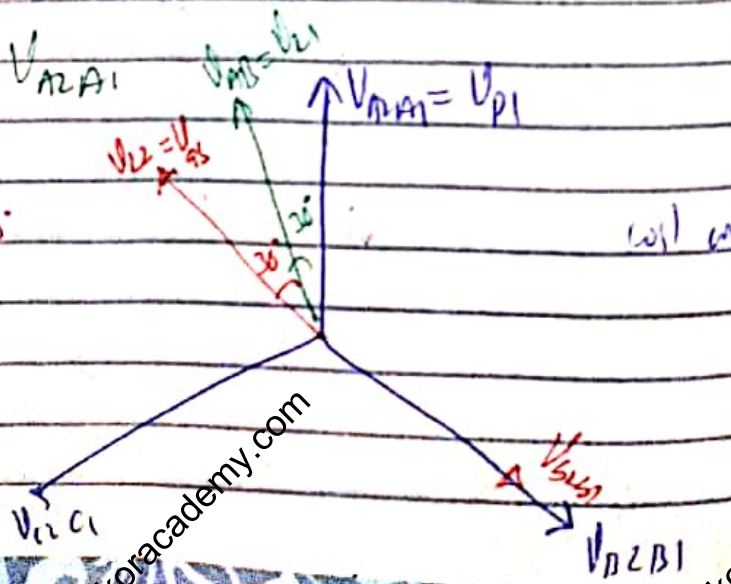



coil connection

② Dy 11

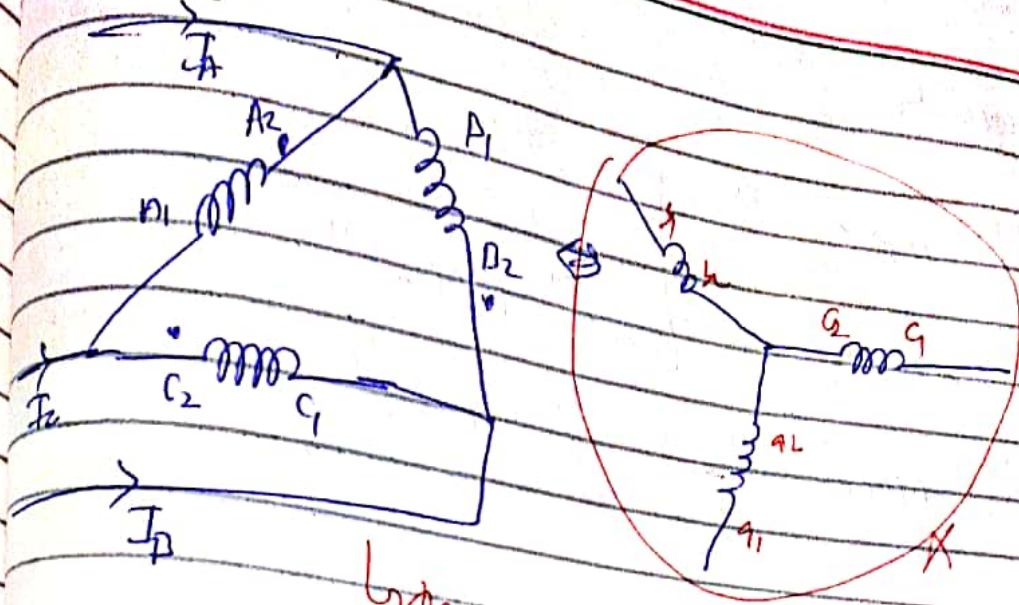


Winding connection in Dy 11

Dy 11

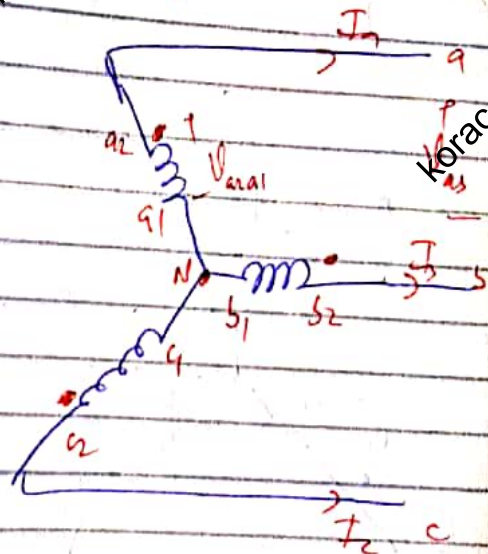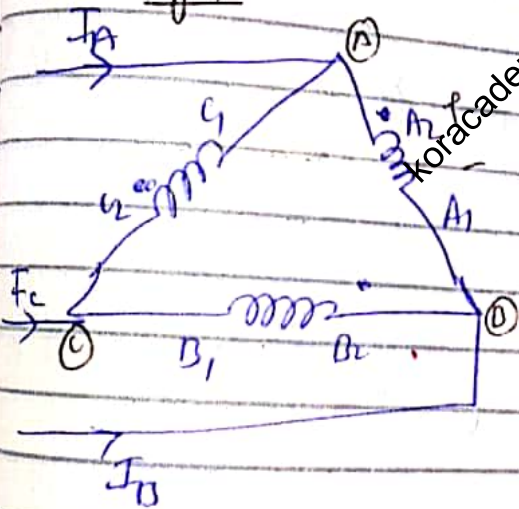

$$V_{P1} = V_{L1} = V_{A2A1} = V_{AB}$$

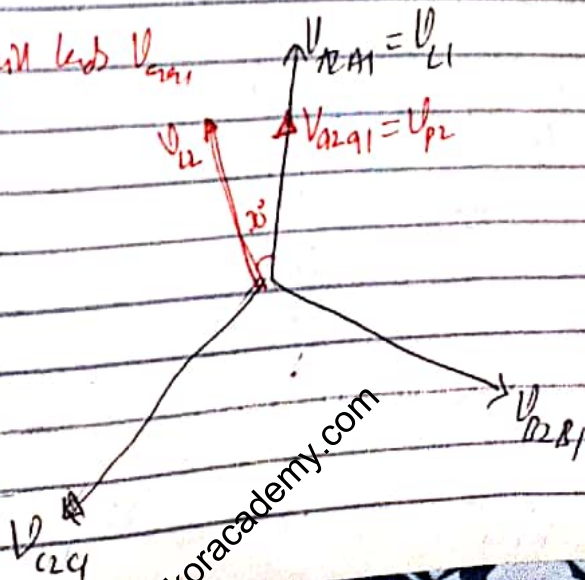
$V_{AB} = \frac{1}{2}$ with leads V_{aa1}
by 30°



coil connection

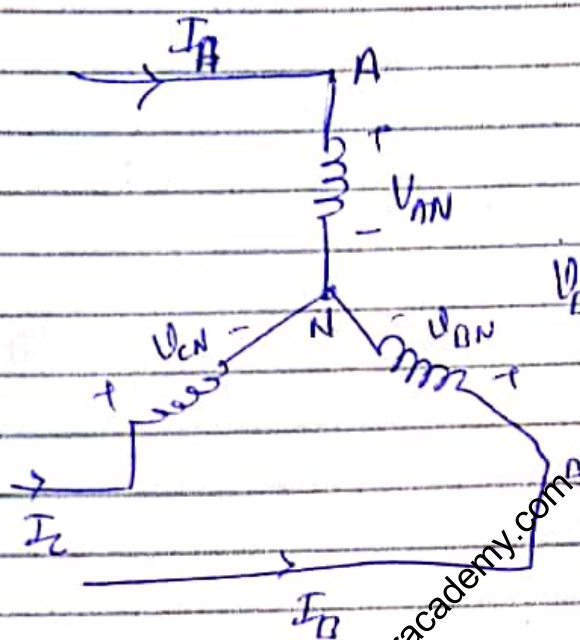Q1 The line A to neutral voltage is $10 \angle 15^\circ$ for a balanced 3 ϕ Y connected load with phase sequence ABC.

The voltage of line B wrt C will be _____?



$V_{BC} = ?$

$V_{AN} = 10 \angle 15^\circ = 10\sqrt{2} \sin(\omega t + 15^\circ)$

$V'_{AN} = 10 \angle 15^\circ - 120^\circ = 10\sqrt{2} \sin(\omega t + 15^\circ - 120^\circ)$

$V_{CN} = 10 \angle 15^\circ + 120^\circ = 10\sqrt{2} \sin(\omega t + 15^\circ + 120^\circ)$

$V_{BC} = V_{BN} - V_{CN} = 10\sqrt{2} \sin(\omega t - 105^\circ) - 10\sqrt{2} \sin(\omega t + 135^\circ)$

$= 10\sqrt{2} \left[2 \cos\left(\frac{\omega t - 105^\circ + \omega t + 135^\circ}{2}\right) \cdot \sin\left(\frac{-105^\circ - 135^\circ}{2}\right) \right]$


$\Rightarrow \bar{V}_{BC} = 20\sqrt{2} \cdot \sin(15^\circ) \cos(\omega t + 15^\circ)$

$\Rightarrow \bar{V}_{BC} = -24.49 \cos(\omega t + 15^\circ)$ Ans.

$\Rightarrow V_{BC} = 24.49 \sin(\omega t - 75^\circ)$

$= 24.49 \angle -75^\circ$

$\sqrt{2}$

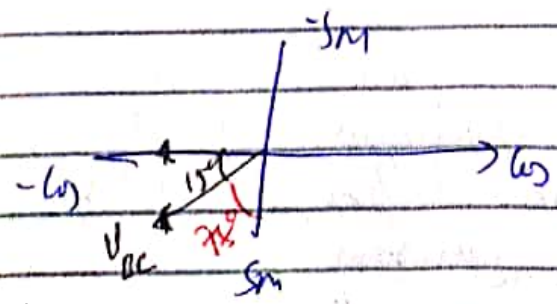

$\Rightarrow V_{BC} = 17.32 \angle -75^\circ$

Ans


method 2

$V_{AN} = 10 \angle 15^\circ$

$= 10 \sqrt{2} \sin(\omega t + 15^\circ)$

In star connection;


V_{AB} will lead V_{AN} by 30° .

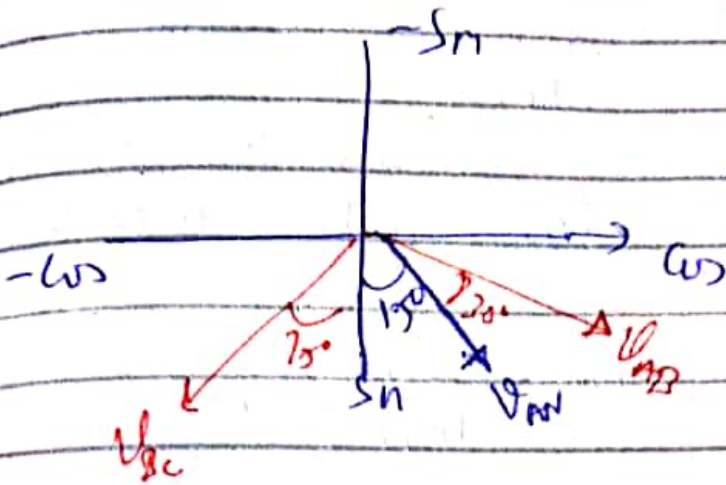

$|V_{AB}| = \sqrt{3} V_{p_{ms}}$

$= 10 \sqrt{3}$

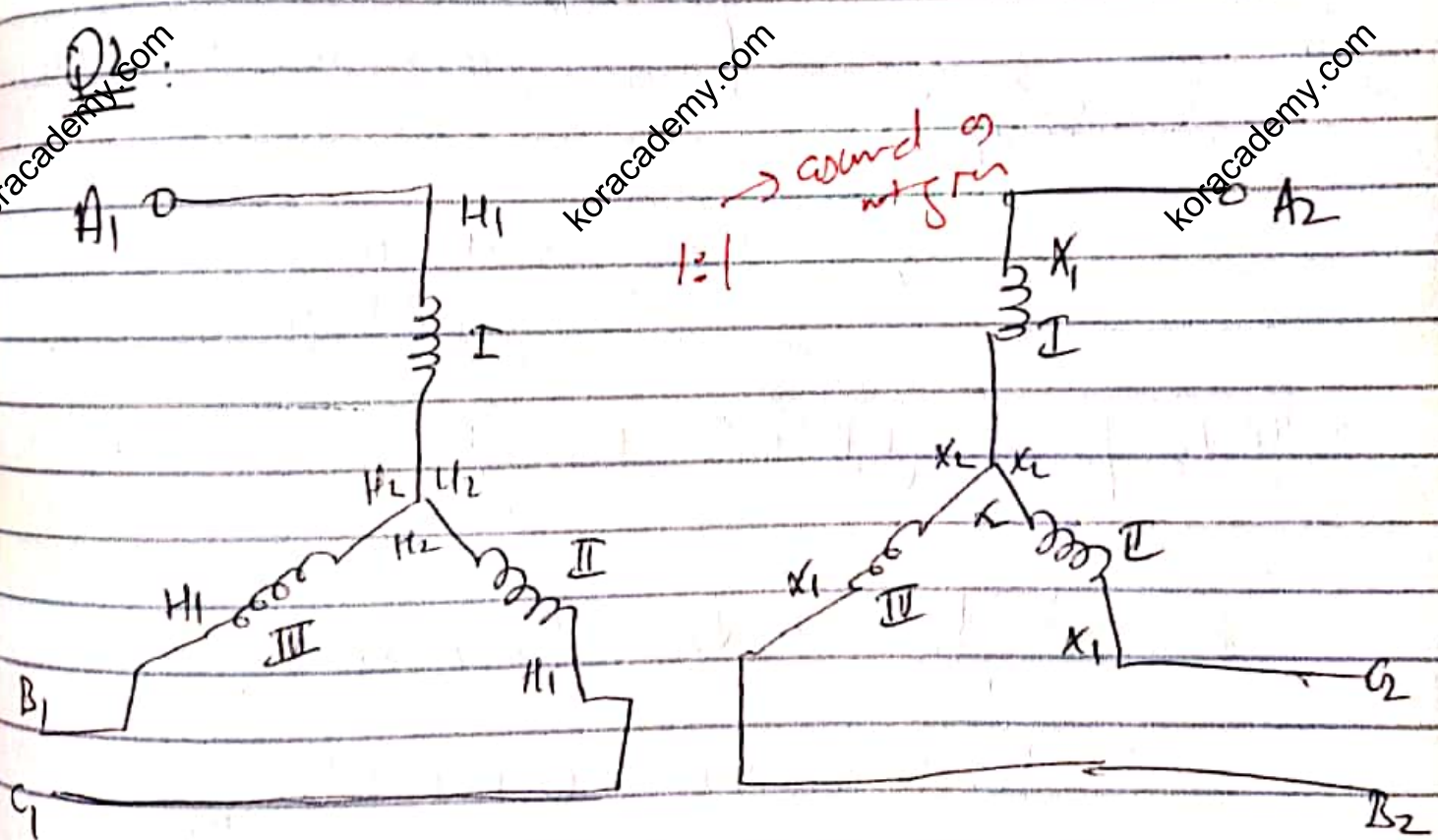$\Rightarrow V_{BC} = 10 \sqrt{3} \angle -75^\circ$
Ans



If the terminals H_1 and H_2 of phase I of the primary is shorted without changing the supply terminals A_1, B_1, C_1 , then phase angle of line voltage $V_{B_2 C_2}$ in secondary is 60° w.r.t $A_2 B_2$ (or $A_1 B_1$)

$$V_{A1N} = V_p \angle 0^\circ = V_{A2N}$$

$$V_{B1N} = V_p \angle -120^\circ = V_{C2N}$$

$$V_{C1N} = V_p \angle 120^\circ = V_{B2N}$$

Now if terminals are reversed:

$$V_{A1N} = -V_p \angle 0^\circ = V_{A2N}$$

$$V_{C1N} = V_p \angle -120^\circ = V_{C2N}$$

$$V_{B1N} = V_p \angle 120^\circ = V_{B2N}$$

$$\Rightarrow V_{A2B2} = V_{A2N} - V_{B2N} = -V_p \angle 0^\circ - V_p \angle 120^\circ$$

$$\Rightarrow V_{A2B2} = V_p \angle -120^\circ$$

$$V_{C2A2} = V_{C2N} - V_{A2N} = V_p \angle -120^\circ - (-V_p \angle 0^\circ)$$

$$\Rightarrow V_{C2A2} = V_p \angle -60^\circ$$

Q3. An 120 KVA, 6000/400 V, Y-Y 3 ϕ , 50 Hz transformer has max loss of 1600 W. The Xformer's maximum efficiency occurs at 3/4 full load. Find the efficiency at full load unity power factor.

$$P_i = 1600 \text{ W}, \quad \eta_{\text{max}} = \frac{3}{4}$$

$$\eta_n = \frac{\eta \text{ VA } \cos \phi}{\eta \text{ VA } \cos \phi + P_i + \eta^2 P_{cu}} \quad \text{--- ①}$$

As $P_i = P_{in} = \frac{P_{out}}{\eta}$

$$\eta = \sqrt{\frac{P_i}{P_{in}}}$$


$$\Rightarrow P_{in} = \frac{P_i}{\eta} = \left(\frac{1600 \times 16}{0.9} \right)$$

Ans

$$P_{in} = 2844.4 \text{ W}$$

① $\Rightarrow \eta = 95.57\%$ Ans

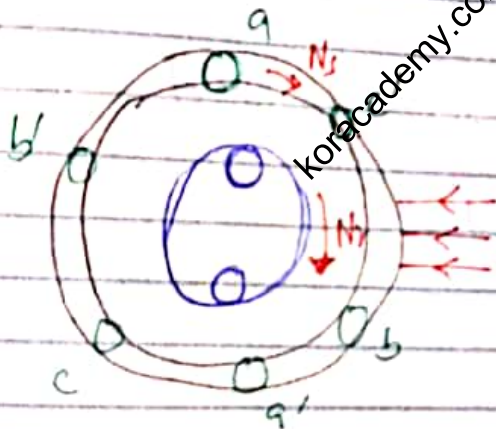Operating Principle of 3 ϕ Induction motor



- stator

- rotor

- 3 ϕ conductors

If this is motor
we have a 3 ϕ supply to
the stator with f_s .

Stator windings are 120°
displaced electrically.

(i) 3 ϕ supply \rightarrow 3 ϕ stator winding \rightarrow rotating magnetic field (stator RMF) rotating with a speed corresponding to stator supply frequency.
$$N_s = \frac{120 f_s}{P}$$
 (say in clockwise direction. \rightarrow)

(ii) Stator winding is stationary and having a RMF (at N_s speed) around it.
Hence there will be a relative motion b/w stator conductor and stator RMF.

Speed of stator RMF wrt stator body = $N_s \cdot 0 = N_s$
and induced emf \propto Relative speed.

Hence there will be an induced emf in the stator conductor (winding).

$$E_{ph(stator)} = E_{ph1} = 4.44 f_s \cdot \phi \cdot T_{ph1} K_{w1}$$

at supply frequency.

[T_{ph} \rightarrow no. of turns per phase.
 K_{w1} is a factor that represents that stator winding is a distributed winding.]

(iii) At starting or at stand still condition, the rotor is stationary. Hence the rotor requires torque as it is not yet present. $N_r = 0$.
Hence the rotor winding will also experience the cutting of stator RMF field. (b/c the field developed in the stator is present in the air gap) and the rotor conductor will feel it as the stator winding does.

Speed of stator RMF wrt rotor at standstill condition
 $= N_s - 0 = N_s$

Hence induced emf \propto relative speed.

$$E_{ph rotor} = E_{ph2} = 4.44 f_s \cdot \phi \cdot T_{ph2} \cdot K_{w2}$$

\rightarrow its frequency $f_r = f_s$

b/c w.r. speed = N_s

$f_r \rightarrow$ rotor frequency in rotor voltage in rotor conductor. (iii) frequency of induced

(iv) Due to this induced emf at standstill condition, there will be a rotor current as rotor circuit is a closed circuit (assumed)

$$I_{r(\text{standstill})} = \frac{E_{ph2}}{Z_r} \text{ amp.}$$

\rightarrow AC current

(current in a conductor \Rightarrow flux)

(v) Here when current will flow, the rotor conductor will also produce MMF in such a direction that it opposes its cause. and this mmf will interact with the stator MMF in the air gap and produce torque on rotor body. (Electromagnetic torque or interaction torque).

Effect	Cause
Torque production	$\downarrow I_r \rightarrow \downarrow E_{ph2} \rightarrow$ Due to relative motion $= N_s - 0$ (to reduce relative speed) $N_s - N_r \leftarrow$ \hookrightarrow clockwise

(vi) Now rotor will start rotation in clockwise direction to oppose its cause (Lenz law) and try to catch up the stator RMF speed (N_s)

Hence 3 ϕ induction motor is a self starting machine.

(vii) Now under running condition

Stator conductor — speed = 0

Stator RMF $\rightarrow N_s$

Rotor $\rightarrow N_r$

a. Speed of stator RMF wrt stator = N_s

b. Speed of stator RMF wrt rotor = $N_s - N_r$

Hence induced emf in rotor conductor,

$$e \propto \text{relative speed} \Rightarrow e \propto N_s - N_r$$

$$E_{\text{ph2}} = 4.44 f_r \cdot \phi \cdot T_{\text{ph2}} \cdot K_{w2}$$

Here will define a term slip (s) = $\frac{N_s - N_r}{N_s}$

(N_s will always be greater than N_r , b/c if they become equal \Rightarrow relative speed = 0 \Rightarrow induced voltage = 0 \Rightarrow torque = 0 \Rightarrow machine will not operate).

$$\Rightarrow N_s - N_r = s N_s$$

And frequency (f) \propto relative speed.

\Rightarrow At standstill condition; $f_r = f_s = \frac{p N_s}{120}$

At running condition; $f_r = \frac{p (N_s - N_r)}{120} = \frac{p s N_s}{120}$

$$\Rightarrow f_r = s f_s$$

$$E_{phz} = 4.44 s f_s \phi T_{phz} K_{w2} = s E_{phz} \text{ standstill}$$


As $0 < s < 1 \Rightarrow E_{phz} < E_{phz} \text{ standstill} \Rightarrow f_r < f_s$

\Rightarrow Maximum emf will be induced in rotor when $N_r = 0$.

At standstill condition; $N_r = 0 \Rightarrow \text{slip} = 1$

(viii). Under running condition, now induced voltage has been reduced and current will also reduce, but still rotor conductors have current hence there will be a rotor rotating magnetic field (RRMF).

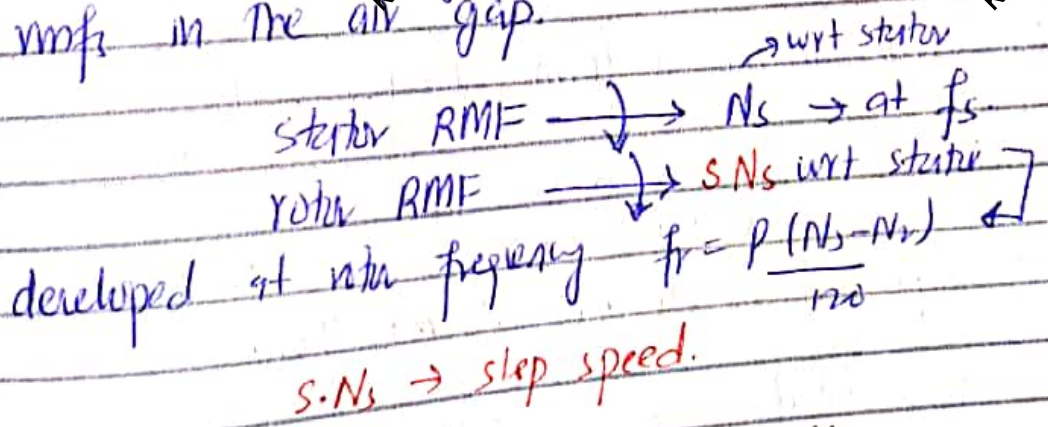Hence under running condition, there will be no mmf in the air gap.





\rightarrow Speed of stator mmf wrt stator = N_s
 \rightarrow Speed of rotor mmf wrt rotor = $s N_s = N_s - N_r$


\rightarrow Speed of rotor RMF wrt stator = $N_r + s N_s = N_s$
 \rightarrow Speed of rotor RMF wrt stator mmf = $N_s - N_s = 0$

\rightarrow Hence we will get a steady state torque and motor will maintain its rotation at N_r always. ($N_r < N_s$).

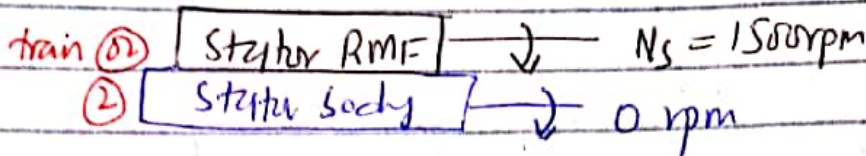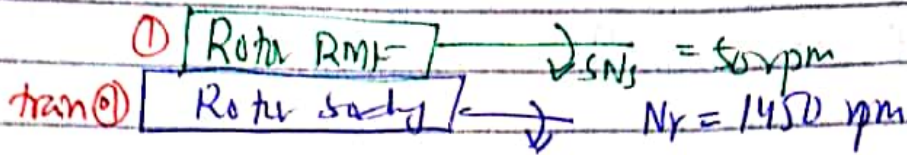Hence for any rotor speed, we will get steady state torque in 3 ϕ induction motor.



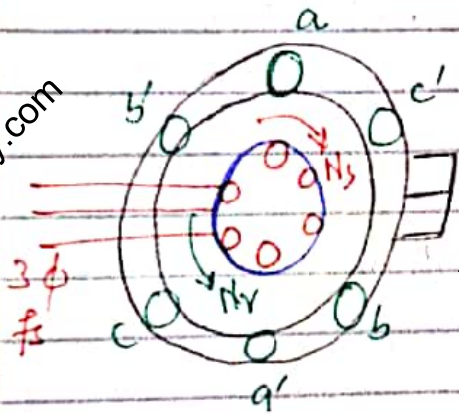Inverted Induction machine (Rotor Fed 3 ϕ I.M)



3 ϕ supply is given to rotor and stator winding is short circuited.

① Initially rotor is at rest condition and giving 3 ϕ supply to 3 ϕ rotor winding at supply freq.

3 ϕ supply \rightarrow 3 ϕ (rotor winding) \rightarrow rotor rotating magnetic field (RRMF) and rotating at supply frequency (f_s).

$$f_s = \frac{PN_s}{120} \rightarrow N_c$$



Rotary conductor will experience a rate of change of flux in the air gap and hence there will be induced emf in the rotary conductor.

$$e \propto \text{relative speed} \propto N_s - 0 \propto N_s$$

↳ corresponding to f_s ←

$$\Rightarrow E_{ph \text{ rotor}} = 4.44 f_s \cdot \phi \cdot T_{ph \text{ rotor}} \cdot K_w \text{ rotor}$$

→ Air gap field → main field flux → here RRMF

(ii) The stator conductor will also experience a change in flux and will also induce emf in stator conductor.

$$e \propto \text{relative speed} \propto N_s$$

↳ corresponding to f_s .



$$E_{ph \text{ stator}} = 4.44 f_s \cdot \phi \cdot T_{ph \text{ stator}} \cdot K_w \text{ stator}$$

(iii) Under this At standstill condition, the induced emf in stator conductor will drive a current as stator winding have a closed path through short circuit, hence will create its own MMF in such a direction that it opposes its cause.

Effect	Cause
emf \rightarrow I \rightarrow stator magnetic field (stator) RMF	Relative motion b/w stator and rotor and RRMF.

(Lenz's law) \Rightarrow Effect will oppose its cause
will try to reduce the relative speed b/w
stator and rotor and RRMF.

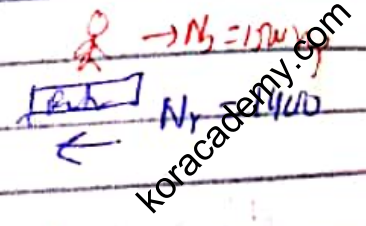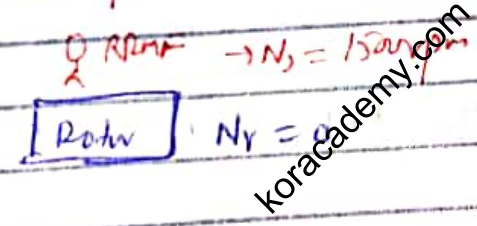\Rightarrow But the stator cannot rotate, so the result will
be that rotor will move in the opposite direction
with speed N_r .



stator rpm.

stator
(clockwise)

Now the speed of rotor RMF w.r.t stator will be
 $N_s - N_r = s N_s$

Hence induced emf $(e) \propto N_s - N_r$

$$\Rightarrow E_{\text{ph stator new}} = 4.44 f_r \phi T_{\text{ph stator}} K_w \text{ stator}$$

where $f_r = \text{rotor frequency} = \frac{P(N_s - N_r)}{120}$

$$\frac{s f_s}{s}$$

(iv) Now the stator RMF will be generated
for hence stator RMF will rotate at a
 $N_s - N_r = sN_s = \text{slip speed}$ speed in the
same direction of RRMF.

→ Speed of rotor RMF wrt stator = $N_s - N_r = sN_s$

→ Speed of rotor wrt stator = N_r

→ Rotor RMF wrt rotor = N_s
= rotor RMF wrt stator + rotor speed wrt stator
 $(N_s - N_r) + N_r = N_s$

→ Speed of stator RMF wrt stator = $N_s - N_r = sN_s$
in the same direction as RRMF.

→ Relative speed b/w rotor RMF and stator RMF
= 0

Hence will produce steady state torque.

$$s = \frac{N_s - N_r}{N_s} \Rightarrow N_r = (1-s)N_s$$

$$\Rightarrow \omega_r = (1-s)\omega_s$$

$$\omega = \frac{2\pi N}{60} \quad \text{and} \quad N_s = \frac{120f}{P}$$

i. Rotor frequency; $f_r = s f_s$
frequency of rotor induced emf under running ^{condition.}

→ not the frequency of rotation of rotor
At standstill, $s = 1 \Rightarrow f_r = f_s$

ii. $E_{2r} = s E_2$ induced emf in rotor.

when rotor is not rotating i.e. $s = 1 \Rightarrow E_{2r} = E_2$

iii. Resistance of rotor winding; $R_{2r} = R_2$
Reactance " " ; $X_{2r} = s X_2$


$$\text{Now } Z_{2r} = R_{2r} + j X_{2r}$$

$$|Z_{2r}| = \sqrt{(R_{2r})^2 + (X_{2r})^2} = \sqrt{R_2^2 + (s X_2)^2}$$

at standstill;

$$|Z_2| = \sqrt{R_2^2 + X_2^2}$$


iv. P.f. $\cos \phi = \frac{R}{Z}$

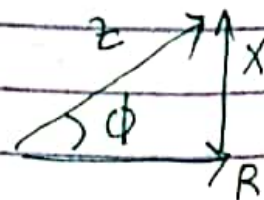


$$\Rightarrow \cos \phi_2 = \frac{R_2}{Z_2}$$

$$\Rightarrow \cos \phi_{2r} = \frac{R_2}{Z_{2r}}$$

→ Rotor equivalent circuit.

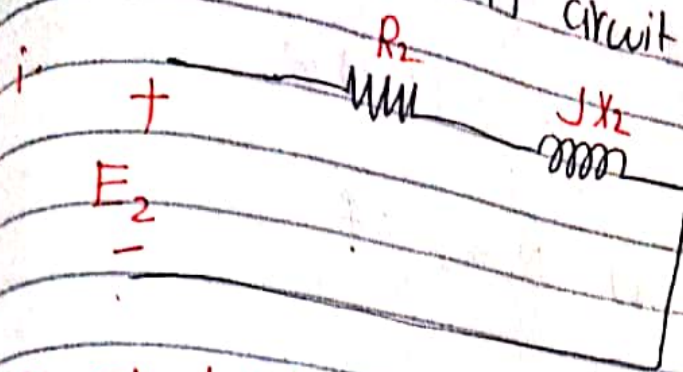

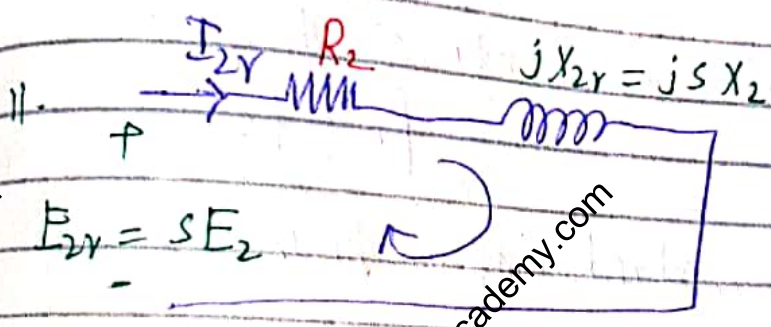At standstill and supply frequency
 $[f_r = f_s]$




At running condition $[f_r = s f_s]$

KVL $\Rightarrow sE_2 = \bar{I}_{2r} R_2 + j \bar{I}_{2r} s X_2$

divide by s

$\Rightarrow \bar{E}_2 = \bar{I}_{2r} \frac{R_2}{s} + j \bar{I}_{2r} X_2$

→ the equivalent circuit:

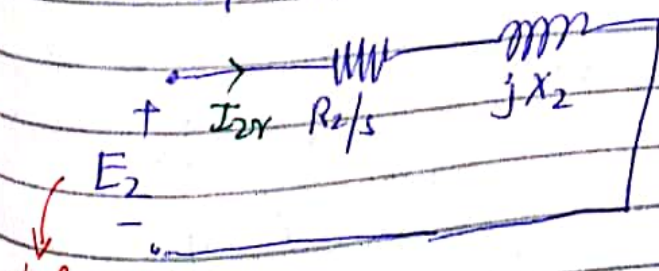

Both circuits are representing the same equivalent circuit under running condition.

at $f_r = f_s$
 But the voltage sources are different which means that the frequency are different.

Power flow equation

$$\text{Rotor i/p Power} = P_g = E_2 I_{2r} \cos \phi$$

$$\text{or } P_g = I_{2r}^2 \frac{R_2}{s} \quad \text{as that is a wattage value.}$$

$$\text{for } 3\phi; P_g = 3 I_{2r}^2 \frac{R_2}{s}$$

$$I_{2r} = \frac{E_2}{\sqrt{\left(\frac{R_2}{s}\right)^2 + (X_2)^2}}$$

$$P_g = 3 \left(\frac{E_2^2}{\left(\frac{R_2}{s}\right)^2 + (X_2)^2} \right) \cdot \frac{R_2}{s}$$

$$= 3 I_{2r}^2 \times \left(R_2 + R_2 \left(\frac{1-s}{s} \right) \right)$$

$$= 3 I_{2r}^2 R_2 + 3 I_{2r}^2 R_2 \left(\frac{1-s}{s} \right)$$

↓
rotor winding loss (P_c)

↓
developed power in rotor (P_d)

$$P_g = P_c + P_d$$

$$P_g : P_c : P_d = 1 : s : 1-s$$

P_m electrical - (stator winding losses + core losses)

$$= P_g \text{ (rotor i/p power or air gap power)}$$

$$P_g = P_c - P_d$$

$$P_d = P_g + P_c$$

→ wattage

$$P_{out} = P_d - \text{rotational losses.}$$

Torque relations

$$T_{Load} = T_{shaft} = T_{out} = \frac{P_{out}}{\omega_r} = \frac{P_d - \text{rot } L_{00}}{\omega_r}$$

$$T_d = \text{developed torque} = \frac{P_d}{\omega_r} = \frac{(1-s)P_g}{(1-s)\omega_s} = \frac{P_g}{\omega_s}$$

if speed is same, we need to divide by ω_r

$$T_d = \frac{P_g}{\omega_s} = \frac{3}{\omega_s} \times I_m^2 \times \frac{R_2}{s} = \frac{3}{\omega_s} \cdot \frac{E_2^2}{\left(\frac{R_2}{s}\right)^2 + X_2^2} \cdot \frac{R_2}{s}$$

At maximum torque;

$$s = R_2 / X_2$$

$$s \propto R_2 \propto \frac{1}{X_2} \propto \frac{1}{f}$$

$$T_{d,max} = \frac{3}{2\omega_s} \cdot \frac{E_2^2}{X_2}$$

does not depend on rotor resistance

Full load torque; $s = s_{fl}$


$$\frac{T_{fl}}{T_{max}} = \frac{2 s_m s_{fl}}{s_f^2 + s_{fl}^2}$$

$$\Rightarrow \frac{T_{fl}}{T_{max}} = \frac{2 s_m}{\frac{s_f^2}{s_{fl}} + 1}$$

starting slip ($s=1$)

$$\Rightarrow I_{2r} = \frac{V_1}{\sqrt{\left(\frac{R_2}{s}\right)^2 + (X_2')^2}}$$
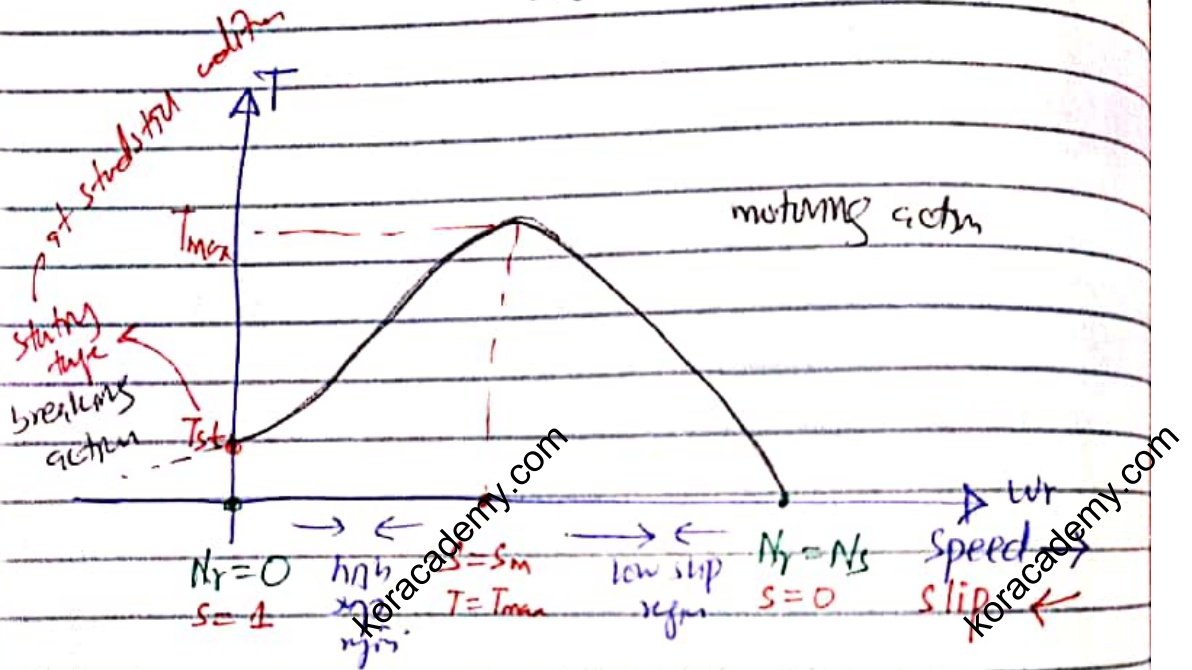
$$\Rightarrow T_d = \frac{3}{\omega_s} \cdot \frac{V_1^2}{\left(\frac{R_2}{s}\right)^2 + (X_2')^2} \cdot \frac{R_2}{s}$$



i- Low slip region. (operating / running region)

$$\uparrow \frac{R_2}{s} \gg X_2 \Rightarrow T_d = \frac{3}{\omega_s} \cdot s \frac{V_1^2}{R_2} \quad T_d \propto s$$

linear \leftarrow

ii- High slip region. (starting region)

$$\downarrow \frac{R_2}{s} \ll X_2 \Rightarrow T_d = \frac{3}{\omega_s} \cdot \frac{V_1^2}{s X_2^2} \cdot R_2$$

$$T_d \propto \frac{1}{s} \rightarrow \text{non linear}$$

$$\Rightarrow T_{st} = \frac{3}{\omega_s} \cdot \frac{V_1^2 R_2}{X_2^2}$$

depends on rotor resistance

koracademy.com

koracademy.com

koracademy.com

koracademy.com


koracademy.com

koracademy.com

koracademy.com

koracademy.com

koracademy.com

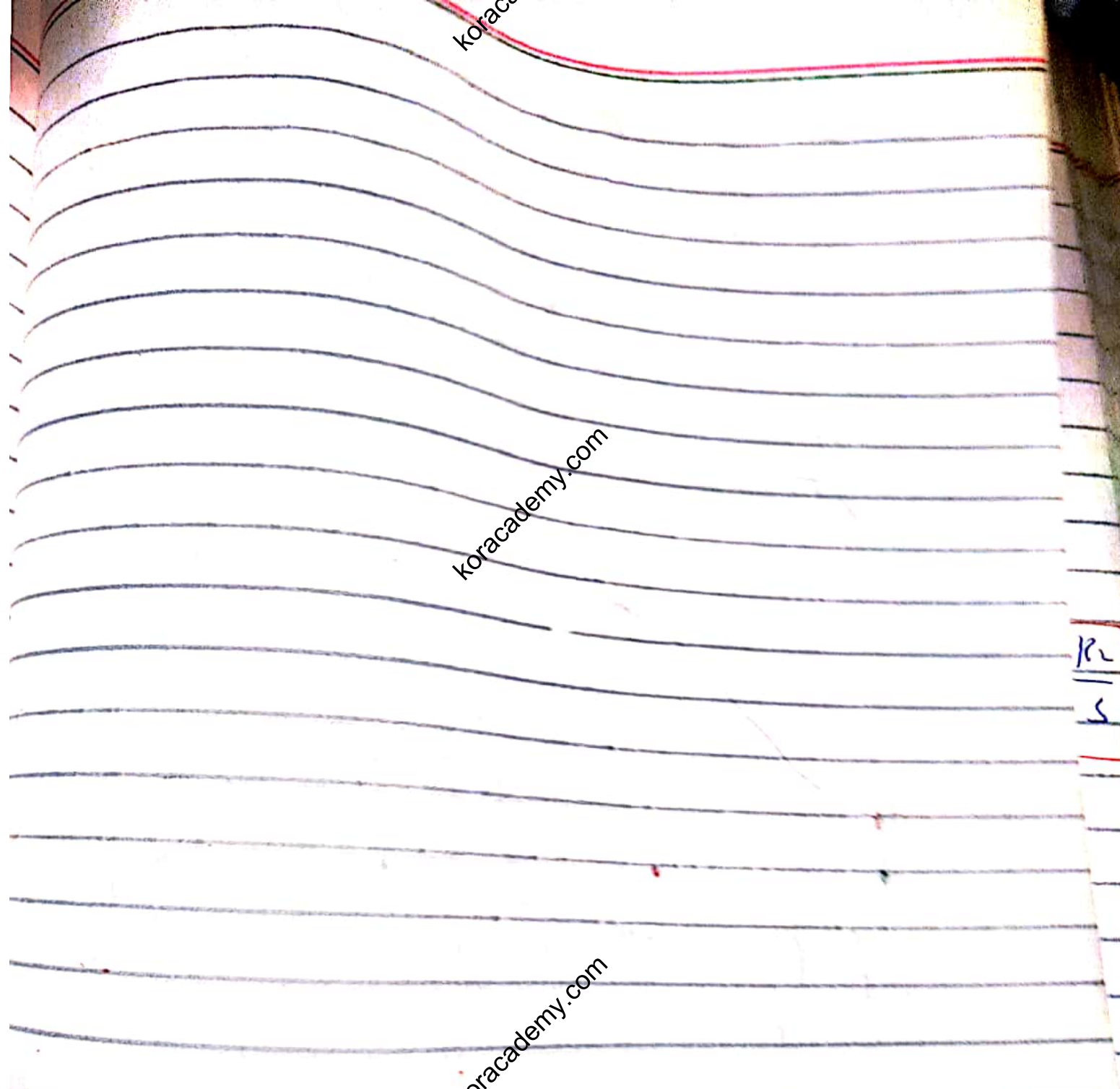

Synchronous Machine

- It is an AC machine.

- We have two types of windings.

① Armature winding → It delivers the AC power to the load.
→ It absorbs AC power from the supply.

Armature of any machine always have AC voltage or AC power.

② Field winding It is supplied from a DC supply to create a fixed pair of poles.

Synchronous machine is a doubly excited machine.

In case of synchronous machine, the induced voltage is a dynamically induced voltage.

↳ there is always a relative motion b/w conductor and field flux.

Conductor in motion and field stationary → dynamic.

① conductor fixed and flux rotating in machine → dynamic

[Conductor is stationary and flux is time varying → static]

↳ Why not in transformer?

B/c coils were stationary but the flux was time varying in nature (no motion so no motional emf).

e & relative motion.


Two produce relative motion, we have two cases;

① Field winding on rotor and armature winding on stator. (Synchronous machine).


② Field winding on stator and armature winding on rotor. (DC machine)

↳ A DC machine can behave as an AC machine if commutator is removed from its construction.

Consider the DC machine;

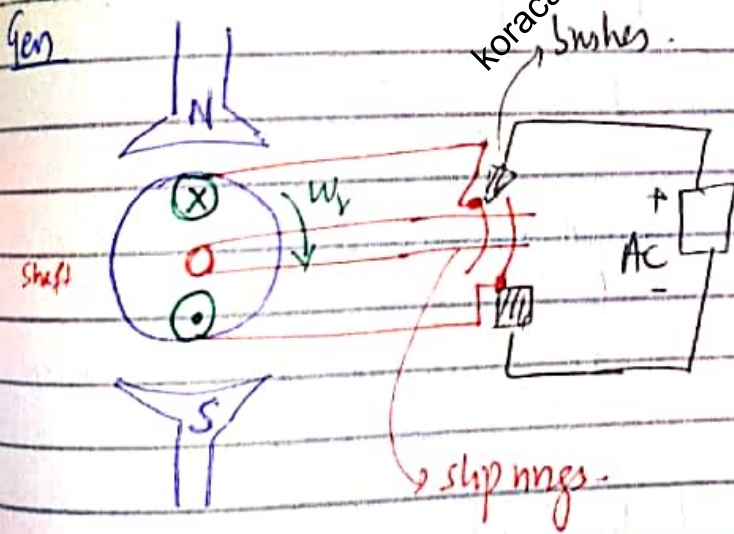


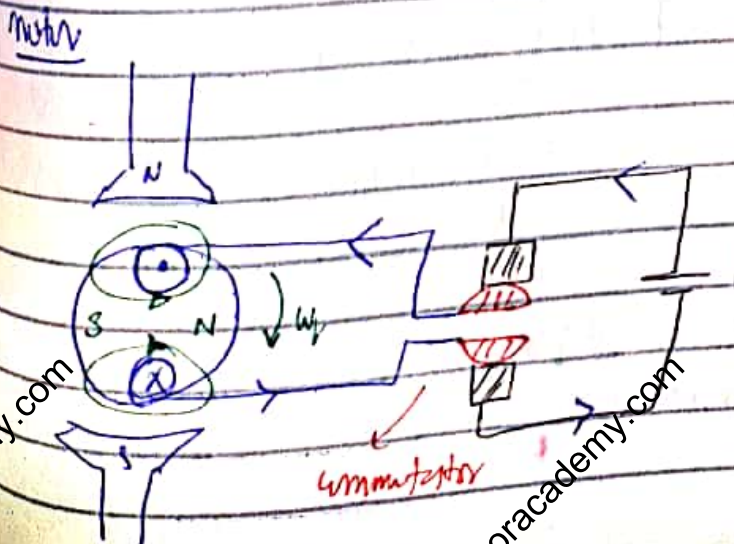DC generator with a slip ring and brush assembly is providing an AC opposite behaving like AC generator.



DC motor with commutator, then if a connecting DC supply is to AC supply to the armature.

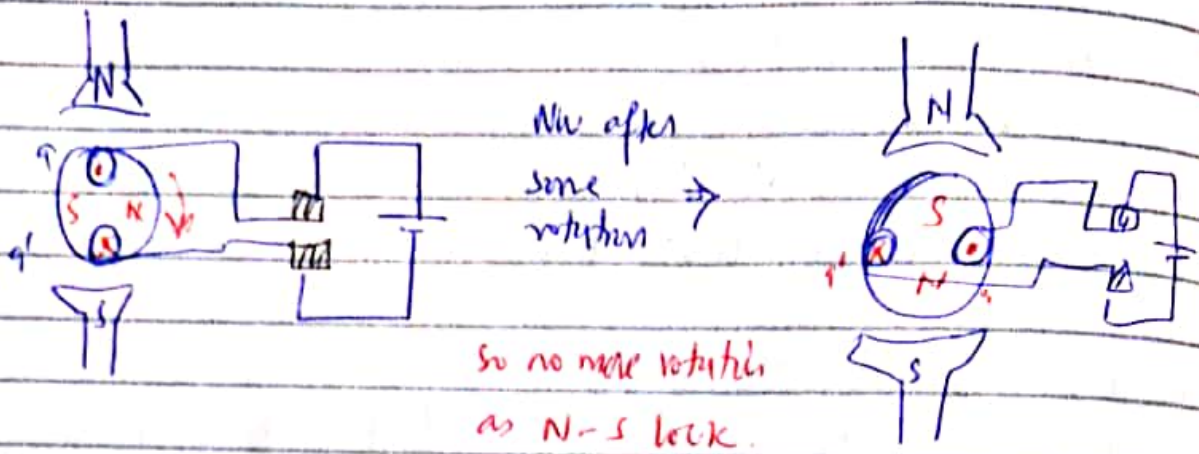If the DC motor is used without a commutator;



In a synchronous machine;

Stator → armature winding → high power winding → AC
Rotor → field winding → low power winding → DC
↳ to develop working MMF or flux.
for high power applications.

There are number of advantages for doing so.

(i) It is very economical and efficient.
(slip rings and insulation cost)

(ii) Efficient cooling.

(iii) A large number of armature conductors can be accommodated on stator easily, or space requirement for rotor will become less, and hence rotor weight reduce.
(moment of inertia, centrifugal forces etc).
mechanical strength

(iv) It will create more mechanical strength.

Synchronous Machine operation


① Rotor construction

Two types.

- i. Salient Pole type rotor \rightarrow SP type SM. $\left\{ \begin{array}{l} \rightarrow \text{Gen} \\ \rightarrow \text{Motor} \end{array} \right.$
- ii. Cylindrical pole type rotor \rightarrow CSM $\left\{ \begin{array}{l} \rightarrow \text{Gen} \\ \rightarrow \text{Motor} \end{array} \right.$

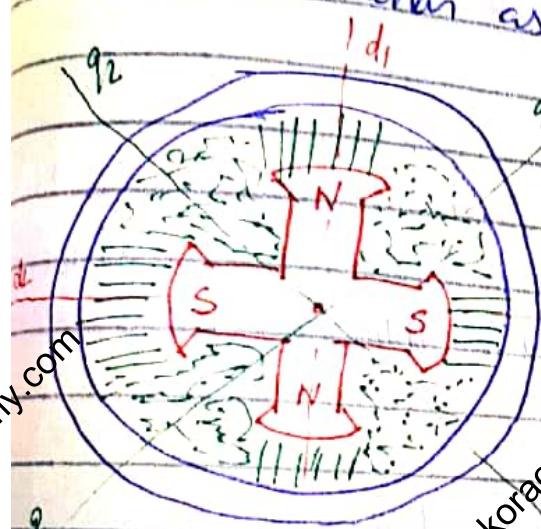i. Salient Pole type rotor

It is also known as **projected pole type rotor**.



4 pole rotor (projected outward)

The air gap is nonuniform \rightarrow air gap \propto poles
 In the d axis region, air gap is small $\Rightarrow R \downarrow$

\rightarrow to electrical fun d. $R = \frac{l}{\mu A}$


In the q axis region air gap is very large $\Rightarrow R \uparrow$

Hence the flux distribution will also be nonuniform.

as $\phi \propto \frac{1}{R}$

$$\boxed{\phi_e = \frac{P}{2} \phi_m}$$

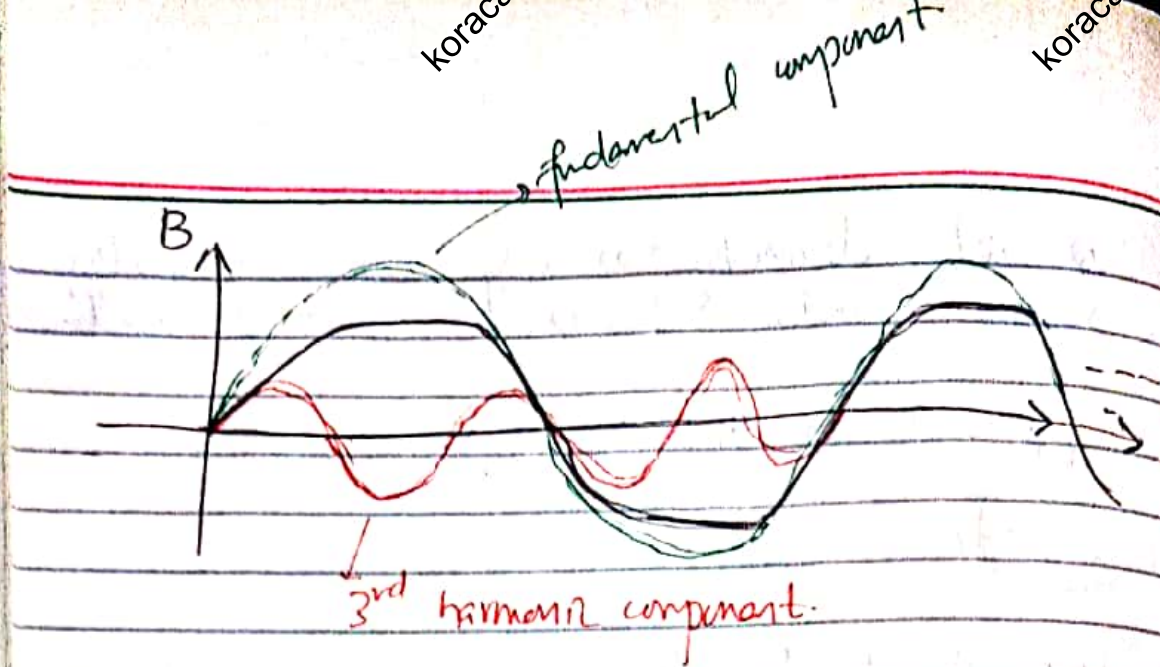Due to minimum air gap along d axis, the flux density will be maximum. And under the pole arc region the flux density is almost constant hence the flux density waveform is somewhat a flat topped wave.



Due to projection of the pole we have **unequal weight distribution** \Rightarrow mechanical strength is poor.

So if it is rotated at a high speed, then the centrifugal forces will damage the rotor due to unequal distribution of force on the rotor body.

That's why it is used for low speed applications.

Speed range = 50 to 1000 rpm

For a 50 Hz supply;

$$N_r = \frac{120f}{P} \Rightarrow P = \frac{120f}{N_r}$$

If speed, $N_r = 50 \Rightarrow P = 120$

If $N_r = 1000 \Rightarrow P = 6$

Hence pole requirement will be very high. (6 to 120)


Such kind of rotor construction is used in hydro power plants as it requires low speed.

The rotor diameter is very large corresponding to stator diameter but axial length is small.

(poles \uparrow \Rightarrow diameter \uparrow)

ii Cylindrical rotor

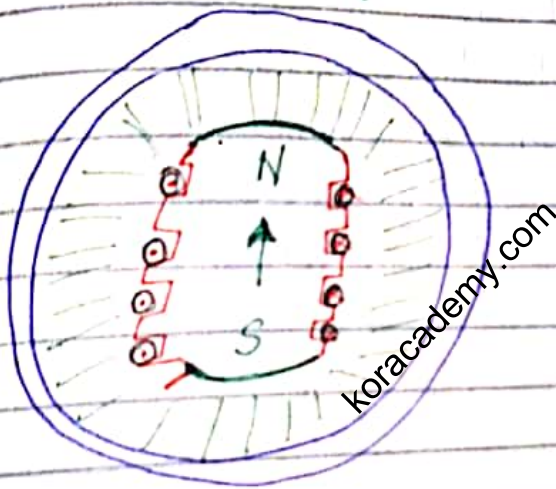i. In a cylindrical rotor, approximately $\frac{2}{3}$ rd area is used for the accommodation of field conductors and remaining portion is used as N or S pole.



ii. Here the poles have been induced with a DC supply i.e. it is not projected.

iii. In this air gap is almost uniform.

\Rightarrow Reluctance will also be uniform.

\Rightarrow Flux distribution will also be uniform.

and here air gap is low \Rightarrow Reluctance is low.

N. Such kind of construction is very useful for high speed applications.

At higher speed the centrifugal forces developed will be uniform over the rotor body, hence it will avoid mechanical damage.

v. Its mechanical stability is very high, hence mechanical strength is also good.

vi. Such construction is useful for;
 1500 to 3000 rpm for 50 Hz supply
 and 1800 to 3600 rpm for 60 Hz supply

$$N_r = \frac{120p}{P}$$

2-4 poles
 2 to 4 poles

$$\rightarrow 1500 = \frac{120(50)}{P} \Rightarrow P = 4$$


$$3000 = \frac{120(5)}{P} \Rightarrow P = 2$$

$$\rightarrow 1800 = \frac{120(60)}{P} \Rightarrow P = 4$$

$$3600 = \frac{120(60)}{P} \Rightarrow P = 2$$

vii. Here the rotor diameter is less as compared to salient machine and axial length will be high.


(2) ϕ_e and ϕ_m and induced emf

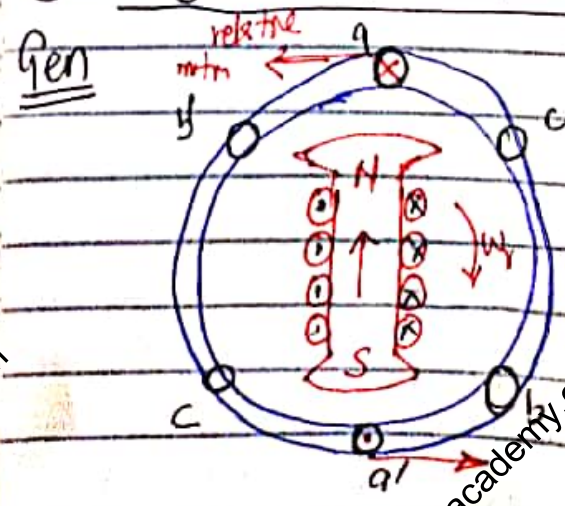

will have N turns
 $\leftarrow a-a' \rightarrow$ phase a
 $N \leftarrow b-b' \rightarrow$ phase b
 At $t=0$ $N \leftarrow c-c' \rightarrow$ phase c

Now to understand the operation, taking one phase...

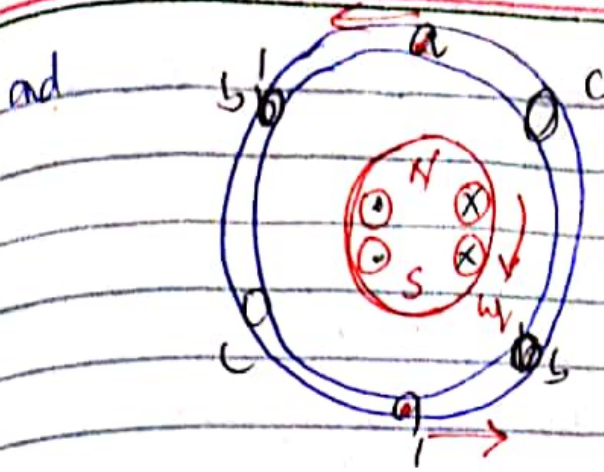
full pitch \Rightarrow physical displacement = 180° electrical.




At $t=0$

Give rotation to the rotor at constant speed (N_r)
 \rightarrow Excite the field winding (DC supply) \rightarrow there will be relative motion b/w stator conductor and rotor flux.

If rotor rotates 60°

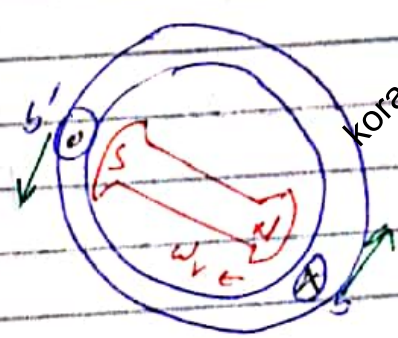


If rotates further 120°

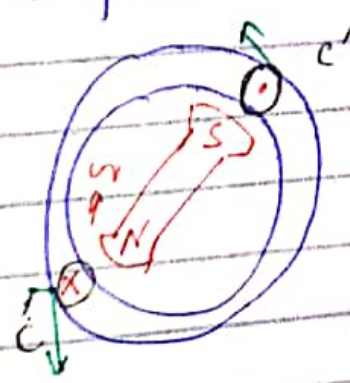


Induced voltage is maximum when the angle b/w flux and velocity component is 90°

$$E_{cd} = E_{max} \cos(\omega t + 120^\circ)$$
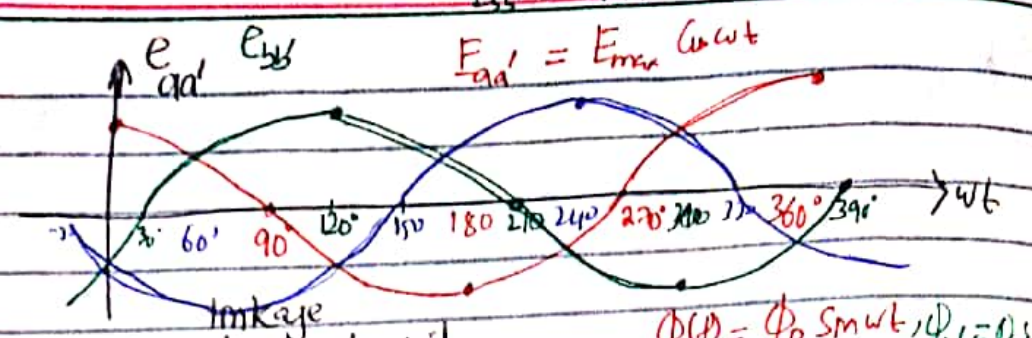
$$E_{bd} = E_{max} \sin(\omega t - 120^\circ)$$



$$E_{ad} = E_{max} \cos \omega t$$

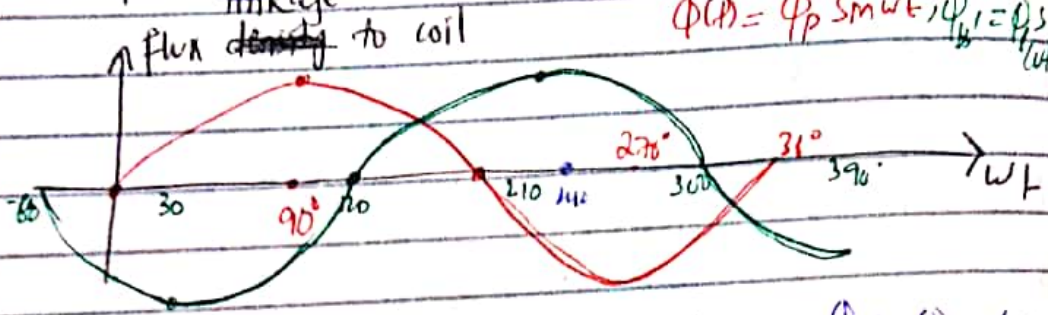

$$\phi(t) = \phi_p \sin \omega t, \quad \phi_b = \phi_p \sin(\omega t - 120^\circ)$$

$$\phi_{cd} = \phi_p \sin(\omega t + 120^\circ)$$

$$Q_e = \frac{P}{2} Q_m$$

$$\frac{dQ_e}{dt} = \frac{P}{2} \frac{dQ_m}{dt} \quad \omega_c = \frac{P}{2} \omega_r$$

$$\Rightarrow 2\pi f_c = \frac{P}{2} \frac{2\pi N_r}{60} \Rightarrow \boxed{N_r = \frac{120f}{P}}$$

constant speed for a particular frequency ← synchronous speed

→ Induced emf $e_{ad} \propto \frac{d\psi}{dt}$, $\psi = N\phi$
 ↓
 flux linkage

$$N = 120^\circ$$

$N_{ph} =$ Total no. of turns
 no. of phases = 3

$$e_{ad} = N_{ph} \frac{d}{dt} = -N_{ph} \frac{d\phi}{dt}$$

$$= -N_{ph} \frac{d\phi_m}{dt} = -N_{ph} \times \phi_m \times \omega \cos \omega t = -E_{max} \cos \omega t$$

$$\Rightarrow e_{ad} = E_{max} \sin(\omega t - 90^\circ)$$

$$E_{rms} = \frac{E_{max}}{\sqrt{2}} = \frac{N_p \phi \omega}{\sqrt{2}}$$

$$\Rightarrow E_{rms} = 4.44 f \phi N_p$$

$$e_{aa'} = N_p \phi \omega \sin(\omega t - 90^\circ)$$

$$e_{bb'} = N_p \phi \omega \sin(\omega t - 210^\circ)$$

$$e_{cc'} = N_p \phi \omega \sin(\omega t + 30^\circ)$$

Hence each phase has same induced voltage as they have same number of turns and each voltage is displaced 120° electrical from each other.

$$E_{am} = E_{bm} = E_{cm} = E_f = \frac{E_{max}}{\sqrt{2}} = 4.44 f \phi N_p$$

$\Rightarrow E_f = 4.44 f \phi N_p$ → true for full
Induced emf due to field excitation only. pitch winding

E_f will lag ϕ_f by 90°

Types of Armature Winding (stator)

- (i) Single Layer
- (ii) Double layer
- (iii) Full pitch
- (iv) Short pitch
- (v) Concentrated
- (vi) Distributed

Conductor: The active length of wire under influence of field flux.

Turn: it is made with the use of conductors.

1 turn \Leftrightarrow 2 conductors.

T turns $\Leftrightarrow \frac{Z}{2}$ conductors $\Rightarrow Z = 2T$

Total no. of conductors per phase; $Z_{ph} = \frac{Z}{3}$


Total no. of turns per phase; $T_{ph} = N_{ph} = \frac{T}{3} = \frac{Z}{6} = \frac{Z_{ph}}{2}$

Coil A coil is formed by connecting number of turns.

1 coil \Leftrightarrow Minimum 1 turn \Leftrightarrow 2 conductors. \rightarrow single

Coil \rightarrow N turns \rightarrow 2 x N conductors \rightarrow N turn coil. turn coil.

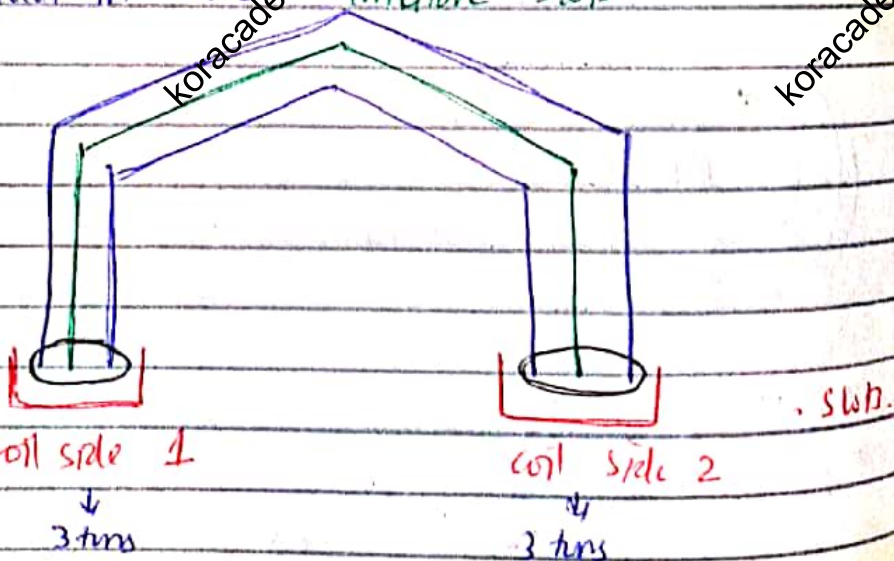Coil sides A coil always have 2 sides and these sides are placed in the armature slots.



In both coil sides, the number of turns remain the same.

Total no. of conductors to make a 3 turn coil = 6.

(does not depend on coil side) $[6 + 6] \times$

Coil span or coil pitch It is the distance b/w two coil sides in terms of electrical degree or mechanical degree or number of slots present in b/w two sides.

coil side 1
of coil

coil span

coil side 2
of coil


= 9 slots (finishing - starting)

Pole Pitch

The centre to centre distance b/w two adjacent poles.

$$1 \text{ Pole pitch} = \frac{(360^\circ)}{P} \text{ (mech)} = \frac{360^\circ}{P} \times \frac{P}{2} = 180^\circ \text{ (electrical)}$$

consider for a 4 pole machine;

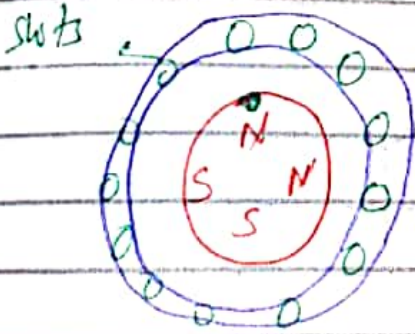

→ revolution

$$1 \text{ pole pitch} = \frac{360^\circ}{4} = 90^\circ \text{ (mechanical)}$$

$$1 \text{ pole pitch} = 90^\circ \times \frac{4}{2} = 180^\circ \text{ (electrical)}$$

In terms of slots;

$$1 \text{ pole pitch} = \frac{\text{No. of slots in stator}}{\text{No. of poles}} \quad \left(\frac{12}{4} \right) \text{ here}$$

slot angle (γ)
slot.

the angle contributed by one

$$\gamma = \frac{360^\circ}{\text{no. of slots}} \text{ (mechanical)}$$

$$\gamma = \frac{360^\circ}{\text{no. of slots}} \times \frac{P}{2} = \frac{180^\circ}{\text{No. of slots/pole}} \text{ (electrical)}$$

An in an example ; 1 pole pitch = $\frac{13}{4}$ m lens of slots

$$\Rightarrow \gamma = \frac{360^\circ}{13} \text{ mechanical}$$

$$\Rightarrow 1 \text{ pole pitch} = \left(\frac{17}{4}\right) \left(\frac{360^\circ}{13}\right) = \frac{360^\circ}{4} \checkmark \text{ electrical}$$

$$1 \text{ pole pitch} = \frac{360^\circ}{4} \times \frac{4}{2} = 180^\circ \text{ electrical}$$

On the basis of pitching the winding is classified into two categories.

① (i) Full Pitch winding

$$1 \text{ pole pitch} = 180^\circ \text{ electrical.}$$

$$\textcircled{a} 1 \text{ pole pitch} = \frac{360^\circ}{P} \text{ mechanical}$$



→ If the distance b/w two coil sides of a coil is 1 pole pitch, then such a winding is known as full pitch winding.

coil span = 1 pole pitch = full pitch winding.

(ii) If the coil span is less than 1 pole pitch, then the winding is known as short pitch winding.

$$\text{coil span} < 1 \text{ pole pitch}$$

Consider a 2 pole machine;

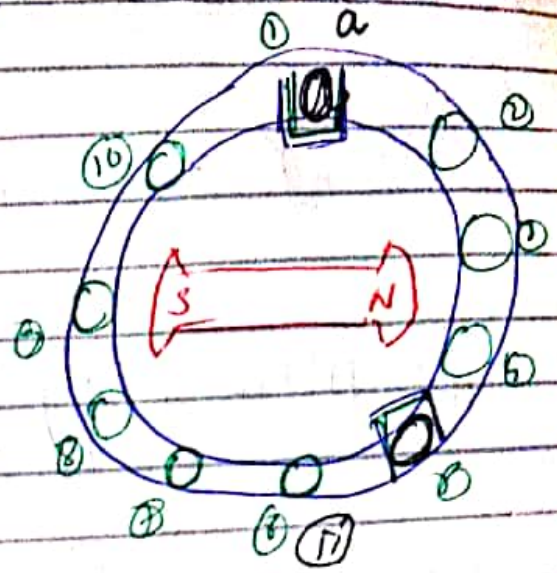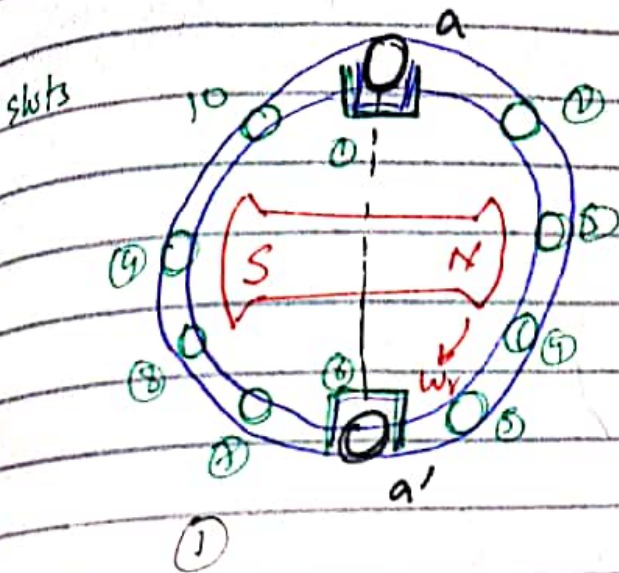

Case i

For a full pitch coil

$$\Phi_p = \frac{4 B_p l r}{p}$$

for $p=2$

$$\Rightarrow \Phi_p = 2 B_p l r$$

Induced emf for a full pitch coil:


$$E_p = 4.44 f \Phi_p N_{ph}$$

↳ per phase rms value.

Case II

~~Short Pitching~~

1 pole pitch = 180°

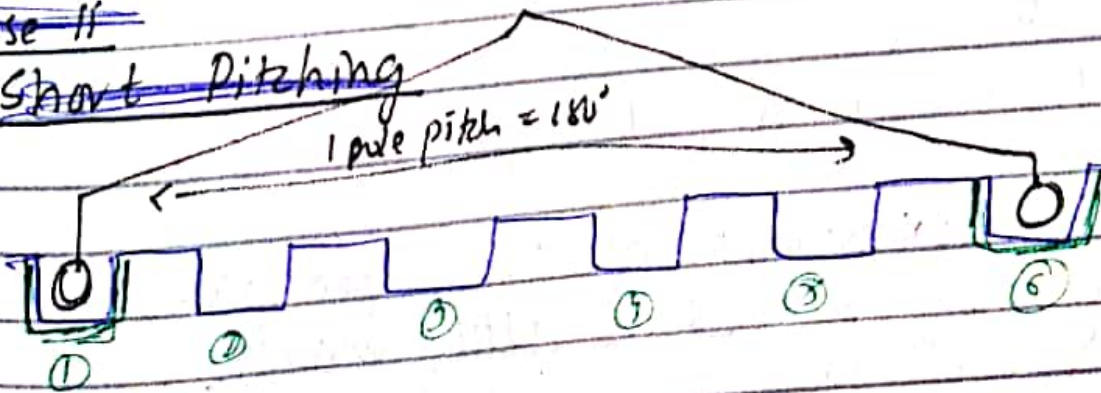

1 pole pitch = 5 slots

total no. of slots = 5 x 2 = 10


Slot angle $\gamma = \frac{360^\circ}{10} = 36^\circ$ electrical-mechanical

① $\gamma = \frac{36^\circ}{2} \times \frac{P}{2} = 36^\circ$ electrical

1 pole pitch = $5 \times 36 = 180^\circ$ electrical.

Case ii

Short Pitching

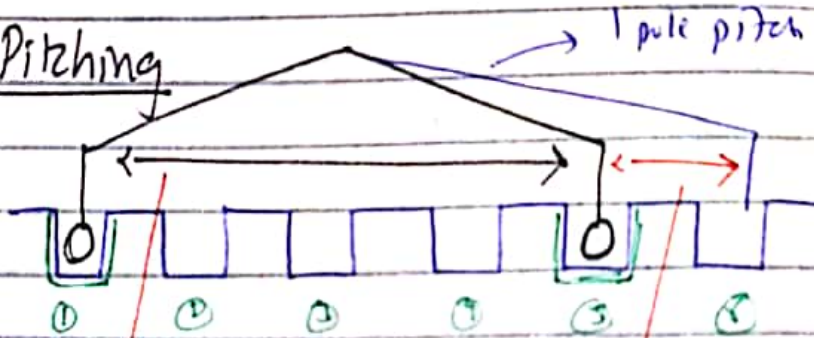

short pitch coil span

$\epsilon =$ short pitch angle

short pitch coil span = $180^\circ - \epsilon$


or electrical angle.

eg here it has shorted by 1 slot \Rightarrow angle of 1 slot = 36°

$\Rightarrow \epsilon = 36^\circ$

\Rightarrow short pitch coil span = $180^\circ - 36^\circ = 144^\circ$

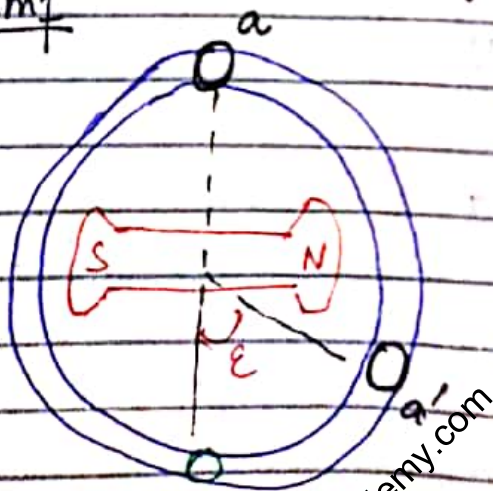Effect of short pitching on Flux per pole and induced emf



Due to short pitching the flux per pole (ϕ_p) will reduce.

The factor by which it reduces is known as pitch factor (K_p).

or consider the second figure for demonstration purpose.

$$\text{As } d\phi = B \cdot dA$$

$$\int d\phi = \int B_p \sin \alpha (l r d\alpha)$$

$$\phi = \int_{\epsilon/2}^{180^\circ - \epsilon/2} B_p \cdot l \cdot r [-\cos \alpha]_{\epsilon/2}^{180^\circ - \epsilon/2}$$

$$= B_p l r \left[-\cos\left(180^\circ - \frac{\epsilon}{2}\right) + \cos \frac{\epsilon}{2} \right]$$

$$\Rightarrow \boxed{\phi_p = 2 B_p l r \cos \frac{\epsilon}{2}}$$

\downarrow
 K_p

$$\text{Pitch factor } (K_p) = \frac{\phi_p \text{ in full pitch winding}}{\phi_p \text{ in short pitch winding}}$$

$$= \frac{2 B_p \cdot l \cdot r \cdot \cos \frac{\epsilon}{2}}{2 B_p \cdot l \cdot r}$$

$$\Rightarrow \boxed{K_p = \cos \frac{\epsilon}{2}}$$

$$0 \leq K_p \leq 1$$

If $k_p = 1 \Rightarrow$ full pitch coil.

$$\text{as } \cos \frac{\epsilon}{2} = 1 \Rightarrow \frac{\epsilon}{2} = \cos^{-1}(1)$$

$$\Rightarrow \boxed{\epsilon = 0}$$

Flux per pole for one pole area;

$$\frac{2\pi r l}{2} \rightarrow 2 B_p \cdot l \cdot r \cdot \cos \frac{\epsilon}{2}$$

$$\boxed{\frac{2\pi r l}{P} \rightarrow 2 B_p \cdot l \cdot r \cdot \cos \frac{\epsilon}{2} \times \frac{2\pi r l}{P} = \frac{4 B_p l r \cos \frac{\epsilon}{2}}{P}}$$

\Rightarrow When coil is full pitch;

$$E_f (fp) = 4.44 f \left(\frac{4 B_p l \cdot r}{P} \right) N_{ph}$$

When coil is short pitched;

$$E_f (sp) = 4.44 f \left(\frac{4 B_p l \cdot r}{P} \right) N_{ph} \cos \left(\frac{\epsilon}{2} \right)$$

Ratio;

$$\boxed{\frac{E_f (sp)}{E_f (fp)} = \cos \left(\frac{\epsilon}{2} \right) = k_p}$$

$$\boxed{E_f (sp) = 4.44 f \Phi_p N_{ph} k_p}$$

$$\boxed{E_f (sp) < E_f (fp)}$$

② concentrated and distributed winding

consider a 3 ϕ synchronous machine. (assuming alternator)
with full pitch winding.

$$\text{no. of phases} = 3$$


$$\text{no. of poles } (P) = 2$$

$$\text{No. of slots available in stator for armature winding} = 18$$

$$\begin{aligned} \text{No. of slots per pole} &= \text{pole pitch (in terms of slots)} \\ &= \frac{18}{2} = 9 = 180^\circ \text{ electrical} = \frac{360^\circ}{2} \text{ mechanical} \end{aligned}$$

$$\text{No. of slots / pole / phase} = m = \frac{\text{no. of slots}}{P \times \text{no. of phase}} = \frac{18}{2 \times 3} = 3$$

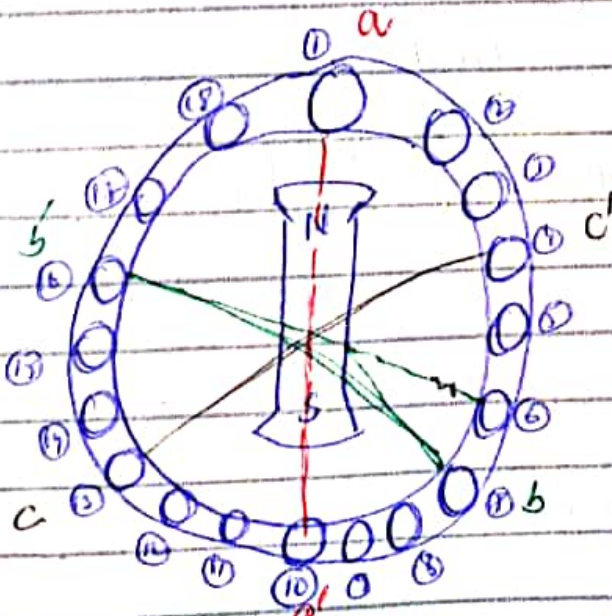
$$\begin{aligned} \text{Slot angle } (\gamma) &= \frac{360^\circ}{18} = 20^\circ \text{ mechanical} \\ &= 20 \times \frac{2}{2} = 20^\circ \text{ electrical} \end{aligned}$$



In a concentrated winding, all the conductors belonging to a phase are placed in one slot in every pole.

In concentrated winding the total induced emf is the algebraic sum of individual inductor emf's (algebraic)

→ Distributed

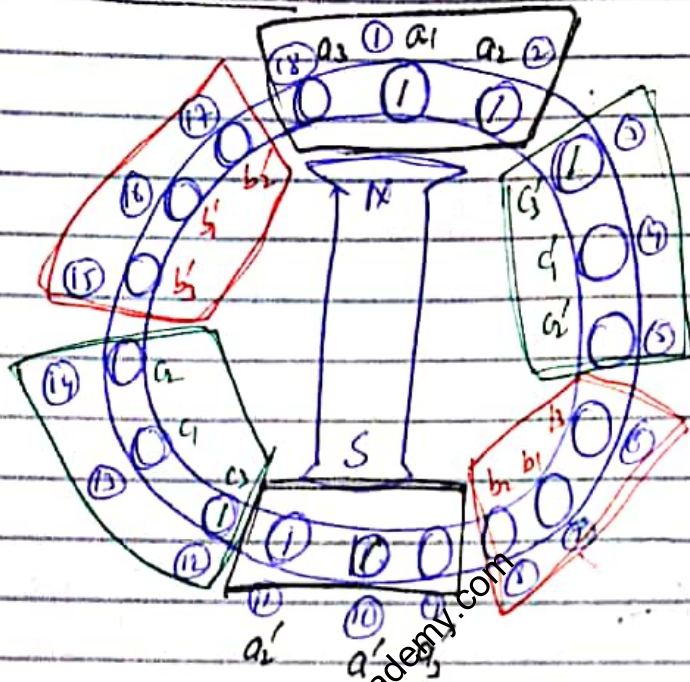

→ Phase belt @ phase spread

↳ The angle covered by one phase under one pole

(here of 60°)

$90 - 30 \rightarrow 60$

$90 - 30 = 60$

In distributed winding, all the coils belonging to a phase are well distributed into a number of slots under every pole.


In distributed winding, the resultant emf is not algebraic summation of the individual coil emfs. That means the resultant emf will be calculated vectorially and induced emf will also get reduced due to distribution of the coil.

→ Assuming each coil in the 18 slots have same magnitude of emf as they have same number of turns.


→ The projection of emf shown in the figure represents the total emf induced in a coil.

$$E = \frac{4.44 f \Phi N}{100}$$
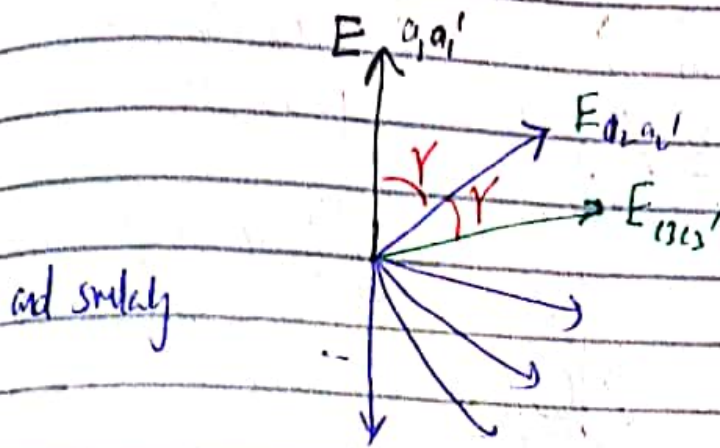
$$\left(\begin{aligned} e_a &= +E/2, & e_{a'} &= -E/2 \\ \Rightarrow e_{aa'} &= e_a - e_{a'} = E \end{aligned} \right)$$




and similarly

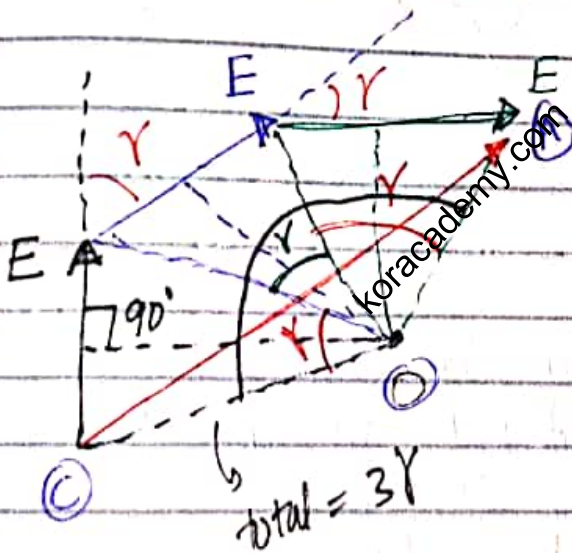

These all are lying on the circumference of circle with centre O .

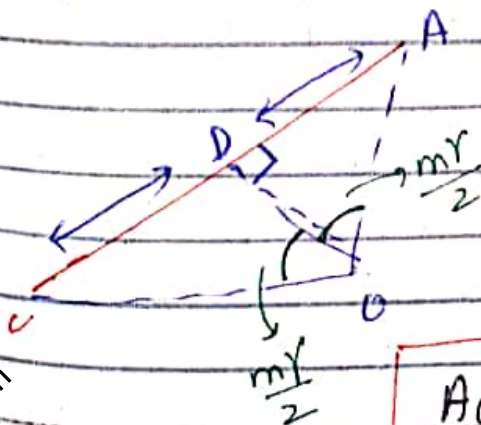Similarly if all the wires are taken, γ will keep on adding $\Rightarrow m\gamma$




$$\sin\left(\frac{m\gamma}{2}\right) = \frac{AD}{OA}$$

$$\Rightarrow AD = OA \sin\left(\frac{m\gamma}{2}\right)$$

$$AC = OA = 2 AD = 2 \sin\left(\frac{m\gamma}{2}\right)$$

for algebraic summation;

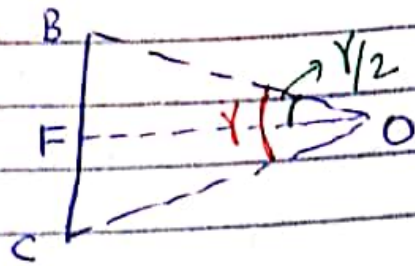

$$\sin\left(\frac{\gamma}{2}\right) = \frac{BF}{OB} = \frac{BF}{OA}$$

$$\Rightarrow BF = OA \sin\left(\frac{\gamma}{2}\right)$$

$$\Rightarrow BC = 2BF = 2OA \sin\frac{\gamma}{2}$$

Algebraic summation

$$= m \times 2OA \sin\frac{\gamma}{2}$$

$$K_d = \frac{\text{Vector sum of induced emf}}{\text{Algebraic summation}} = \frac{2OA \sin\left(\frac{m\gamma}{2}\right)}{m \cdot 2OA \sin\left(\frac{\gamma}{2}\right)}$$

$$\Rightarrow K_d = \frac{\sin\left(\frac{m\gamma}{2}\right)}{m \sin\left(\frac{\gamma}{2}\right)}$$

↳ Distribution factor. @ belt factor

also;

$$K_d = \frac{\text{Induced emf with distributed winding}}{\text{Induced emf with concentrated winding}}$$

$$= \frac{2OA \sin\left(\frac{m\gamma}{2}\right)}{m \cdot 2OA \sin\left(\frac{\gamma}{2}\right)} = \frac{\sin\left(\frac{m\gamma}{2}\right)}{m \sin\left(\frac{\gamma}{2}\right)}$$

Now if we are using distributed winding;

$$E_{ms}(ph) = 4.44 f \Phi_p N_{ph} K_d$$

$$\rightarrow K_d = \frac{\sin \left(\frac{mY}{2} \right)}{m \sin \left(\frac{Y}{2} \right)}$$

$m = \text{no. of slots per pole per phase} = \frac{\text{No. of slots}}{P \cdot n (\text{no. of phases})}$

$$Y = \frac{360^\circ}{\text{no. of slots}} \quad (\text{mechanical})$$

$$\therefore Y = \frac{360^\circ}{\text{no. of slots}} \times \frac{P}{2} \quad (\text{electrical})$$

$$mY = \text{phase spread} = \delta = \left(\frac{\text{No. of slots}}{P} \right) \left(\frac{360^\circ}{\text{no. of slots}} \right)$$

$$\Rightarrow \delta = 60^\circ \text{ electrical}$$

$$\text{or } \left(\frac{12}{P} \right) \text{ mechanical.}$$

if writing generally;

$$\delta = mY = \frac{\text{No. of slots}}{P \cdot n} \times \frac{360^\circ}{\text{no. of slots}} = \frac{360^\circ}{P \cdot n} \text{ mechanical}$$

$$= \frac{360^\circ}{P \cdot n} \left(\frac{P}{2} \right) = \frac{180^\circ}{n} \text{ electrical}$$

$n \rightarrow \text{no. of phases.}$

For a single ϕ system;

$$\delta = \frac{180^\circ}{1} = 180^\circ \text{ electrical}$$

For 2 ϕ ;

$$\delta = \frac{180^\circ}{2} = 90^\circ \text{ electrical}$$

For 3ϕ .

$$\delta_{\phi} = \frac{180^\circ}{3} = 60^\circ \text{ electrical}$$

\Rightarrow

$$K_d = \frac{\sin\left(\frac{\delta}{2}\right)}{m \sin\left(\frac{\delta}{2m}\right)}$$

$$m\gamma = \delta$$

$$\gamma = \left(\frac{\delta}{m}\right)$$

in terms of phase spread.

Fractional slot winding

If m is an integer value i.e. (1, 2, 3, 4, ...) \rightarrow distributed winding.

If m is a fraction \rightarrow fractional winding.

$$\text{Here } m = \frac{S_k}{P_k}$$

Here:

$$K_d = \frac{\sin\left(\frac{\delta}{2}\right)}{S_k \cdot \sin\left(\frac{\delta}{2S_k}\right)}$$

$$\text{If } \underline{\underline{\gamma}} \ll 15^\circ \Rightarrow \sin\left(\frac{\gamma}{2}\right) \approx \frac{\gamma}{2} \text{ (radians)}$$

$$\Rightarrow K_d = \frac{\sin\left(\frac{m\gamma}{2}\right)}{m \frac{\gamma}{2}} = \frac{\sin\left(\frac{\delta}{2}\right)}{\frac{\delta}{2}}$$

all angles
in electrical.

\rightarrow Uniformly distributed winding
where numerator is in radians. (multiply by $\frac{1}{180}$)

$$\text{ad } \boxed{E_{ph} = 44 f \Phi_p N_{ph} K_d}$$

Impact of harmonics on K_p , K_d and Φ_p and induced voltage.

(i) Flux / Pole

$$\Phi_p = \frac{4 B_p l r}{p} \quad \dots \text{ when there is no harmonics (fundamental flux)}$$

$$\Phi_{pn} = \frac{4 B_{pn} l r}{n \cdot p} \quad \rightarrow \text{for } n^{\text{th}} \text{ harmonic}$$

$$\text{for } n=1 \Rightarrow \Phi_{p1} = \frac{4 B_{p1} l r}{p} \quad \rightarrow \text{fundamental}$$

$$n=3 \Rightarrow \Phi_{p3} = \frac{4 B_{p3} l r}{3p} \quad \rightarrow 3^{\text{rd}} \text{ harmonic component}$$


$$n=5 \Rightarrow \Phi_{p5} = \frac{4 B_{p5} l r}{5p} \quad \rightarrow 5^{\text{th}} \text{ harmonic component}$$

$$\frac{\Phi_{p3}}{\Phi_{p1}} = \frac{B_{p3}}{3/B_{p1}} = \left(\frac{B_{p3}}{B_{p1}} \right) \left(\frac{1}{3} \right)$$

$$\frac{\Phi_{p5}}{\Phi_{p1}} = \left(\frac{B_{p5}}{B_{p1}} \right) \frac{1}{5}$$


$$\boxed{\frac{\Phi_{pn}}{\Phi_{p1}} = \left(\frac{B_{pn}}{B_{p1}} \right) \times \frac{1}{n}}$$

Consider a two pole machine;

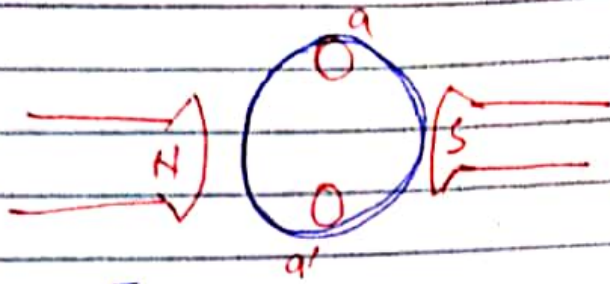

$$\Phi_p = \int_0^\pi B_p \sin \alpha \cdot l \cdot r \, d\alpha = B_p l r [\cos \alpha]_0^\pi$$
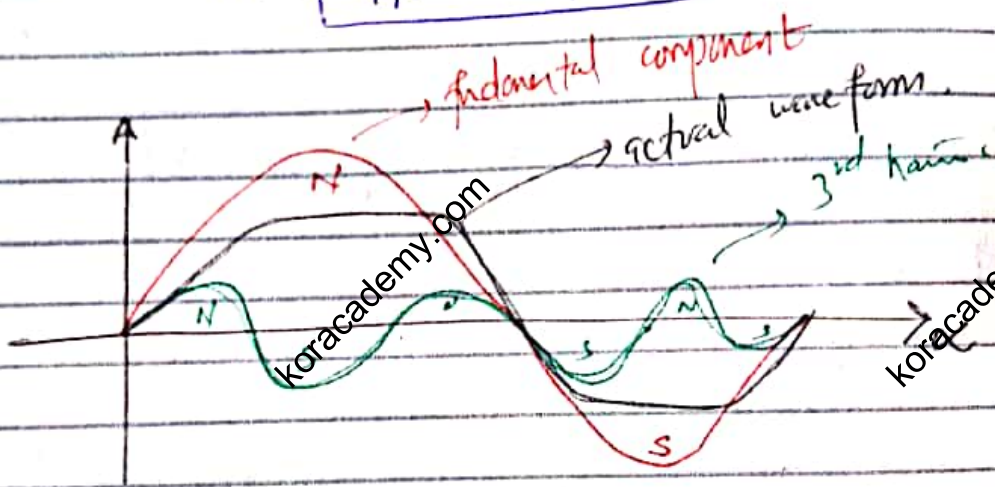
$$\Rightarrow \boxed{\Phi_p = 2 B_p l r}$$



Considering the third harmonic only;

$$B = B_{p3} \sin 3\alpha$$

$$\Rightarrow \Phi_{p3} = \int_0^\pi B_{p3} \sin 3\alpha \cdot l \cdot r \, d\alpha$$

$$= \frac{B_{p3} \cdot l \cdot r}{3} (1+1) = \frac{2 B_{p3} \cdot l \cdot r}{3}$$

↳ divided by the harmonic number.

Generally, for any n and p ;

$$\boxed{\Phi_{pn} = \frac{4 B_{pn} l r}{n p}}$$

ii. Pitch Factor (k_p)

For n^{th} harmonic,

$$k_{pn} = \cos\left(\frac{n\epsilon}{2}\right)$$

If $n=1 \Rightarrow k_{p1} = \cos\left(\frac{\epsilon}{2}\right) \rightarrow$ due to fundamental harmonic in flux.

If $n=3 \Rightarrow k_{p3} = \cos\left(\frac{3\epsilon}{2}\right) \rightarrow$ due to 3rd harmonic in flux.

To eliminate harmonics,

$$k_{pn} = 0$$

$$\Rightarrow \cos\left(\frac{n\epsilon}{2}\right) = 0 \Rightarrow \frac{n\epsilon}{2} = \cos^{-1} 0$$

$$\Rightarrow \frac{\epsilon}{2} = \frac{\pi}{2n} \Rightarrow \boxed{\frac{\epsilon}{n} = \frac{\pi}{n}} = \left(\frac{180^\circ \text{ electrical}}{n}\right)$$

eg to eliminate 3rd harmonic:

$$\epsilon = \frac{180^\circ}{3} = 60^\circ$$

$$\Rightarrow k_{p3} = \cos\left(\frac{3 \times 60^\circ}{2}\right) = \cos 90^\circ = 0$$

$$k_{p5} = \cos\left(\frac{5 \times 60^\circ}{2}\right) = \cos 150^\circ \rightarrow 5^{\text{th}} \text{ harmonic will exist.}$$

Both cannot be eliminated at the same time by ϵ is taken to eliminate 3rd as its amplitude is higher so it will have a higher ripple.

(iii) Distribution factor (K_d)

$$K_{dn} = \frac{\sin\left(\frac{mnr}{2}\right)}{m \sin\left(\frac{nr}{2}\right)} \rightarrow \text{Generalized expression}$$

If $\gamma \ll 15^\circ$;

$$K_{dn} = \frac{\sin\left(\frac{n\sigma}{2}\right)}{\frac{n\sigma}{2}}$$

For fractional slot winding:

$$K_{dn} = \frac{\sin\left(\frac{n\sigma}{2}\right)}{s_k \sin\left(\frac{n\sigma}{2s_k}\right)}$$

N- Induced emf

$$E_{ph} = 4.44 f \Phi_p N_{ph} \rightarrow \text{fundamental for full pitch and concentrated winding.}$$

Generalized in harmonic form:

$$E_{ph(n)} = 4.44 (nf) \Phi_{pn} (K_{pn} K_{dn}) N_{ph}$$

$$K_{wn} = K_{pn} \times K_{dn}$$

→ winding factor

If $n=1 \Rightarrow E_{ph1} = 4.44 f \Phi_{p1} K_{p1} K_{d1} N_{ph}$

If $n=3 \Rightarrow E_{ph3} = 4.44 (3f) \Phi_{p3} K_{p3} K_{d3} N_{ph}$

If $n=5 \Rightarrow E_{ph5} = 4.44 (5f) \Phi_{p5} K_{p5} K_{d5} N_{ph}$

If ratios;
$$\frac{E_{ph5}}{E_{ph1}} = \frac{5 \Phi_{p5} K_{w5}}{\Phi_{p1} K_{w1}}$$

Similarly
$$\frac{E_{ph3}}{E_{ph1}} = \frac{3 \Phi_{p3} K_{w3}}{\Phi_{p1} K_{w1}}$$

Generalizing;

$$\frac{E_{phn}}{E_{ph1}} = \frac{n \Phi_{pn} K_{wn}}{\Phi_{p1} K_{w1}}$$

Total rms voltage;

$$E_{ph \text{ ms}} = \sqrt{E_{ph1}^2 + E_{ph2}^2 + E_{ph5}^2 + E_{ph7}^2 + \dots}$$

As this is a 3 ϕ system;

$$E_{ph a} = E_{m1} \sin \omega t + E_{m3} \sin 3\omega t + E_{m5} \sin 5\omega t + \dots$$

$$E_{ph b} = E_{m1} \sin(\omega t - 120^\circ) + E_{m3} \sin(3\omega t - 3 \times 120^\circ) + E_{m5} \sin(5\omega t - 5 \times 120^\circ) + \dots$$

$$E_{ph c} = E_{m1} \sin(\omega t + 120^\circ) + E_{m3} \sin(3\omega t + 3 \times 120^\circ) + E_{m5} \sin(5\omega t + 5 \times 120^\circ) + \dots$$

$$\rightarrow \sin(3\omega t + 3(120)) = \sin(3\omega t)$$

$$\rightarrow \sin(5\omega t + 5(120)) = \sin(5\omega t + 120^\circ)$$

Case i Star connected armature winding.



There exists fundamental and 3, 5, 7, ... harmonics in phase voltage.

For line voltage;

$$E_{ab} = E_a - E_b = [E_{m1} \sin \omega t - E_{m1} \sin(\omega t - 120^\circ)] + [E_{m3} \sin 3\omega t - E_{m3} \sin(3\omega t - 120^\circ)] + \dots$$

$$E_{bc} = E_b - E_c$$

$$E_{ca} = E_c - E_a$$

In line voltage there will be no triplet harmonics (3rd, 9th ...)

$$E_{ph\ rms} = \sqrt{E_{m1}^2 + E_{m3}^2 + E_{m5}^2 + \dots}$$

$$E_{line\ rms} = \sqrt{3} \times E_{ph\ rms} = \sqrt{3} \sqrt{E_{m1}^2 + E_{m3}^2 + \dots}$$

Case ii In delta connection.




$$E_a + E_b + E_c = 0 + 3 E_{m3} \sin 3\omega t + 0$$

$$= 3 E_{m3} \sin 3\omega t$$

A current will circulate; \rightarrow

$$I_{c3} = \frac{3 E_{m3} S_{11} Z_{ut}}{3Z}$$

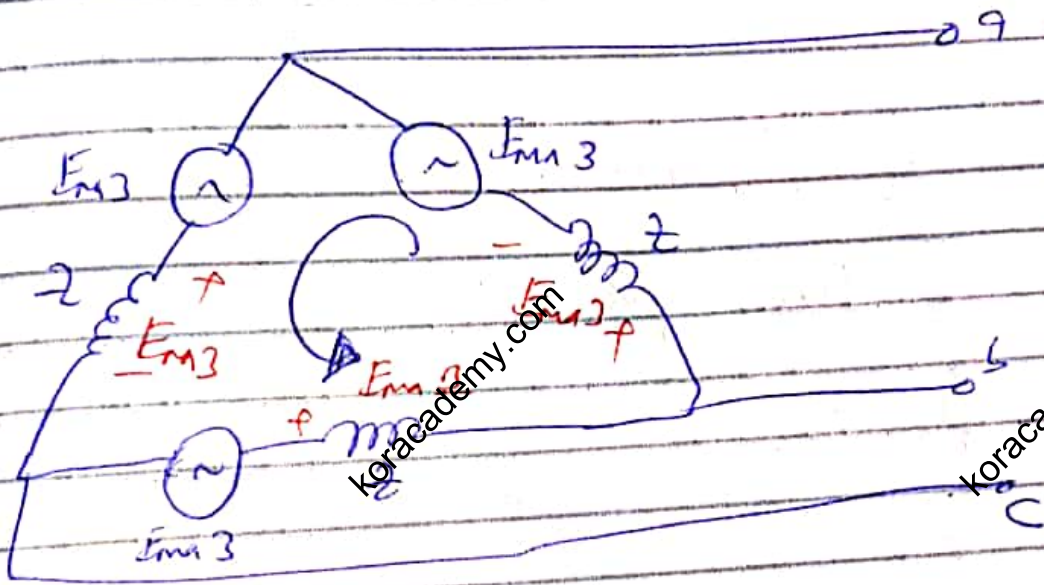1 $I_{c3} = \frac{E_{m3}}{Z} \rightarrow$ due to 3rd harmonic.



$$E_{ca} = 0, E_{bc} = 0, E_{ca} = 0$$

In delta connection, no 3rd harmonic in line and phase voltage both.
 (If it developed but would not exist s/c the circulating current will nullify it).

$$E_{Ph_{ms}} = E_{line_{ms}} = \sqrt{E_{Ph1}^2 + E_{Ph3}^2 + E_{Ph5}^2}$$