

POWER SYSTEM ANALYSIS


Power System 1

- Transmission line parameter.
- Performance of transmission line.
- Static power equation.
- Voltage control.
- Power factor correction.
- Distribution system.

Power System 2

- Fault.
- Stability.
- Load flow.

Single Line Diagram

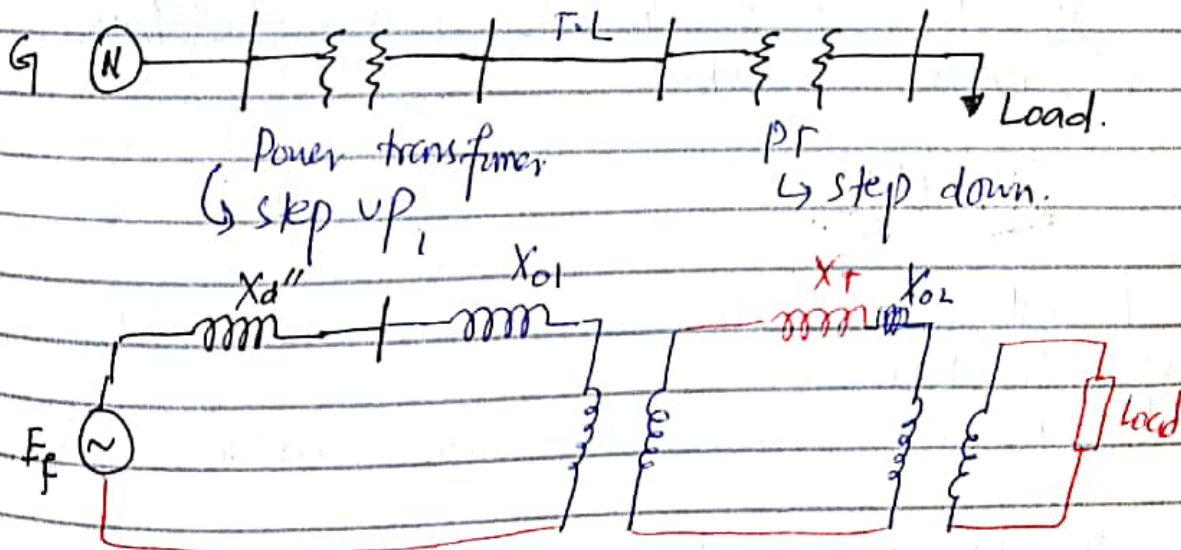

We do not have a series network b/c of transformer; so it is very difficult to find the solution. (current and voltages).

The solution to the problem is to represent the system in per unit.

$$\text{Per unit} = \frac{\text{Actual value}}{\text{Base value}}$$

Advantages of per unit?

- The ratings of devices are in kVs, MVAs so the calculations may be difficult.

In per unit, the range would be near to 1 (somewhat less or greater).

The reactance/resistance of transformer in pu is same in primary and secondary. which means that if we do not draw the magnetic part of circuit ($\oint \mathcal{E}$), still it would be fine, b/c the reactance on both sides (X_{01} and X_{02}) is same; so we can draw a series circuit.

Per Unit

Actual value will have a unit, i.e. say current eg 2A, 5A etc.

Base value will be the rated current.

Similarly for impedance, the actual value will be in ohms, whereas the base value will depend on its MVA and voltage rating.

Say impedance; $Z_{pu} = \frac{Z(\Omega)}{Z_b}$

where

$$Z_b = \frac{V_b}{I_b} = \frac{V_{rated}}{I_{rated}} \times \frac{V_{rated}}{V_{rated}} = \frac{V_{rated}^2}{VA}$$

$$\Rightarrow Z_{pu} = \frac{Z(\Omega)}{V_{rated}^2} \times (VA)$$

Normally the ratings are in MVA, not in VA.

$$\Rightarrow Z_{pu} = \frac{Z(\Omega) \times MVA}{(KV)^2}$$

(Note: The original image has some scribbles and corrections over this formula, including '3φ MVA' and 'per phase' written over 'MVA', and 'phase voltage' written over '(KV)^2'.)

pu values are unitless.

* pu quantities (values) are defined in per phase only. * Its not a 3φ value.

Transformers may be connected in star (Y) or delta (Δ).

Y Connection

$$\text{As } Z_{pu} = \frac{Z(\Omega) \times MVA}{(KV)^2}$$

(Annotations: '3φ MVA' above MVA, 'per phase' below MVA, 'phase voltage' below (KV)^2)

$$= Z(\Omega) \times \frac{MVA / 3}{\left(\frac{KV_L}{\sqrt{3}}\right)^2} \quad \boxed{Z_{pu} = Z(\Omega) \times \frac{3\phi MVA}{(KV_L)^2}}$$

D. Connection

$$Z_{pu} = Z_{(\Omega)} \times \frac{MVA}{(KV)^2} = Z_{(\Omega)} \times \frac{MVA/3}{(KV_L)^2}$$

b/c \downarrow
 ϕ and L V are equal.

$$\Rightarrow Z_{pu} = \frac{1}{3} Z_{(\Omega)} \times \frac{MVA}{(KV_L)^2}$$

Y Connection

$$Z_{pu} = Z_{(\Omega)} \times \frac{MVA}{(KV)^2}$$

✓
Chmic value does not depend on anything.
(MVA or KV ratings)


$$Z_{pu} \propto 3\phi MVA$$
$$Z_{pu} \propto \frac{1}{(KV)^2}$$

$$\frac{Z_{pu}(\text{new})}{Z_{pu}(\text{old})} = \frac{(MVA)_{\text{new}}}{(MVA)_{\text{old}}} \times \left(\frac{(KV_b)_{\text{old}}}{(KV_b)_{\text{new}}} \right)^2$$

$$\Rightarrow Z_{pu}(\text{new}) = Z_{pu}(\text{old}) \times \frac{(MVA)_{\text{new}}}{(MVA)_{\text{old}}} \times \left(\frac{V_b(\text{old})}{V_b(\text{new})} \right)^2$$

The pu impedance in primary and secondary is same?

Consider; $R_{01} = 1 \Omega$

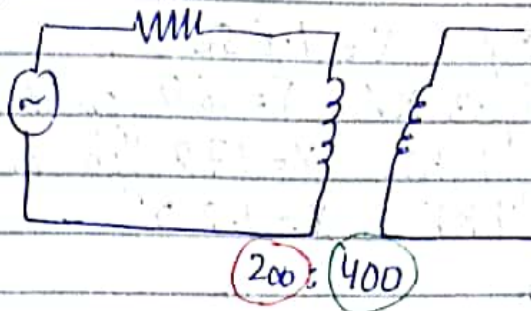


Rating = 1 KVA.

$$R_{01} (\text{pu}) = R_{01} (\Omega) \frac{VA}{V_b^2} = 1 \times \frac{1000}{(200)^2} = \frac{1}{40} \text{ pu}$$

b/c V_b of primary is 200

→ If R_{01} is referred to secondary;

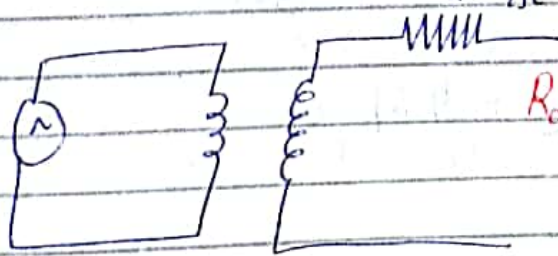

$$R_{01}' = R_{01} \times \left(\frac{N_2}{N_1} \right)^2$$

$$1 \times \left(\frac{400}{200} \right)^2 = 4 \Omega$$


$$R_{01}' (\text{pu}) = R_{01}' (\Omega) \times \frac{VA}{V_b^2} = 4 \times \frac{1000}{(400)^2}$$

$$\Rightarrow R_{01}' (\text{pu}) = \frac{1}{40} \text{ pu} \checkmark$$

Initially we were getting 3 lops in the diagram (eg);
So now with the help of pu, we draw a single diagram known as Reactance diagram.
(1 lap)

REACTANCE DIAGRAM

Case 1 When reactance are given in ohm.

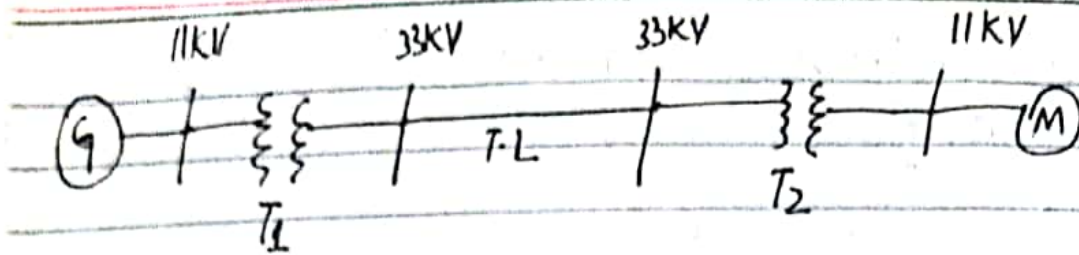

$$G: 30 \text{ MVA}, 11 \text{ KV}, X = 1.6 \Omega$$

$$T_1: 15 \text{ MVA}, 11/33 \text{ KV}, X = 16 \Omega / \text{ph on HV side.}$$

$$T_2: 15 \text{ MVA}, 33/11 \text{ KV}, X = 17 \Omega / \text{ph on LV side.}$$

$$M: 25 \text{ MVA}, 11 \text{ KV}, X = 1.2 \Omega$$

$$T.L: 20.5 \Omega / \text{ph}$$

Draw reactance diagram by taking any base value.

Considering 30 MVA, 11 KV as base. at generating station.


$$X_G (\text{pu}) = X_{\Omega} \times \frac{\text{MVA}_{\text{base}}}{(\text{KV}_b)^2} = 1.6 \times \frac{30}{11^2} = 0.396 \text{ pu}$$

$$X_{T_1} (\text{pu}) = \left(\frac{16 \times 30}{11^2} \right) \times X = 16 \times \frac{30}{33^2} = 0.44 \text{ pu}$$

$$X_{T_2} (\text{pu}) = 17 \times \frac{30}{11^2} = 4.21 \text{ pu}$$

$$X_{T.L} (\text{pu}) = 20.5 \times \frac{30}{33^2} = 0.564 \text{ pu}$$
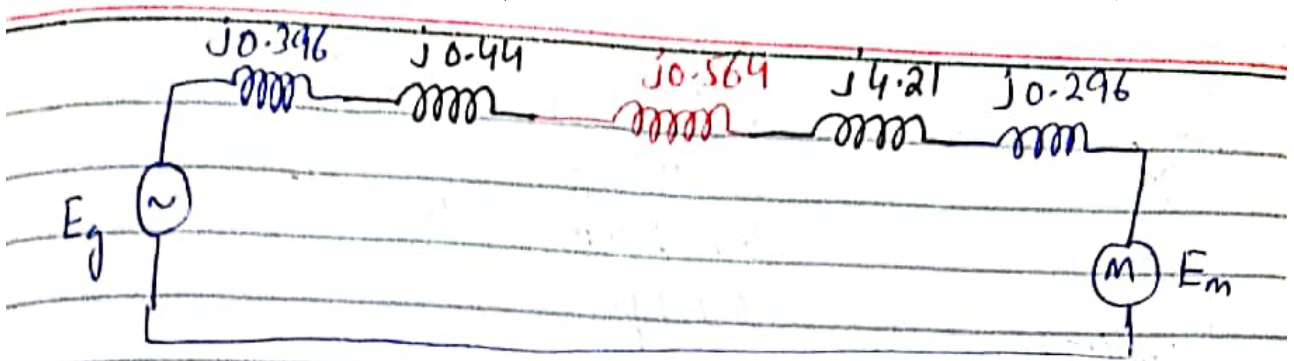
$$X_M (\text{pu}) = 1.2 \times \frac{30}{11^2} = 0.297 \text{ pu.}$$




considering 30MVA at 11 KV.

The pu values can be different but the actual value of current and voltage across each element will remain the same.

Case 2.

When reactances are given in per unit.

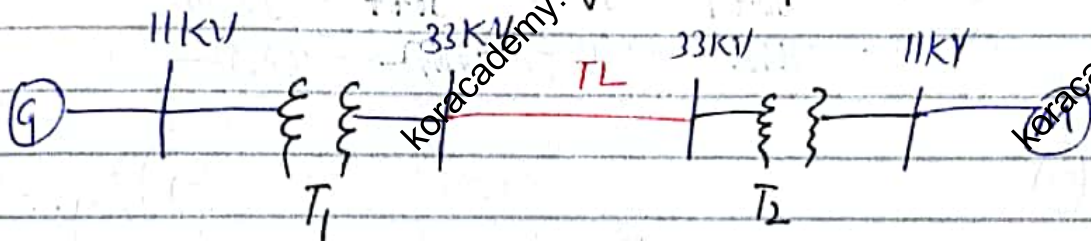

G : 30 MVA, 11 KV, $X = 0.2$ pu

T_1 : 15 MVA, 11/33 KV, $X = 0.1$ pu

T_2 : 15 MVA, 33/11 KV, $X = 0.1$ pu

M : 25 MVA, 11 KV, $X = 0.2$ pu

T.L: 26.5 Ω /ph

Draw reactance diagram taking 100MVA, 11 KV as base at G .

We know that;

$$Z_{pu(new)} = Z_{pu(old)} \times \frac{(MVA)_{new} \times \left(\frac{V_{s(old)}}{V_{b(new)}}\right)^2}{(MVA)_{old}}$$

$$Z_{pu(new)} = 0.2 \times \frac{100}{30} \times \left(\frac{11}{KV}\right)^2 = 0.67 \text{ pu}$$

$$X_{T1(new)} = 0.1 \times \frac{100}{15} \times \left(\frac{11kV}{11kV} \right)^2 = 0.67 pu$$


(or if secondary side $\left(\frac{33kV}{33kV} \right)^2$)

$$X_{T2 pu(new)} = X_{T1(new)} = 0.67 pu$$


↳ All ratings are same.

$$X_{M(new)} = 0.2 \times \frac{100}{25} \times \left(\frac{11kV}{11kV} \right)^2 = 0.8 pu$$
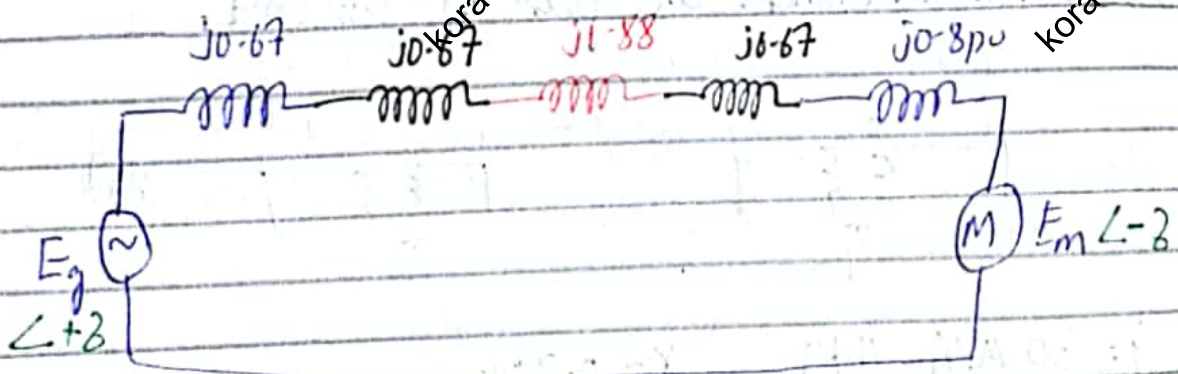
$$X_{T2} = X_{(T2)} \times \frac{MVA}{(kV)^2} = 20.5 \times \frac{100}{33^2} = 1.88 pu$$



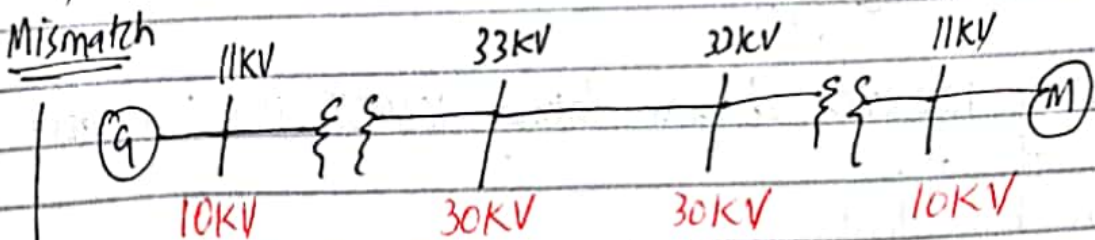* Case 3 Draw reactance diagram by taking 100MVA, 10kV as base for data in Q2.



When $V_{old} \neq V_{new}$

$$X_{G(new)} = 0.2 \times \frac{100}{30} \times \left(\frac{11}{10} \right)^2 =$$

$$X_{r_{new}} = 0.1 \times \frac{100}{15} \times \left(\frac{11}{10}\right)^2 =$$

$\left(\frac{33}{30}\right)^2$

$$X_{TL_{new}} = X_{r_{new}}$$

$$X_{m(new)} = 0.2 \times \frac{100}{25} \times \left(\frac{11}{10}\right)^2 =$$


$$X_{T_{ps}} = 20.5 \times \frac{100}{(30)^2} =$$

3 ϕ Symmetrical Fault

A fault is known as symmetrical fault after the fault the magnitude as well as the phase difference w.r. the voltages will remain same as before the fault.



Consider,

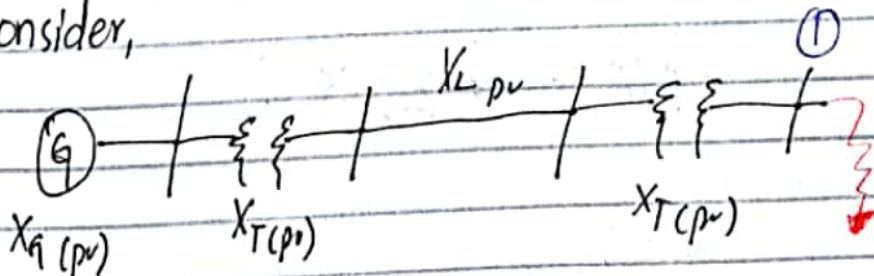


Assumption pu value is given on common base.

Consider a fault occurs at bus (1).

We see that no load is connected \Rightarrow the current flowing in the TL prior to fault is zero.

So after the fault, a current (fault current) will flow.

First draw the reactance diagram;

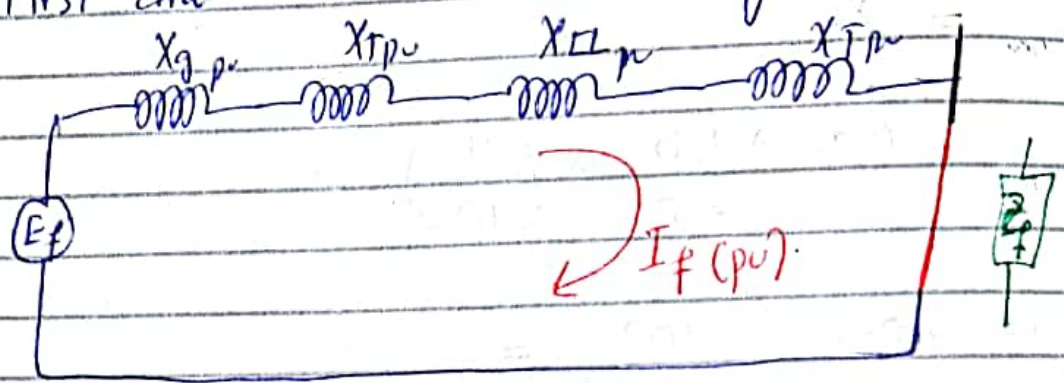

We will also have some fault impedance (means the fault/line has not directly touched the ground).

→ If not given, consider it zero.

$$I_f (pu) = \frac{E_f (pu)}{X_{eq} (pu) + Z_f (pu)}$$

As $pu = \text{Actual} / \text{Base}$

$$\Rightarrow I_f (A) = I_f (pu) \times I_b$$

If three phase power;


$$\sqrt{3} V_L I_L = 3\phi \text{ MVA}$$

$$\Rightarrow I_b = \frac{\text{MVA}}{\sqrt{3} V_L}$$

$$\Rightarrow I_f (A) = I_f (pu) \times \frac{\text{MVA}}{\sqrt{3} V_L}$$

Short Circuit MVA is used to define the rating of a circuit breaker.

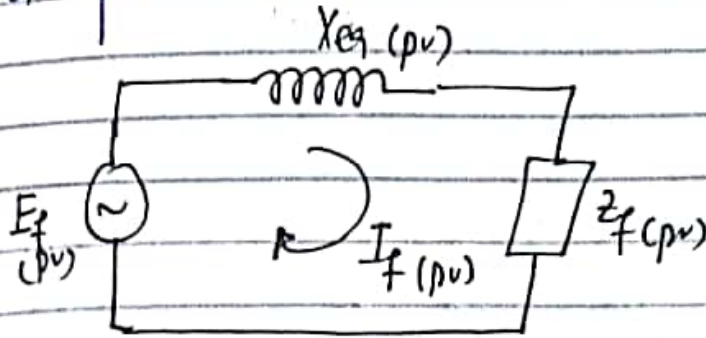→ The amount of power that can flow when a fault occurs.



1st method

$$\text{SCMVA} = \sqrt{3} E_f I_f$$

Actual.

2nd method


$$(\text{SCMVA})_{pu} = E_f (pu) \times I_f (pu)$$

$$\text{For } 3\phi; (\text{SCMVA})_{pu} = 3 E_f (pu) \times I_f (pu) \times X$$

$$(\text{SCMVA})_{\text{actual}} = (\text{SCMVA})_{pu} \times (\text{3}\phi \text{MVA})_{\text{base}}$$

pu values are defined per phase only.


Q. Find SCMVA;

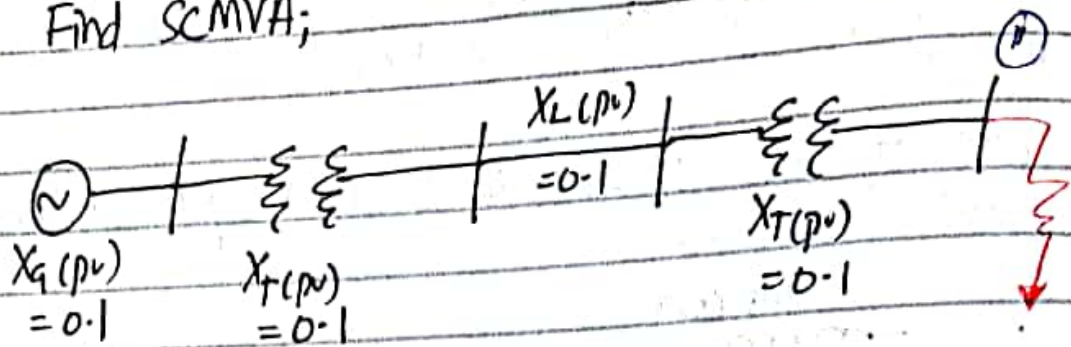

50MVA, $E_f = 11\text{KV}$

Method 1 Fault current = ?

Reactance diagram;

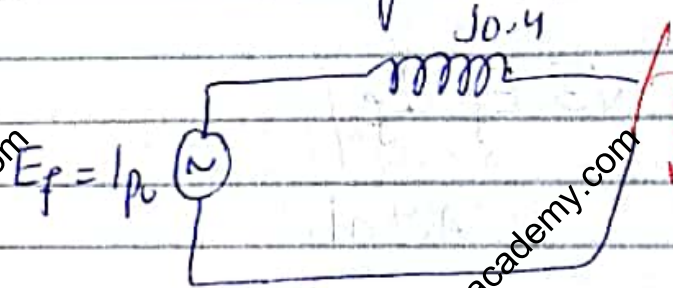

$$I_{f(pu)} = \frac{E_f(pu)}{X_{total}}$$

$$= \frac{1}{j0.4}$$

$$\Rightarrow I_{f(pu)} = -j 2.5 \text{ pu} = 2.5 \text{ pu} \angle -90^\circ$$

$$\Rightarrow I_{f(\text{actual})} = I_{f(pu)} \times \frac{\text{MVA}}{\sqrt{3} V_L} = 2.5 \times \frac{50 \times 10^6}{\sqrt{3} \times 11 \times 10^3}$$

$$\Rightarrow I_{f(\text{actual})} = 6.56 \text{ KA}$$

$$\begin{aligned} \text{SCMVA} &= \sqrt{3} \times V_L \times I_f \\ &= \sqrt{3} \times 11 \times 10^3 \times 6.56 \times 10^3 \end{aligned}$$

$$\text{SCMVA} = 125 \text{ MVA}$$

Method 2

$$I_f (pu) = \frac{1}{j0.4} = -j2.5 pu$$

$$(SCMVA)_{pu} = E_f (pu) \times I_f (pu)$$

$$= 1 \times 2.5 = 2.5 pu$$

$$(SCMVA)_{actual} = 2.5 pu \times (base) = 500$$

$$= 125 MVA$$


Method 3 (MVA method)

In this method, we find the SCMVA of all the equipment individually

$$SCMVA = \frac{MVA}{pu}$$

	MVA	X _{pu}	SCMVA
Generator	50	j0.1	500
X _{former}	50	j0.1	500
T.L	50	j0.1	500

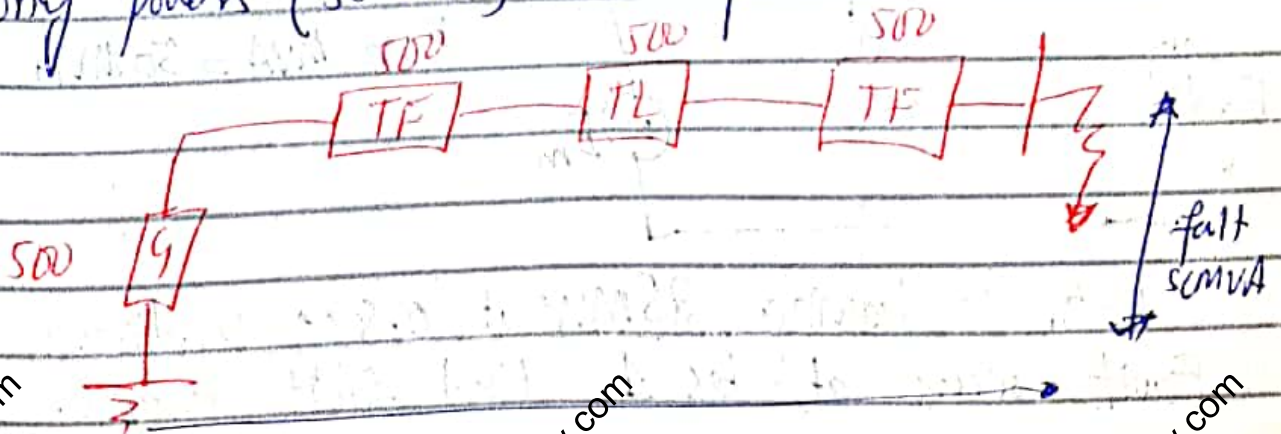Now we draw the equivalent MVA circuit, in which only powers (SCMVA) are represented.



As for a number of same capacitors connected in series;

$$C_{eq} = \frac{C}{n}$$

$$\Rightarrow \text{SCMVA} = \frac{500}{4} = 125 \text{ MVA}$$

→ If the reactances are given in ohms?

$$\text{SCMVA} = \frac{\text{MVA}}{X_{pu}} = \frac{\text{MVA} \times (\text{kV})^2}{X(\Omega) \times \text{MVA}}$$


$$\Rightarrow \boxed{\text{SCMVA} = \frac{(\text{kV})^2}{X(\Omega)}}$$

We can also find the fault current easily;

$$\text{ie } \text{SCMVA} = E_{pu} \times I_f(\text{pu})$$

$$= \sqrt{3} E_L \times I_f(\text{A})$$

Thevenin Concept

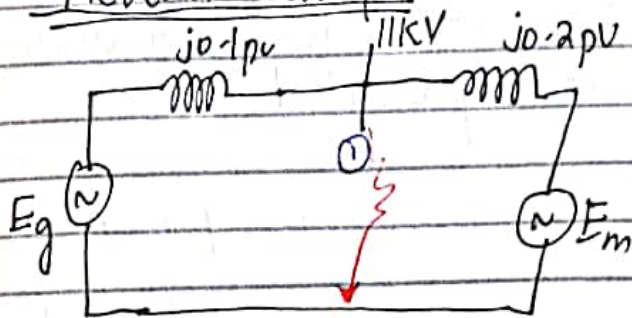


Base MVA = 50 MVA

Motor is drawing 25 MW at 0.8 pf leading.
Fault occurs at bus 1. Find fault current.

needed

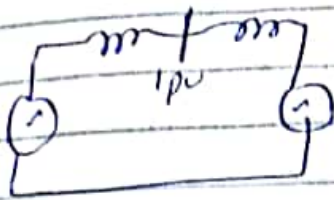First we need to find current before fault.



$$V_{pu} = \frac{11 \text{ kV}}{11 \text{ kV}} = 1 \text{ pu}$$

$$P_m = \frac{25}{50} = 0.5 \text{ pu}$$

MW = MVA

PF

$$\text{Now } V_{pu} I_{pu} \cos \phi = P = 0.5$$

$$I_{pu} = \frac{0.5}{1 \times 0.8} = 0.625 \angle 36.86^\circ$$

$$E_g = (V_{pu} + I_{pu} \times j0.1)$$


$$= 1 + 0.625 \angle 36.8^\circ \times j0.1$$

$$E_g = 0.9638 \angle 2.97$$

$$E_m = 1 - j0.2 \times 0.625 \angle 36.86$$

$$= 1.0796 \angle -5.315$$

The after fault circuit will be as;

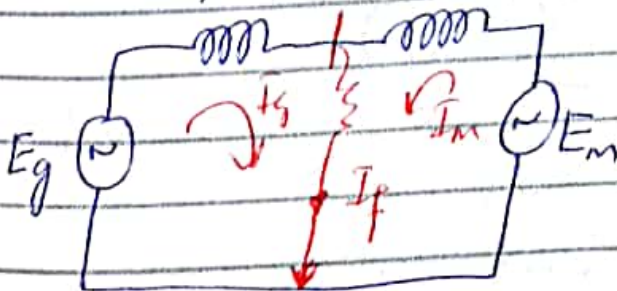

The current delivered by the ~~fault~~ ^{gen} will not reach the load (motor)

and motor will also behave

as generator and supply power to the short circuit path.

$$I_f = I_g + I_m$$

$$I_f = \frac{E_g}{j0.1} + \frac{E_m}{j0.2}$$

$$= 9.638 \angle -87.03^\circ + 5.398 \angle -95.315^\circ$$



$$\rightarrow I_f = 14.999 \angle -90^\circ$$

(If system was not loaded, $E_g = 1 \text{ pu}$ no E_m)

Using Thevenin concept;


The pre fault circuit

OR

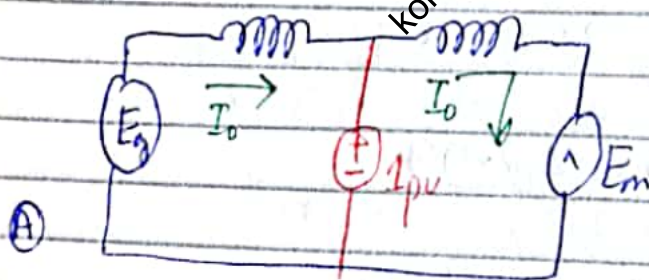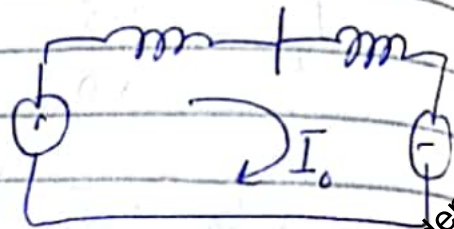

No current will flow through the 1 pu voltage source.

The circuit after fault will be;

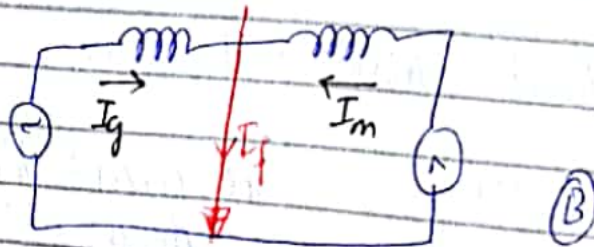

Say we short E_g and E_m ,



The superposition of (A) and (C) will give us current after the fault is (B).

Now if add together (algebraic sum) the currents of (A) and (C), it will give us the current in (B).

$$\text{ie } I_g = I_0 + \Delta I_g$$
$$\text{and } I_m = -I_0 + \Delta I_m$$

$$\Rightarrow I_f = I_g + I_m = \boxed{\Delta I_g + \Delta I_m} = I_f$$

The polarity is opposite so that when it is superimposed, it becomes a shunted path.

From fig; $\Delta I_g = \frac{1}{j0.1} = -j10 \text{ pu}$


$$\Delta I_m = \frac{1}{j0.2} = -j5 \text{ pu}$$

$$\Rightarrow I_f = -j15 \text{ pu} = 15 \text{ pu} < -90^\circ$$

Similarly, $(SCMVA)_{pu} = E_{(pu)} \times I_f \text{ (pu)}$
 $= (0.9638 \times 15)$

of the same.

Questions.

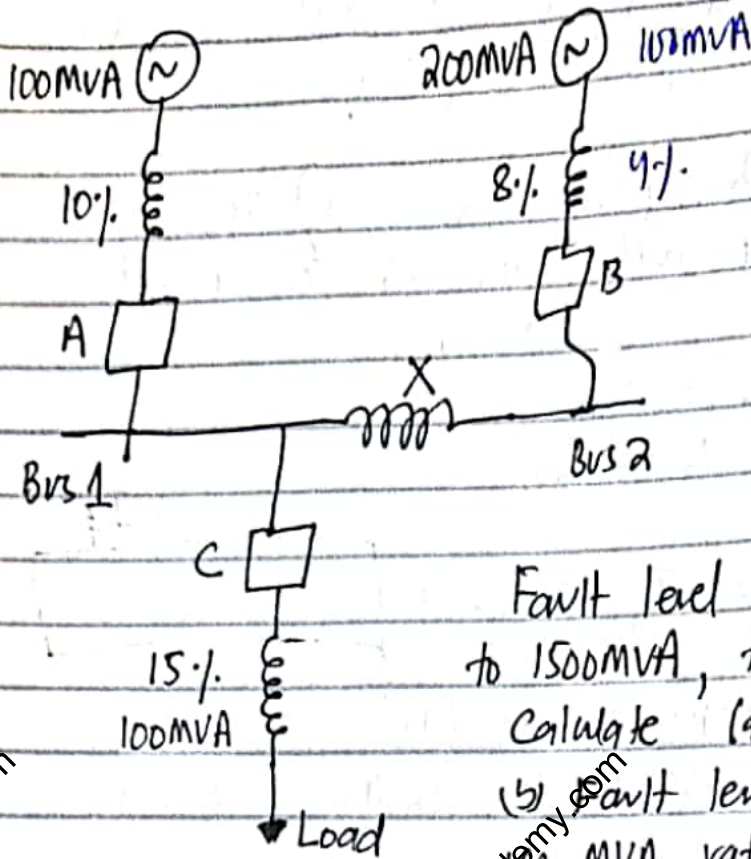

Fault level on Bus 1 is restricted to 1500MVA, take 100MVA base.
 Calculate (a) Reactor X
 (b) Fault level on bus 2.
 (c) MVA rating of CB 'C'

On 100MVA

$$SCMVA = 1500 \text{ MVA}$$


$$(SCMVA)_{pu} = \frac{1500}{100} = 15 \text{ pu} = E_{f(pu)} \times I_{f(pu)}$$

$$E_{pu} = 1 \text{ pu}$$

$$\Rightarrow I_{f(pu)} = 15 \text{ pu at bus 1.}$$

$$\text{As } I_{f(pu)} = \frac{E_{(pu)}}{X_{(pu)}} \Rightarrow X_{(pu)} = \frac{1}{15}$$

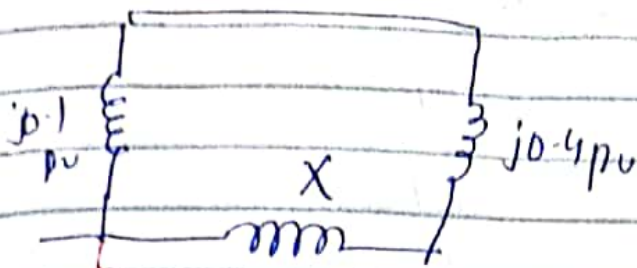If fault occurs at bus 1, the net reactance diagram is shown as:



$$X_{eq} = \frac{1}{15} \text{ pu}$$

$$(0.04 + X) \parallel 0.1 = \frac{1}{15}$$

$$\frac{(0.04 + X)(0.1)}{0.04 + X + 0.1} = \frac{1}{15}$$

$$\Rightarrow X = j0.16 \text{ pu}$$

(b) SCMVA in bus 2 = ?

$$X_{eq} = (0.1 + 0.16) \parallel 0.04$$


$$X_{eq} = \frac{0.26 \times 0.04}{0.26 + 0.04} = j0.3467 \text{ pu}$$

$$I_f (\text{pu}) = \frac{E (\text{pu})}{X (\text{pu})} = \frac{1}{j0.3467} = 28.84 \text{ pu} \quad \angle -90^\circ$$

$$\text{Now, } (SCMVA)_{pu} = E_f (\text{pu}) \times I_f (\text{pu}) = 28.84 \text{ pu}$$

$$(SCMVA)_{act} = 28.84 \text{ MVA}$$


Repeating by MVA method;

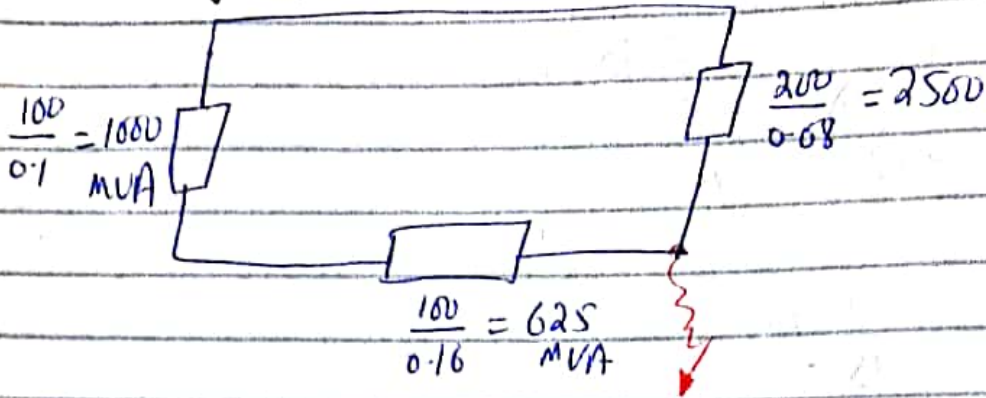

$$SCMVA = \left(\frac{1000 \times 625}{1000 + 625} \right) + 2500$$

$$\Rightarrow \boxed{SCMVA = 2884 \text{ MVA}}$$

(c)

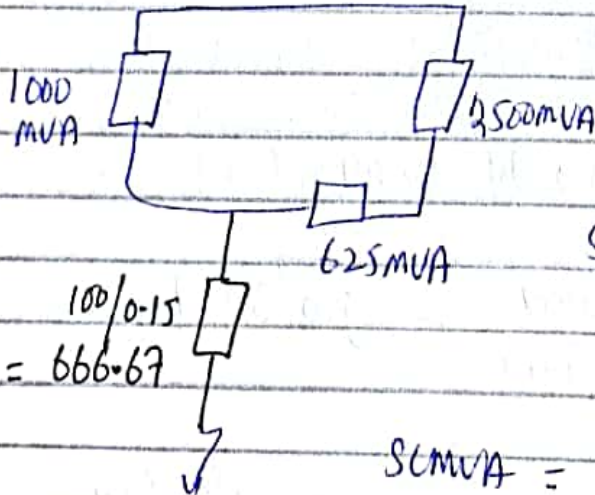


$$SCMVA = \left(\frac{2500 \times 625}{3125} \right) + 1000$$

= 1500 half

$$SCMVA = \frac{1500 \times 666.67}{1500 + 666.67}$$
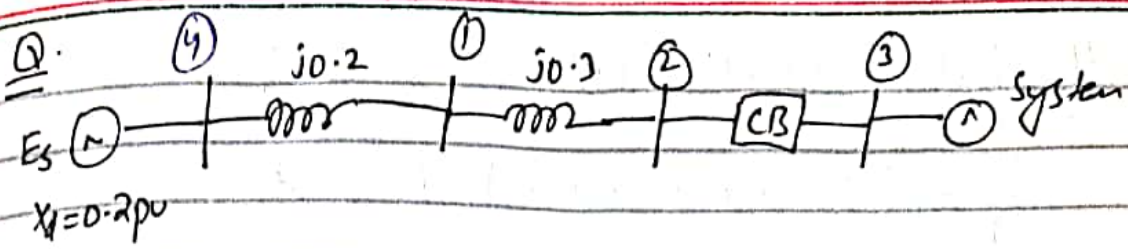
$$\Rightarrow \boxed{SCMVA = 461.53 \text{ MVA}}$$




3 ϕ fault current at bus 1 is 5 pu.
 Find fault current at bus 3.

$$I_f (pu) = 5 pu = \frac{E (pu)}{X_{eq} (pu)} = \frac{1}{X_{eq} (pu)}$$

$$\Rightarrow X_{eq} (pu) = \frac{1}{5} = 0.2 pu$$

→ across bus 3

Reactance diagram

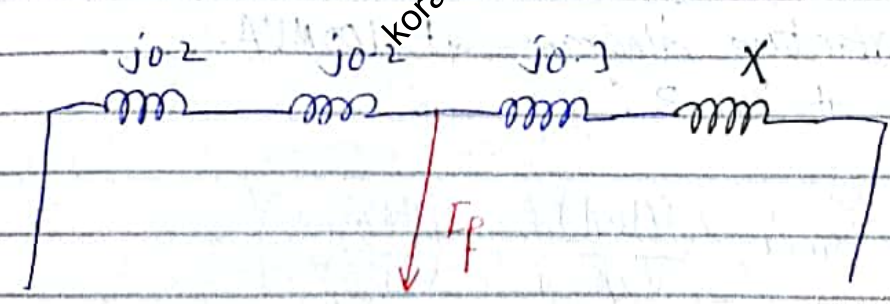

$$0.4 \parallel 0.3 + n = \frac{(0.4)(0.3 + n)}{0.7 + n} = 0.2$$

$$\Rightarrow X = \frac{1}{10} = 0.1 pu$$

If fault occurs at bus 3;

$$X_{eq} = 0.7 \parallel 0.1 = \frac{7}{80} pu$$


$$I_f (M) = \frac{I_f (M)}{X_{pu}} = \frac{1.4}{7/80} = 1.4 pu$$

If fault occurs at bus (1),

$$X_{eq} = (0.1 + 0.2 + 0.3) \parallel 0.2$$

$$I_f = \frac{1}{X_{eq}}$$

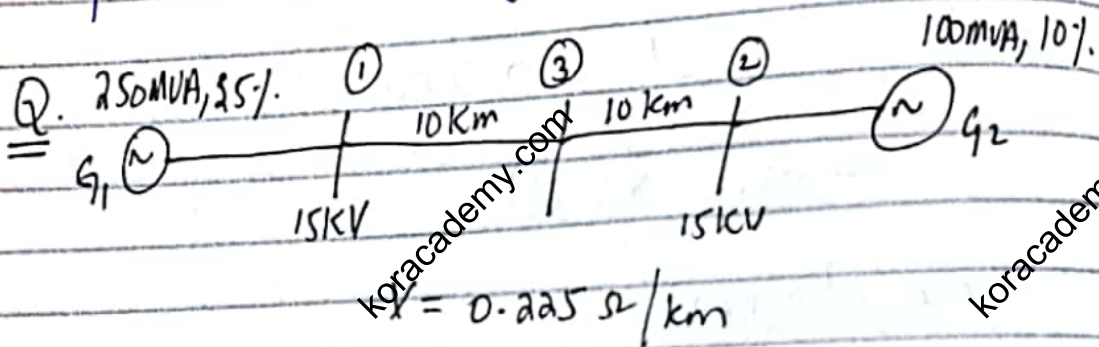If base MVA is given, we can find SC MVA.



- Draw reactance diagram at 100 MVA.
- SC MVA at Bus 3.


$$X_{G1_{new}} = X_{G1_{old}} \times \frac{(MVA)_{new}}{(MVA)_{old}} \times \left(\frac{(KV_b)_{old}}{(KV_b)_{new}} \right)^2$$

$$= 0.25 \times \frac{100}{250} \times \left(\frac{15}{15} \right)^2 = j0.1$$

$$X_{G2} = j0.1 \text{ pu}$$

$$X_{TL} = 0.225 \times 10 = 2.25 \text{ ohm}$$
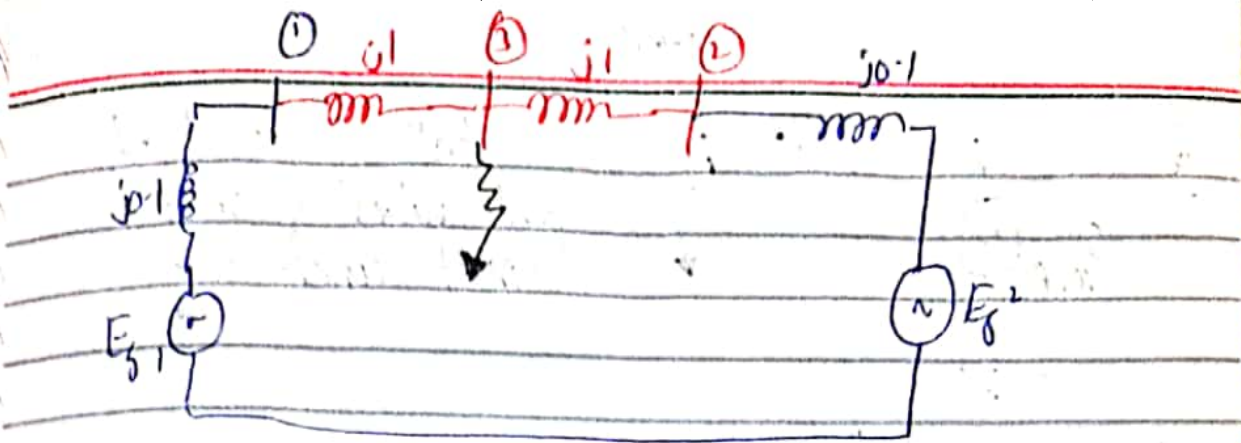
$$X_{TL(\text{pu})} = \frac{2.25 \times 100}{15^2} = j 1 \text{ pu}$$



$$(b) X_{eq} = (j0.1 + j1) \parallel (j0.1 + j1) = \frac{1.1 \times 1.1}{2.2}$$


$$\Rightarrow X_{eq} = \cancel{1.8182} \text{ pu} = 0.55 \text{ pu}$$

$$I_{f(p.u)} = \frac{1}{X_{pu}} = \frac{1}{0.55} = 1.8181 \text{ pu}$$

$$\text{SCMVA}_{pu} = E_{f1} \times I_{f1} = 1.8181 \text{ pu}$$

$$\text{SCMVA} = 1.8181 \times 100 = \boxed{181.81 \text{ MVA}}$$

Or by shortest MVA method.

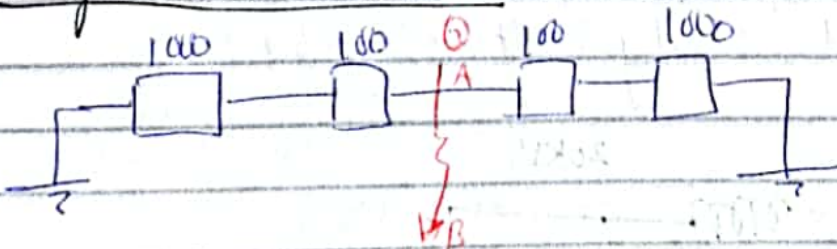


$$\text{SCMVA} = \frac{1000 \times 1000}{1100} + \frac{100 \times 100}{100 + 100} = 181.81 \text{ MVA}$$

$X_d \rightarrow$ Reactance at steady state.

$X_d'' \rightarrow$ Subtransient reactance.

$X_d' \rightarrow$ transient reactance.

$$\boxed{X_d'' < X_d' < X_d}$$

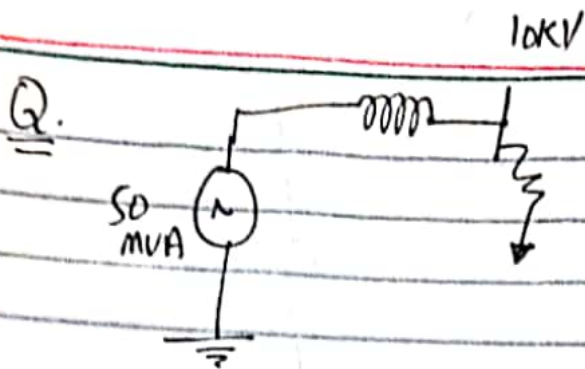

Ratio of initial and final values of short circuit current = ?


$$X_d = j1 \text{ pu}, \quad X_d'' = j0.2 \text{ pu}$$

$$I_{\text{initial}} I_f = \frac{1}{X_d''} = \frac{1}{j0.2} = -j5 \text{ pu}$$

$$I_{\text{final}} I_f = \frac{1}{X_d} = \frac{1}{j1} = -j1$$

$\frac{I_{\text{initial}}}{I_{\text{final}}} = 5$

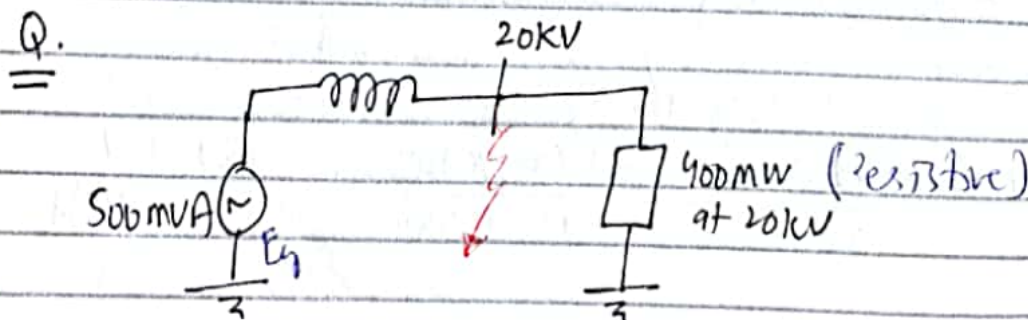At fault we take X_d'' , after 3 to 4 cycles we take X_d' and after 6 to 7 cycles we take about steady state i.e. X_d .



$$X_d'' = 0.2 \text{ pu}, \quad X_d = 1 \text{ pu}$$

Find initial rms current of generator when symmetrical fault occurs at load terminal.

→ When E_g is not given, we cannot find the fault current; in loading condition.

→ Under no load condition, $E_g = 20 \text{ kV}$ and no current will flow

But here loaded $\rightarrow E_g > 20 \text{ kV}$

Re Fault Case

$$P_{(pu)} = \frac{400}{500} = 0.8 \text{ pu} = V_{pu} I_{pu} \cos\phi$$

Resistive load $\Rightarrow \cos\phi = 1$

$$\text{Also } V_{pu} = 20/20 = 1 \text{ pu}$$

$$\Rightarrow I_{pu} = 0.8$$

$\rightarrow X$

$$E_g = 1 \angle 0^\circ + 0.8 \angle 0^\circ \times 1 \text{ pu}$$


$$E_g = 1.28 \angle 38.65^\circ$$

No fault


$$I_{f(pu)} = \frac{E_g(pu)}{X_d''} = \frac{1.28}{0.2}$$

$$\Rightarrow I_{f(pu)} = 6.4 \text{ pu}$$

Doing using Thevenin Concept

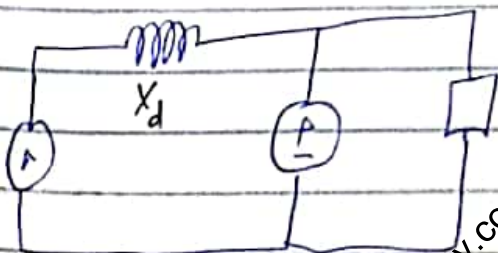

pre fault

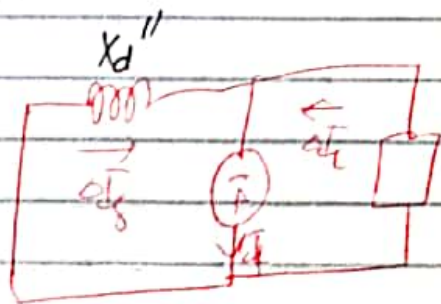

Thevenin


$$I_f = I_f + I_L$$

$$I_f = -j5 + 1 < 0 = 5.09 \text{ pu} \quad \text{purely } 6.47 \text{ ?}$$

This is 5/c in one circuit we have X_d and in the other we have X_d'' .

So for superposition we need them to be same.

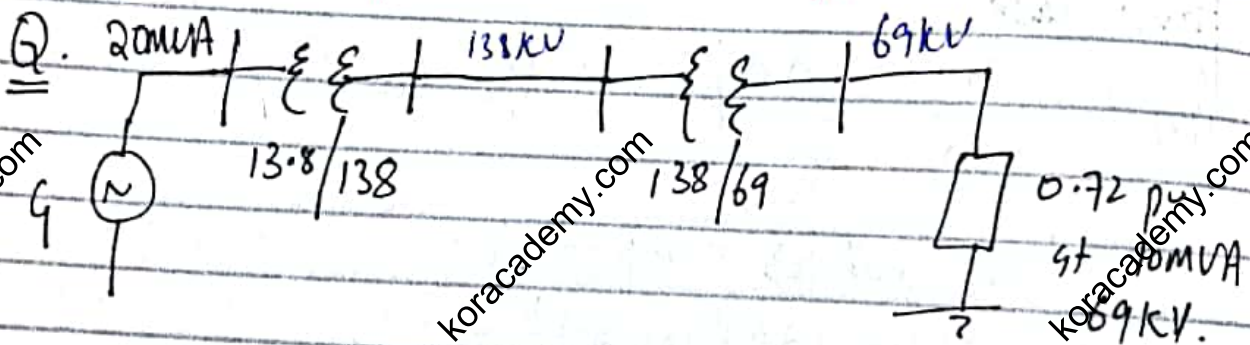So Thevenin concept cannot be applied here.



The eq value of load at gen end will be ?

$$X_{pu(new)} = X_{pu(old)} \frac{(MVA)_{new}}{(MVA)_{old}} \left(\frac{(kV)_old}{(kV)_{new}} \right)^2$$



$$= (0.72) \left(\frac{20}{10} \right) \left(\frac{69}{13.8} \right)^2$$

$$\Rightarrow \boxed{X_{pu(new)} = 36 \text{ pu.}}$$


LOAD FLOW STUDIES

Ybus matrix \rightarrow stability analysis.
 Zbus matrix \rightarrow fault analysis.

Consider;

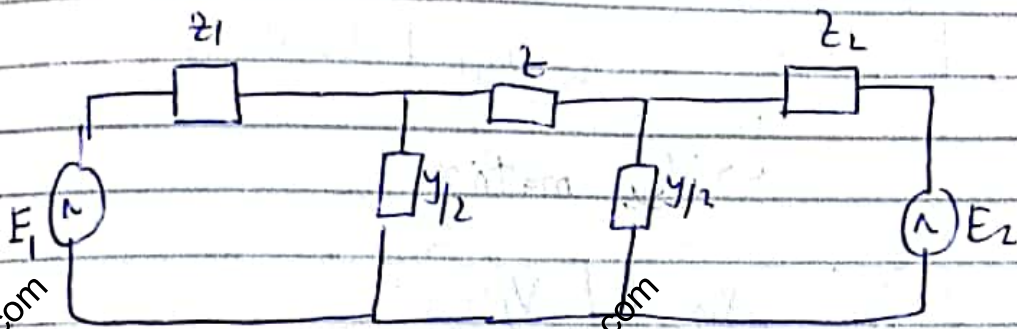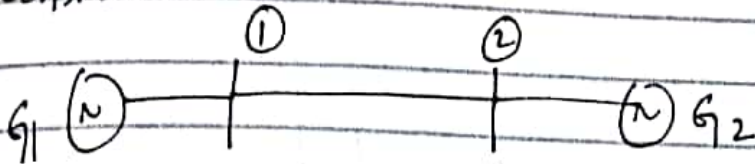


Converting to current source;

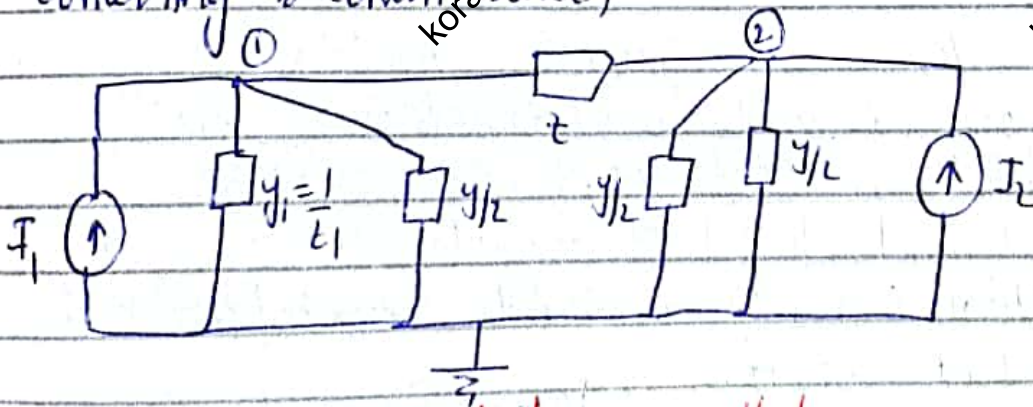

Admittance \rightarrow added in parallel.

$$y_1 + y_{1/2} = y_{10} \rightarrow \text{Adm of bus 1 wrt ground.}$$
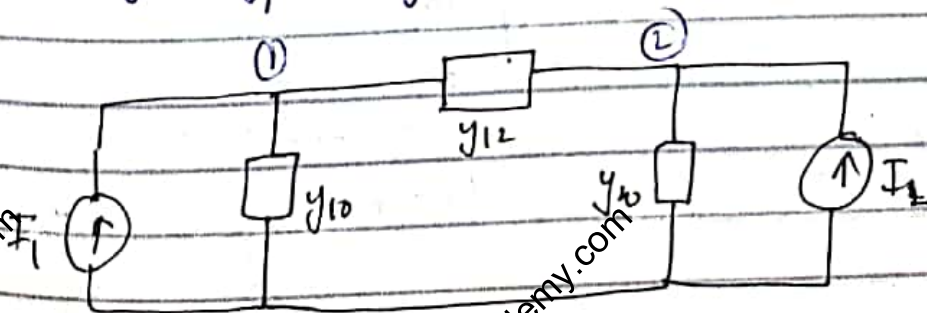
$$y_2 + y_{2/2} = y_{20} \rightarrow \text{Adm of bus 2 wrt ground.}$$



$$I_1 = (Y_{11} - Y_{12})V_1 + (Y_{11} - 0)V_2$$

$$\Rightarrow I_1 = (Y_{10} + Y_{12})V_1 - Y_{12}V_2$$

$$I_2 = -Y_{12}V_1 + (Y_{20} + Y_{12})V_2$$


In matrix form;

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{10} + Y_{12} & -Y_{12} \\ -Y_{12} & Y_{20} + Y_{12} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

↳ Y_{bus} matrix

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

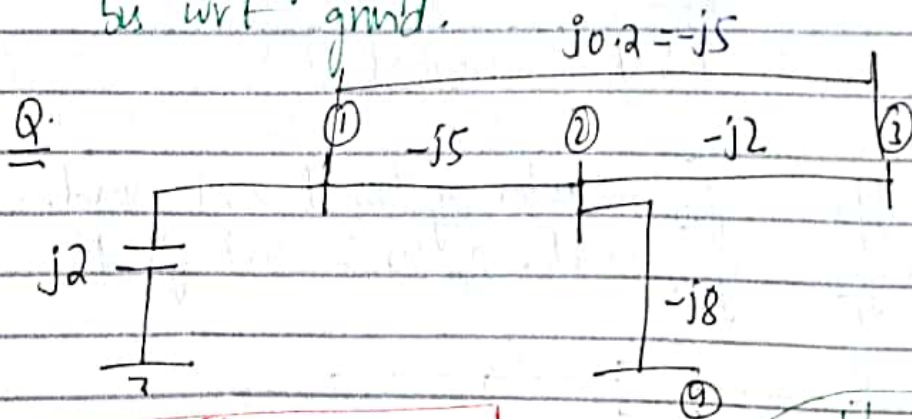- ① The Y_{bus} is a symmetric matrix
- ② Diagonal element is summation of admittance connected at that bus.
- ③ Off diagonal element = - (adm s/w two buses)
- ④ Addition of row/column = Adm connected at that bus wrt ground.



— adm —

$$Z = R + j\omega L = j\omega L$$

$$Z = j() \text{ } \mu$$

$$Y = -j() \text{ } \mu$$

$$X_c = Z_c = \dots / j\omega C = -j$$

$$Y = g() + \dots$$

$$Y = \frac{1}{R} + jB$$

↳ susceptance

$$y_{12} = -j5, \quad y_{23} = -j2, \quad y_{24} = -j8$$

$$y_{10} = j2$$

$$\begin{bmatrix} y_{12} + y_{10} & -y_{12} & -y_{13} & -y_{14} \\ -y_{21} & y_{23} + y_{12} + y_{24} & -y_{23} & -j24 \\ -y_{31} & -y_{32} & y_{23} & -y_{34} \\ -y_{41} & -y_{42} & -y_{43} & y_{24} \end{bmatrix}$$

$$\begin{bmatrix} -j3 & +j5 & 0 & 0 \\ +j5 & -j15 & +j2 & +j8 \\ 0 & j2 & -j2 & 0 \\ 0 & j8 & 0 & -j8 \end{bmatrix}$$

$Y_{bus} \rightarrow$ Sparse matrix \rightarrow many elements = zero
less storage

Now if another X_{trans} line n added s/w
(1) and (2) with $X = j0.2$

The new Y_{bus} matrix will be;

$$\begin{bmatrix} -j8 & +j5 & +j5 & 0 \\ +j5 & -j15 & j2 & j8 \\ +j5 & j2 & -j7 & 0 \\ 0 & j8 & 0 & -j8 \end{bmatrix}$$

Classification of Bus

1. Slack bus / Reference bus / Swing bus

known = V, δ

unknowns = P, Q

Slack bus is a generator bus only.

$$P_{\text{slack}} + P_{\text{gen}} = P_{\text{loss}} + P_{\text{demand}}$$

$$P_{\text{slack}} = P_{\text{demand}} + P_{\text{loss}} - P_{\text{gen}}$$

2. Generator bus / PV bus

known = P, V

unknowns = Q, δ

$$\text{No. of PV bus} = \text{Total no. of buses} - 1$$

For i^{th} bus,

$$Q_{gi \text{ min}} < Q_{gi} < Q_{gi \text{ max}}$$

If this condition is violated

$$Q_{gi} < Q_{gi \text{ min}} \rightarrow Q_{gi} = Q_{gi \text{ min}}$$

$$Q_{gi} > Q_{gi \text{ max}} \rightarrow Q_{gi} = Q_{gi \text{ max}}$$

\rightarrow PV bus is converted to PQ bus.

3. Load Bus / PQ bus


$P, Q = \text{known}$ $V, \delta = \text{unknown}$

$$\text{No. of PQ bus} = \text{Total buses} - \text{Slack bus} - \text{PV bus}$$

4. Voltage Controlled bus.

The bus where compensation is applied for voltage control.

Type of PV bus -

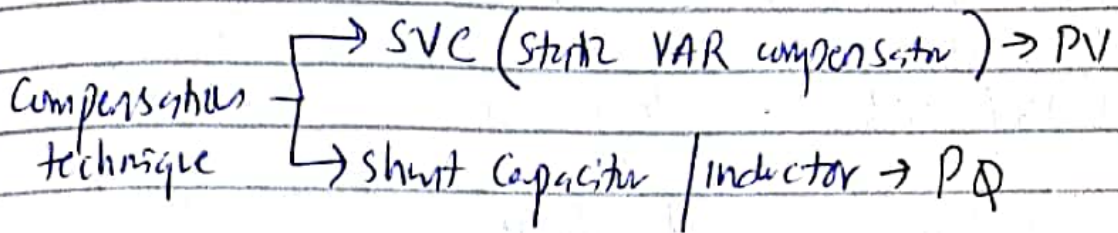

Q. 100 buses, 10 gen buses; size of Jacobian.

$$\text{Jacobian} = (2PQ + PV) \times (2PQ + PV)$$

$$\text{Gen bus} = 10 \begin{cases} 1 \text{ slack} \\ \text{PV bus} = 9 \end{cases}$$


$$\begin{aligned} \text{PQ bus} &= \text{total} - \text{gen buses} \\ &= 100 - 10 = 90 \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{Jacobian matrix size} &= (2 \times 90 + 9) \\ &= 189 \times 189 \end{aligned}$$

Symmetrical Fault: The voltages and currents are displaced at 120° before and after the fault.


Unsymmetrical Fault: The voltages and currents before the fault are 120° displaced whereas after the fault their magnitude is also different and they are not at 120° .

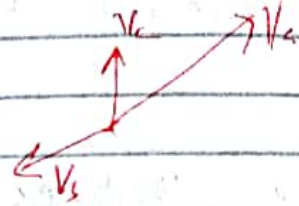- ↳ Line to ground fault
- ↳ Double line to ground fault
- ↳ Line to line fault.



Fortescue Theorem

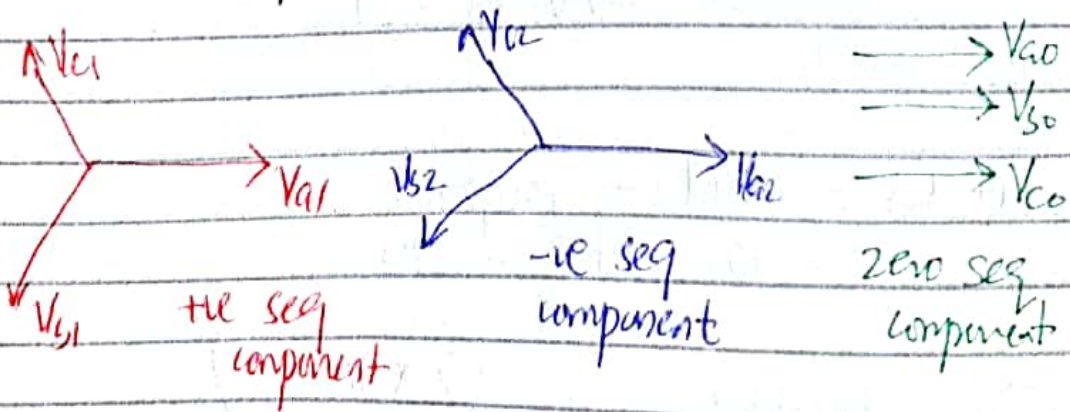We can resolve n unsymmetrical phasors into $n-1$ symmetrical phasors and one cophasal.



$$\begin{aligned}
 V_a &= V_{a1} + V_{a2} + V_{a0} \\
 V_b &= V_{b1} + V_{b2} + V_{b0} \\
 V_c &= V_{c1} + V_{c2} + V_{c0}
 \end{aligned}$$

Shift operator; $a = 1 \angle 120^\circ$, $a^2 = 1 \angle 240^\circ$

$$1 + a + a^2 = 0$$

$$V_{b0} = V_{a0} \quad , \quad V_{b1} = |V_{a1}| \angle 240^\circ = a^2 V_{a1}$$

$$V_{b2} = a V_{a2} \quad , \quad V_{c0} = V_{a0} \quad , \quad V_{c1} = a V_{a1}$$

$$V_{c2} = a^2 V_{a2}$$

$$\Rightarrow V_a = V_{a0} + V_{a1} + V_{a2}$$

$$V_b = V_{a0} + a^2 V_{a1} + a V_{a2}$$

$$V_c = V_{a0} + a V_{a1} + a^2 V_{a2}$$

In matrix form;

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}$$

$$[V]^{abc} = [A] [V]^{012}$$

$$\Rightarrow [V]^{012} = [A]^{-1} [V]^{abc}$$

$$\Rightarrow \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

Similarly for currents;


$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

and

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

- Star = 3 phase 4 wire system.
- Delta = 3 phase 3 wire system.

consider a star connection;

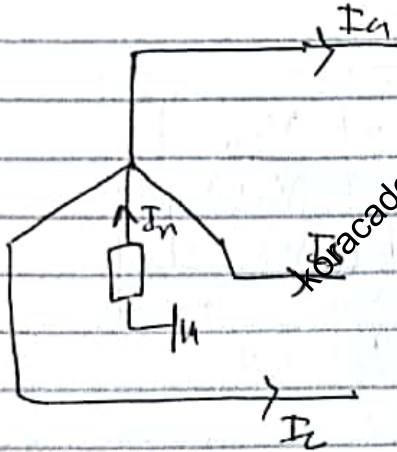

$$I_n = I_a + I_b + I_c$$

$$\begin{aligned} \textcircled{1} \quad V_{ab0} &= \frac{1}{3} [V_{a0} + V_{b0} + V_{c0}] \\ &= \frac{1}{3} [V_a - V_b + V_b - V_c + V_c - V_a] \\ &= 0 \end{aligned}$$

No zero sequence component of line voltage in star connection.

$$\textcircled{1} \quad I_n = I_a + I_b + I_c$$


$$I_n = [I_{a0} + I_{a1} + I_{a2}] + [I_{a0} + a^2 I_{a1} + a I_{a2}] + [I_{a0} + a I_{a1} + a^2 I_{a2}]$$

$$= 3 I_{a0} + I_{a1} (1 + a + a^2) + I_{a2} (1 + a + a^2)$$

$$\Rightarrow \boxed{I_n = 3 I_{a0}}$$

In neutral component unit, the zero seq components are absent.

Consider a delta connection;

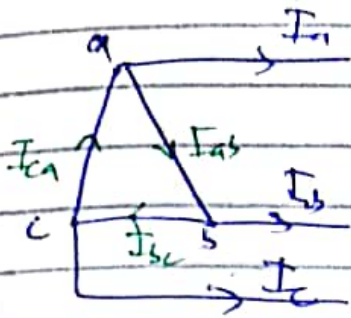

$$\textcircled{1} \quad I_n = 0$$

$$\textcircled{2} \quad I_{ab} = [I_{ab0} + I_{ab1} + I_{ab2}]$$

Zero seq component of current is present in phase.

$$\textcircled{3} \quad I_a = [I_{ca} - I_{ab}], \quad I_b = [I_{ab} - I_{bc}]$$

$$I_c = [I_{bc} - I_{ca}]$$

$$I_{a0} = \frac{1}{3} [I_a + I_b + I_c] = 0$$

No zero seq component in current in line.

In symmetrical fault:

$$\text{Complex } 3\phi \text{ power} = \sqrt{3} V_L I_L^* = 3 V_p I_p^*$$

In unsymmetrical fault,



$$3\phi \text{ complex } P = 3 [V_{a0} I_{a0}^* + V_{a1} I_{a1}^* + V_{a2} I_{a2}^*]$$

(actual value)

$$3 \phi \text{ complex power (pu)} = \left[\frac{V_{a0} I_{a0}^*}{(pu)} + \frac{V_{a1} I_{a1}^*}{(pu)} + \frac{V_{a2} I_{a2}^*}{(pu)} \right]$$

(pu)


Sequence network of star connected load.

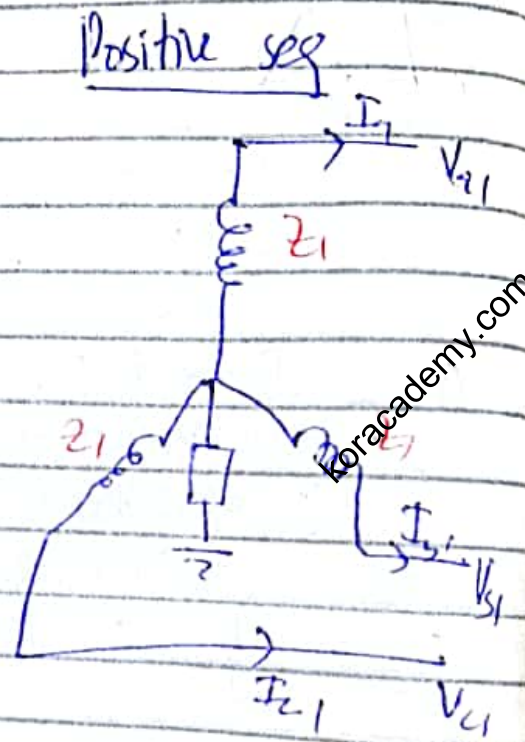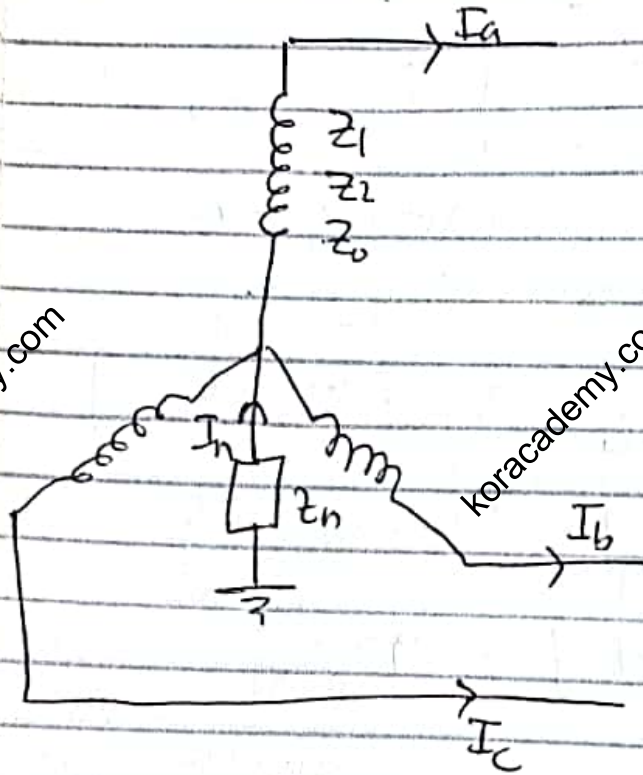

$$I_{a1} = \frac{V_{a1}}{Z_1}, \quad I_{b1} = \frac{V_{b1}}{Z_1}, \quad I_{c1} = \frac{V_{c1}}{Z_1}$$


$$I_n = 0$$

Per phase equivalent circuit;

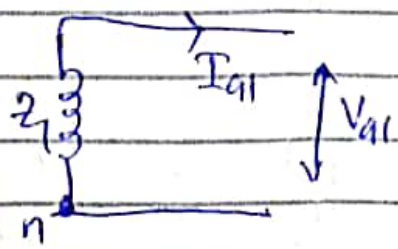


$$V_{a1} = -I_{a1} Z_1$$

Negative sequence network

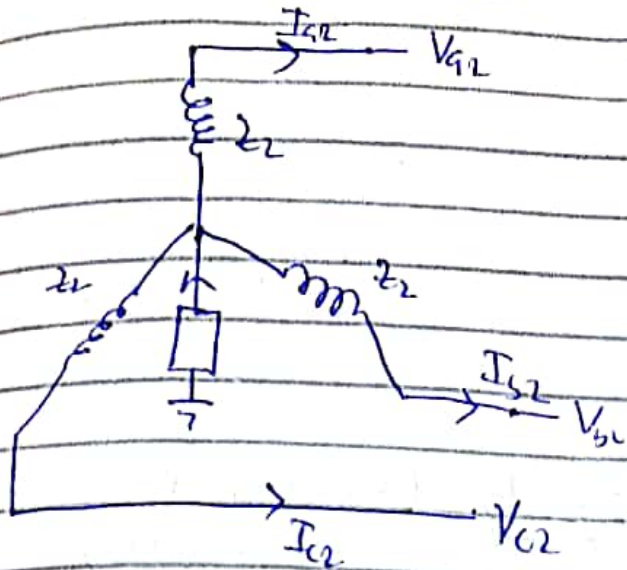


$$I_n = 0$$

per phase equivalent ckt.

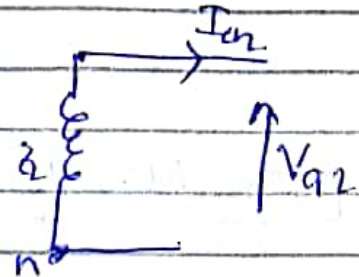

$$V_{g2} = -I_{n2} z_2$$

Zero sequence network

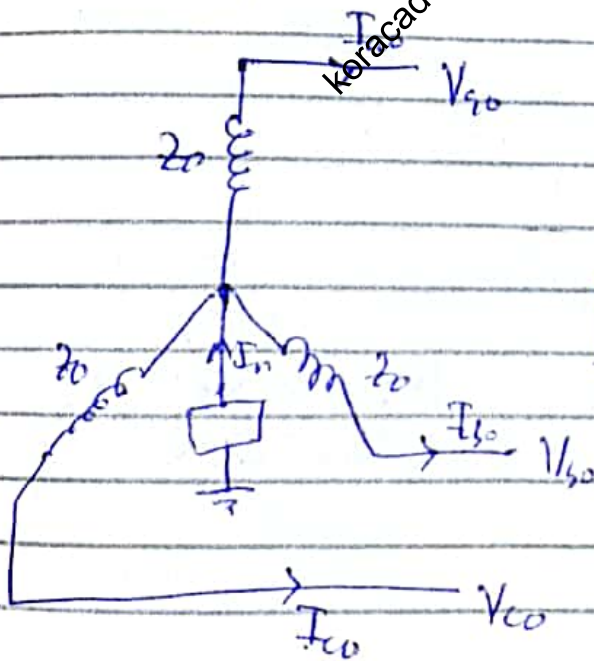


$$I_n = 3I_{a0}$$

$$V_n = -I_n z_n = -3I_{a0} z_n$$

$$= -I_{a0} 3z_n$$

Per phase eq. ckt.:

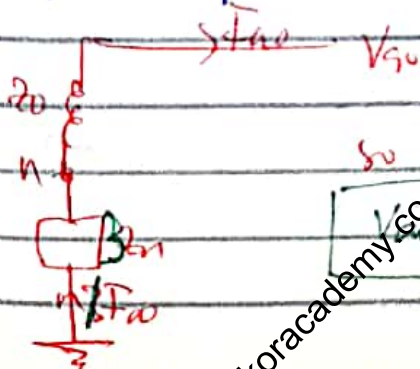


different currents cannot flow in series (\$I_{a0}\$ and \$3I_{a0}\$)

so we make \$z_n\$ as \$3z_n\$.

$$V_{g0} = -I_{a0} (z_0 + 3z_n)$$

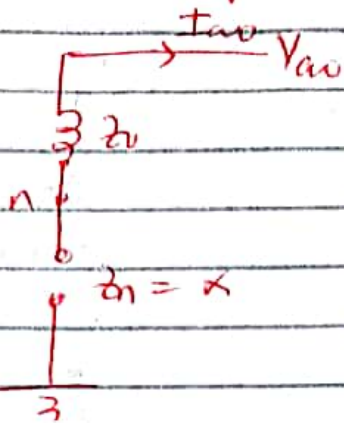→ If star with ungrounded; $\Rightarrow Z_n = \infty$



Sequence Network of Alternator (Synchronous Generator)


Generally we take star connection.

Positive seq component

rotation of rotor = fixed = anticlockwise

the seq emf is present.


-ve seq emf = 0 seq emf = 0

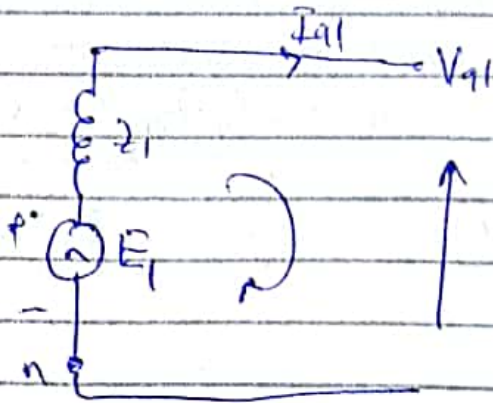

$$V_{q1} = E_1 - I_{q1} Z_1$$


we will get -ve seq emf if we change direction of rotation of rotor

-ve seq

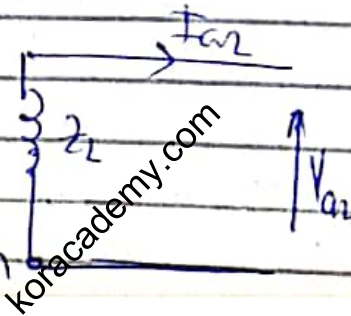


$$V_{q2} = -I_{q2} Z_2$$

Alternate circuit;

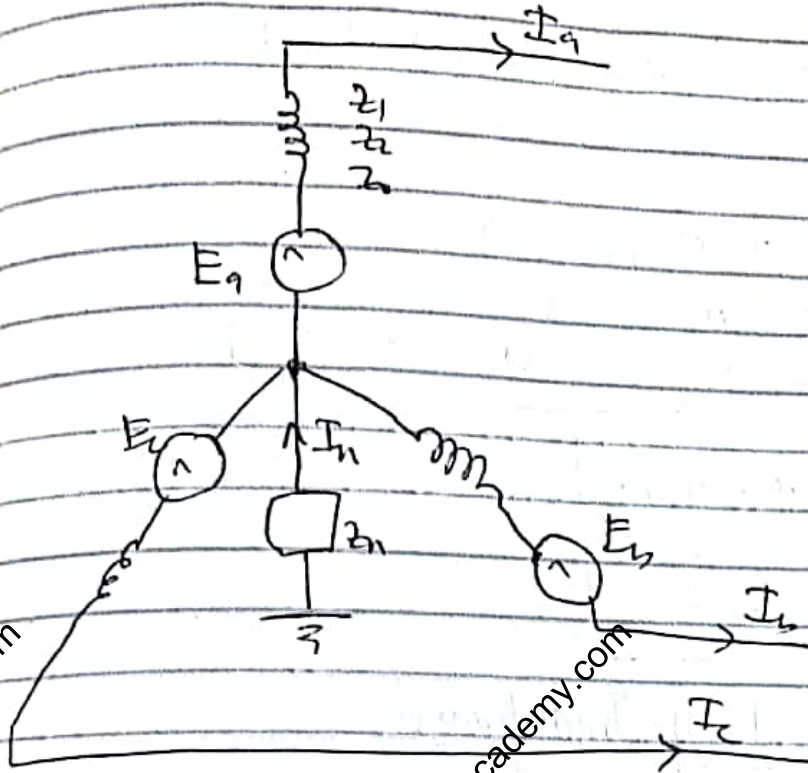

Zero seq network

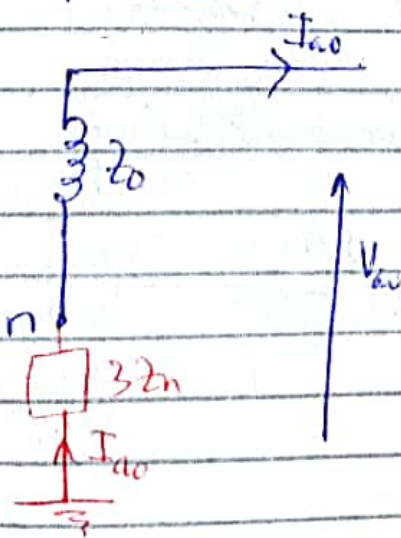

$$V_n = (3I_{ao}) z_n = I_{ao} \left(\frac{3}{z_n} \right)$$

$$V_{ao} = -I_{ao} (z_0 + 3z_n)$$

$$z_{0\text{eq}} = z_0 + 3z_n$$

Transmission Line

- a _____
- b _____
- c _____

Here the tree, -ve and 0 seq impedance comes from two components
 - self impedance
 - mutual impedance.

$Z_{aa} = Z_{bb} = Z_{cc} = Z_s = \text{self impedance}$

$Z_{ab} = Z_{bc} = Z_{ca} = Z_m = \text{mutual inductance}$


$$\begin{bmatrix} Z_0 \\ Z_1 \\ Z_2 \end{bmatrix} = \begin{bmatrix} Z_s + 2Z_m & 0 & 0 \\ 0 & Z_s - Z_m & 0 \\ 0 & 0 & Z_s - Z_m \end{bmatrix}$$

$$\begin{aligned} Z_0 &= Z_s + 2Z_m \\ Z_1 &= Z_s - Z_m \\ Z_2 &= Z_s - Z_m \end{aligned}$$




Sequence Network of Transformer

Transformer = static device = if phase sequence is changed, so no change in impedance.

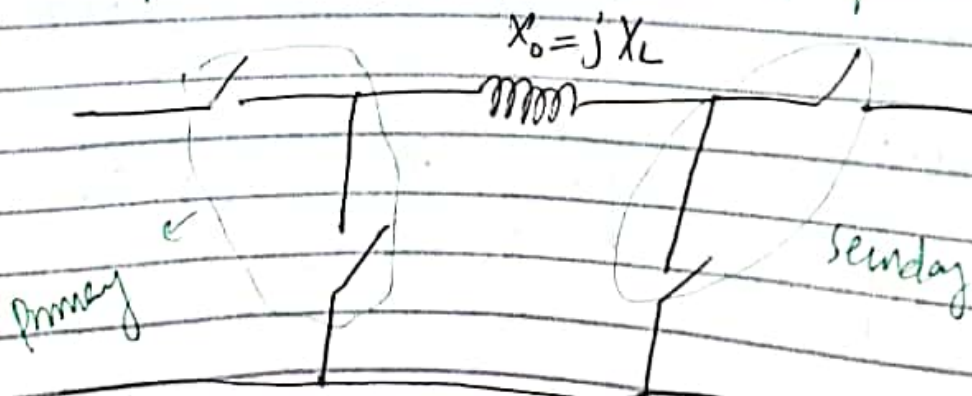
In transformer, +ve seq impedance = -ve seq imp = 0 seq imp



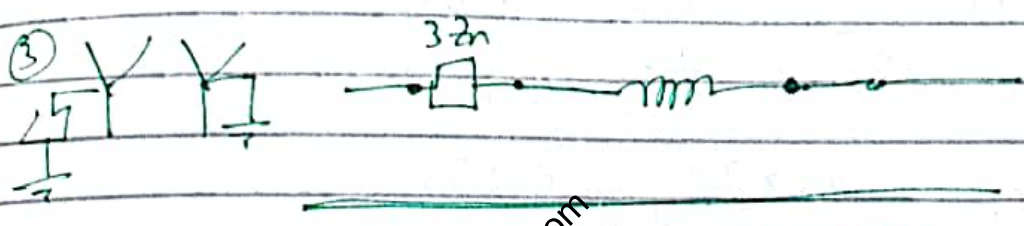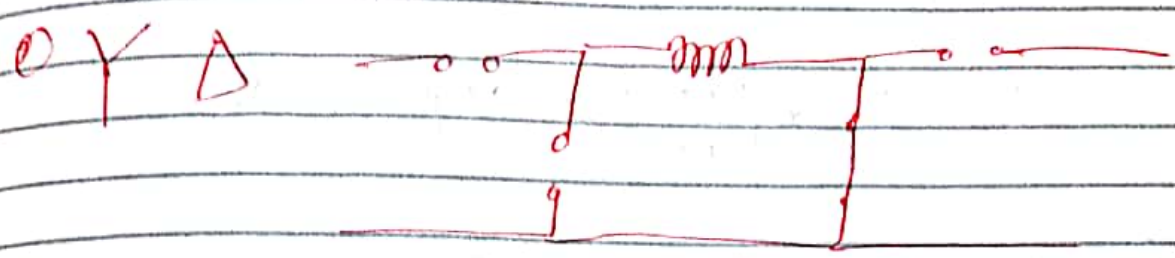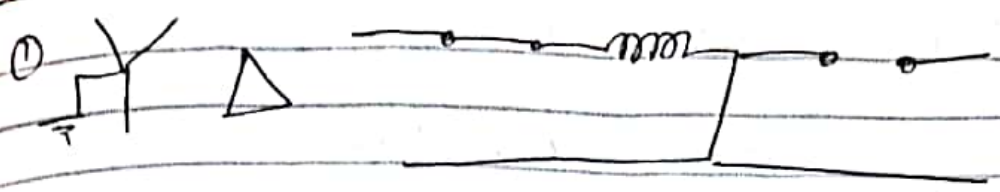series switch = active \rightarrow Star connection (grounded)
parallel switch = active \rightarrow delta



$$X_{eq} = X_L + 3\Omega$$

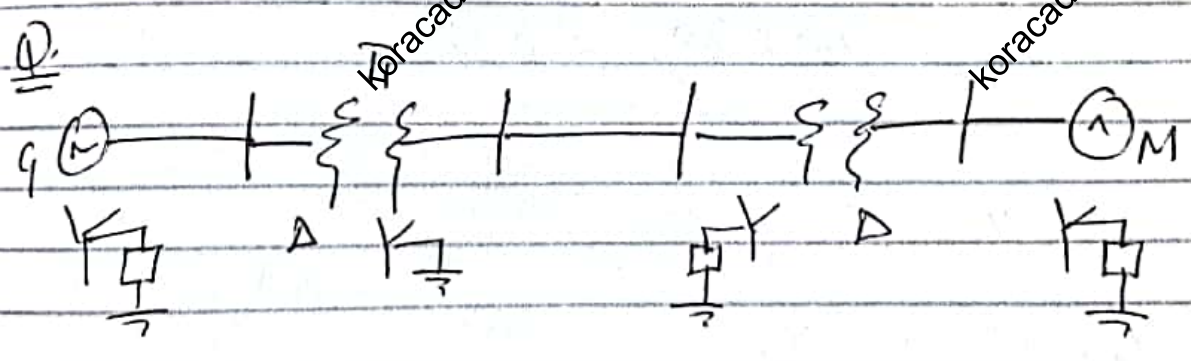

- G: 25 MVA, 11 kV, 0.2 pu
- T₁: 30 MVA, 10 kV / 60 kV, 0.2 pu
- T₂: 30 MVA, 60 kV / 10 kV, 0.2 pu
- M: 15 MVA, 10 kV, X = 0.25 pu
- TL: X_s = 100 Ω, X_n = 20 Ω

Assume the, re ad 0 seq networks of G, M and TL are equal.

Draw the, -re ad 0 seq reactance diagram

Seq base = 30MVA, 10KV

$$X_G = 0.2 \times \frac{30}{25} \times \left(\frac{11}{10}\right)^2 = 0.2904 \text{ pu}$$

$$X_{T1} = 0.2 \times \frac{30}{30} \times \left(\frac{10}{10}\right)^2 = 0.2 \text{ pu} = X_{T2}$$


$$X_M = 0.25 \times \frac{30}{15} \times \left(\frac{10}{10}\right)^2 = 0.5 \text{ pu}$$

$$TL \quad X_{Sp} = 100 \times \frac{30}{60^2} = 0.833 \text{ pu}$$

$$X_{mp} = 2 \times \frac{30}{60^2} = 0.167 \text{ pu}$$

$$X_1 = X_2 = X_s - X_m$$


$$X_0 = X_s + 2 X_m$$

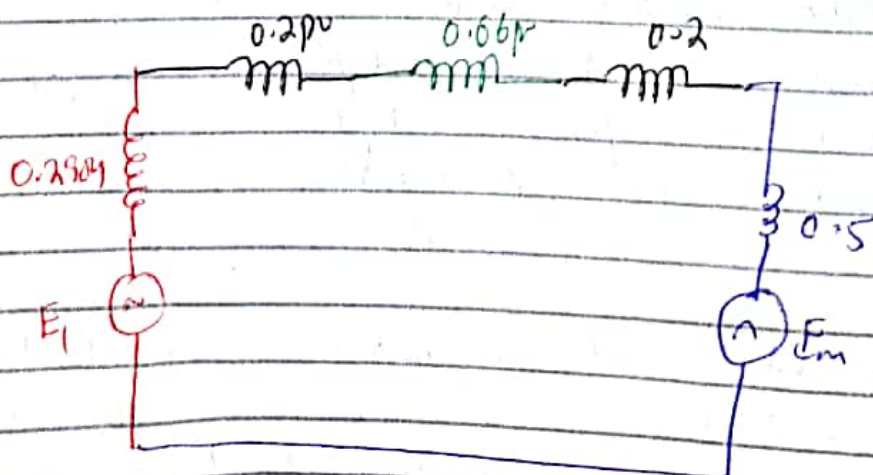


G, TL, T, M

the seq network.


-ve seq network

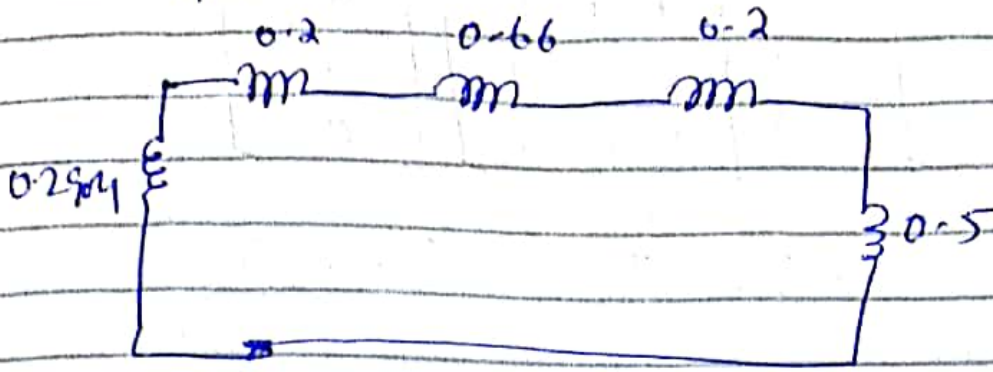

Zero seq network

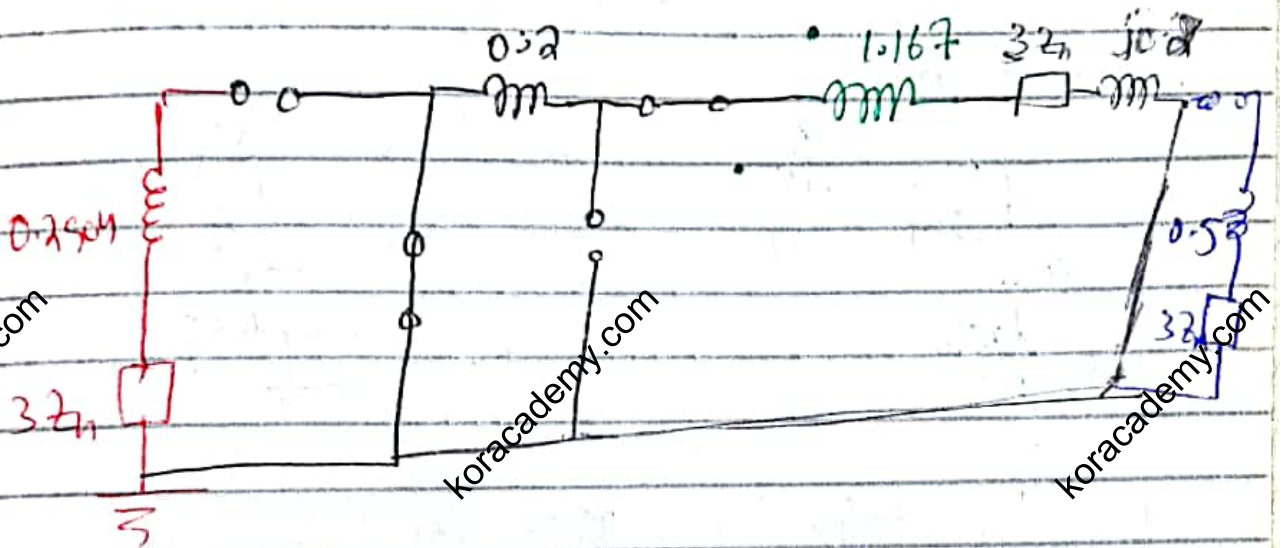

Line to Ground Fault

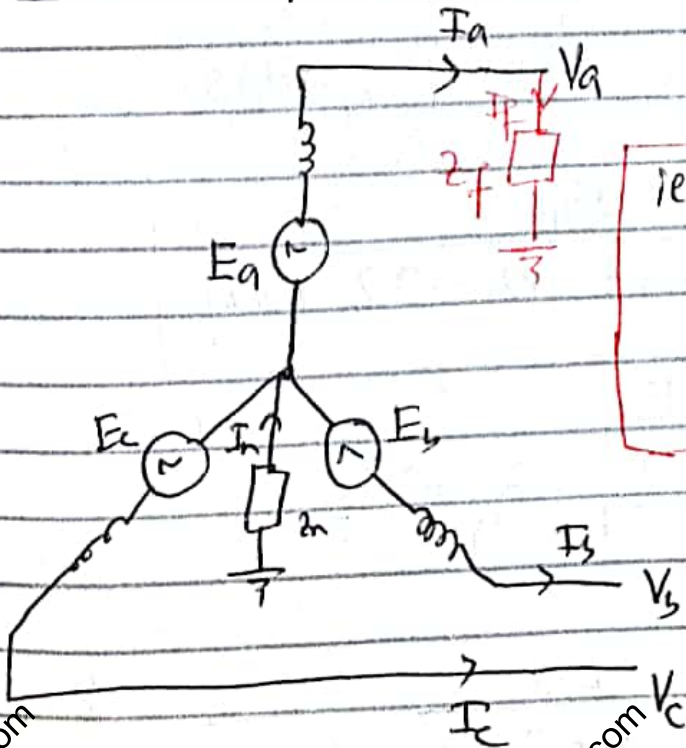

System is at no load.

ie before fault

$$I_a = I_b = I_c = 0$$

$V_a, V_b, V_c \rightarrow$ balanced.

If fault occurs at A;

$$I_a \neq 0$$

$$I_b = I_c = 0$$

$V_a, V_b, V_c \rightarrow$ unbalanced

$$V_a = I_f 2f = I_a 2f$$

$$I_a = I_f$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix}$$

$$I_{a0} = I_{a1} = I_{a2} = \frac{I_a}{3} = \frac{I_f}{3}$$

$$I_f = 3 I_{a0}$$

Equivalent circuit;



As $I_{a0} = \frac{V_{a0}}{z_0 + 3z_n}$, $I_{a1} = \frac{V_{a1}}{z_1}$, $I_{a2} = \frac{V_{a2}}{z_2}$

$$V_a = I_f z_f = 3 I_{a0} z_f = I_{a0} (3 z_f)$$

$$I_{a0} = I_{a1} = I_{a2} = \frac{E_{a1}}{z_1 + z_2 + z_0 + 3z_n + 3z_f}$$

$$\text{or } I_{a0} = \frac{E_{a1}}{z_{1eq} + z_{2eq} + z_{0eq} + 3z_f} \quad (\text{pu})$$

where $z_{0eq} = z_0 + 3z_n$

$$\Rightarrow I_f = 3 I_{a0} = \frac{3 E_{a1}}{z_1 + z_2 + z_0 + 3(z_n + z_f)} \quad (\text{pu})$$

to find actual current;

$$I_f (A) = I_f (MVA) \times \frac{MVA}{\sqrt{3} \times V_L}$$

Short Circuit MVA

The power delivered by the source during fault is known as SCMVA

Method 1

$$SCMVA = E_a (V) \times I_f (A)$$

actual value

↓
phase voltage
from first figure

Method 2

$$P_{3\phi} = 3 [E_{a1} I_{a1}^* + E_{a2} I_{a2}^* + E_{a0} I_{a0}^*]$$

↓
actual value.

$$SCMVA = 3 E_{a1} (V) \cdot I_{a1}^* (A)$$

↳ phase value

Method 3

$$(SCMVA)_{pu} = E_{a1} (pu) \cdot I_{a1}^* (pu)$$

$$\Rightarrow SCMVA = (SCMVA)_{pu} \times 3\phi \text{ base } SCMVA.$$


Q. 100MVA, 11KV → line voltage

$Z_1 = Z_2 = 0.1 pu$ $Z_0 = 1 pu$ $Z_n = 0.15 pu = Z_f$
 L-G fault occurs at a phase.

Find:

$I_f (pu)$, $I_f (A)$, $scMVA$, $scMVA_{pu}$
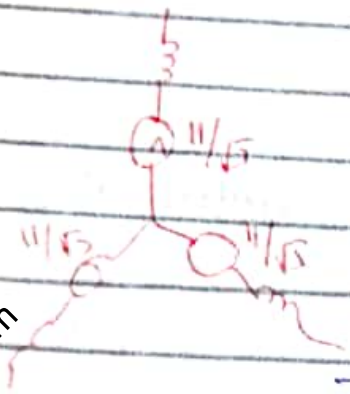
$$\rightarrow I_f (pu) = \frac{3 E_{a1}}{Z_1 + Z_2 + Z_0 + 3Z_n + 3Z_f}$$



$$I_f = \frac{3}{0.1 + 0.1 + 1 + 0.15 + 0.15}$$

$$\Rightarrow I_f (pu) = 5 pu$$

$$I_{a0} = I_{a1} = I_{a2} = \frac{I_f}{3} = \frac{5}{3} pu$$

$$\rightarrow I_f (A) = I_f (pu) \times \frac{MVA}{\sqrt{3} V_L} = 5 \times \frac{110 M}{\sqrt{3} \times 11 k}$$

$$\Rightarrow I_f (A) = 26.24 kA$$

$$\rightarrow scMVA = E_{a1} (ph) \times I_f (A) = \frac{11000}{\sqrt{3}} \times 26.4 \times 10^3$$

$$= 166.67 MVA$$

M2

$$scMVA = 3 E_{a1} I_{a1}^*$$

$$= 3 \times \frac{11000}{\sqrt{3}} \times \frac{5}{3} \times \frac{100}{\sqrt{3}} \times 11 k$$

$$= 166.67 MVA$$


$$MVA (SCMVA)_{pu} = E_{q1}(pu) \times I_{q1}(pu)$$

$$= \frac{1}{3} \times \frac{5}{3} = \frac{5}{3} pu$$

$$(SCMVA) = \frac{5}{3} \times 100 = \frac{500}{3} = 166.67 \text{ MVA.}$$


Method 4

The pu equivalent circuit

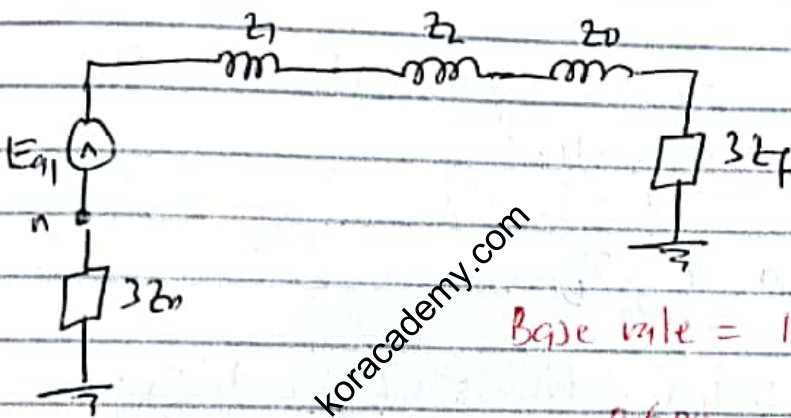


Base value = 100 MVA

eq circuit

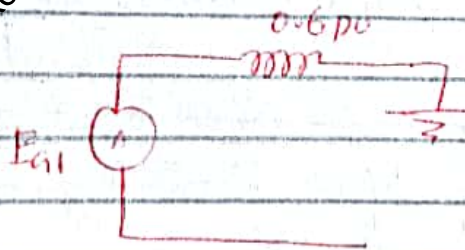

$$SCMVA = \frac{100}{0.6} = \frac{500}{3} = 166.67 \text{ MVA}$$

Line to Line Fault

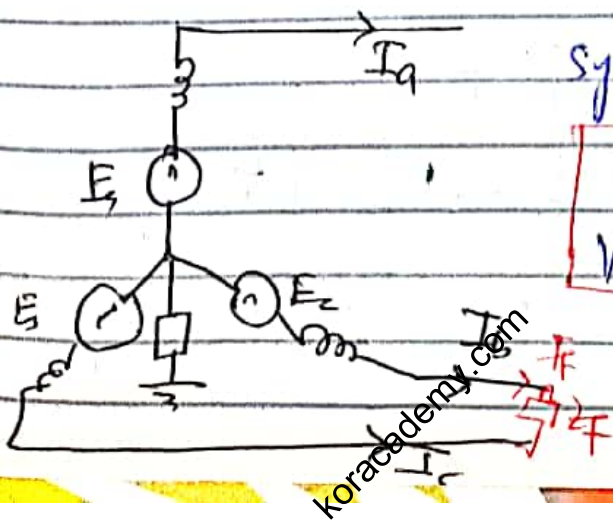

Before fault;
System is at no load.

$$I_a = I_b = I_c$$

$$V_a, V_b, V_c \rightarrow \text{balanced}$$

After fault;

$$I_b = I_f = -I_c$$

$$V_b - V_c = I_f Z_f$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ I_b \\ -I_b \end{bmatrix}$$

$$I_{a0} = \frac{1}{3} [I_b - I_b] = 0$$

No zero seq component of current will flow in line to line fault.

$$I_{a1} = \frac{1}{3} [a - a^2] I_b$$

$$= \frac{1}{3} [1 \angle 120^\circ - 1 \angle 240^\circ] I_f = \frac{1}{3} \sqrt{3} j I_f$$

$$\Rightarrow I_f = -j \sqrt{3} I_{a1} = |\sqrt{3} I_{a1}| \angle -90^\circ$$

$$I_{a2} = \frac{1}{3} [a^2 - a] I_b = -I_{a1}$$

$$I_{a2} = -I_{a1}$$

Now As


$$V_b - V_c = I_f Z_f$$

$$[V_{a0} + a^2 V_{a1} + a V_{a2}] - [V_{a0} + a V_{a1} + a^2 V_{a2}] = I_f Z_f$$

$$\Rightarrow (-a + a^2) V_{a1} + (-a^2 + a) V_{a2} = -j \sqrt{3} I_{a1} Z_f$$

$$j\sqrt{3} V_{q1} - j\sqrt{3} V_{q2} = -j\sqrt{3} I_{q1} z_f$$

$$V_{q1} - V_{q2} = I_{q1} z_f$$

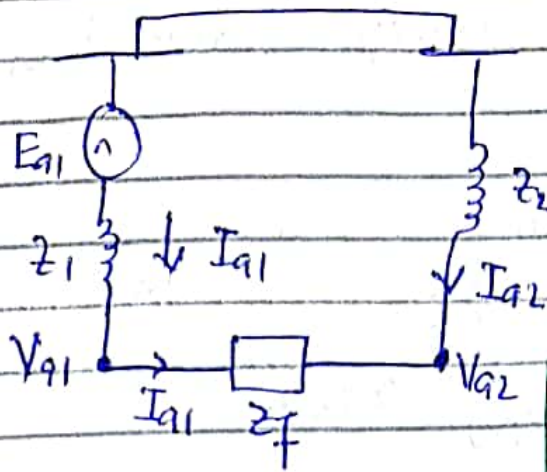

$$I_{q1} = \frac{E_{q1}}{z_1 + z_2 + z_f}$$

$$I_f = \frac{\sqrt{3} E_{q1}}{z_1 + z_2 + z_f}$$

M1

$$SCMVA = (\vec{E}_b - \vec{E}_c) \times I_f (A)$$

$$= (|E| \angle -120^\circ - |E| \angle -240^\circ) I_f (A)$$

$$SCMVA = \sqrt{3} |E| \times I_f (A)$$

phase value

M2

$$3 \phi \text{ puw} = SCMVA = 3 \left[E_{q1} (V) \times I_{q1} (V) \right]$$

M3

$$SCMVA = E_{q1} (pu) \times I_{q1} (pu)$$

Q. 100 MVA, 11 KV. $z_1 = z_2 = z_0 = 0.1 \text{ pu}$
 $z_n = z_f = 0.05 \text{ pu}$
 Line to line fault occurs b/w b and c phases.

Find $I_f \text{ (pu)}$, $I_f \text{ (A)}$, SCMVA (pu) , SCMVA (MVA) .

$$I_f \text{ (pu)} = \frac{\sqrt{3} E_{G1} \text{ (pu)}}{z_1 + z_2 + z_f} = \frac{\sqrt{3}}{0.25}$$

$$I_f \text{ (pu)} = 4\sqrt{3} \text{ pu}$$

$$I_f \text{ (A)} = I_f \text{ (pu)} \times \frac{\text{MVA}}{\sqrt{3} \times V_L} = \frac{4\sqrt{3} \times 100 \text{ M}}{\sqrt{3} \times 11 \text{ k}}$$

$$I_f \text{ (A)} = 36.3 \text{ kA}$$

$$1. \text{ SCMVA} = \sqrt{3} |E| \times I_f \text{ (A)}$$

$$= \sqrt{3} \times 11 \text{ k} \times 36.3 \text{ k} = 400 \text{ MVA}$$

$$ii. \text{ SCMVA} = E_{G1} \text{ pu} \times I_{G1} \text{ pu}$$

$$\text{where } I_{G1} \text{ (pu)} = \frac{E_{G1} \text{ pu}}{z_1 + z_2 + z_f}$$


$$\text{SCMVA}_{\text{pu}} = 4.$$

$$\text{SCMVA} = 4 \times 100 = 400 \text{ MVA}$$

$$\begin{aligned}
 \text{M. } \text{SCMVA} &= 3 E_{q1} (V) \cdot I_{q1} (\text{A}) \\
 &= 3 \times \frac{11000}{\sqrt{3}} \times \frac{I_f}{\sqrt{3}} \left(\frac{38.63 \text{ kVA}}{\sqrt{3}} \right)
 \end{aligned}$$

$$\rightarrow \text{SCMVA} = 400$$

Double Line to Ground Fault

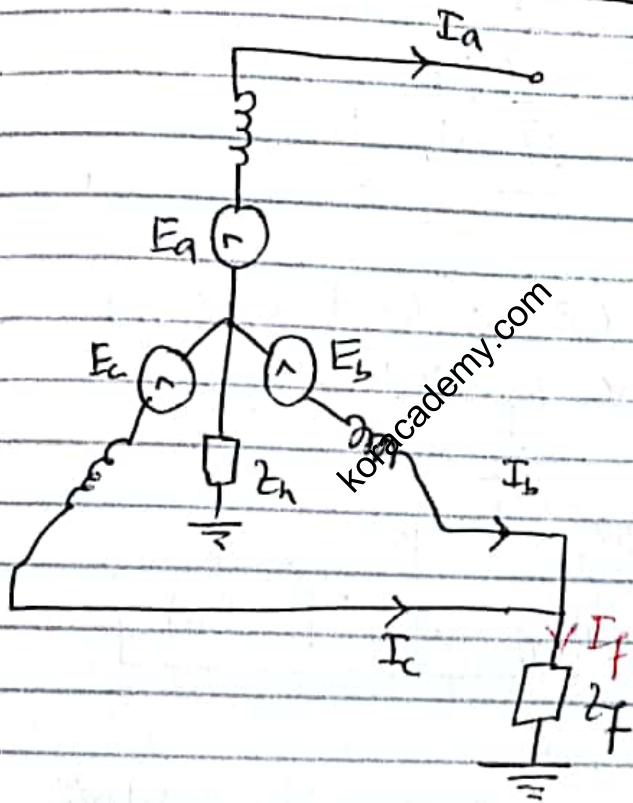

$$V_b = V_c = I_f Z_f$$


$$I_a = 0$$

$$I_f = 3 I_{q0}$$

$$I_f = I_b + I_c$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

The equivalent circuit;

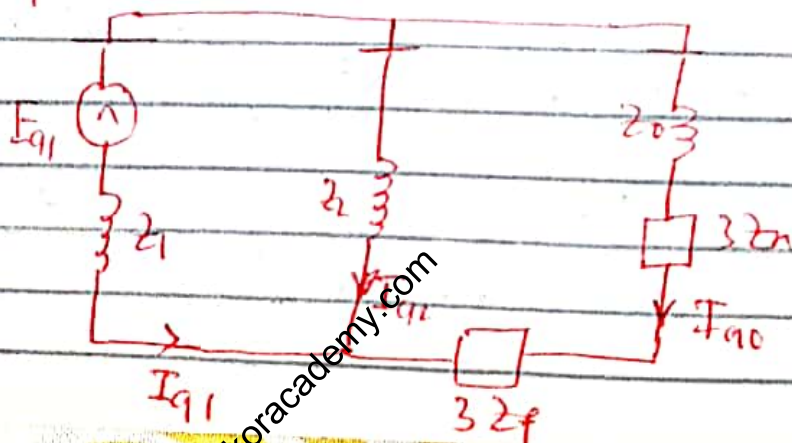

$$I_{a1} = \frac{E_{a1}}{z_1 + (z_2 \parallel z_0 + 3z_n + 3z_f)} \quad (pu)$$

KCL @ current divider:

$$I_{a0} = -I_{a1} \left(\frac{z_2}{z_2 + z_0 + 3z_n + 3z_f} \right) \quad pu$$

$$I_f = 3 I_{a0}$$

$$I_f (A) = I_f (pu) \times \frac{MVA}{\sqrt{3} kV}$$

For SCMVA:

We will install CB in that arm where we have emp (tie seg network).

$$SCMVA = E_{a1} pu \times I_{a1} pu$$

$$SCMVA = (SCMVA)_{pu} \times 3\phi \text{ MVA}$$

Q. 100 MVA, 11 kV. $z_1 = z_2 = z_0 = 0.1 pu$
 $z_n = z_f = 0.05$

Find $I_f (pu)$, $I_f (A)$, SCMVA.

$$I_{a0} = - \frac{I_{a1} z_2}{z_2 + (z_0 + 3z_n + 3z_f)} = 1.11 pu$$

$$I_{a1} = \frac{E_{a1}}{z_1 + [z_2 \parallel (z_0 + 3z_n + 3z_f)]} \approx 5.55 pu$$

$$I_f = 3 I_{a0} = 3.33 \text{ pu}$$

$$I_f (\text{A}) = 3.33 \times \frac{100}{\sqrt{3} \times 11} = 17.47 \text{ kA}$$

$$I_{q1} (\text{A}) = 5.55 \times \frac{100}{\sqrt{3} \times 11} = 29.12 \text{ kA}$$

$$S_{\text{cmVA}} = E_{q1} \times I_{q1} = 5.55$$

$$S_{\text{cmVA}} (\text{act}) = 5.55 \times 100 = 555 \text{ MVA}$$

Q. 20 MVA, 6.6 kV star connected alternator.


$X_q \Rightarrow X_{q1} = X_{q2} = j0.1$, $X_{q0} = j0.04$

Neutral of alternator is connected to ground with a reactance of $j0.05 \text{ pu}$. It is connected

with a T-L having $X_{T1} = X_{T2} = j0.1$ and $X_{T0} = j0.3 \text{ pu}$.

L-G fault occurs at T-L.

Find voltage of neutral wrt ground.

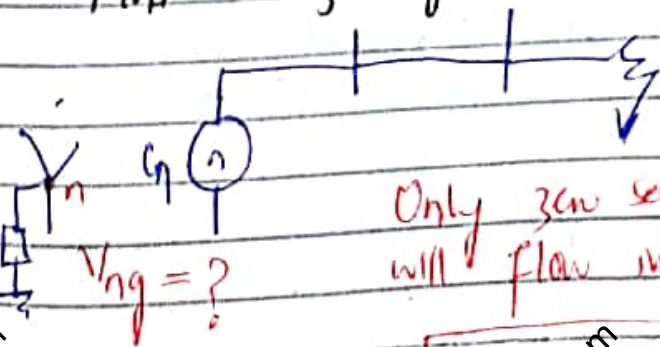

Only zero seq component of current will flow in neutral.

$$I_n = 3 I_{a0}$$

$$V_{ng} = I_n X_n = 3 I_{a0} X_n$$

$$I_{a0} = ?$$

$$\text{In LG fault } I_{a0} = I_{a1} = I_{a2} = \frac{E_{a1 pu}}{X_{1eq} + X_{2eq} + X_{0eq}}$$

where

$$X_{1eq} = X_{G1} + X_{T1} = j0.2$$

$$X_{2eq} = X_{G2} + X_{T2} = j0.2$$

$$X_{0eq} = (X_{G0} + 3X_n) + X_{T0} = j0.49$$

$$\Rightarrow I_{a0} = \frac{1}{j0.89} =$$

$$\Rightarrow V_{ng} = 3 I_{a0} X_n = 3 \times \frac{1}{0.89} \times 0.05 \\ = 0.168 \text{ pu}$$


$$V_{ng} (V) = V_{ng pu} \times V_{sae} = 0.168 \times \frac{6.6 \text{ kV}}{\sqrt{3}} \\ = 642.8 \text{ V.}$$

Q. Symmetrical component of line voltage in pu are;
 $V_{a1} = X \angle \theta_1$, $V_{a2} = Y \angle \theta_2$

The phase to neutral seq voltage are;

$$V_{n1} = \frac{Y}{\sqrt{3}} \angle \theta_1 - 30^\circ, \quad V_{n2} = \frac{Y}{\sqrt{3}} \angle \theta_2 + 30^\circ$$

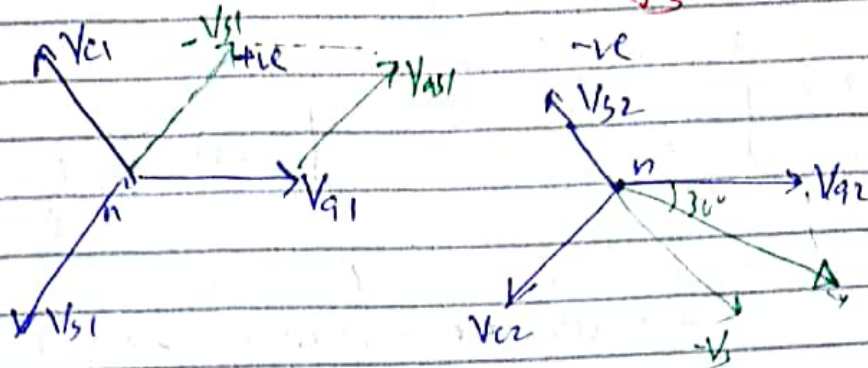
$$V_L = \sqrt{3} V_p \quad \text{①}, \quad V_p = \frac{V_L}{\sqrt{3}}$$




$$V_{q1} = \frac{V_{s1}}{\sqrt{3}} \angle -36^\circ$$

lagging by 30°


V_p leading V_L by 30°

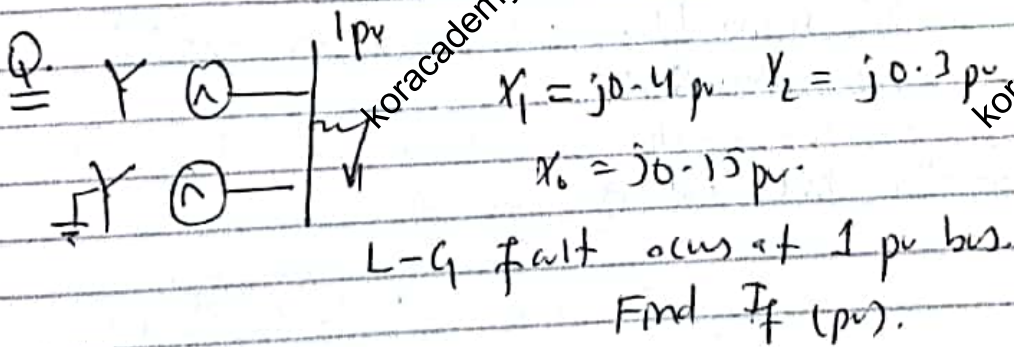

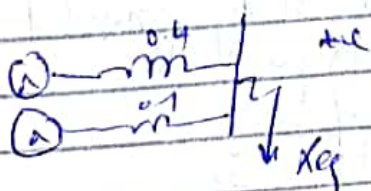
$$I_f \text{ (pu)} = 3 I_{f0} = \frac{3 E_{c1}}{X_{1eq} + X_{2eq} + X_{0eq}}$$


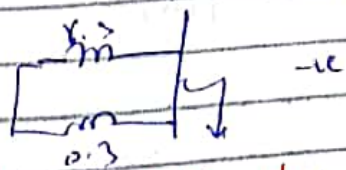
$$X_{1eq} = 0.4 \parallel 0.4 = 0.2 \text{ pu}$$



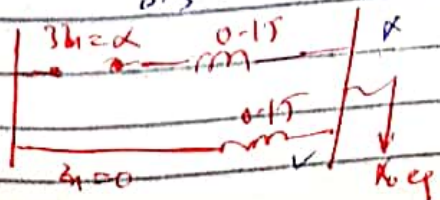
$$X_{2eq} = 0.3 \parallel 0.3 = 0.15 \text{ pu}$$



$$X_{0eq} = j0.15$$
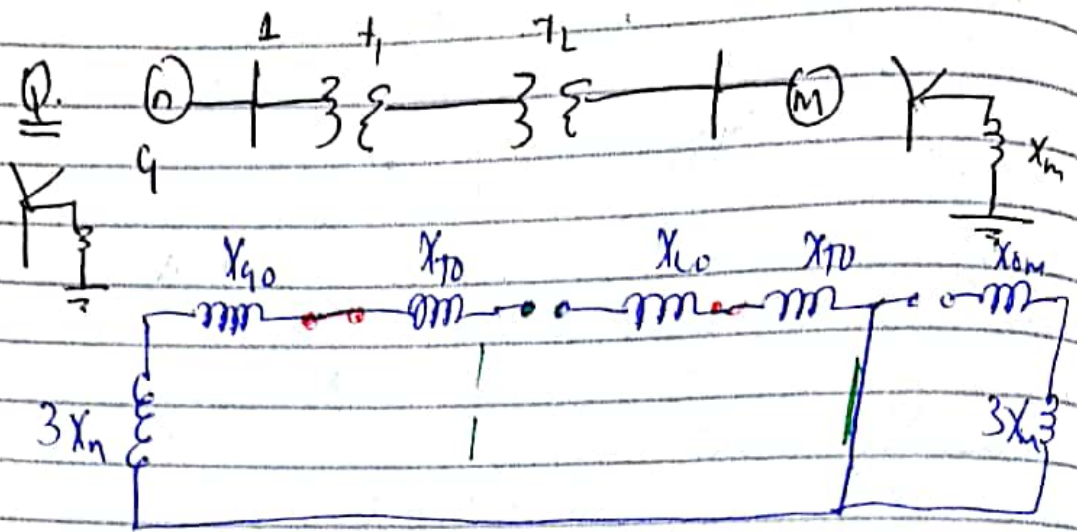
$$\Rightarrow I_f (A) = \frac{3 \times 1}{0.5} = 6 \text{ pu}$$




1. p shorted \rightarrow p B star and grounded

no parallel so no delta, o.c \rightarrow s is star connected but ungrounded.

2. p seems switch shorted \rightarrow star with grounded.

parallel short \rightarrow delta

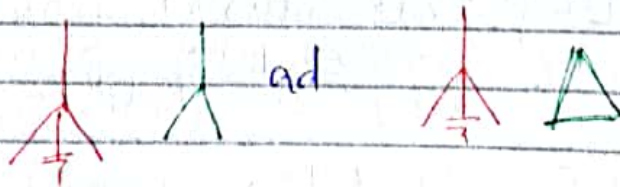

Q. 100 MVA, 25 kV Neutral D solidly grounded.
 $X_1 = X_2 = 0.2 \text{ pu}$ $X_0 = 0.05 \text{ pu}$

L-G fault occurs at terminal of generator; $I_f (A) B$

$$I_f = 3I_{f0} = \frac{3E_{f1}}{2 + 2 + 2 + 3X_n + 3X_{f1}}$$


$$I_f = \frac{3}{0.45} = 6.67 \text{ pu}$$

$$I_f(A) = I_f(M) \times \frac{MVA}{\sqrt{3} V_L}$$

$$= 6.67 \times \frac{100}{\sqrt{3} \times 25} = 15.39 \text{ KA.}$$

Stability

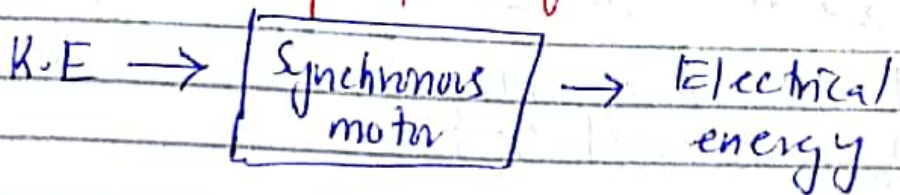Speed governor → keep speed of motor constant.



$$\frac{1}{2} J \omega_{sm}^2 \downarrow$$

$$\uparrow \downarrow N_s = \frac{120}{P} f \downarrow$$

① Voltage stability

overvoltage or undervoltage

Range 0.95 pu to 1.05 pu
ie $\pm 5\%$ of V_{rated} .

② Frequency stability

$$K.E. \downarrow \uparrow \Rightarrow N_s \downarrow \uparrow \Rightarrow f \downarrow \uparrow$$

Range 49.5 Hz to 50.5 Hz
ie $\pm 1\%$ of f_{rated} .

③ Angular stability (change in rotor angle when disturbance occurs)

(a) Steady state stability (swing equation)
Change in δ when small disturbance occurs in system.

(b) Transient stability (Equal area criteria)
 $\delta(t)$ when large disturbance occurs.

(c) Dynamic stability
 Small disturbance but periodic.

Mechanical parameters to Electrical

$$KE = \frac{1}{2} J \omega_{sm}^2 \rightarrow \boxed{\text{Alternator}} \rightarrow P = \frac{E V \sin \delta}{X}$$

J = moment of inertia
 ω_{sm} = mechanical speed

$$As \quad \omega_m = \frac{2\pi}{P} \omega_e \rightarrow \frac{d\omega_m}{dt} = \frac{2\pi}{P} \frac{d\omega_e}{dt}$$

$$\omega_s = \frac{2\pi}{P}$$

$$\boxed{\omega_{sm} = \frac{2\omega_s}{P}}$$

$$KE = \frac{1}{2} \left[J \frac{2^2 \omega_s^2}{P} \right] \omega_s \rightarrow \boxed{KE = \frac{1}{2} [M] \omega_s}$$

MJ-sec / elect radian = unit $\leftarrow M = 2KE / \omega_s \leftarrow$ inertia constant

Also $\boxed{KE = GH}$ G = base MVA
 H = inertia constant.

$$\Rightarrow \frac{1}{2} M \omega_s = GH$$

$$\Rightarrow \boxed{M = \frac{2GH}{\omega_s} = \frac{2GH}{2\pi f} = \frac{GH}{\pi f} = \frac{GH}{180.1}}$$

MJ-sec / elect radian


MJ-sec / elec deg

$$M_{pu} = \frac{M}{G} = \frac{H}{\pi f}$$

Also $H = \frac{KE}{G} = \frac{\text{Energy}}{\text{power}} = t$

unit of H $\left\{ \begin{array}{l} \rightarrow \text{sec} \\ \rightarrow \text{MJ/MVA} \end{array} \right.$

Swing Equation

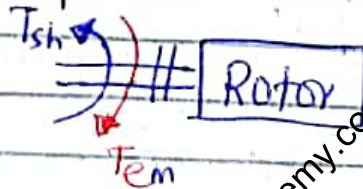

when no disturbance; $T_{sh} = T_{em} \Rightarrow$ stable system

Disturbance \Rightarrow change in T_{em} .

$$T_{sh} - T_{em} = T_J + T_D$$

\swarrow inertia torque \searrow damping torque

For worst case analysis; $T_D = 0$

$$\Rightarrow T_J = T_{sh} - T_{em}$$

$$\Rightarrow \boxed{J \frac{d^2 \theta_m}{dt^2} = T_{sh} - T_{em}}$$

$$W_{sm} \left(J \frac{d^2 \theta_m}{dt^2} \right) = (T_{sh} - T_{em}) W_{sm}$$


$$J \cdot \frac{2}{P} \cdot W_s \cdot \frac{2}{P} \frac{d^2 \theta_e}{dt^2} = T_m - P_e$$

$$\left[J \left(\frac{2}{p} \right)^2 \omega_s \right] \frac{d^2 \theta_e}{dt^2} = P_m - P_e$$

$$M \frac{d^2 \theta_e}{dt^2} = P_m - P_e$$

For synchronous machine; $\theta_e = \omega_s t + \delta(t)$

Rotor;

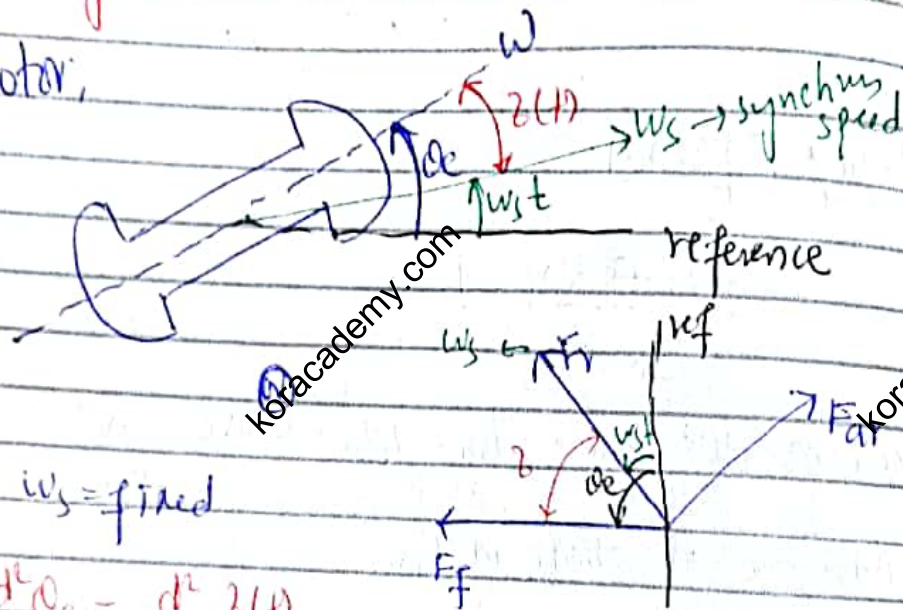

$\omega_s = \text{fixed}$

$$\frac{d^2 \theta_e}{dt^2} = \frac{d^2 \delta(t)}{dt^2}$$

$$\Rightarrow \boxed{M \frac{d^2 \delta(t)}{dt^2} = P_m - P_e}$$

↳ Swing equation

Relation of δ with power

$\delta \rightarrow \text{angle}$, $\frac{d}{dt} \delta \rightarrow \text{speed}$, $\frac{d^2}{dt^2} \delta \rightarrow \text{angular acceleration}$

$$M \alpha = P_m - P_e$$

under steady state; $\boxed{P_m = P_e}$

$$M \alpha = 0 \Rightarrow \boxed{\alpha = 0}$$

$$\frac{d^2 \delta}{dt^2} = 0 \Rightarrow$$

$$\frac{d\delta}{dt} = \text{constant}$$

$$\Downarrow$$

$$\text{speed} = \text{constant}$$

Now when disturbance occurs, there are two possibilities;

i: $P_m - P_e > 0$

$$\Rightarrow M \alpha > 0$$

$$\Rightarrow \text{Acceleration } \alpha > 0$$

$$\Rightarrow \text{Speed of rotor will increase}$$

ii: $P_m - P_e < 0$


$$M \alpha < 0$$

$$\Rightarrow \alpha < 0 \quad \text{Deceleration.}$$

$$\Rightarrow \text{Speed of rotor will decrease.}$$

For 2 machine system:

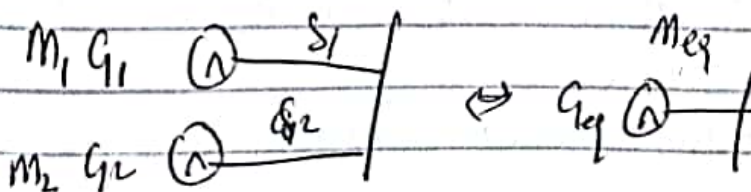if two alternators are connected in parallel.



(a) coherent operation

Frequency is same and $\delta_1 = \delta_2 = \delta$

$$M_1 \frac{d^2 \delta_1}{dt^2} = P_{m1} - P_{e1} \quad \text{--- (1)}$$

$$m_2 \frac{d^2 \delta_2}{dt^2} = P_{m2} - P_{e2} \quad \text{--- (1)}$$


$$\text{(1) + (2)} \Rightarrow \frac{(m_1 + m_2)}{2} \frac{d^2 \delta}{dt^2} = (P_{m1} + P_{m2}) - (P_{e1} + P_{e2})$$

$$\Rightarrow \begin{cases} M_{eq} = M_1 + M_2 \\ P_{meq} = P_{m1} + P_{m2} \\ P_{eq} = P_{e1} + P_{e2} \end{cases}$$

$$\frac{G_{eq} H_{eq}}{\pi f} = \frac{G_1 H_1}{\pi f} + \frac{G_2 H_2}{\pi f}$$

$$\Rightarrow H_{eq} = \frac{G_1 H_1 + G_2 H_2}{G_{eq}} \quad \begin{matrix} \rightarrow \text{individual} \\ \rightarrow \text{common base} \end{matrix}$$

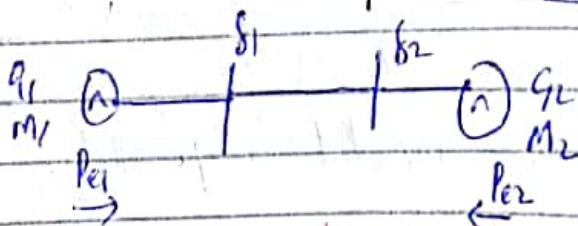(b) Incoherent operation $\delta_1 \neq \delta_2$



Real power always flow from high rotor angle to low rotor angle.

Say $\delta_1 > \delta_2 \Rightarrow$ power will flow from 1 to 2.

I will behave like generator as 2 will behave like motor

$$P_{e2} = P_{e1}$$

Now summing equations;

$$M_1 \frac{d^2 \delta_1}{dt^2} = P_{m1} - P_{e1} \quad - (1) \times M_2$$

$$\text{or } M_2 \frac{d^2 \delta_2}{dt^2} = P_{m2} - P_{e2} \quad - (2) \times M_1$$

(1)-(2)

$$\Rightarrow M_1 M_2 \frac{d^2 (\delta_1 - \delta_2)}{dt^2} = (P_{m1} M_2 - P_{m2} M_1) - (P_{e1} M_2 - P_{e2} M_1)$$

$$\text{or } P_{e2} = -P_{e1}$$

$$\Rightarrow M_1 M_2 \frac{d^2 (\delta_1 - \delta_2)}{dt^2} = (P_{m1} M_2 - P_{m2} M_1) - (P_e (M_1 + M_2))$$

Divide by $M_1 + M_2$

$$\Rightarrow \frac{M_1 M_2}{M_1 + M_2} \frac{d^2 (\delta_1 - \delta_2)}{dt^2} = \frac{P_{m1} M_2 - P_{m2} M_1}{M_1 + M_2} - P_e$$

↓
Mech eqn must exist


↓
mechanical eqn

↓
equivalent electrical power

$$\text{As } \frac{G H_{eq}}{\pi f} = M_{eq}$$

$$\Rightarrow H_{eq} = \frac{M_{eq} \cdot \pi f}{G}$$

Steady state stability

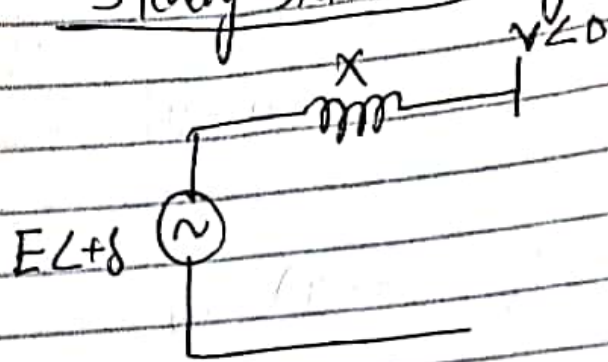

Power delivered by machine.

$$P = \frac{EV}{X} \sin \delta$$

Under no fault;
(steady)

$$P_{e0} = \frac{EV}{X} \sin \delta_0 = P_m$$

$$\delta_0 \rightarrow \text{initial rotor angle } \delta^0 = \sin^{-1} \left(\frac{P_{e0}}{P_{max}} \right)$$

After disturbance:

$$\delta = \delta_0 + \Delta \delta$$

$$\begin{aligned} \rightarrow P_e &= \frac{EV}{X} \sin(\delta_0 + \Delta \delta) \\ &= P_{max} \sin(\delta_0 + \Delta \delta) \end{aligned}$$

$$P_e = P_{max} [\sin \delta_0 \cos \Delta \delta + \cos \delta_0 \sin \Delta \delta]$$

For small disturbance;

$$\cos \Delta \delta \approx 1, \quad \sin \Delta \delta \approx \Delta \delta$$

$$P_e = P_{max} [\sin \delta_0 + \Delta \delta \cos \delta_0]$$

$$P_e = P_{max} \sin \delta_0 + \Delta \delta P_{max} \cos \delta_0$$

$$P_e = P_{e0} + \frac{\partial P_e}{\partial \delta} \Big|_{\delta = \delta_0} \Delta \delta$$

$$P_e = P_{max} \sin \delta_0 \quad \frac{\partial P_e}{\partial \delta} \Big|_{\delta = \delta_0} = P_{max} \cos \delta_0$$

A swing equation

$$M \frac{d^2 \delta}{dt^2} = P_m - P_e$$

$$= P_m - P_{e0} - \left. \frac{dP_e}{d\delta} \right|_{\delta=\delta_0} \cdot \Delta \delta$$

$$\Rightarrow M \frac{d^2 \delta}{dt^2} = - \left. \frac{dP_e}{d\delta} \right|_{\delta=\delta_0} \cdot \Delta \delta$$

$$\text{As } \delta = \delta_0 + \Delta \delta$$

$$\Rightarrow \frac{d}{dt} \delta = \frac{d}{dt} \Delta \delta$$

$$\Rightarrow \frac{d^2}{dt^2} \delta = \frac{d^2}{dt^2} \Delta \delta$$

$$\Rightarrow M \frac{d^2 \Delta \delta}{dt^2} + \left. \frac{dP_e}{d\delta} \right|_{\delta=\delta_0} \cdot \Delta \delta = 0$$

$$\Rightarrow \frac{d^2 \Delta \delta}{dt^2} + \frac{K}{M} \Delta \delta = 0$$

$$\text{where } K = \left. \frac{dP_e}{d\delta} \right|_{\delta=\delta_0}$$


$$\left(D^2 + \frac{K}{M} \right) \Delta \delta = 0$$

$$D = \pm \sqrt{\frac{-K}{M}} \quad \text{roots.}$$

i. $K < 0$ \Rightarrow $D =$ equal and real roots.

$$\text{Response: } \Delta \delta = C_1 e^{\sqrt{\frac{K}{M}} t} + C_2 e^{-\sqrt{\frac{K}{M}} t}$$

Unstable

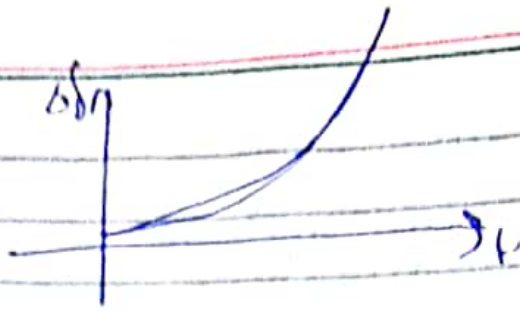


ii. $k > 0$ \Rightarrow roots are complex.

$$D = \pm j \sqrt{k/m}$$


Response, $\Delta\delta = C_1 \cos\left(\sqrt{\frac{k}{m}} t\right) + C_2 \sin\left(\sqrt{\frac{k}{m}} t\right)$

marginal
state

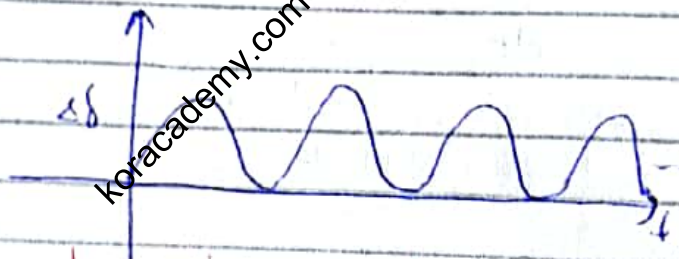

The damping type will try to damp these oscillations.

stable

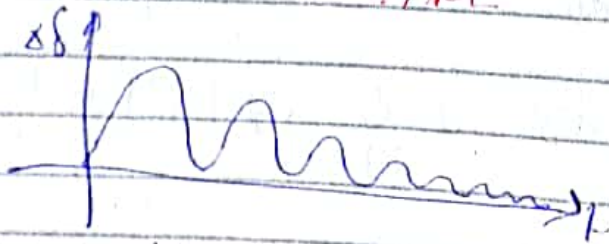

frequency of oscillation,

$$\omega = j \sqrt{\frac{\frac{\partial P_e}{\partial \delta}}{m} \Big|_{\delta = \delta_0}}$$

$$\omega = \sqrt{\frac{\frac{dP_e}{d\delta} \Big|_{\delta = \delta_0}}{GH}} \quad \text{rad/s}$$

Stability criteria (conclusion)

① $\frac{\partial P_e}{\partial \delta} > 0$, $P_{max} \cos \delta > 0$ stable, $\delta \in (0, 90)$

② $\frac{\partial P_e}{\partial \delta} < 0$ unstable, $\delta \in (90, 180)$
 $P_{max} \cos \delta < 0$


③ $\frac{\partial P_e}{\partial \delta} = 0$ marginally stable, $\delta = 90^\circ$
 $P_{max} \cos \delta = 0$

max steady state limit $P_e = P_{max} \sin \delta = P_{max}$

$\hookrightarrow \delta = 90^\circ$

$\delta > 90^\circ \rightarrow$ unstable stable

④ Max steady state limit = P_{max} .

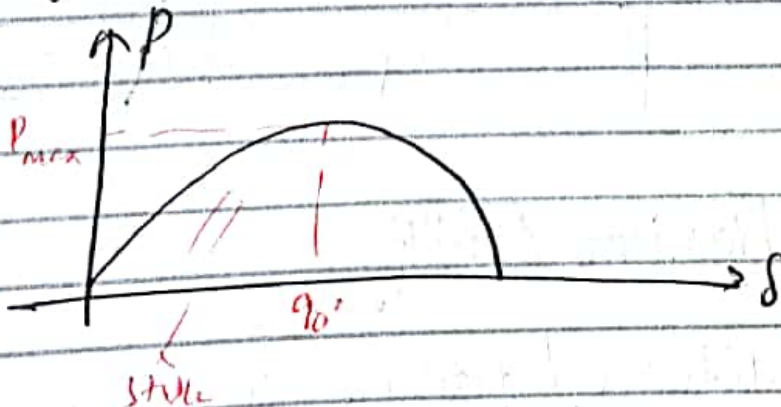

Method to improve steady state limit

$$P_{max} = \frac{EV}{X}$$




To increase P_{max}

- ① Increase excitation (emp) over excited condition
- ② Decrease reactance $X \downarrow$
 - \hookrightarrow bundling of conductors
 - \hookrightarrow double circuit line / parallel line

→ Series compensation.

① By use of SVC (static VAR compensator)

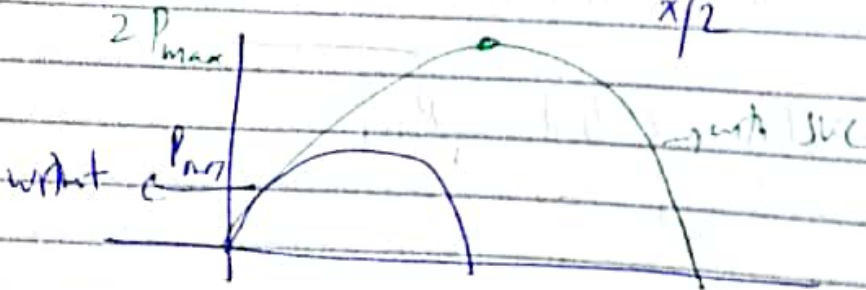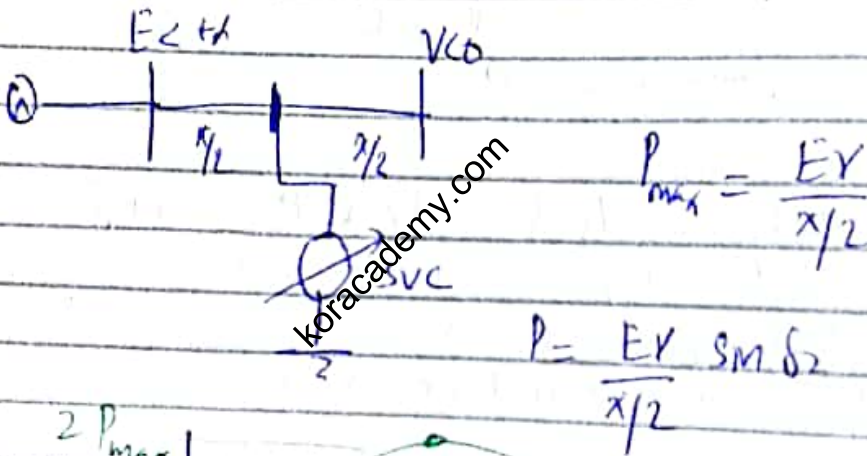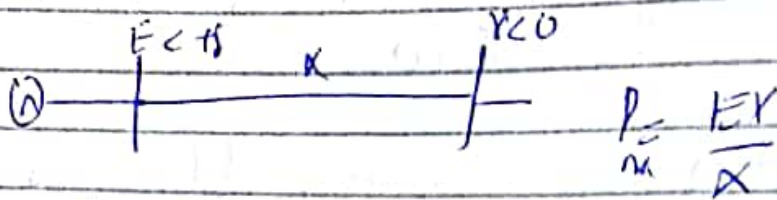will inject reactive power and will not absorb any real power.



Transient Stability

large disturbance / disturbance for a longer duration / continuous disturbance

↳ short circuit fault.

↳ contingency → removal of any instrument from transmission line due to fault / disturbance

Critical clearing time (t_{CR}) maximum time taken by C.B to maintain the system in synchronism.
(the max time to remove fault)

time taken by CB to remove fault $\leq t_{CR}$

Assumptions-

1. Neglect saturation. ($I_f \rightarrow E_f$)
2. Neglect saliency (cylindrical rotor)
3. Neglect damping.
4. Neglect winding resistance
5. Frequency = constant
6. Speed governor is deactivated.
7. Automatic voltage regulator (AVR) is deactivated.

Equal Area Criteria

As swing equation;

$$m \frac{d^2 \delta}{dt^2} = P_m - P_e = P_a \quad \rightarrow \text{accelerating power}$$

$$\rightarrow 2 \frac{d\delta}{dt} \frac{d^2 \delta}{dt^2} = \left(\frac{P_a}{M} \right) 2 \frac{d\delta}{dt}$$

$$\rightarrow \int \frac{d}{dt} \left(\frac{d\delta}{dt} \right)^2 dt = \int \frac{2 P_a}{M} \frac{d\delta}{dt} dt$$

$$\rightarrow \left(\frac{d\delta}{dt} \right)^2 = \int \frac{2 P_a}{M} d\delta$$


$$\Rightarrow \frac{d\delta}{dt} = \sqrt{\frac{2P_a}{M} d\delta}$$

$$\Rightarrow \boxed{\frac{d\delta}{dt} = \sqrt{\frac{2}{M} \int P_a d\delta}}$$

↳ during the fault.

$$\textcircled{17} \quad \boxed{\frac{d\delta}{dt} = \sqrt{\frac{2}{M} \int (P_m - P_{\max} \sin \delta) d\delta}}$$

alternate form of swing equation.

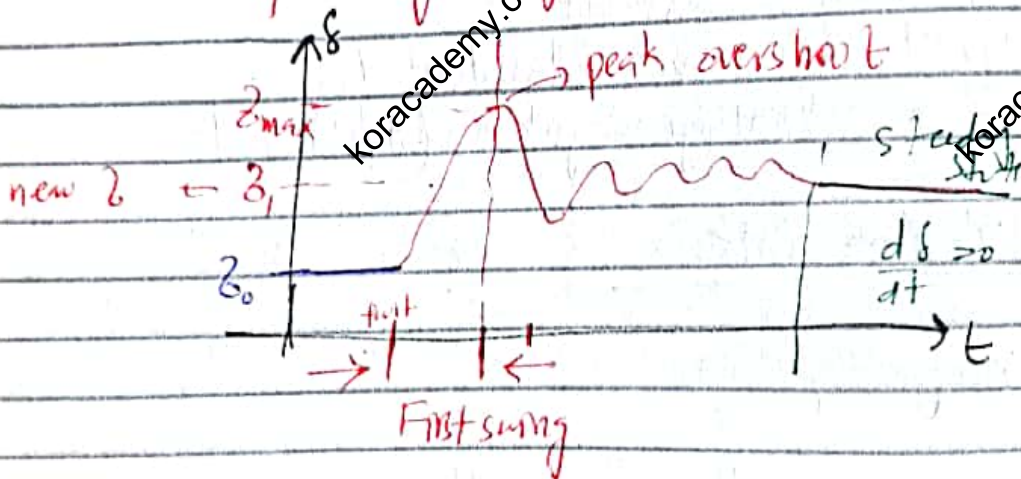

Under steady state; $\frac{d\delta}{dt} = 0$


$$\Rightarrow \boxed{\int P_a d\delta = 0}$$

↳ Area under accelerating part = Area under decelerating part

↳ Equal area criterion

↳ (seeing swing equation graphically)

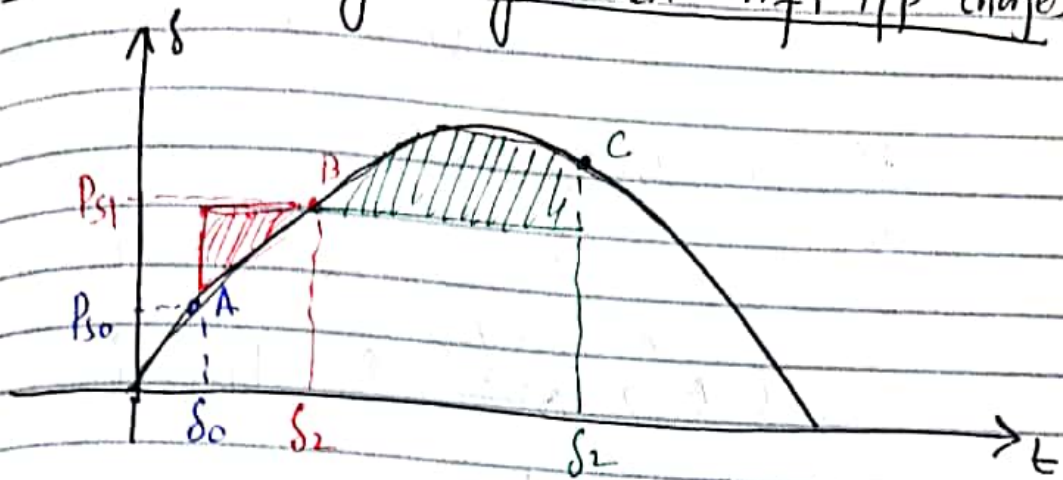Transient stability analysis when shaft i/p changes.



$$P_0 = P_e = P_{max} \sin \delta_0 \rightarrow \text{steady state.}$$

Suddenly increase shaft power from P_{s0} to P_{s1} (i/p P_s)

$$m \frac{d^2 \delta}{dt^2} = P_{s1} - P_e = P_a > 0$$


rotor \rightarrow accelerate $\Rightarrow \omega \uparrow$

$$\frac{d\delta}{dt} = \omega - \omega_s$$

$$\frac{d\delta}{dt} > 0$$

\rightarrow rotor angle \uparrow

Say for example;

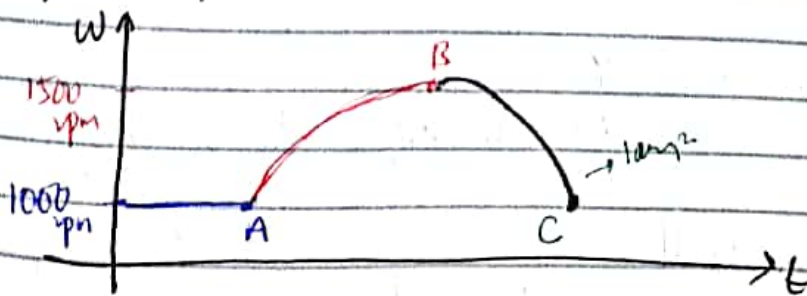

At point B;
 electrical power also increases $P_{max} \sin \delta$ at same
 equal to P_{mech} at δ_2

$$P_s = P_e \Rightarrow P_a = 0$$

↳ no acceleration

$$\rightarrow 1500 - 1000 = 500$$

$$\frac{d\delta}{dt} = \omega - \omega_s > 0$$

↳ rotor angle will still increase.

Now as $\delta \uparrow \Rightarrow P_{max} \uparrow \Rightarrow P_{elect} \uparrow$
 (say due to inertia)

From B to C

$$P_e > P_s$$

$$P_a < 0$$

↳ deceleration

$$\frac{d\delta}{dt} = \omega - \omega_s > 0$$

↳ rotor angle still increase

At point C.

$$P_e > P_s$$

$$P_a < 0$$

↳ Deceleration.

$$\frac{d\delta}{dt} = \omega - \omega_s = 0$$

↳ rotor angle will not increase further

In a nutshell;

AB → acceleration

BC → deceleration

CB → deceleration

BA → acceleration

and this repeats

a few cycles and

finally it will become stable at a new operating point (B).

Applying equal area criteria to the first swing;

$$\text{i.e. } \int P_a d\delta = 0$$


$$\int_{\delta_0}^{\delta_1} (P_{s1} - P_e) d\delta = \int_{\delta_1}^{\delta_2} (P_e - P_{s1}) d\delta$$

$$\int_{\delta_0}^{\delta_1} (P_s - P_{max} \sin \delta) d\delta = \int_{\delta_1}^{\delta_2} (P_{max} \sin \delta - P_s) d\delta$$

$$P_s (\delta_1 - \delta_0) - P_{max} (\cos \delta_0 - \cos \delta_1) = P_{max} (\cos \delta_1 - \cos \delta_2) - P_s (\delta_2 - \delta_1)$$

Limit / Range of C?

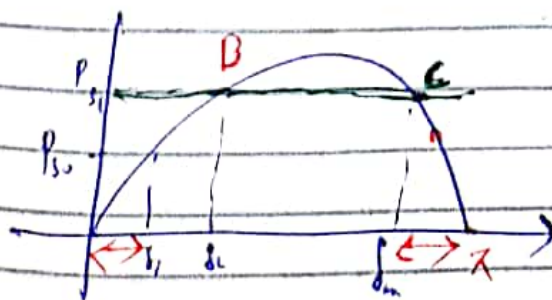↳ Both angle $\delta_2 = \delta_{max} = ?$ (range)



$$\delta_{max} = \pi - \delta_1$$

$\delta_1 = ?$

As $P_{s1} = P_{max} \sin \delta_1$

$$\delta_1 = \sin^{-1} \left(\frac{P_{s1}}{P_{max}} \right)$$

What if we take C beyond this point?

B to C - deceleration.

$$\text{At } C, P_{s1} = P_e$$


If δ is further increased ω ; $P_e < P_{s1}$

\hookrightarrow rotor speed increases (ω) \Rightarrow acceleration
 \hookrightarrow It will never decelerate again.

B/c after C ; P_{s1} is always greater than P_e .

\hookrightarrow acceleration

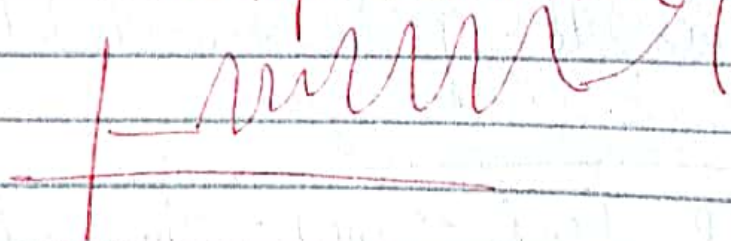\hookrightarrow will keep on increasing
over damped. \neq instability



$\delta_{max} \rightarrow$ max rotor angle below which the system will not lose synchronism.

\ominus the angle above which system will lose synchronism.

Generally mechanical power does not increase, we have disturbance on electrical side.